

Started on Monday, 25 February 2019, 9:30 AM

State Finished

Completed on Monday, 18 March 2019, 6:19 PM


Time taken 21 days 7 hours

Grade 100.00 out of 100.00

Question 1

Correct

Mark 20.00 out of 20.00

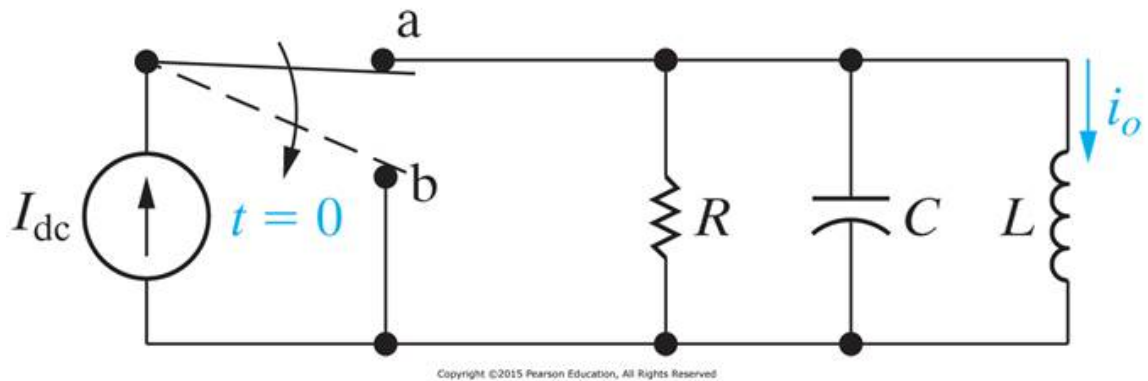

P12.48_10ed

The switch moves from position a to position b at $t = 0$.

Given: $I_{DC} = 5$ Amps

The Laplace Transform of $i_0(t)$ is $I_0(s) = \frac{I_{DC} \left[s + \frac{1}{RC} \right]}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$

a) Use the initial-value theorem to find the initial value of $i_0(t = 0^+)$.

$$i_0(t = 0^+) = \boxed{5} \checkmark \text{ A}$$

b) Use the final-value theorem to find the final value of $i_0(t \rightarrow \infty)$. (∞ is infinity)


$$i_0(t \rightarrow \infty) = \boxed{0} \checkmark \text{ A}$$

Correct

Marks for this submission: 20.00/20.00.

Question 2

Correct

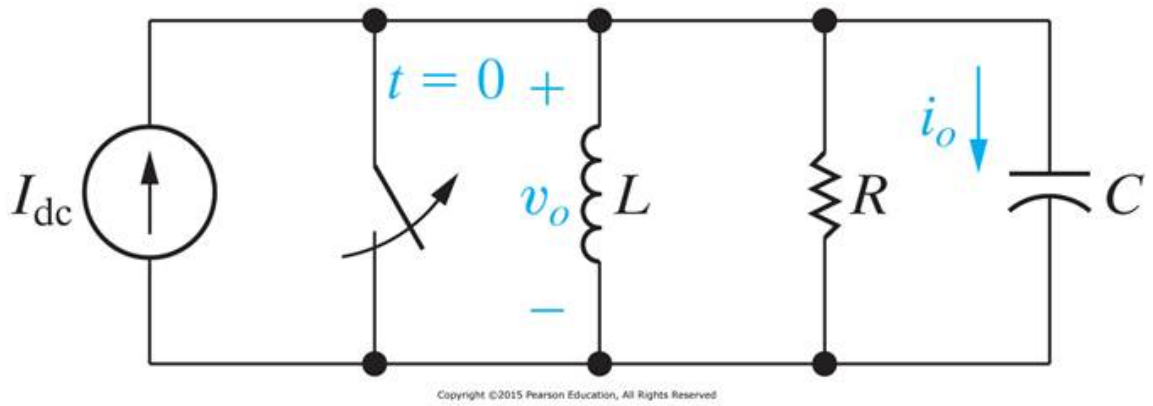Mark 20.00 out of
20.00

P12.47_10ed

Given: $I_{DC} = 3$ AmpsThe Laplace Transform of $v_0(t)$ and $i_0(t)$ are

$$V_0(s) = \frac{\frac{I_{DC}}{C}}{s^2 + s\frac{1}{RC} + \frac{1}{LC}}$$

$$I_0(s) = \frac{sI_{DC}}{s^2 + s\frac{1}{RC} + \frac{1}{LC}}$$

a) Use the initial-value theorem to find the initial value of $v_0(t = 0^+)$.

$$v_0(t = 0^+) = \boxed{0} \checkmark \text{ V}$$

b) Use the final-value theorem to find the final value of $v_0(t = \infty)$. (∞ is infinity)

$$v_0(t = \infty) = \boxed{0} \checkmark \text{ V}$$

c) Use the initial-value theorem to find the initial value of $i_0(t = 0^+)$.

$$i_0(t = 0^+) = \boxed{3} \checkmark \text{ A}$$

d) Use the final-value theorem to find the final value of $i_0(t = \infty)$. (∞ is infinity)

$$i_0(t = \infty) = \boxed{0} \checkmark \text{ A}$$

Correct

Marks for this submission: 20.00/20.00.

Question 3

Correct

Mark 20.00 out of 20.00

P12.47b_8ed

Given
$$F(s) = \frac{8s^3 + 89s^2 + 311s + 300}{s(s+2)(s+3)(s+5)}$$

a) Find the initial value of $f(t)$ for this $F(s)$.

$$f(t=0^-) = 8 \quad \checkmark$$

b) Find the final value of $f(t)$ for this $F(s)$.

$$f(t \rightarrow \infty) = 10 \quad \checkmark$$


Correct

Marks for this submission: 20.00/20.00.

Question 4

Correct

Mark 20.00 out of 20.00

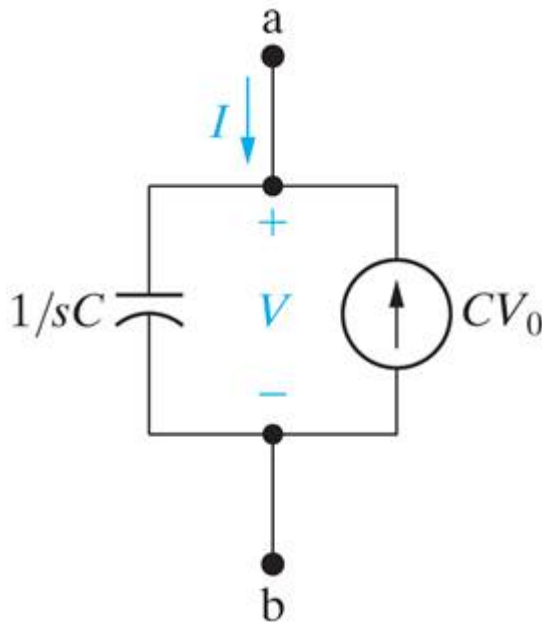

P13.02_10ed

Find the Thévenin Equivalent of this circuit.

Select one:


- ☒ a. $V_{Th} = V_{ab} = V_0/s$ $Z_{Th} = 1/(sC)$ \checkmark
- ☐ b. $V_{Th} = V_{ab} = V_0/s$ $Z_{Th} = sC$
- ☐ c. $V_{Th} = V_{ab} = V_0$ $Z_{Th} = sC$
- ☐ d. $V_{Th} = V_{ab} = 1/s$ $Z_{Th} = V_0/(sC)$

Correct

Marks for this submission: 20.00/20.00.

Question 5

Correct

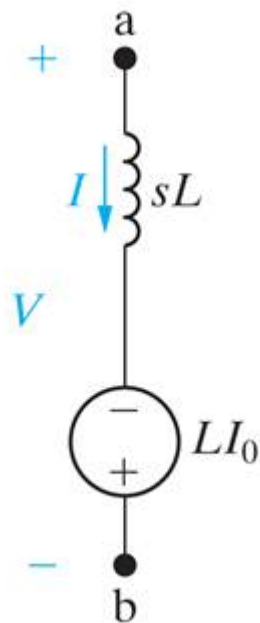Mark 20.00 out of
20.00

P13.03_10ed

Find the Norton Equivalent of this circuit.

Select one:

- ☒ a. $I_N = I_{ab} = -I_0/s$ $Z_{Th} = sL$ ✓
- ☐ b. $I_N = I_{ab} = I_0/s$ $Z_{Th} = sL$
- ☐ c. $I_N = I_{ab} = -I_0$ $Z_{Th} = sL$
- ☐ d. $I_N = I_{ab} = -I_0/s$ $Z_{Th} = 1/(sL)$

Correct

Marks for this submission: 20.00/20.00.

◀ Homework 7 - Chapter 12

Jump to... ▼

Homework 9 - Chapter 13 ►