

Started on Sunday, 12 February 2017, 3:25 PM

State Finished

Completed on Sunday, 12 February 2017, 3:25 PM


Time taken 7 secs

Grade 90.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

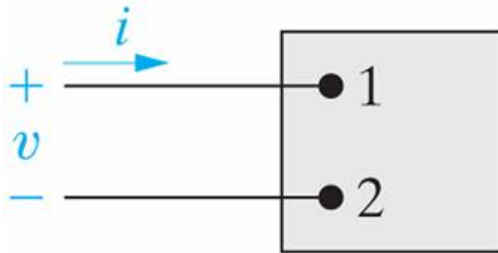

P10.01c_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 625 \cos(\omega t + 40^\circ) \text{ V}$$

$$i = 4 \sin(\omega t + 240^\circ) \text{ A}$$

$P =$ ✓ W ✓ Watts

$Q =$ ✓ VAR ✓ VARs

Numeric Answer

$P = -427.5 \text{ W}$ delivering

$Q = -1,174.6 \text{ VAR}$ delivering


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

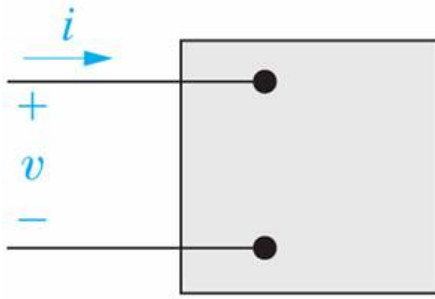

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01c_9ed

For the following set of values, calculate P , Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

$$c) v = 400 \cos(\omega t + 30^\circ) \text{ V} \quad i = 10 \sin(\omega t + 240^\circ) \text{ A}$$

$$P = \boxed{-1000} \checkmark \text{ W} \quad \boxed{\text{Delivering}} \checkmark \text{ Watts}$$

$$Q = \boxed{-1732.05} \checkmark \text{ VARs} \quad \boxed{\text{Delivering}} \checkmark \text{ VARs}$$

Numeric Answer

$$c) P = -1,000 \text{ W del} \quad Q = -1,732.05 \text{ VAR del}$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

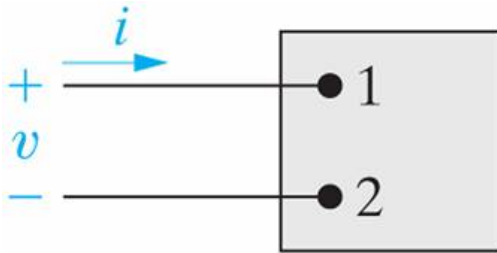

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01b_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 75 \cos(\omega t - 15^\circ) \text{ V} \quad i = 16 \cos(\omega t + 60^\circ) \text{ A}$$

$$P = \boxed{155.29} \checkmark \text{ W} \quad \boxed{\text{Absorbing}} \checkmark \text{ Watts}$$

$$Q = \boxed{-579.56} \checkmark \text{ VAR} \quad \boxed{\text{Delivering}} \checkmark \text{ VARs}$$

Numeric Answer

$$P = 155.3 \text{ W abs} \quad Q = -579.6 \text{ VAR del}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

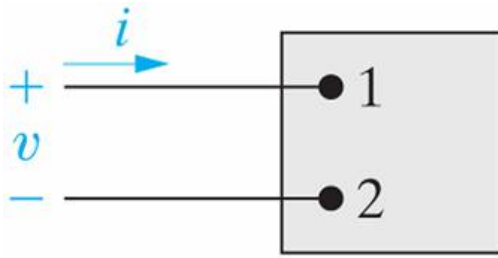

P10.01a_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 340 \cos(\omega t + 60^\circ) \text{ V} \quad i = 20 \cos(\omega t + 15^\circ) \text{ A}$$

$$P = 2404.163 \text{ W Absorbing Watts}$$

$$Q = 2404.163 \text{ VAR Absorbing VARs}$$

Numeric Answer

$$P = 2,404.16 \text{ abs} \quad Q = 2404.16 \text{ VAR abs}$$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

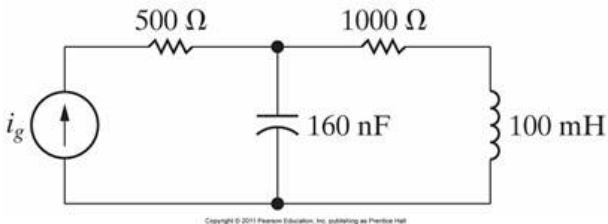

P10.05_9ed

Find the average power delivered by the ideal current source $i_g = 4 \cos(5,000 t) \text{ mA}$ (milli Amp).

$$P_g = -12 \text{ mW (milli Watt) "+" = absorbed, "-" = delivered}$$

Numeric Answer

$$P_g = -12 \text{ mW (milli Watt)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

P10.11b_9ed

A laser printer is rated at 90 W at 115V_{rms}.

a) Calculate the rms value of the current drawn by the laser printer.

$$i_{\text{printer,rms}} = 0.7826 \quad \checkmark \text{ Arms}$$

b) Calculate the peak magnitude of the voltage fed to the laser printer.

$$V_{\text{peak}} = 162.634 \quad \checkmark \text{ V}$$

Numeric Answer

$$\text{a) } i_{\text{printer,rms}} = 0.7826 \text{ A}_{\text{rms}}$$

$$\text{b) } V_{\text{peak}} = 162.6346 \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

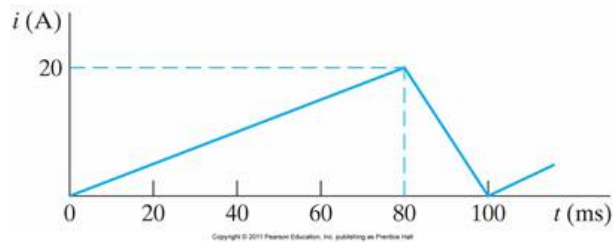

P10.13_9ed

Given: The period of the waveform is 100 ms (milli sec).

a) Find the rms value of the periodic waveform shown in the figure.

$$I_{\text{rms}} = 11.55 \quad \checkmark \text{ A}_{\text{rms}}$$

b) Given that the periodic waveform dissipates an average power of 1,280 W in a resistor. What is the value of the resistor?

$$R = 9.6 \quad \checkmark \Omega \text{ (Ohm)}$$

Numeric Answer

$$\text{a) } I_{\text{rms}} = 11.5470 \text{ A}_{\text{rms}}$$

$$\text{b) } R = 9.6 \Omega \text{ (Ohm)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

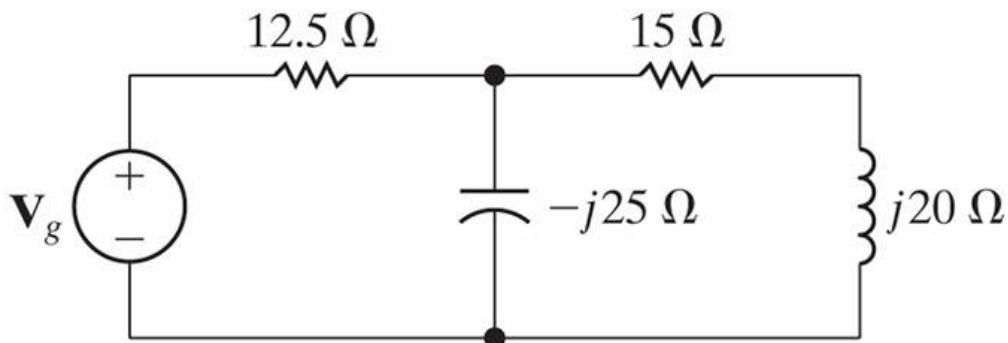

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P10.16_9ed

The voltage V_g is 240 at angle 0° V_{rms} (240 V_{rms} at angle zero degrees)

a) Find the average and reactive power for the voltage source V_g .

$$S_g = -1084.24 + j 271.06 \text{ VA}$$

b) Is the voltage source absorbing or delivering average power? **Delivering** Watts

c) Is the voltage source absorbing or delivering magnetizing VARs? **Absorbing** VARs

d) Find the average and reactive powers associated with each element in this circuit.

$$P_{12.5\Omega} = 271.06 \text{ W}$$

$$Q_{-j25\Omega} = -1355.29 \text{ VAR}$$

$$P_{15\Omega} = 813.18 \text{ W}$$

$$Q_{j20\Omega} = 1084.24 \text{ VAR}$$

Numeric Answer

a) $S_g = -1,084.224 + j 271.056 \text{ VA}$

b) The source is delivering -1,084.224 Watts

c) The source is absorbing 271.056 VARs.

d) $P_{12.5\Omega} = 271.08 \text{ W}$

$Q_{-j25\Omega} \text{ (Capacitor)} = -1,355.280 \text{ VAR}$

$P_{15\Omega} = 813.173 \text{ W}$

$Q_{j20\Omega} \text{ (Inductor)} = 1,084.23 \text{ VAR}$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Incorrect

Mark 0.00 out of 10.00

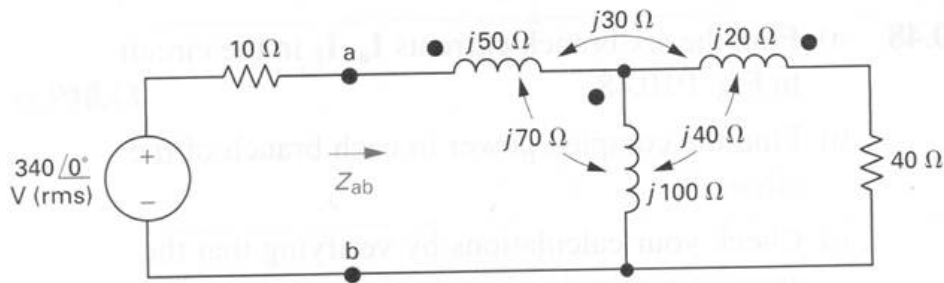

P10.53_6ed

a) Find the average power absorbed/delivered by the 40 Ω (Ohm) resistor.

$P_{\text{avg},40\Omega} = 576000 \text{ W}$ ✗ W “+” = absorbed and “-” = delivered

b) Find the average power absorbed/delivered by the ideal sinusoidal voltage source.

$P_{\text{avg,source}} = 34000 \text{ W}$ ✗ W

Numeric Answer

a) $P_{\text{avg},40\Omega} = 1,440 \text{ W}$ Absorbed

b) $P_{\text{avg,source}} = -1,700 \text{ W}$ Delivered


Incorrect

Marks for this submission: 0.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

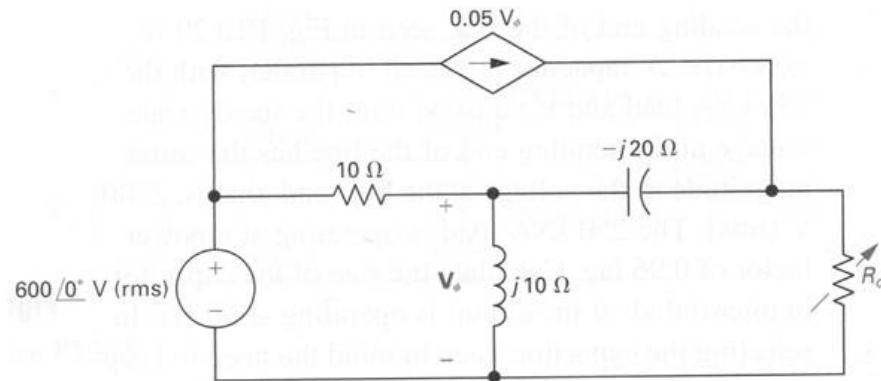

P10.33_6ed

The variable resistor R_0 in this circuit is adjusted until maximum average power is delivered to R_0 .

a) What is the value of R_0 in Ohms?

$R_0 = 20 \text{ } \checkmark \text{ } \Omega \text{ (Ohm)}$

b) Calculate the average power delivered to R_0 in this maximum average power condition.

$P_{R_0} = 9000 \text{ } \checkmark \text{ } \text{W}$

c) If R_0 is replaced with variable impedance Z_0 , what is the maximum average power that can be delivered to Z_0 ?

$P_{Z_0} = 12000 \text{ } \checkmark \text{ } \text{W}$

Numeric Answer

a) $R_0 = 20 \text{ } \Omega \text{ (Ohm)}$

b) $P_{R_0} = 9,000 \text{ W}$

c) $P_{Z_0} = 12 \text{ kW}$

Correct

Marks for this submission: 10.00/10.00.

