

Started on Wednesday, 5 April 2017, 11:01 AM

State Finished

Completed on Wednesday, 5 April 2017, 11:44 AM

Time taken 42 mins 52 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 5.00 out of 5.00

Q1a

Find the Laplace Transform of $\left\{ \frac{d}{dt} \cos \omega t \right\}$

Select one:

- ☐ a. $\frac{1}{s^2 + \omega^2}$
- ☒ b. $\frac{-\omega^2}{s^2 + \omega^2}$ ✓
- ☐ c. $\frac{-s^2}{s^2 + \omega^2}$
- ☐ d. $\frac{\omega}{s^2 + \omega^2}$

Correct

Marks for this submission: 5.00/5.00.

Question 2

Correct

Mark 15.00 out of 15.00

Q2c

Given

$$F(s) = \frac{25(s+3)}{(s+6)(s^2+6s+25)} = \frac{25(s+3)}{(s+6)(s+3-j4)(s+3+j4)}$$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

$$f(t) = [-3 \checkmark e^{-6 \checkmark t} + 5 \checkmark e^{-3 \checkmark t} \cos(4 \checkmark t + -53.13 \checkmark^\circ)] u(t)$$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

Mark 10.00 out of
10.00

Q3d

Given: $F(s) = \frac{40(s+4)}{(s+1)(s+5)}$ which has an inverse transform $f(t)$.

a) Find the initial value of $f(t = 0)$.

$$f(t = 0) = \boxed{40} \checkmark$$

b) Find the final value of $f(t \rightarrow \infty)$


$$f(t \rightarrow \infty) = \boxed{0} \checkmark$$

Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

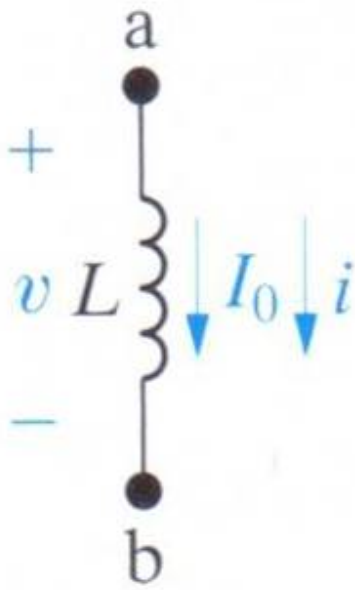Mark 10.00 out of
10.00

Q4c

Given: This inductor has a value of 10 mH (milli H) and has an initial current of 10 A at $t = 0^-$.

Identify the Frequency Domain parallel form of the inductor.

Select one:

- ☒ a. $I = \frac{V}{s(10 \times 10^{-3})} + \frac{10}{s}$ ✓
- ☐ b. $V = s(1 \times 10^{-3})(10) - 0.01$
- ☐ c. $V = s(1 \times 10^{-6})(10) - 0.0001$
- ☐ d. $I = \frac{V}{s(10 \times 10^{-6})} + \frac{10}{s}$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 15.00 out of 15.00

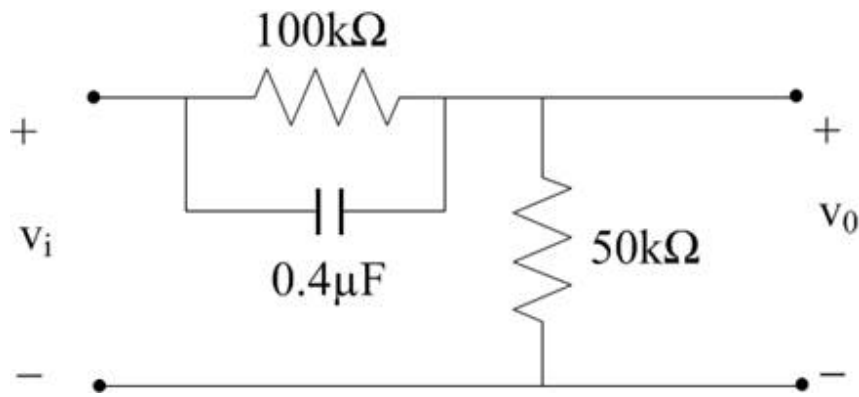

Q5b

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = (s + 25) / (s + 75)$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

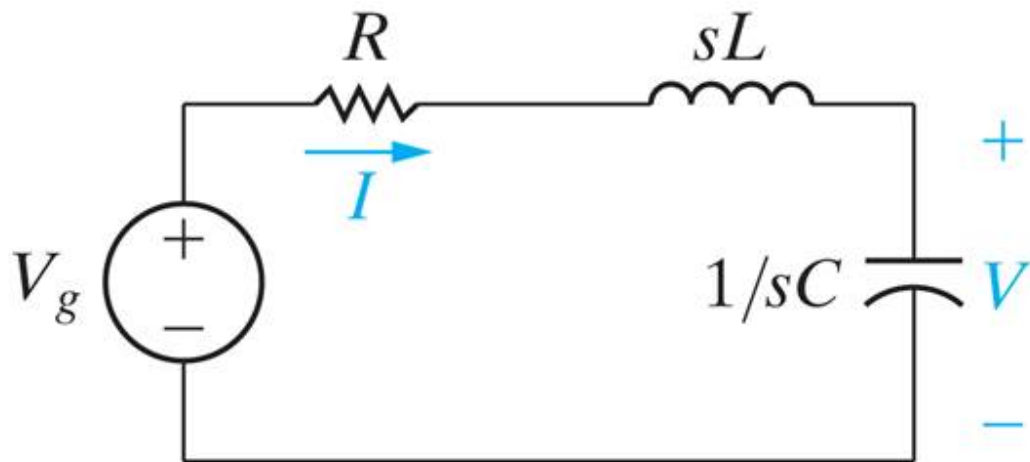

Q6b

Given: There is no energy stored in this circuit prior to $t = 0$.The voltage source $V_g = 25 \text{ V}$ for $t \geq 0^+$. $R = 250 \text{ } \Omega$ (Ohm) $L = 1 \text{ H}$ $C = 2 \text{ mF}$ (milli F)Find defined voltage V in the s domain.

$$V(s) = 12500 / [s(s^2 + 250s + 500)]$$

Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

Mark 15.00 out of 15.00

Q7a

Given: $F(s) = \frac{6(3s+11)}{(s+1)(s+2)}$

Find the partial fraction expansion of this transfer function.

$$F(s) = \boxed{48} \checkmark / (s+1) + \boxed{-30} \checkmark / (s+2)$$


Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

Mark 15.00 out of 15.00

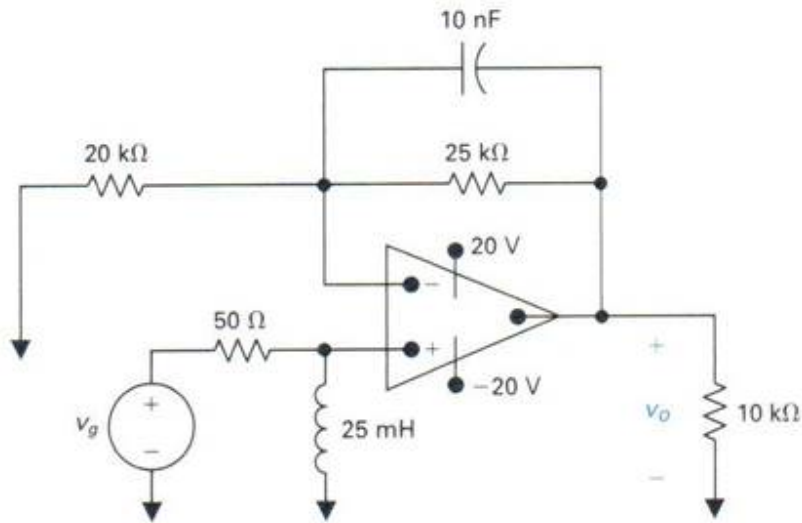

Q8b

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s+9,000)}{(s+2,000)(s+4,000)}$$

Find the steady-state response when the input $v_g(t) = 18 \cos(30,000 t)$ V.

$$v_o(t)_{\text{steady-state}} = [\boxed{18.6} \checkmark \cos(\boxed{30000} \checkmark t + \boxed{-5.3} \checkmark^\circ)] u(t) \text{ V}$$

Correct

Marks for this submission: 15.00/15.00.