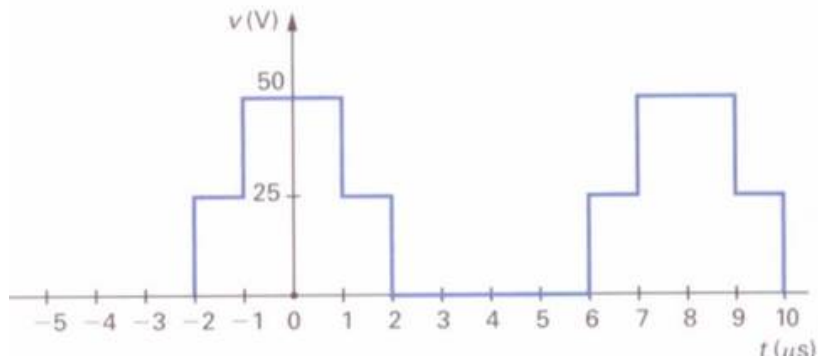


Home ► My courses ► EEE117-2019S-Sec1 ► Homework ► Homework 14 - Chapter 16

Started on Wednesday, 1 May 2019, 1:43 PM**State** Finished**Completed on** Wednesday, 1 May 2019, 1:43 PM**Time taken** 29 secs**Grade** 100.00 out of 100.00**Question 1**

Correct

Mark 11.00 out of 11.00



P16.08b_6ed

Use waveform symmetry and find the Fourier series coefficients for this periodic waveform.

a) Find ω_0 in radians per second.

$$\omega_0 = 785398 \checkmark \text{ rad/sec}$$

b) Find f_0 in Hertz.

$$f_0 = 125000 \checkmark \text{ Hz}$$

c) Find a_v .

$$a_v = 18.75 \checkmark \text{ Volts}$$

d) Find a_k .

$$a_k = 50 \checkmark / (k\pi) [\sin(k\pi/2) + \sin(k\pi/4)] \text{ Volts}$$

e) Find b_k .


$$b_k = 0 \checkmark \text{ for all } k$$

Correct

Marks for this submission: 11.00/11.00.

Question 2

Correct

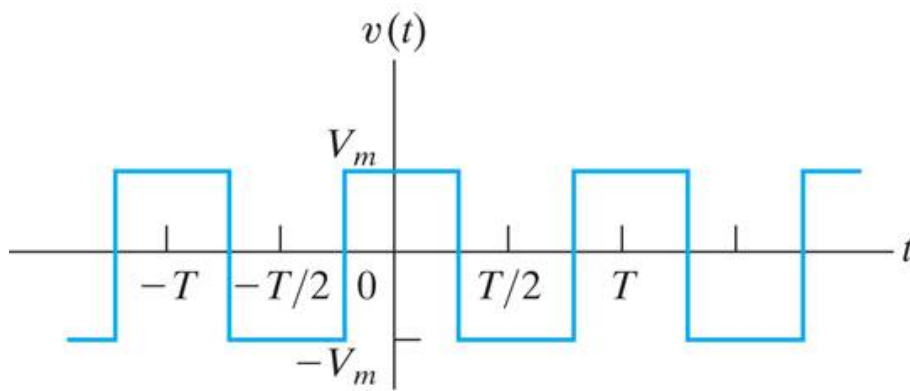Mark 11.00 out of
11.00

P16.13a_10ed

Use waveform symmetry and find the Fourier series coefficients for this periodic waveform.

a) Find a_v .

$$a_v = \boxed{0} \checkmark \text{ Volts}$$

b) Find a_k .

$$a_k = \left(\boxed{4} \checkmark V_m / k\pi \right) \sin(k\pi / \boxed{2} \checkmark) \text{ Volts for } k \text{ odd}$$

c) Find b_k .

$$b_k = \boxed{0} \checkmark \text{ for all } k$$


Correct

Marks for this submission: 11.00/11.00.

Question 3

Correct

Mark 11.00 out of 11.00

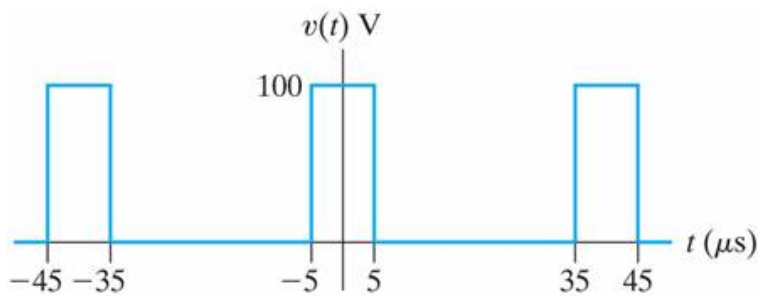

P16.19b_9ed

Given:
$$v(t) = 25 + \frac{200}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{4}\right) \cos(n\omega_0 t) \text{ Volts}$$

The Fourier Series for this waveform using the Alternative Trigonometric Form given by

$$f(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

Determine:

The average value $a_v =$ ✓ Volts

$A_1 =$ ✓ Volts and $\theta_1 =$ ✓ ° (Degrees)

$A_2 =$ ✓ Volts and $\theta_2 =$ ✓ ° (Degrees)

$A_3 =$ ✓ Volts and $\theta_3 =$ ✓ ° (Degrees)

$A_4 =$ ✓ Volts and $\theta_4 =$ ✓ ° (Degrees)

$A_5 =$ ✓ Volts and $\theta_5 =$ ✓ ° (Degrees)


Correct

Marks for this submission: 11.00/11.00.

Question 4

Correct

Mark 11.00 out of 11.00

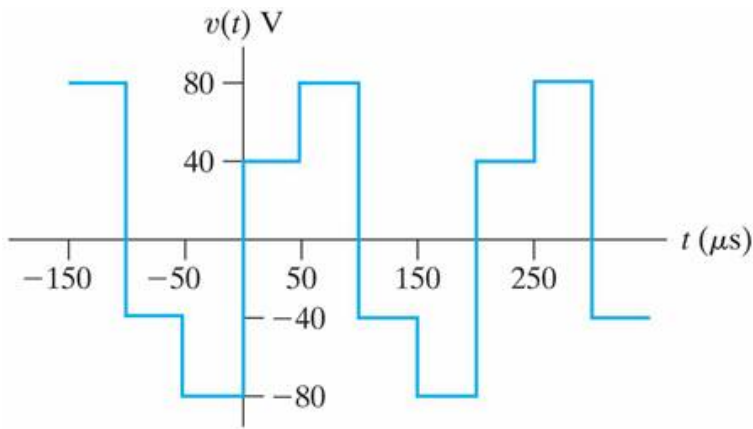

P16.19a_9ed

Given:

$$v(t) = \frac{-80}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{2}\right) \cos(n\omega_0 t) + \frac{240}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin(n\omega_0 t)$$

Rewrite the Fourier Series for this waveform using the Alternative Trigonometric Form given by

$$f(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

The alternate form is

For $n = 1, 5, 9, \dots$ $A_n =$ ✓ / $n\pi$

angle $\theta_n =$ ✓ ° (Degrees, CW from the origin)

For $n = 3, 7, 11, \dots$ $A_n =$ ✓ / $n\pi$

and angle $\theta_n =$ ✓ ° (Degrees, CW from the origin)

CW = Clock-wise



Correct

Marks for this submission: 11.00/11.00.

Question 5

Correct

Mark 11.00 out of 11.00

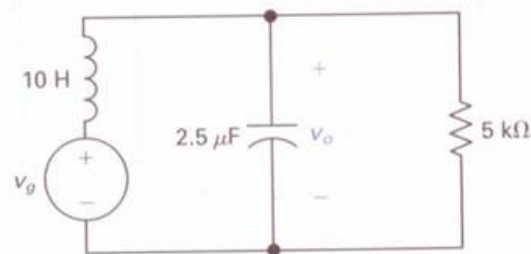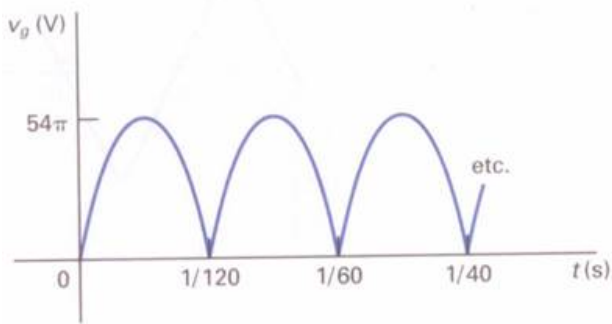

P16.27_6ed

The full-wave rectified sine-wave voltage is applied to the circuit shown.

Find the circuit's response $v_o(t)$ by using the first four nonzero Fourier series terms.

$$v_{o,avg}(t) = 108 \text{ Volts}$$

$$v_{o,1}(t) = 5.41 \cos(240 \pi t + 6.52^\circ) \text{ Volts}$$

$$v_{o,2}(t) = .2574 \cos(480 \pi t + 3.09^\circ) \text{ Volts}$$

$$v_{o,3}(t) = .0485 \cos(720 \pi t + 2.04^\circ) \text{ Volts}$$


Correct

Marks for this submission: 11.00/11.00.

Question 6

Correct

Mark 11.00 out of 11.00

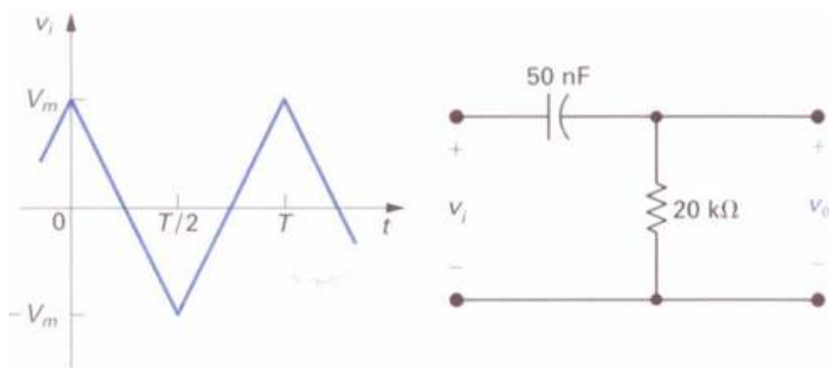

P16.23_6ed

Given: The maximum amplitude of the input signal is $V_m = 450 \pi^2$ mV (milli V) with a period $T = 2\pi$ ms (milli sec) ($\pi = \text{pi}$).

$$v(t) = \left[V_m \right] - \frac{4V_m t}{T} \text{ over the interval } 0 \leq t \leq \frac{T}{2}$$

$$v(t) = \frac{4V_m t}{T} - 3V_m \text{ over the interval } \frac{T}{2} \leq t \leq T$$

You should be able to simplify the Fourier series to

$$v(t) = 3.6 \sum_{n=1,3,5,\dots}^{\infty} \frac{\cos(n\omega_0 t)}{n^2}$$

The periodic triangular-wave voltage is applied to the filter circuit shown.

Estimate the filter circuit's output (response) $v_o(t)$ from the first three nonzero Fourier series terms.

$$v_{o,1}(t) = 2.54 \cos(1000 t + 45^\circ) \text{ Volts}$$

$$v_{o,3}(t) = .38 \cos(3000 t + 18.4^\circ) \text{ Volts}$$

$$v_{o,5}(t) = .14 \cos(5000 t + 11.3^\circ) \text{ Volts}$$


Correct

Marks for this submission: 11.00/11.00.

Question 7

Correct

Mark 11.00 out of 11.00

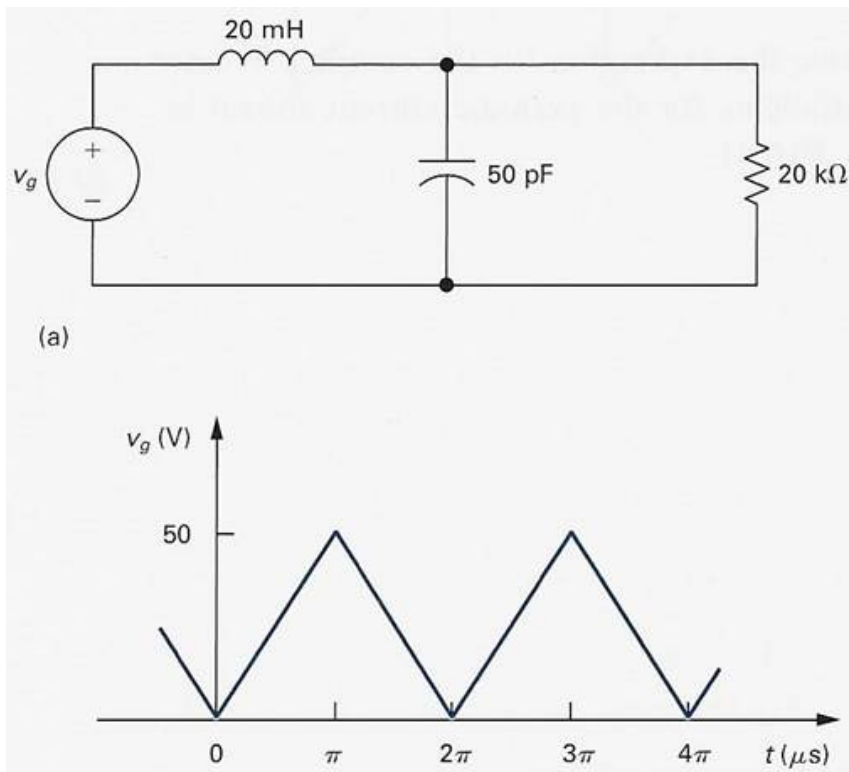

P16.38_6ed

The triangular-wave voltage source is applied to this circuit.

The equation for the function $= 50 \times 10^6 t / \pi$ for $0 \leq t \leq \pi\text{ }\mu\text{s}$ (micro sec)

Estimate the average power delivered to the $20\text{ k}\Omega$ (kilo (Ohm) resistor when the circuit is in steady-state operation.


$P_{20\Omega, \text{steady-state}} = 41.6$ ✓ mW (milli W)

Correct

Marks for this submission: 11.00/11.00.

Question 8

Correct

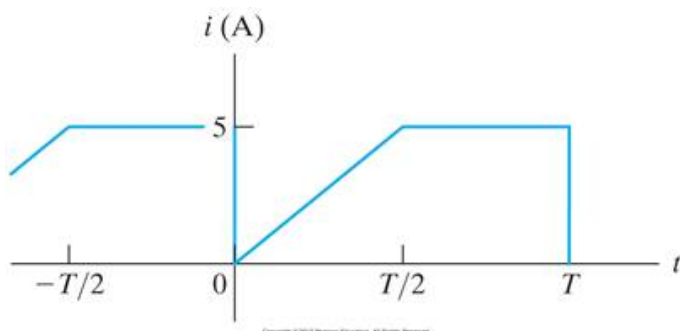Mark 11.00 out of
11.00

P16.33_10ed

The periodic current waveform is applied to a 2.5 k Ω (kilo Ohm) resistor.

Given: $i(t) = \frac{I_m}{T/2} t$ for $0 \leq t \leq T/2$ and $i(t) = I_m$ for $T/2 \leq t \leq T$ where $I_m = 5$ A

a) Use the first three nonzero terms in the Fourier Series representation of $i(t)$ to estimate the average power dissipated in the 2.5 k Ω (kilo Ohm) resistor.

$P_{2.5 \text{ k}\Omega, \text{estimate}} = 40.4$ ✓ kW (kilo Watt)

b) Calculate the exact value of the average power dissipated in the 2.5 k Ω (kilo Ohm) resistor. Hint: You must use the rms integral for the current waveform.

$P_{2.5 \text{ k}\Omega, \text{exact}} = 41.67$ ✓ kW (kilo Watt)

c) Find the error in % between the exact and approximate power calculations from part a) and part b). ("True" = Exact)

$$\% \text{Error} = \frac{\text{True Value} - \text{Estimate}}{\text{True Value}} \times 100$$


% Error = 3.05 ✓ "-" under estimate "+" = over estimate

Correct

Marks for this submission: 11.00/11.00.

Question 9

Correct

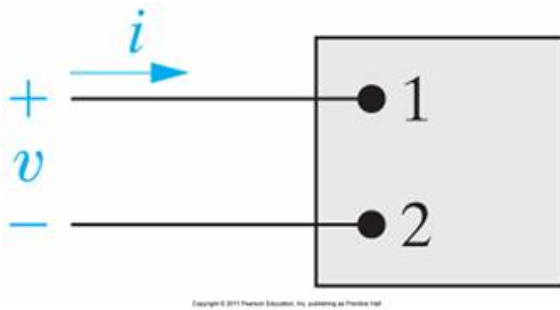Mark 12.00 out of
12.00

P16.35_6ed

The voltage and current at the terminals of this network are

$$v(t) = 80 + 200 \cos(500t + 45^\circ) + 60 \sin(1,500t) \text{ Volts}$$

$$i(t) = 10 + 6 \sin(500t + 75^\circ) + 3 \cos(1,500t - 30^\circ) \text{ Amps}$$

a) What is the average power at element's terminals?

$$P = 1145 \text{ W}$$

b) What is the rms value of the voltage?

$$V_{\text{rms}} = 168 \text{ V}_{\text{rms}}$$

c) What is the rms value of the current?

$$I_{\text{rms}} = 11 \text{ A}_{\text{rms}}$$

Correct

Marks for this submission: 12.00/12.00.

◀ Homework 13 - Chapter 15 and 16

Jump to... ▼

Quiz 1 - Chapter 9 ►