

[Home](#) ► [My courses](#) ► [EEE117-2017S-Tatro](#) ► [Exams and Quizzes](#) ► [Quiz 10 - Chapter 15](#)

Started on	Wednesday, 26 April 2017, 10:57 AM
-------------------	------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 26 April 2017, 11:32 AM
---------------------	------------------------------------


Time taken	34 mins 42 secs
-------------------	-----------------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 100.00 out of 100.00

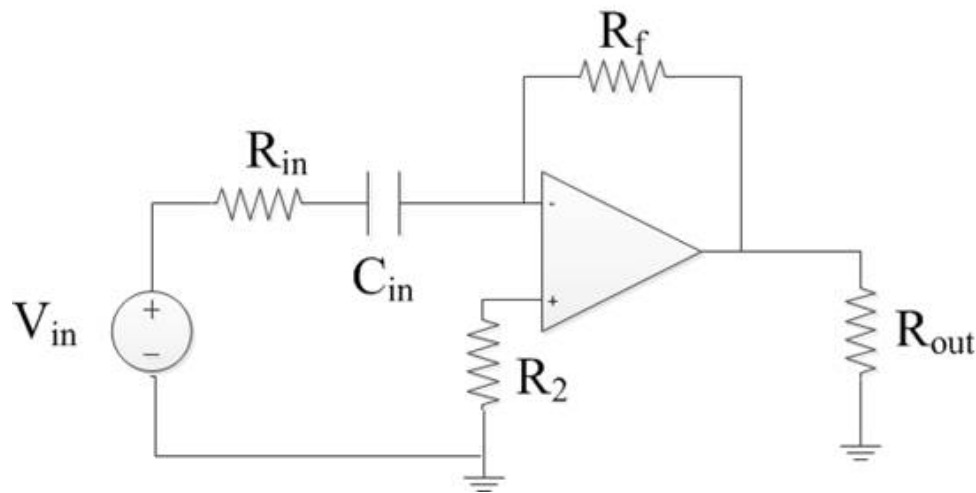

Quiz 10a

Given: $R_{in} = 10 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_f = 10 \text{ k}\Omega$ (kilo Ohm) $R_2 = 10 \text{ }\Omega$ (Ohm) $R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $V_{in} = 20 \cos(\omega t)$ Volts

You can assume the opamp is ideal and has power input rails at +20V and -20V.

In your answers below, report the magnitude as positive and the angle between $-180 \leq \theta \leq -0^\circ$.a) Calculate the phasor voltage across resistor R_{out} when the input voltage frequency $\omega = \text{zero rad/sec}$. $V_{Rout}(\omega = 0) = 0$ ✓ at angle -90 ✓° (Degrees) Voltsb) Calculate the phasor voltage across resistor R_{out} when the input voltage frequency $\omega = 100 \text{ rad/sec}$. $V_{Rout}(\omega = 100) = 2$ ✓ at angle -95.71 ✓° (Degrees) Voltsc) Calculate the phasor voltage across resistor R_{out} when the input voltage frequency $\omega = 1,000 \text{ rad/sec}$. $V_{Rout}(\omega = 1,000) = 14.14$ ✓ at angle -135 ✓° (Degrees) Voltsd) Calculate the phasor voltage across resistor R_{out} when the input voltage frequency $\omega = 5,000 \text{ rad/sec}$. $V_{Rout}(\omega = 5,000) = 20$ ✓ at angle -168.7 ✓° (Degrees) Volts**Correct**

Marks for this submission: 100.00/100.00.