

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY myand IS
PORT ( A, B : IN STD_LOGIC;
      C : OUT STD_LOGIC
);
END myand;
ARCHITECTURE dataflow OF myand IS
BEGIN
    C <= A and B;
END dataflow;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY fa IS
PORT ( A, B, Cin : IN STD_LOGIC;
      Cout, S : OUT STD_LOGIC
);
END fa;
ARCHITECTURE dataflow OF fa IS
signal M: std_logic;
BEGIN
    M <= A xor B;
    S <= M xor Cin;
    Cout <= ( M and Cin ) or ( A and B );
END dataflow;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY rca4 IS
Port ( A, B: in std_logic_vector(3 downto 0);
      Cin: in std_logic;
      Cout: out std_logic;
      S: out std_logic_vector(3 downto 0));
END rca4;
ARCHITECTURE structural OF rca4 IS
component fulladder
PORT (A, B, Cin : IN STD_LOGIC;
      Cout, S : OUT STD_LOGIC
);
end component;
signal CR: STD_LOGIC_VECTOR(3 downto 0);
BEGIN
    U0: fulladder port map ( A => A(0), B => B(0),
                          Cin => Cin,
                          Cout=> CR(0), S => S(0)
);
    U1: fulladder port map ( A => A(1), B => B(1),
                          Cin => CR(0),
                          Cout=> CR(1), S => S(1)
);
    U2: fulladder port map ( A => A(2), B => B(2),
                          Cin => CR(1),
                          Cout=> CR(2), S => S(2)
);
    U3: fulladder port map ( A => A(3), B => B(3),
                          Cin => CR(2),
                          Cout=> CR(3), S => S(3)
);
END structural;

```

```

--Unsigned 8x4-bit Multiplier
module multiplier(A, B, RES);
input [7:0] A;
input [3:0] B;
output [11:0] RES;
assign RES = A * B;
endmodule

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY myand_tb IS
END myand_tb;
ARCHITECTURE beh OF myand_tb IS
component myand
PORT( A, B : IN STD_LOGIC;
      C : OUT STD_LOGIC );
end component;
signal TA, TB : STD_LOGIC;
signal TC: STD_LOGIC;
BEGIN
    uut: myand port map (
        A => TA, B => TB,
        C => TC );
    Process
    Begin
        TA <='0'; TB<='0';
        Wait for 10 ns;
        TA <='0'; TB<='1';
        Wait for 10 ns;
        TA <='1'; TB<='0';
        Wait for 10 ns;
        TA <='1'; TB<='1';
        Wait for 10 ns;
        Wait;
    End process;
END beh;

```

```

Library ieee;
Use ieee.std_logic_1164.all;
Entity dff is
Port ( d, clk: in std_logic;
      q: out std_logic );
End dff;
Architecture beh of dff is
begin
    process( clk )
    begin
        -- if (rising_edge( clk ) ) then
            q <= d;
        end if;
    end process;
End beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY dff_tb IS
END dff_tb;
ARCHITECTURE beh OF dff_tb IS
component dff
PORT (
    d, clk: IN STD_LOGIC;
    q : OUT STD_LOGIC
);
end component;
signal d, clk, q : STD_LOGIC;
BEGIN
    uut: dff port map ( d => d,
                      clk => clk, q => q );
    Process
    Begin
        clk <= '0'; Wait for 10 ns;
        Clk <= '1'; Wait for 10 ns;
    End process;
    Process
    Begin
        d <='0'; Wait for 8 ns;
        d <='1'; Wait for 20 ns;
        d <='0'; Wait for 8 ns;
        Wait;
    End process;

```

```

Process
Begin
    clk <= '0'; Wait for 10 ns;
    Clk <= '1'; Wait for 10 ns;
End process;
Process
Begin
    d <='0'; Wait for 8 ns;
    d <='1'; Wait for 20 ns;
    d <='0'; Wait for 8 ns;
    Wait;
End process;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY shiftreg IS
PORT ( Din, clk, clr : IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(3 downto 0)
);
END shiftreg;
ARCHITECTURE beh OF shiftreg IS
signal W: std_logic_vector(3 downto 0);
BEGIN
    process( clk, clr )
    begin
        if (clr = '1') then
            W <= "0000";
        elsif (rising_edge( clk)) then
            W(3) <= Din;
            W(2) <= W(3);
            W(1) <= W(2);
            W(0) <= W(1);
        end if;
    end process;
    Q <= W;
END beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY mux IS
PORT( A, B,C,D : IN STD_LOGIC;
      SEL: IN STD_LOGIC_VECTOR(1 downto 0);
      DOUT : OUT STD_LOGIC
);
END mux;
ARCHITECTURE design OF mux IS
BEGIN
    DOUT <= A WHEN SEL = "00" ELSE
           B WHEN SEL = "01" ELSE
           C WHEN SEL = "10" ELSE
           D;
END design;

```

```

/library ieee;
use ieee.std_logic_1164.all;
package MY_PACK is
function PARITY (X : std_logic_vector)
return std_logic;
end MY_PACK;
package body MY_PACK is
function PARITY (X : std_logic_vector)
return std_logic is
variable TMP : std_logic;
begin
    --TMP:= '0';
    TMP := X(0);
    --for J in X'range loop
    for J in 1 to X'high loop
        TMP := TMP xor X(J);
    end loop;
    -- works for any size X
    return TMP;
end PARITY;
end MY_PACK;

```

```

library ieee;
use ieee.std_logic_1164.all;
use work.MY_PACK.all;

entity PAR is
port( db: in std_logic_vector(7 downto 0);
      dw: in std_logic_vector(15 downto 0);
      pb, pw: out std_logic);
end PAR;

architecture ARCH1 of PAR is
begin
    pb <= PARITY(db);
    pw <= PARITY(dw);
end ARCH1;

```

Even Parity and Odd Parity

Examples

even

ab_parity (f_even)

00_0

01_1

10_1

11_0

f_even = a xor b

odd

ab_parity (f_odd)

00_1

01_0

10_0

11_1

f_odd = not (a xor b);

ADD/SUBTRACT

Modulo 2 uses XOR

0 ± 0 = 0;

0 ± 1 = 1;

1 ± 0 = 1;

1 ± 1 = 0

MULTIPLICATION

```

  1 0 1 1
x 0 1 0 1
-----
  1 0 1 1
 0 0 0 0
 0 1 0 0 1 1
-----


```

DIVISION

```

      1 0 0 0 1 rem. 1 0 1
1 0 0 1 1 | 1 0 0 1 0 0 1 1 0
          1 0 0 1 1
          -----
            1 0 1 1 0
            1 0 0 1 1
            -----
              1 0 1
              -----
                1 rem. 1 0 1 0
1 1 0 0 1 | 1 0 0 1 1
          1 1 0 0 1
          -----
            1 0 1 0
            -----
              1 rem. 1 0 1 0
1 0 0 1 1 | 1 0 0 1
          1 0 0 1 1
          -----
            1 0 1 0
            -----

```

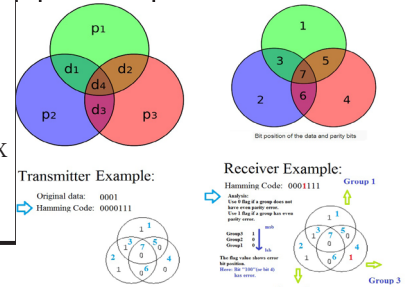

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity hamming is
Port ( hamdin: in std_logic_vector(3 downto 0);
      hamout: out std_logic_vector(7 downto 1) );
end hamming;
architecture Behavioral of hamming is
signal p: std_logic_vector(4 downto 1);
begin
    p(1) <= hamdin(3) xor hamdin(1) xor hamdin(0);
    p(2) <= hamdin(3) xor hamdin(2) xor hamdin(0);
    p(4) <= hamdin(3) xor hamdin(2) xor hamdin(1);
    hamout <= p(1) & p(2) & hamdin(3) & p(4) & ham-
din(2) & hamdin(1) & hamdin(0);
end Behavioral;

```

```


LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY moorefsm IS
PORT ( reset, a, clk : IN STD_LOGIC;
      y: OUT STD_LOGIC
);
END moorefsm;
ARCHITECTURE beh OF moorefsm IS
type state_type is (S0, S1);
signal cs, ns: state_type;
BEGIN
  Process(reset, clk)
  Begin
    If (reset = '1') then
      cs <= S0;
    elsif (rising_edge(clk)) then
      cs <= ns;
    end if;
  End process;
  Process(cs, a)
  Begin
    Case (cs) is
      When S0 => y <= '0';
        If (a='1') then
          ns <= S1;
        else
          ns <= S0;
        end if;
      When S1 => y <= '1';
        If (a='1') then
          ns <= S1;
        else
          ns <= S0;
        end if;
      When others=> y<= '0'; ns <= S0;
    end case;
  end process;
END beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY moorefsm_tb IS
END moorefsm_tb;
ARCHITECTURE beh OF moorefsm_tb IS
component moorefsm
PORT (
      reset, a, clk : IN STD_LOGIC;
      y: OUT STD_LOGIC
);
end component;
signal reset, a, clk : STD_LOGIC;
signal y: STD_LOGIC;
BEGIN
  Uut: moorefsm port map ( reset=> reset,
                           a=> a, clk=> clk,
                           y=> y );
  reset <= '1', '0' after 5 ns, '0' after 100 ns;
  clk <= '0', '1' after 10 ns, '0' after 20 ns,
        '0' after 30 ns, '1' after 40 ns,
        '0' after 50 ns, '1' after 60 ns,
        '0' after 70 ns, '1' after 80 ns,
        '0' after 90 ns, '1' after 100 ns;
  a <= '0', '1' after 12 ns, '0' after 56 ns;
END beh;


```

 

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY mealyfsm IS PORT
( reset, a, clk : IN STD_LOGIC;
  y: OUT STD_LOGIC );
END mealyfsm;
ARCHITECTURE beh OF mealyfsm IS
type state_type is (SO,SI);
signal cs, ns: state_type;
BEGIN
  Process(reset, clk)
  Begin
    If(reset = '1') then
      cs <= SO;
    elsif (rising_edge(clk)) then
      cs <= ns;
    end if;
  End process;
  Process(cs, a)
  Begin
    Case (cs) is
      When SO => If (a='1') then
        ns <= SI; y <= '1';
      else
        ns <= SO; y <= '0';
      end if;
      When SI => If (a='1') then
        ns <= SI; y <= '0';
      else
        ns <= SO; y <= '1';
      end if;
      When others=> y<= '0'; ns <= SO;
    end case;
  end process;
END beh;


```

 

```

library IEEE;
use IEEE.std_logic_1164.all;
entity fsm is
port ( clk, reset, x1 : IN std_logic;
      outp : OUT std_logic
);
end entity;
architecture beh1 of fsm is
type state_type is (s1,s2,s3,s4);
signal state, next_state: state_type;
begin
  process1: process (clk, reset)
  begin
    if (reset = '1') then
      state <= s1;
    elsif (clk = '1' and clk'Event) then
      state <= next_state;
    end if;
  end process process1;
  process2 : process (state, x1)
  begin
    case state is
      when s1 =>
        if x1='1' then
          next_state <= s2;
        else
          next_state <= s3;
        end if;
      when s2 => next_state <= s4;
      when s3 => next_state <= s4;
      when s4 => next_state <= s1;
    end case;
  end process process2;
  process3 : process (state)
  begin
    case state is
      when s1 => outp <= '1';
      when s2 => outp <= '1';
      when s3 => outp <= '0';
      when s4 => outp <= '0';
    end case;
  end process process3;
end beh1;

```

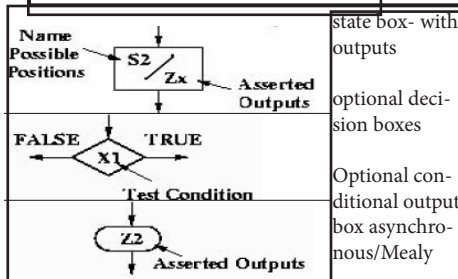

Library ieee;

```

Use ieee.std_logic_1164.all;
entity prob1 is
port (a, b, reset: in std_logic;
      q1, q2: out std_logic);
end prob1;
architecture circuit of prob1 is
signal clk, m, d1, t1, t2: std_logic;
begin
  clk <= a nand m;
  m <= b nand clk;
  d1 <= not t2;
  process ( clk , reset)
  begin
    if (reset= '1') then t1 <= '0';
    elsif (rising_edge(clk)) then
      t1 <= d1;
    end if;
  end process;
  process ( clk , reset)
  begin
    if (reset= '1') then t2 <= '0';
    elsif (falling_edge(clk)) then
      t2 <= t1;
    end if;
  end process;
  q1 <= t1; q2 <= t2;
end circuit;

```

5. CRC Error Detection

Message = 110101

Generating Polynomial = 101

```

11010100... 101 * 111 01
101
111
101
100
101
110
101
110
101
11

```

Quotient (has no function in CRC calculation)


Remainder = CRC checksum

Message with CRC = 11010111

```

Library ieee; --tb for that circuit
Use ieee.std_logic_1164.all;
entity prob1_tb
entity prob1_tb
architecture beh of prob1_tb is
signal a, b, reset: std_logic;
signal q1, q2: std_logic;
component prob1 (a, b, reset: in std_l
q1, q2: out std_logic);
end component;
begin
  uut: prob1 port map ( a=> a, b=> b,
                       reset=>reset, q1=>q1, q2=>q2 );
  process
  begin
    reset <= '1';
    wait for 5 ns;
    reset <= '0';
    wait for 100 ns;
    wait;
  end process;
  b <= not a;
  process
  begin
    a <= '1'; wait for 10 ns;
    a <= '0'; wait for 5 ns;
    a <= '1'; wait for 5 ns;
    a <= '0'; wait for 5 ns;
    a <= '1'; wait for 5 ns;
    a <= '0'; wait for 5 ns;
    wait;
  end process;
end process;
end beh;

```

 

```

Library ieee;
Use ieee.std_logic_1164.all;
entity prob2_fsm_tb
entity prob2_fsm_tb;
architecture beh of prob2_fsm_tb is
signal w, Reset, Clk: std_logic;
signal M, N:: std_logic;
component prob2_fsm ( w, Reset,
                      Clk: in std_logic;
                      M, N: out std_logic );
end component;
begin
  uut: prob2_fsm port map ( w,
                           Reset, Clk, M, N);
  w <= '1', '0' after 15 ns;
  Reset <= '0', '1' after 35 ns;
  process
  begin
    Clk <= '1'; wait for 10 ns;
    Clk <= '0'; wait for 10 ns;
  end process;
  process ( Clk , Reset)
  begin
    if( Reset = '1') then
      cs <= SA ;
    elsif (rising_edge(Clk)) then
      cs <= ns ;
    end if;
  end process;
  M <= '1' when (cs=SC) else '0';
  N <= w when (cs=SB) else '0';
end beh;

```

```

Use ieee.std_logic_1164.all;
entity prob2_fsm is
port( w, Reset, Clk: in std_logic;
      M, N: out std_logic );
End prob2_fsm;
Architecture beh of prob2_fsm is
type st is ( SA, SB, SC );
signal cs, ns: st;
begin
  process ( w , cs )
  begin
    case (cs)
      when SA=> if (w = '0') then
        ns <= SA ;
      else
        ns <= SB ;
      end if;
      when SB=> if(w = '0') then
        ns <= SA ;
      else
        ns <= SC ;
      end if;
      when SC=> if (w = '0') then
        ns <= SA ;
      else
        ns <= SC ;
      end if;
      when others=> ns <= SA;
    end case;
  end process;

```

```


LIBRARY IEEE; --LFSR
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY lfsr IS
PORT ( reset, clk: IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(4 downto 1)
      );
END lfsr;
ARCHITECTURE beh OF lfsr IS
signal W: std_logic_vector(4 downto 1);
BEGIN
process( clk, reset )
begin
if (reset='1') then
W <= ( 1=>'1', others => '0' );
elsif (rising_edge( clk)) then
W <= W(3 downto 2) & ( W(1) xor W(4) ) & W(4);
end if;
end process;
Q <= W;
END beh;

```

```

LIBRARY IEEE; --lfsr tb
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY lfsr_tb IS
End lfsr_tb;
ARCHITECTURE beh OF lfsr_tb IS
Component lfsr
PORT ( reset, clk: IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(4 downto 1)
      );
END Component;
signal reset, clk: std_logic;
signal Q: std_logic_vector(4 downto 1);
BEGIN
out: lfsr port map( reset=>reset, clk=>clk, Q=>Q );
Process
Begin
Clk <= '0';
Wait for 10 ns;
Clk <= '1';
Wait for 10 ns;
End process;
Process
Begin
reset <= '1';
Wait for 6 ns;
reset <= '0';
Wait for 40 ns;
Wait;
End process;
END beh;

```

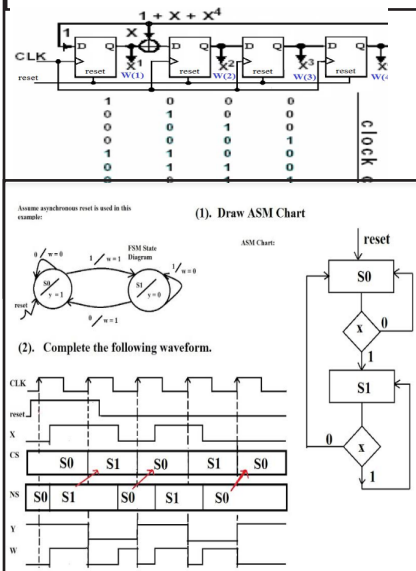

```

library ieee; --Clock division
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity display_counter_vhd is
Port( clk: in std_logic;
      load: in std_logic;
      updown: in std_logic;
      din: in std_logic_vector (3 downto 0);
      cntout: out std_logic_vector (3 downto 0);
      led: out std_logic_vector (3 downto 0);
      clkout: out std_logic
      );
end display_counter_vhd;
architecture behavioral of display_counter_vhd is
signal cnt_div: std_logic_vector (9 downto 0);
signal cnt: std_logic_vector (3 downto 0);
signal clk2: std_logic;
begin
process(clk)
begin
if rising_edge( clk) then
if(cnt_div = 999) then --(N-1), here N=1000
cnt_div <= (others => '0');
clk2 <= '1';
elsif (cnt_div < 499) then --(N/2 - 1)
cnt_div <= cnt_div + 1;
clk2 <= '1';
else
cnt_div <= cnt_div + 1;
clk2 <= '0';
end if;
end if;
end process;
process( clk2, load, updown)
--process active on event of clk2,load, or updown
begin
if(load = '1') then
cnt <= din;
elsif rising_edge( clk2) then
if(updown = '1') then
cnt <= cnt + 1;
else
cnt <= cnt - 1;
end if;
end if;
end process;
cnt_out <= cnt; --output count
clkout <= clk2; --output clk
led <= cnt; --led output value
end behavioral;

```

```

library ieee;
use ieee.std_logic_1164.all;
entity mytt is
port( A, B: in std_logic_vector(5 downto 0);
      Y: out std_logic_vector(11 downto 0));
end mytt;
architecture arch_tt of mytt is
constant C: std_logic_vector(2 downto 0) := "100";
begin
process(A,B)
begin
Y(2 downto 0) <= A(2 downto 0);
Y(3) <= A(3) and B(3);
Y(5 downto 4) <= (A(5) and B(5)) & (A(4) or B(4));
Y(8 downto 6) <= B(2 downto 0);
Y(11 downto 9) <= C;
end process;
end arch_tt;

```

```

library ieee; --pos edge dff
use ieee.std_logic_1164.all;
entity flop is
port( CLK, D : in std_logic;
      Q : out std_logic
      );
end flop;
architecture archi of flop is
begin
process (CLK)
begin
if (rising_edge(CLK)) then
Q <= D;
end if;
end process;
end archi;

```

```

library ieee; --p.edg sync set
use ieee.std_logic_1164.all;
entity flop is
port( C, D, S : in std_logic;
      Q : out std_logic );
end flop;
architecture archi of flop is
begin
process (C)
begin
if (C'event and C='1') then
if (S='1') then
Q <= '1';
else
Q <= D;
end if;
end if;
end process;
end archi;

```

```


library ieee; --4b p.edg clk, asy set, clk en
use ieee.std_logic_1164.all;
entity flop is
port( C, CE, PRE : in std_logic;
      D: in std_logic_vector(3 downto 0);
      Q : out std_logic_vector (3 downto 0)
      );
end flop;
architecture archi of flop is
begin
process (C, PRE)
begin
if (PRE='1') then
Q <= "1111";
elsif (C'event and C='1') then
if (CE='1') then
Q <= D;
end if;
end if;
end process;
end archi;

```

```

library ieee; --tristate
use ieee.std_logic_1164.all;
entity three_st is
port( T, I : in std_logic;
      O : out std_logic
      );
end three_st;
architecture archi of three_st is
begin
process (I, T)
begin
if (T='0') then
O <= I;
else
O <= 'Z';
end if;
end process;
end archi;


```

 


c	a	f
0	0	Z
0	1	1
1	0	0
1	1	1

<pre> library ieee; --4b up/down counter, asy. reset use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity counter is port(C, CLR, UP_DOWN : in std_logic; Q: out std_logic_vector(3 downto 0)); end counter; architecture archi of counter is signal tmp: std_logic_vector(3 downto 0); begin process (C, CLR) begin if (CLR='1') then tmp <= "0000"; elsif (C'event and C='1') then if (UP_DOWN='1') then tmp <= tmp + 1; else tmp <= tmp - 1; end if; end if; end process; Q <= tmp; end archi; </pre>	<pre> library ieee; -- 8b Sft-L Reg, Pedg Clk, Asy CLR, S I/O use ieee.std_logic_1164.all; entity shift is port(C, SI, CLR : in std_logic; SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C, CLR) begin if (CLR='1') then tmp <= (others => '0'); elsif (C'event and C='1') then tmp <= tmp(6 downto 0) & SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --decoder use ieee.std_logic_1164.all; entity dec is port (sel: in std_logic_vector (2 downto 0); res: out std_logic_vector (7 downto 0)); end dec; architecture archi of dec is begin res <= "00000001" when sel = "000" else "00000010" when sel = "001" else "00000100" when sel = "010" else "00001000" when sel = "011" else "00010000" when sel = "100" else "00100000" when sel = "101" else "01000000" when sel = "110" else "10000000"; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity my_block is port(I1 : in std_logic; I2 : in std_logic; O : out std_logic); end my_block; architecture arch1 of my_block is ... end arch1; library ieee; use ieee.std_logic_1164.all; entity top is port(DI_1, DI_2, DI_3, DI_4 : in std_logic; DOUT1, DOUT2 : out std_logic); end top; architecture top_arch of top is component my_block port (I1 : in std_logic; I2 : in std_logic; O : out std_logic); end component; begin inst1: my_block port map (I1=>DI_1, I2=>DI_2, O=>DOUT1); inst2: my_block port map (DI_3, DI_4, DOUT2); end top; </pre>
<pre> library ieee; --8b Sft L Reg, P.Edg Clk, S.i/O use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity shift is port(C, SI : in std_logic; SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C) begin if (C'event and C='1') then for i in 0 to 6 loop tmp(i+1) <= tmp(i); end loop; tmp(0) <= SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --8b Sft L Reg, P.Edg Clk, Asy Load, S I/O use ieee.std_logic_1164.all; entity shift is port(C, SI, ALOAD : in std_logic; D : in std_logic_vector(7 downto 0); SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C, ALOAD, D) begin if (ALOAD='1') then tmp <= D; elsif (C'event and C='1') then tmp <= tmp(6 downto 0) & SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --decoder use ieee.std_logic_1164.all; entity dec is port (sel: in std_logic_vector (2 downto 0); res: out std_logic_vector (7 downto 0)); end dec; architecture archi of dec is begin with sel select res <= "00000001" when "000", "00000010" when "001", "00000100" when "010", "00001000" when "011", "00010000" when "100", "00100000" when "101", "01000000" when "110", "10000000" when others; end archi; </pre>	<pre> library ieee; --priority encoder use ieee.std_logic_1164.all; entity priority is port (sel : in std_logic_vector (7 downto 0); code :out std_logic_vector (2 downto 0)); end priority; architecture archi of priority is begin code <= "000" when sel(0) = '1' else "001" when sel(1) = '1' else "010" when sel(2) = '1' else "011" when sel(3) = '1' else "100" when sel(4) = '1' else "101" when sel(5) = '1' else "110" when sel(6) = '1' else "111" when sel(7) = '1' else "000"; end archi; </pre>
<pre> library ieee; --unsigned 8b adder/subtractor use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity addsub is port(A, B : in std_logic_vector(7 downto 0); OPER : in std_logic; RES : out std_logic_vector(7 downto 0)); end addsub; architecture archi of addsub is begin RES <= A + B when OPER='0' else A - B; end archi; </pre>	<pre> library ieee; --4-1 mux if statement use ieee.std_logic_1164.all; entity mux is port (a, b, c, d : in std_logic; s : in std_logic_vector (1 downto 0); o : out std_logic); end mux; architecture archi of mux is begin process (a, b, c, d, s) begin if (s = "00") then o <= a; elsif (s = "01") then o <= b; elsif (s = "10") then o <= c; else o <= d; end if; end process; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity mux is port (a, b, c, d : in std_logic; s : in std_logic_vector (1 downto 0); o : out std_logic); end mux; architecture archi of mux is begin process (a, b, c, d, s) begin case s is when "00" => o <= a; when "01" => o <= b; when "10" => o <= c; when others => o <= d; end case; end process; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; use ieee.std_logic_arith.all; use ieee.std_logic_unsigned.all; entity adder is port(A, B : in std_logic_vector(7 downto 0); SUM : out std_logic_vector(7 downto 0); CO : out std_logic); end adder; architecture archi of adder is signal tmp: std_logic_vector(8 downto 0); begin tmp <= conv_std_logic_vector((conv_integer(A) + conv_integer(B)),9); SUM <= tmp(7 downto 0); CO <= tmp(8); end archi; -- Or: Res <= ("0" & A) + ("0" & B); </pre>
<pre> library ieee; --Concatenation use ieee.std_logic_1164.all; entity mytt2 is port(A, B : in std_logic_vector(2 downto 0); Y: out std_logic_vector(14 downto 0)); end mytt2; architecture arch_t of mytt2 is constant C: std_logic_vector(2 downto 0) := "100"; begin Y <= A & B & C & C & "110"; end arch_t; </pre>	<pre> library ieee; --comparator use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; entity compar is port(A, B : in std_logic_vector(7 downto 0); CMP : out std_logic); end compar; architecture archi of compar is begin CMP <= '1' when A >= B else '0'; end archi; </pre>		

 
```
//pmidterm dff with not and
module prob2(clk,d,rst,y);
input clk,d,rst;
output y;
reg y,n;
wire m;
assign m=d&~y;
always @(posedge clk or negedge rst)
begin
if (~rst)
begin
n<=0; y<=0;
end
else
begin
n<=m; y<=n;
end
end
endmodule
```



```
//state machine to find 0110
module fsm_detector(reset, clk, a, y);
input reset, a, clk;
output y;
reg y;
parameter s_idle = 3'b000, s1=3'b001,
s2=3'b010, s3=3'b011, s4=3'b100;
reg [2:0] cs, ns;
always @(posedge clk or posedge reset)
begin
if(reset) cs <= s_idle;
else cs <= ns;
end
always @(cs or a)
begin
case(cs)
s_idle: if(a) ns = s1;
else ns = s1;
s1: if(a) ns = s2;
else ns = s1;
s2: if(a) ns = s3;
else ns = s1;
s3: if(~a) ns = s4;
else ns = s_idle;
s4: if(a) ns = s2;
else ns = s1;
default: ns = s_idle;
endcase
end
always @(cs or a)
begin
case(cs)
s_idle: y = 0;
s1: y = 0;
s2: y = 0;
s3: if(~a) y = 1;
else y = 0;
s4: y = 0;
default: y = 0;
endcase
end
endmodule
```

 

```
//Unsigned 8x4-bit Multiplier
module compar(A, B, RES);
input [7:0] A;
input [3:0] B;
output [11:0] RES;
assign RES = A * B;
```


```
Dataflow
assign y=a&b;
behaviorial design
always @(posedge clk)
begin
```

```
//Shift register (4 bit)
module dffb(clk,clr,load,sft,db,qb);
input clk, clr, load, sft;
input [3:0] db;
output [3:0] qb;
reg [3:0] qb;
always @(posedge clr or posedge clk)
begin
if (clr) qb<=0;
else if (load)
qb<=db;
else if (sft)
qb<={1'b0; qb[3:1]};
//qb[3]<=1'b0;
//qb[2]<=qb[3];
//qb[1]<=qb[2];
//qb[0]<=qb[1];
end
endmodule


timescale 1ns/1ps
module dffa_tb;
reg clk, clr, load;
reg [3:0] da;
wire [3:0] qa;
dffa uut ( clk, clr, load, da, qa );
initial clk = 0;
always #10 clk = ~ clk;
initial
begin
clr = 1; da = 4'b1011;
#24 clr = 0; load = 1;
#24 load = 0;
#60 $stop;
end
endmodule
```

```
//8-bit Shift-Left Reg w/ PosEdge Clk,
//Async paralel Load, Serial In, Serial Out
module shift (C, ALOAD, SI, D, SO);
input C, SI, ALOAD;
input [7:0] D;
output SO;
reg [7:0] tmp;
always @(posedge C or posedge ALOAD)
begin
if (ALOAD)
tmp <= D;
else
tmp <= {tmp[6:0], SI};
end
assign SO = tmp[7];
endmodule
```


```
//Moore State Machine
module moore_fsm(rst, clk, a, y);
input rst, clk, a;
output y;
reg y;
parameter s0=1'b0, s1=1'b1;
reg cs, ns;
//state register block
always @(posedge rst or posedge clk)
begin
if (rst) cs<=s0;
else cs<=ns;
end
//combinational next state block
always @(cs or a)
begin
case (cs)
s0: if (a) ns=s1;
else ns=s0;
s1: if (a) ns=s1;
else ns=s0;
default: ns=s0;
endcase
end
//output combinational block
always @(cs)
begin
case(cs)
s0: y=0;
s1: y=1;
default: y=0;
endcase
end
endmodule
```

 

```
module moore_fsm(clk,rst,a,y); //moore fsm
input clk, rst,a;
output [1:0] y;
reg [1:0] y;
parameter s0=3'b000, s1=3'b0001, s2=3'b010,
s3=3'b011, s4=3'b100;
reg [2:0] cs, ns;
always @(posedge clk or posedge rst)
begin
if (rst) cs<=s0;
else cs<=ns;
end
always @(cs or a)
begin
case (cs)
s0: if(a) ns = s1;
else ns = s0;
s1: if(~a) ns = s2;
else ns = s0;
s2: if(a) ns = s3;
else ns = s0;
s3: if(a) ns = s4;
else ns = s2;
s4: if(a) ns = s1;
else ns = s2;
default: ns = s0;
endcase
end
always@(cs )
begin
case(cs)
s0: y = 2'b00;
s1: y = 2'b11;
s2: y = 2'b01;
s3: y = 2'b11;
s4: y = 2'b10;
default: y = 2'b00;
endcase
end
endmodule
```

 

```
//finite state machine, 3 states
module fsm(clk,rst,a,y);
input clk,rst,a;
output y;
reg y;
parameter s0=2'b00, s1=2'b01, s2=2'b10;
reg [1:0] cs,ns;
always @(posedge clk or posedge rst)
begin
if (rst) cs<=s0;
else cs<=ns;
end
always @(cs or a)
begin
case (cs)
s0: if (a) ns=s1;
else ns=s0;
s1: if (~a) ns=s2;
else ns=s0;
s2: if (a) ns=s2;
else ns=s1;
default: ns=s0;
endcase
end
always @(cs or a)
begin
case (cs)
s0: y=0;
s1: if (a) y=1;
else y=0;
s2: y=1;
default: y=0;
endcase
end
endmodule
```

 

Metastability

- The output of an edge-triggered flipflop has two valid states: high and low. To ensure reliable operation, designs must meet the timing req. The input to the flipflop must be stable for a min time before the clock edge (register setup time or t_{SU}) and a min time after the clock edge (register hold time or t_H). Specific values for t_{SU} and t_H are provided in each device family data sheet.
- In non-synchronous systems, if the asynch. input signals violate a flipflop's timing requirements, the output of the flipflop can become metastable. Metastable outputs oscillate/hover between high and low states for some time = system failure. Therefore, you must analyze the metastability characteristics of a device to determine the reliability of a non-synchronous design. In synchronous systems, the input signals always meet the flipflop's timing requirements; therefore, metastability does not occur.
- Violating a flipflop's setup or hold time can cause its output to become metastable. When a flipflop is in a metastable ("in between") state, the output hovers at a voltage level between high and low, causing the output transition to be delayed beyond the specified clock-to-output delay (t_{CO}). The additional time beyond t_{CO} that a metastable output takes to resolve to a stable state is called the settling time (t_{MET}). Not every transition that violates the setup or hold times results in a metastable output. Generally, flipflops will quickly return to a stable state
- When a flipflop's data input complies with minimum setup (t_{SU}) and hold (t_H) times, the output passes from one stable state to another (i.e., from high to low or low to high) without an additional delay.
- However, when a flipflop's data input violates the setup or hold time, the flipflop is marginally triggered, and the output may not immediately resolve to either of the two stable states within the specified time. This marginal triggering can cause the output to glitch or to remain temporarily at a metastable state between the high and low logic levels, taking longer to return to a stable state. Either condition increases the delay from the clock transition to a stable output.

$$MTBF = \frac{e^{(C_2 \times t_{MET})}}{C_1 \times f_{CLOCK} \times f_{DATA}}$$


- The f_{CLOCK} parameter refers to the system clock frequency while the f_{DATA} parameter refers to the data transfer frequency. The t_{MET} parameter is the additional time allowed by the system for the flipflop to settle to a stable state. The constants C_1 and C_2 vary according to the process technology used to manufacture the device.
- The constants C_1 and C_2 are determined by plotting the natural log of MTBF versus t_{MET} and performing a linear regression analysis on the data. The y- intercept and slope of the resulting line determine the values of C_1 and C_2 . The formulas for the constants C_1 and C_2 are shown below

$$C_2 = \frac{\Delta \ln(MTBF)}{\Delta t_{MET}}, \quad C_1 = \frac{e^{(C_2 \times t_{MET})}}{MTBF \times f_{CLOCK} \times f_{DATA}}$$

- [Given settling time (t_{MET}).] The t_{MET} delay is the additional time required for the flipflop to resolve to a legal state, i.e. the difference between the minimum system clock period and the actual clock period. You can also use the metastability equation to determine the t_{MET} delay required for a given MTBF value.

$$t_{MET} = \frac{\ln(MTBF \times f_{CLOCK} \times f_{DATA} \times C_1)}{C_2}$$

- Reduce metastability in a system.:If an asynchronous signal is fed to several flipflops, the probability that a metastable event increases. Avoid metastability by using output of the synchronizing flipflop throughout the system rather than asynchr. signal.
- Avoid the negative effects of metastability by adding the t_{MET} calculated for a specific MTBF to the worst-case timing delay calculations, giving the output of the synchronizing flipflops time to settle. Faster devices provide faster t_{CO} and t_{SU} times, which provide additional time for the t_{MET} delay without sacrificing overall system speed.
- Metastability only affects flipflops used to synchronize data from asynch. systems. Good metastability characteristics: add a small t_{MET} delay to the t_{CO} delay to achieve a high MTBF value.

 

Time Behavior of Combinational Networks

Gate Delays

- When input to a logic gate is changed, the output will not change immediately.
- The switching elements within a gate take a finite time to react to a change (transition) in input.
- Such delay is called the propagation delay of the logic gate (t_p)
- The propagation delay for a 0 to 1 output change (t_{pLH}) may be different than the delay for a 1 to 0 change (t_{pHL}).
- gate delay: Δ time at inp to cause change at outp
- min delay: typical/nominal delay – max delay for both worst case and best case
- rise time: time for output to transition from low to high voltage
- fall time: time for output to transition from high to low voltage
- pulse width: time that an output stays high or stays low between changes

Effect of gate delays


- The analysis of combinational circuits ignoring delays can predict only the steady-state behavior of a circuits. That is they predict a circuit's output as a function of its inputs under the assumption that the inputs have been stable for a long time, relative to the delays into the circuit's electronics.
- A circuit's output may produce a short pulse (often called a glitch) at a time when steady state analysis predicts that the output should not change.
- A Race condition is when a device's output depends on 2(+) nearly simultaneous events to occur, and where which signal arrives first will change the output of the circuit.

Glitch/Hazard


- A **glitch** is an unwanted pulse at the output of a combinational logic network – a momentary change in an output that should not have changed.
- A circuit with the potential for a glitch is a **hazard**.
- A circuit with hazard may or may not have a glitch depending on input patterns and the electric characteristics of the circuit.
- Hazards are potential unwanted transients that occur in the output when different paths from input to output have different propagation delays.
- The fundamental strategy for eliminating an hazard is to add redundant prime implicants (extra prime implicants won't change F, but can cause F to be asserted independently of the change to the input that cause the hazard).
- A properly designed two level AND-OR circuit based on a SoP expression has no static 0-hazards. A static 0-hazard would exist only if both a variable and its complement were connected to the same AND gate, which would be a nonsense ($A \cdot A' \cdot X = 0$)
- A properly designed two level OR-AND circuit of a Product Of Sums expression has no static 1-hazards. A static 1-hazard would exist only if both a variable and its complement were connected to the same OR gate, which would be a nonsense ($A + A' + X = 1$)

Dynamic Hazard

 
- If there are 3+ paths from an input or its complement to the output, the circuit has the potential for a dynamic hazard.
- 3+ paths only in a multi-level networks.
- If you need a hazard free network, it is best to use a 2-level network and use the techniques shown earlier to eliminate the static hazards.




Detection of Static 1-hazards

 


Detection of static 0-hazards

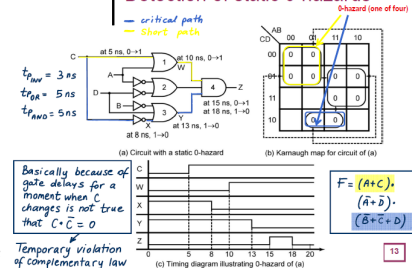

Dynamic hazard example

 

Removing the static hazard

 

TAG Boundary Scan

- Bed-of-nails printed circuit board tester gone
- We put components on both sides of PCB & replaced DIPs with flat packs to reduce inductance
- Nails would hit components
- Reduced spacing between PCB wires
- Nails would short the wires
- PCB Tester must be replaced with built-in test delivery system - JTAG does that
- Need standard System Test Port and Bus
- Integrate components from different vendors
- Test bus identical for various components
- One chip has test hardware for other chips

Tap Controller Signals

- Test Access Port (TAP) includes these signals:
- Test Clock Input (TCK) -- Clock for test logic
- Can run at different rate from system clock
- Test Mode Select (TMS) -- Switches system from functional to test mode
- Test Data Input (TDI) -- Accepts serial test data and instructions -- used to shift in vectors or one of many test instructions
- Test Data Output (TDO) -- Serially shifts out test results captured in boundary scan chain (or device ID or other internal registers)
- Test Reset (TRST) -- Optional asynchronous TAP controller reset

Boundary Scan Instructions

SAMPLE/PRELOAD

- This instruction causes the TDI and TDO to be connected to the Boundary Scan Register (BSR).
- However, the device is left in its normal functional mode. During this instruction, the BSR can be accessed by a data scan operation to take a sample of the functional data entering and leaving the device.
- The instruction is also used to preload test data into the BSR prior to loading an EXTEST instruction.

Purpose:

1. Get snapshot of normal chip output signals
2. Put data on boundary scan chain before next instruction

EXTEST

- This instruction causes the TDI and TDO to be connected to the Boundary Scan Register (BSR). The device's pin states are sampled with the 'capture DR' JTAG state and new values are shifted into the BSR with the 'shift DR' state; these values are then applied to the pins of the device using the 'update DR' state.
- DR: data register

EXTEST Instruction

- Purpose: Test off-chip circuits and board-level interconnections

INTEST

- This instruction causes the TDI and TDO lines to be connected to the Boundary Scan Register (BSR). While the EXTEST instruction allows the user to set and read pin states, the INTTEST instruction relates to the core-logic signals of a device.

INTEST Instruction Purpose:

1. Shifts external test patterns onto component
2. External tester shifts component responses out

DCODE




- Instruction Purpose: Connects the component device identification register serially between TDI and TDO
- In the Shift-DR TAP controller state
- Allows board-level test controller or external tester to read out component ID
- Required whenever a JEDEC identification register is included in the design

HIGHZ


- Instruction Purpose: Puts all component output pin signals into highimpedance state
- Control chip logic to avoid damage in this mode
- May have to reset component after HIGHZ runs
- Optional instruction

BYPASS Instruction

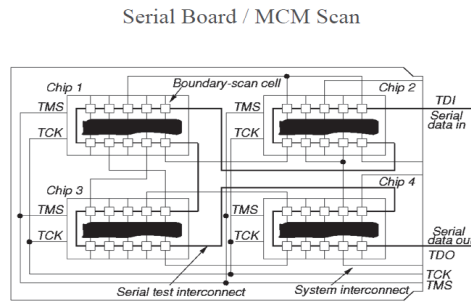 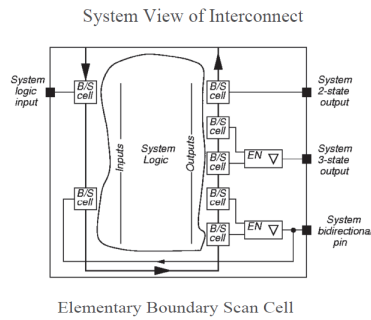
- Purpose: Bypasses scan chain with 1-bit register



Parallel Board / MCM Scan

 

Independent Path Board / MCM Scan

 

SRAM

Reading

- Steps
- Setup address lines
- Activate read line
- Data available after specified amount of time

Writing

- Sequence of steps
- Setup address lines
- Setup data lines
- Activate write line

SRAM Cell

