

**Started on** Thursday, 21 September 2017, 1:07 PM

**State** Finished

**Completed on** Friday, 22 September 2017, 1:37 PM


**Time taken** 1 day

**Grade** 10.0 out of 10.0 (100%)

### Question 1

Correct

Mark 2.0 out of 2.0

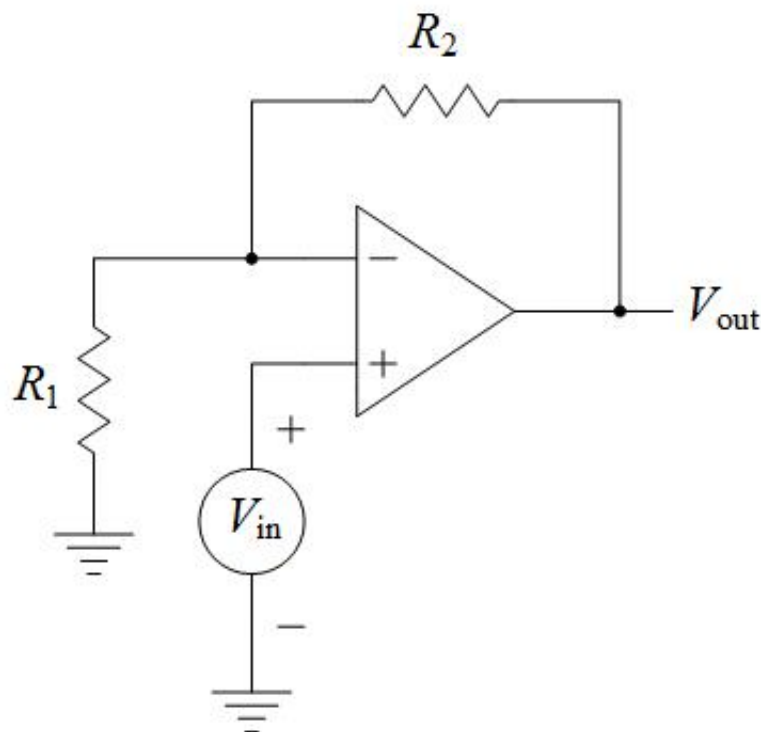

For the operational amplifier circuit shown, what is the percentage error in the closed-loop voltage gain due to the finite open-loop voltage gain of the opamp? Assume that the opamp has an open-loop voltage gain of 69 V/V, and is ideal in all other respects. Use  $R_1 = 1.9\text{k}\Omega$  and  $R_2 = 55.5\text{k}\Omega$ .

Answer:



The correct answer is: -30.45

**Correct**

Marks for this submission: 2.0/2.0.

**Question 2**

Correct

Mark 2.0 out of 2.0

The Slew Rate of an integrated circuit opamp is the maximum frequency which the opamp can amplify with a gain larger than one.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 2.0/2.0.

**Question 3**

Correct

Mark 2.0 out of 2.0

Above the -3dB frequency of an integrated circuit opamp, the open-loop voltage gain will :

Select one:

- ☐ a. Decrease with decreasing frequency
- ☐ b. Be equal to the frequency of the signal divided by the unity gain frequency
- ☐ c. Change by 6dB if the frequency changes by an decade
- ☒ d. Change by 20dB if the frequency changes by a decade ✓
- ☐ e. All of these

The correct answer is: Change by 20dB if the frequency changes by a decade

**Correct**

Marks for this submission: 2.0/2.0.

**Question 4**

Correct

Mark 2.0 out of 2.0

The maximum frequency sine wave which an opamp can output at full amplitude without hitting the slew rate limit is called the Full-power Bandwidth.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.


**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Correct

Mark 2.0 out of 2.0

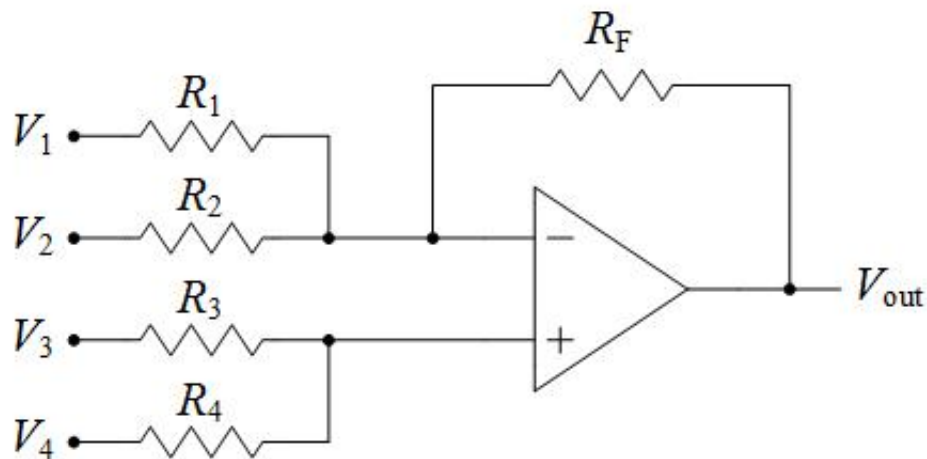

For the operational amplifier circuit shown, what is the output voltage if  $V_1 = 0.106\text{V}$ ,  $V_2 = 0.649\text{V}$ ,  $V_3 = 0.629\text{V}$  and  $V_4 = 1.122\text{V}$ ? Assume that the opamp is ideal, and use  $R_1 = 9.1\text{k}\Omega$ ,  $R_2 = 2.6\text{k}\Omega$ ,  $R_3 = 7.3\text{k}\Omega$ ,  $R_4 = 6.9\text{k}\Omega$  and  $R_F = 3.3\text{k}\Omega$ .


Answer: 1.46



The correct answer is: 1.460

**Correct**

Marks for this submission: 2.0/2.0.

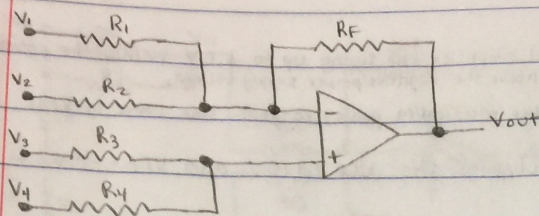

For the opamp circuit, what is the output voltage if  $V_1 = 0.106V$ ,

$V_2 = 0.649V$ ,  $V_3 = 0.629V$ , and

$V_4 = 1.122V$ ? Assume the opamp is

ideal, and use  $R_1 = 9.1k$ ,  $R_2 = 2.6k$ ,

$R_3 = 7.3k$ ,  $R_4 = 6.9k$ , and  $R_F = 3.3k$

$$\frac{V_a - 0.106}{9100} + \frac{V_a - 0.649}{2600} + \frac{V_a - V_{out}}{3300} = 0$$

$$V_a \left[ \frac{1}{9100} + \frac{1}{2600} + \frac{1}{3300} \right] - V_{out} \left[ \frac{1}{3300} \right] = \frac{0.106}{9100} + \frac{0.649}{2600}$$

$$\textcircled{1} V_a [0.000797536] - V_{out} [0.00030303] = 0.000261264$$

$$\frac{V_a - 0.629}{7300} + \frac{V_a - 1.122}{6900} = 0$$


$$V_a \left[ \frac{1}{7300} + \frac{1}{6900} \right] = \frac{0.629}{7300} + \frac{1.122}{6900}$$

$$V_a [0.000281914] = 0.000248773$$

$$\textcircled{2} V_a = \frac{0.000248773}{0.000281914} = 0.8824V$$

$$(0.8824)(0.797536) - 0.261264 = V_{out} [0.30303]$$
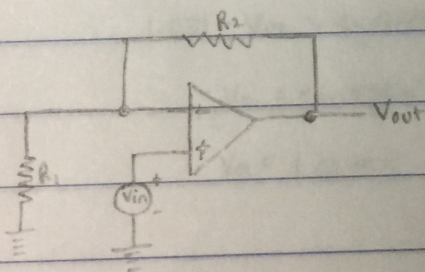
$$\frac{0.442481766}{0.30303} = \boxed{1.46V} = V_{out}$$



For the operational amplifier, what is the percentage error

in the closed-loop voltage gain due to the finite open-loop

voltage gain of the opamp? Open loop voltage gain  $69V/V$

$R_1 = 1.9k\Omega$ ,  $R_2 = 55.5k\Omega$

$$-1 \left[ 1 + \left( \frac{R_2}{R_1} \right) \right] = \boxed{-30.21}$$