

Chapter 9 Sinusoidal Steady-State Analysis – Homework Solutions
James W. Nilsson and Susan A. Riedel, *Electric Circuits*, 6th Edition, 2001

Problems 3 a thru h, 6 a & b, 9, 14, 16, 23, 29, 36, 39, 45, 47, 48, 49

- 3 a) 170 V
 b) 60 Hz
 c) 376.99 rads/sec
 d) -1.05 rads
 e) -60°
 f) 16.67 msec
 g) $t = 2.78$ msec
 h) $v(t) = 170 \sin(120 \pi t)$ Volts
- 6 a) $y = 483.8 \cos(300 t - 48.49^\circ)$
 b) $y = 120.5 \cos(377 t + 4.8^\circ)$
- 9 a) $Z_C = -j 20 \Omega$ and $Z_L = j 2 \Omega$. Redraw the circuit with all the phasor info
 b) $V = 46.5 < 34.46^\circ$ Volts
 c) $v_{ss}(t) = 46.5 \cos(50,000 t + 34.46^\circ)$ Volts
- 14 $i_{ss}(t) = 1.5 \cos(5,000 t + 36.87^\circ)$ mA
- 16 a) $f = 5/\pi \cong 1.59$ Hz
 b) $i_{ss}(t) = 50 \cos(10 t)$ mA
- 23 $Z_{ab} = 50 < -53.15^\circ \Omega$ in polar form
- 29 a) $Z = 5 < 72^\circ \Omega$
 b) $T = 50 \mu s$
- 36 $Z_{TH} = 3,500 - j 12,000 \Omega$ and also redraw the equivalent circuit
- 39 $Z_{TH} = 50 - j 25 \Omega$ and $I_{Norton} = 6.4 - j 4.8$ Amp
 Redraw the circuit in the Norton equiv form.
- 45 $I_g = 3 < -90^\circ$ Amp (what is this in rectangular form?)
- 47 $V_o = 15.81 < 18.4^\circ$ Volts

48 $V_{oss} = 11.31 \cos (5,000 t - 45^\circ) \text{ Volts}$

49 $V_{oss} = 12 \cos (5,000 t) \text{ Volts}$

9.3 $v = 170 \cos(120\pi t - 60^\circ)$ Volts

a) $V_m = \underline{170V}$

b) $f = \frac{\omega}{2\pi} = \frac{120\pi}{2\pi} = \underline{60 \text{ Hz}}$

c) $\omega = 120\pi \text{ rads/sec} = \underline{376.99 \text{ rads/sec}}$

d) $\phi = -60^\circ = -60^\circ \left(\frac{\pi}{180^\circ}\right) = -\frac{\pi}{3} = -1.05 \text{ rads}$

e) $\phi = -60^\circ$

f) $T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$

g) Find $t \geq 0$ for $v = 170V$ i.e. $\cos(0) = 1$

$$120\pi t - \frac{\pi}{3} = 0 \Rightarrow 120\pi t = \frac{\pi}{3} \Rightarrow t = \frac{1}{360}$$

$t = \underline{2.78 \text{ ms}}$

h) shift left $\frac{125}{18} \text{ ms} = \frac{.125}{18} \text{ sec}$

$$v = 170 \cos \left[120\pi \left(t + \frac{.125}{18} \right) - \frac{\pi}{3} \right]$$

$$= 170 \cos \left(120\pi t + 120\pi \left(\frac{.125}{18} \right) - \frac{\pi}{3} \right)$$

$$= 170 \cos \left(120\pi t + \frac{15\pi}{18} - \frac{\pi}{3} \right)$$

$$= 170 \cos \left(120\pi t + \frac{9\pi}{18} \right)$$

$$\frac{9\pi}{18} = \frac{\pi}{2} = 90^\circ$$

$$= 170 \cos(120\pi t + 90^\circ)$$

$\underline{v = 170 \sin(120\pi t) \text{ Volts}}$

9.6

$$a) y = 100 \cos(300t + 45^\circ) + 500 \cos(300t - 60^\circ)$$

$$\begin{aligned} Y &= 100 \angle 45^\circ + 500 \angle -60^\circ \\ &= 100(\cos 45^\circ + j \sin 45^\circ) + 500[\cos(60^\circ) - j \sin(60^\circ)] \\ &= 70.7 + j 70.7 + 250 - j 433 \\ &= 320.7 - j 362.3 \\ &= \sqrt{320.7^2 + 362.3^2} \angle \tan^{-1}\left(\frac{-362.3}{320.7}\right) \end{aligned}$$

$$= 483.8 \angle -48.49^\circ$$

$$y = \mathcal{P}^{-1}\{Y\} = \underline{483.8 \cos(300t - 48.49^\circ)}$$

$$b) y = 250 \cos(377t + 30^\circ) - 150 \sin(377t + 140^\circ)$$

$$\begin{aligned} Y &= 250 \angle 30^\circ - 150 \angle (140^\circ - 90^\circ) \\ &= 250 \angle 30^\circ - 150 \angle 50^\circ \\ &= (216.5 + j 125) - (96.42 + j 114.91) \\ &= 120.5 \angle 4.8^\circ \end{aligned}$$

$$y = \underline{120.5 \cos(377t + 4.8^\circ)}$$

$$c) y = 60 \cos(100t + 60^\circ) - 120 \sin(100t - 125^\circ) + 100 \cos(100t + 90^\circ)$$

$$\begin{aligned} Y &= 60 \angle 60^\circ - 120 \angle -125^\circ - 90^\circ + 100 \angle 90^\circ \\ &= 152.88 \angle 32.94^\circ \end{aligned}$$

$$y = \underline{152.88 \cos(100t + 32.94^\circ)}$$

9.6.

$$d) y = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$$

$$Y = 100 \angle 40^\circ + 100 \angle 160^\circ + 100 \angle -80^\circ$$


$$= (76.6 + j 64.279) + (-93.969 + j 34.20) + (17.36 - j 98.48)$$

$$= -0.009 + j 0.079$$

$$= 0.08 \angle -83.5^\circ \quad \text{pretty much} = \text{zero}$$

$$\underline{\underline{y \approx 0}}$$



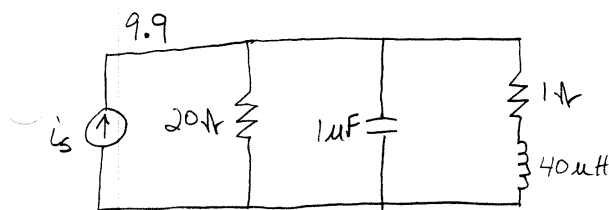

$$i_s = 20 \cos(50,000t - 20^\circ) \text{ A}$$


$$I = 20 \angle -20^\circ \text{ A}$$

$$Z_{R_1} = 20 \Omega \quad Z_{R_2} = 1 \Omega$$

$$Z_C = jX_C = j \frac{1}{\omega C} = j(-20) \Omega$$

$$Z_L = j\omega L = j2 \Omega$$

a)

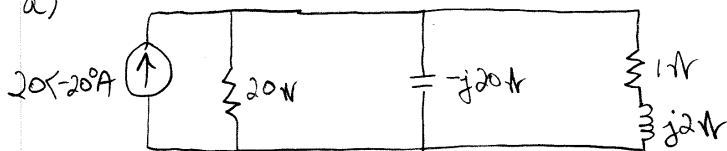

$$b) \quad Z_{eq} = 20 \parallel (-j20) \parallel (1 + j2)$$

$$\text{so } \frac{1}{Z_{eq}} = \frac{1}{20} + j \frac{1}{20} + \frac{1}{1 + j2} = Y_{eq} \text{ (in terms of admittance)}$$

$$Y_{eq} = 0.05 + j0.05 + \frac{1 - j2}{(1 + j2)(1 - j2)}$$

$$= 0.05 + j0.05 + 0.5 - j0.4 = 0.25 - j0.35 \text{ S}$$

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{0.25 - j0.35} = (1.351 + j1.892) \Omega$$

$$= 2.32 \angle 54.46^\circ \Omega$$

$$\text{so } V = I Z_{eq} = (20 \angle -20^\circ \text{ A}) (2.32 \angle 54.46^\circ \Omega)$$


$$= \underline{\underline{46.5 \angle 34.46^\circ \text{ Volts}}}$$

9.9

c) $V_{ss} = 46.5 \cos(50,000t + 34.46^\circ) \text{ Volts}$

50 SHEETS
100 SHEETS
200 SHEETS



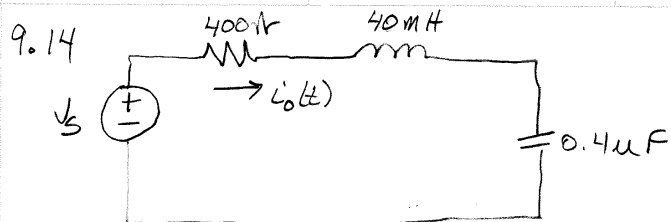

$$u_s = 750 \cos 5000t \text{ mV}$$

Find $i_{ss}(t)$

$$Z_L = j\omega L = j(5000)(40 \text{ mH}) = j200 \Omega$$

$$Z_C = j\left(\frac{-1}{\omega C}\right) = -j500 \Omega$$

$$Z_{eq} = 400 \Omega + j200 \Omega - j500 \Omega = (400 - j300) \Omega \\ = 500 \angle -36.87^\circ$$

$$V = 750 \angle 0^\circ$$


$$I = \frac{V}{Z} = \frac{750 \angle 0^\circ \text{ mV}}{500 \angle -36.87^\circ \Omega} = 1.5 \angle 36.87^\circ \text{ mA}$$

so

$$i_{ss}(t) = \underline{\underline{1.5 \cos(5000t + 36.87^\circ) \text{ mA}}}$$

Note that current leads the voltage

9.16

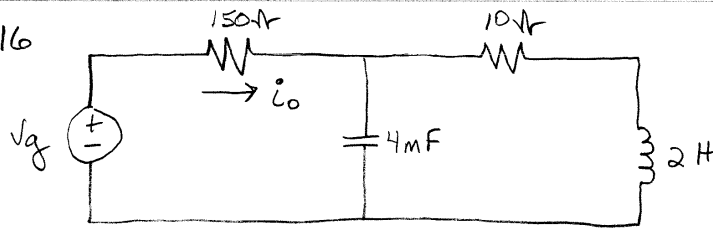

ω changed until v_g "in phase" with i_o
 (remember in class we showed this means the behavior
 of the circuit is purely resistive)

a) $Z_{eq} = 150 \Omega + \left[j\left(\frac{1}{\omega C}\right) \parallel (10 \Omega + j\omega 2H) \right]$

$$= 150 + \frac{1}{j\left(\frac{1}{\omega C}\right)} + \frac{1}{10 + j\omega 2}$$

$$= 150 + j\omega(4 \times 10^{-3}) + \frac{10 - j\omega 2}{100 + 4\omega^2}$$

= real (only) when imaginary terms cancel.

$$\therefore j\omega(4 \times 10^{-3}) = \frac{-j\omega 2}{100 + 4\omega^2}$$

$$100 + 4\omega^2 = 500 \Rightarrow \omega^2 = 100$$

$$\omega = 10 \text{ rad/sec} = 2\pi f$$

$$f = \frac{10}{2\pi} = \frac{5}{\pi} \approx \underline{\underline{1.59 \text{ Hz}}}$$

9.16



b) Given $V_g = 10 \cos \omega t$ volts at $\omega = 10 \text{ rad/s}$ (part a)
find i_{ss}

$$Z_{eq} = 150 + \left[\frac{10}{10 + 4\omega^2} \right]^{-1} \quad \text{we have found where the imaginary terms cancel - so } j \text{ in terms ignored.}$$

$$= 150 + \left[\frac{10}{500} \right]^{-1} = 150 + 50 = 200 \Omega$$

$$\mathbf{I} = \frac{\mathbf{V}}{Z_{eq}} = \frac{10 \angle 0}{200 \angle 0} = 50 \angle 0^\circ \text{ mA}$$

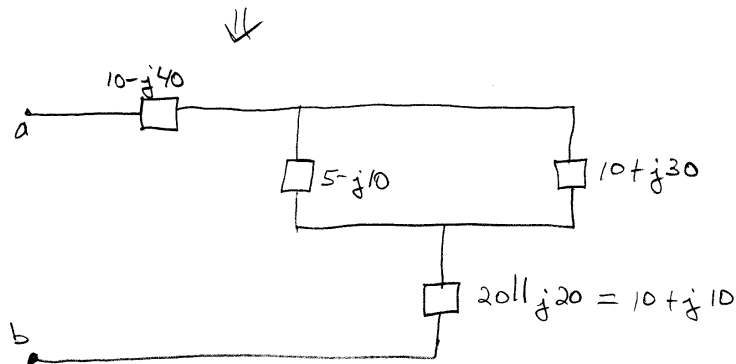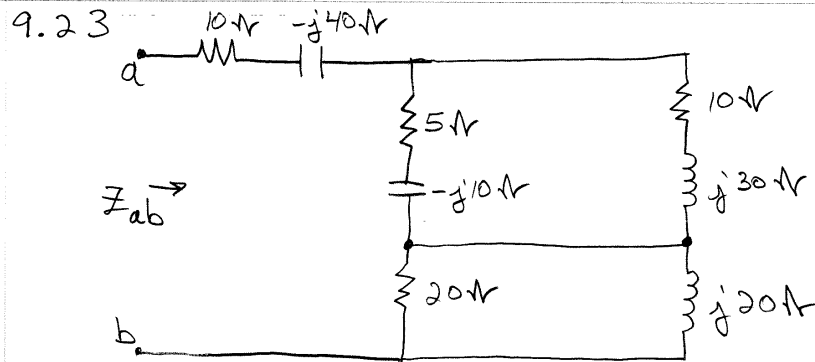
$$\underline{i_{ss} = 50 \cos 10t \text{ mA}}$$



$$20 \parallel j20 = \frac{20(j20)}{20 + j20} = \frac{j400}{20(1+j)} = \frac{j20(1-j)}{1+j(1-j)} = \frac{20 + j20}{2} = 10 + j10$$

$$(5-j10) \parallel 10+j30 = \frac{(5-j10)(10+j30)}{(5-j10) + (10+j30)} = \frac{350 + j50}{15 + j20}$$


$$= \frac{6250 - j250}{625} = 10 - j10$$

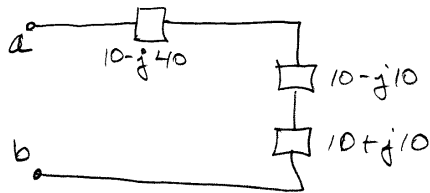

$$Z_{ab} = (10-j40) + (10-j10) + (10+j10) = (30-j40) \Omega$$

$$= 50 \angle -53.15^\circ \Omega$$

9.29

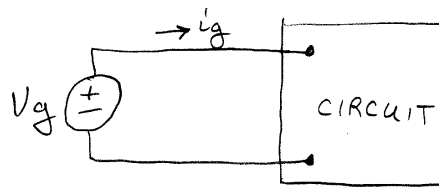

$$V_g = 150 \cos(8000\pi t + 20^\circ) \text{ Volts}$$

$$i_g = 30 \sin(8000\pi t + 38^\circ) \text{ Amps}$$


$$a) Z_{\text{circuit}} = \frac{V}{I} = \frac{150 \angle 20^\circ}{30 \angle 38^\circ - 90^\circ} = \frac{150 \angle 20^\circ}{30 \angle -52^\circ} = \underline{\underline{5 \angle 72^\circ}}$$

b) Current lags voltage by 72° = how many μsec ?

$$2\pi f = 8000\pi \Rightarrow f = 4000 \text{ Hz} \Rightarrow T = \frac{1}{f} = 250 \mu\text{s}$$

so every $T = 250 \mu\text{sec}$ the angular freq ω goes thru 2π
(or equivalently goes thru 360°)
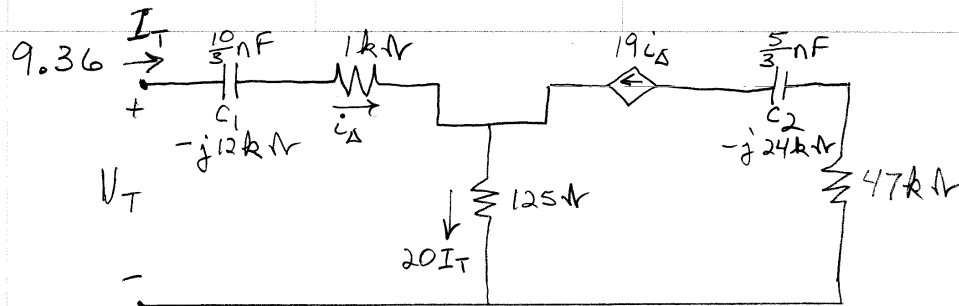
$$\text{thus } t = 72^\circ \left(\frac{250 \mu\text{sec}}{360^\circ} \right) = \underline{\underline{50 \mu\text{sec}}}$$



$$\omega = 25,000 \text{ rad/sec}$$

$$\text{Note } i_A = I_{\text{test}}$$

find Z_{th}

$$Z_{C1} = j \left(\frac{-1}{\omega C_1} \right) = -j12 \text{ k}\Omega$$



$$Z_{C2} = j \left(\frac{-1}{\omega C_2} \right) = -j24 \text{ k}\Omega$$

$$V_T = I_T (1 - j12) \text{ k}\Omega + 20 I_T (125 \text{ }\Omega)$$


$$= I_T [(1 - j12) + 2.5] \text{ k}\Omega$$

$$= I_T (3.5 - j12) \text{ k}\Omega$$

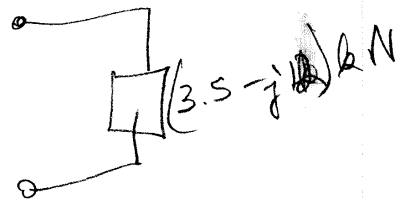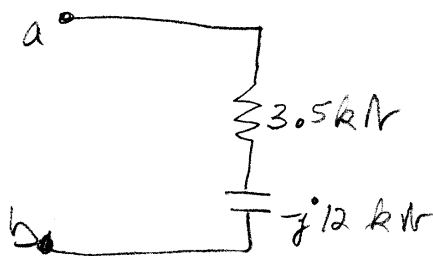
$$Z_{Th} = \frac{V_T}{I_T} = \underline{(3.5 - j12) \text{ k}\Omega} = (3,500 - j12,000) \Omega$$



9.39

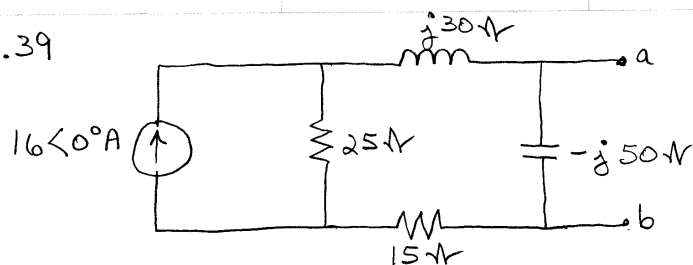

find the Norton Equiv.

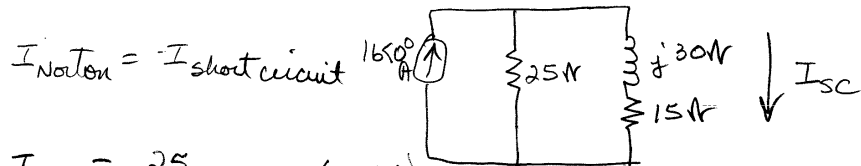



$$I_{sc} = \frac{25}{25 + 15 + j30} (16 \angle 0^\circ) \quad \text{by current divider rule}$$

$$= \frac{25}{40 + j30} (16 \angle 0^\circ) = 6.4 - j4.8 \text{ Amp}$$

$$Z_{Th} = (-j50) \parallel (j30 + 25 + 15)$$
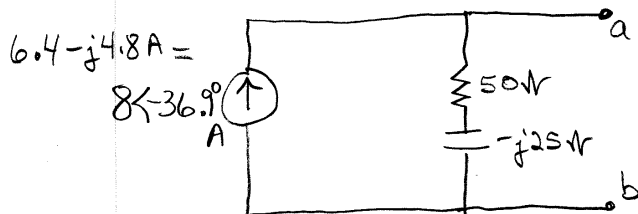
$$= \frac{(-j50)(40 + j30)}{-j50 + 40 + j30} = 50 - j25 \Omega$$



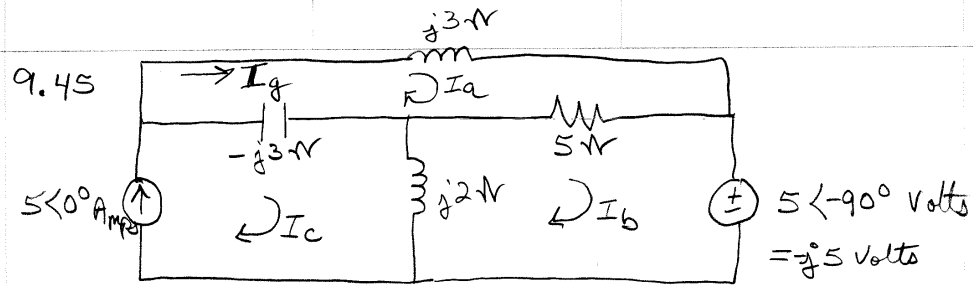

Find the phasor I_g by mesh current analysis

Note that $I_c = 5\angle 0^\circ$

loop a

$$I_a(j3\Omega) + (5\Omega)(I_a - I_b) - j3\Omega(I_a - 5\angle 0^\circ) = 0$$

$$I_a(5) - I_b(5) + (j3\Omega)(5\angle 0^\circ) = 0$$

$$I_a(5) + I_b(-5) = \frac{j15\text{ Volt}}{-j15\text{ Volt}}$$

loop b

$$(j2\Omega)(I_b - 5) + 5\Omega(I_b - I_a) - j5V = 0$$

$$I_a(-5) + I_b(5 + j2\Omega) - j10V - j5V = 0$$

$$I_a(-5) + I_b(5 + j2\Omega) = j15V$$


sub in from loop a

$$I_a(-5) + (I_a + j3V)(5 + j2\Omega) = j15V$$

$$I_a[(-5 + 5) + j2] + j15 - 6 = j15$$

$$I_a(j2) = 6$$
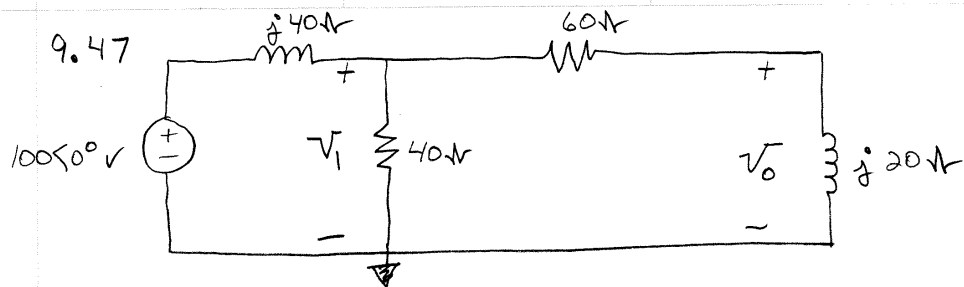
$$I_a = \frac{6}{j2} = -j3\text{ Amp} = \underline{I_g = 3\angle -90^\circ\text{ Amp}}$$



find V_0 by node voltage method

$$\frac{V_1}{40\Omega} + \frac{V_1 - 100}{j40\Omega} + \frac{V_1}{60 + j20\Omega} = 0$$

notice I write only V_1 (V_0 then found later)


do the math & $V_1 = 30 - j40$ Volts

$$V_0 = \frac{j20}{60 + j20} (V_1) \quad \text{by voltage divider rule}$$

$$= \frac{j20}{60 + j20} (30 - j40) = \frac{j}{3 + j} (30 - j40)$$

$$= \frac{1 + 3j}{10} (30 + j40) = -9 + j13 \text{ Volts}$$
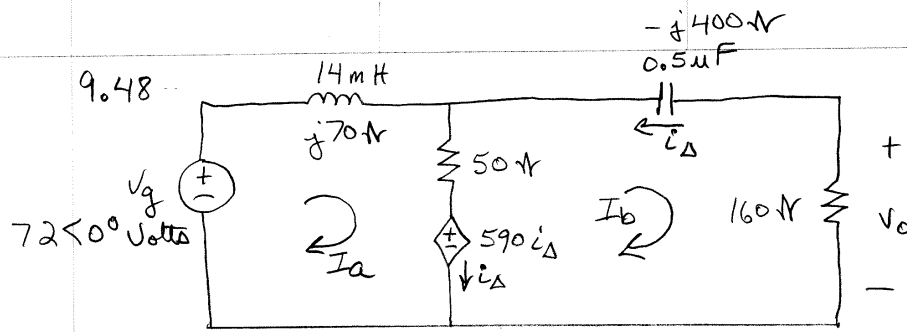
$$= \underline{\underline{15.81 \angle -55.3^\circ \text{ Volts}}}$$



$$v_g = 72 \cos 5000t \text{ volts}$$

Note $I_b = -i_\Delta$

find $v_{o_{ss}}$ by mesh-current method

$$Z_L = j\omega L = j(5000)(14 \times 10^{-3} \text{ H}) = j70 \Omega$$

$$Z_C = j\left(\frac{-1}{\omega C}\right) = j\left(\frac{-1}{5000 \cdot 0.5 \times 10^{-6}}\right) = -j400 \Omega$$

loop a

$$72 = (50 + j70)I_a - 50I_b + 590(-I_b)$$

loop b


$$(-50)I_a - 590(-I_b) + (50 + 160 - j400)I_b = 0$$

Solve these equations

$$I_b = (50 - j50) \text{ mA}$$

$$V_o = (160 \Omega) I_b = 8 - j8 \text{ volts} = 11.31 \angle -45^\circ$$
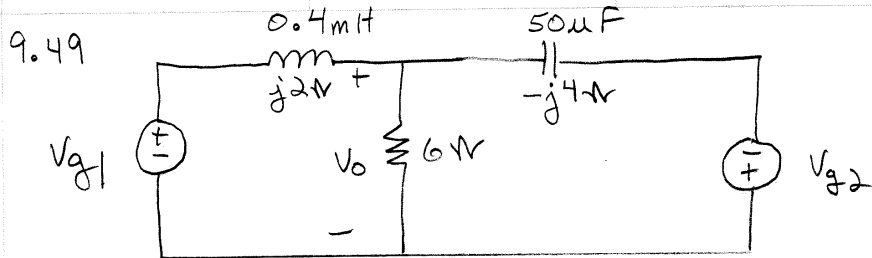
$$v_{o_{ss}} = 11.31 \cos(5000t - 45^\circ) \text{ volts}$$



$$V_{g1} = 10 \cos(5000t + 53.13^\circ) \text{ Volts}$$

$$\vec{V}_{g1} = 10 \angle 53.13^\circ = 6 + j8 \text{ Volts}$$

$$V_{g2} = 8 \sin 5000t = 8 \cos(5000t - 90^\circ) \text{ Volts}$$

$$\vec{V}_{g2} = 8 \angle -90^\circ = -j8 \text{ Volts}$$

Find V_{0ss} by the node voltage method

$$Z_L = j\omega L = j2\Omega$$

$$Z_C = j\left(\frac{1}{\omega C}\right) = -j4\Omega$$

$$\frac{V_0 - (6 + j8)}{j2\Omega} + \frac{V_0}{6} + \frac{V_0 + (-j8)}{-j4} = 0$$

Be careful here - note the source polarity!

Solving this equation gives us

$$V_0 = 12 \angle 0$$

so

$$\underline{\underline{V_{0ss} = 12 \cos(5000t) \text{ Volts}}}$$