

Started on Wednesday, 20 February 2019, 10:55 AM**State** Finished**Completed on** Wednesday, 20 February 2019, 11:55 AM**Time taken** 1 hour**Grade** 90.00 out of 100.00**Question 1**

Correct

Mark 10.00 out of 10.00

Q1bConsider the sinusoidal voltage $v(t) = 100 \cos(240 \pi t + 45^\circ) \text{ V}_{\text{rms}}$.

a) What is the maximum amplitude of the voltage?

$$V_m = 141.42 \text{ V}$$

b) What is the frequency of $v(t)$ in hertz?

$$f = 120 \text{ Hz}$$

c) What is the frequency of $v(t)$ in radians per second?

$$\omega = 753.98 \text{ rad/sec}$$

d) What is the phase angle in radians?

$$\phi \text{ (phi)} = 0.785 \text{ radians}$$

e) What is the period in milliseconds?

$$T = 8.33 \text{ ms (milli sec)}$$

Numeric Answer

a) $V_m = 141.4214 \text{ V}$

b) $f = 120 \text{ Hz}$

c) $\omega = 753.9822 \text{ rad/sec}$

d) $\phi \text{ (phi)} = 0.7854 \text{ radians}$

e) $T = 8.3333 \text{ ms (milli sec)}$

Correct

Marks for this submission: 10.00/10.00.

Question 2

Incorrect

Mark 0.00 out of
10.00

Q2d

Given: $x(t) = 350 \cos(300 t + 15^\circ) + 375 \cos(300 t + 50^\circ)$

Use the concept of the phasor to combine this sinusoidal function into a single trigonometric expression in the form similar to $x(t) = A \cos(\omega t + \theta^\circ)$.

Magnitude A of $x(t) =$ ✗

Angle θ of $x(t) =$ ✗ Degrees

Numeric Answer


$x(t) = 691.4857 \cos(300 t + 33.1229^\circ)$

Incorrect

Marks for this submission: 0.00/10.00.

Question 3

Correct

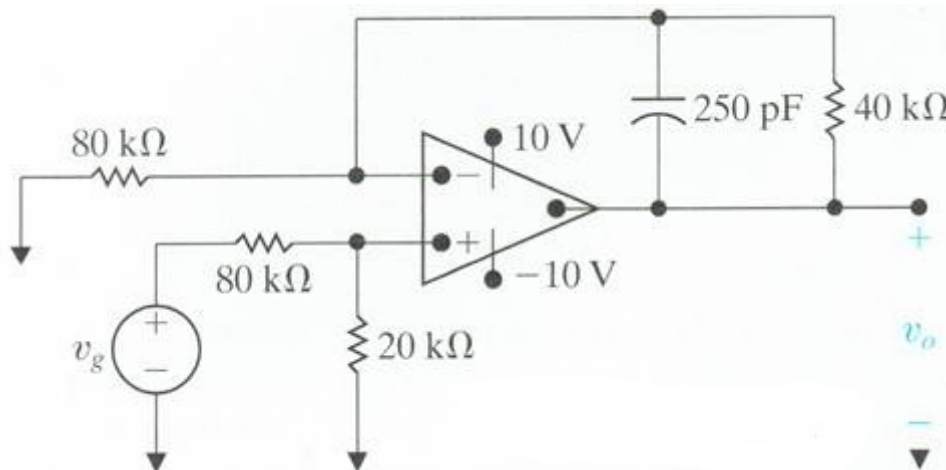Mark 15.00 out of
15.00

Q3e

Assume the operational amplifier is ideal.

Given $v_g(t) = 30.0 \text{ V}$ (a constant voltage)

Find the steady-state output $v_o(t)$.

$v_o(t) =$ ✓ Volts

Numeric Answer

$v_o(t) = 9.0 \text{ V}$ since the opamp is in the linear region.


Correct

Marks for this submission: 15.00/15.00.

Question 4

Correct

Mark 15.00 out of 15.00

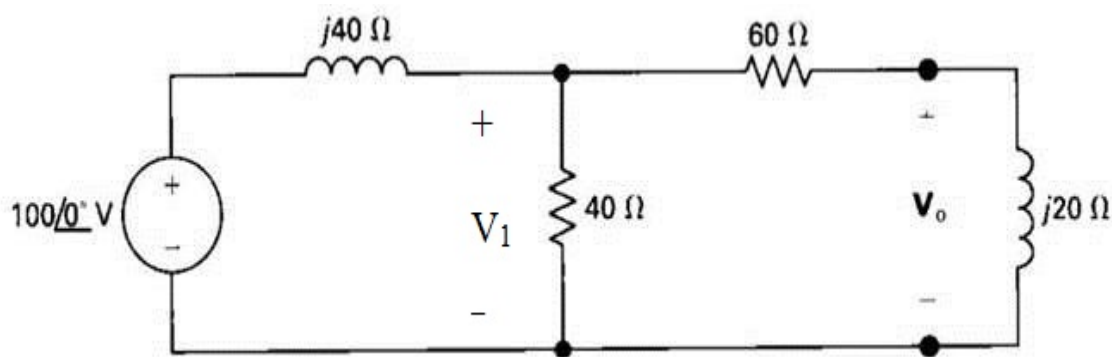

Q4a

Find the phasor voltages V_0 and V_1 . I suggest you use the Node Method. $V_0 =$ ✓ at angle ✓ ° (Degrees) Volts $V_1 =$ ✓ at angle ✓ ° (Degrees) Volts

Express your answer as a positive magnitude and then the angle in the appropriate quadrant.


Numeric Answer $V_0 = 15.811$ at angle 18.43° Volts $V_1 = 50.0$ at angle -53.13° Volts**Correct**

Marks for this submission: 15.00/15.00.

Question 5

Correct

Mark 15.00 out of 15.00

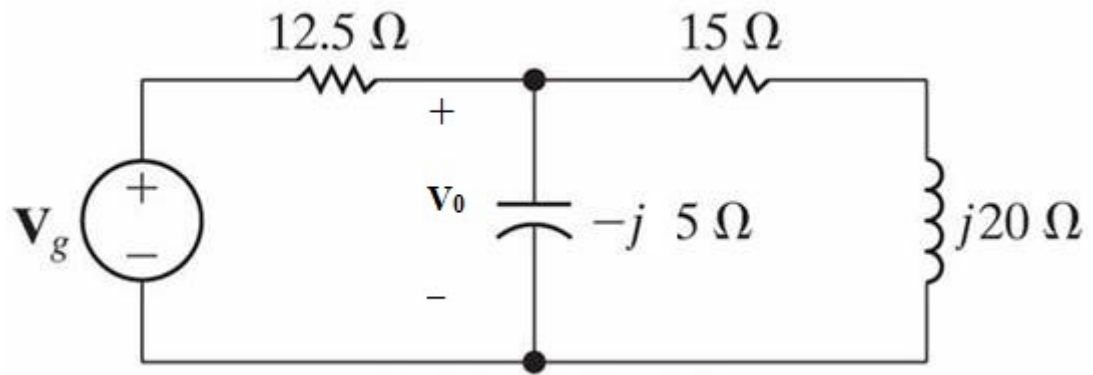

Q5b

Given:

The voltage source $V_g = 160$ at angle 0° V_{rms}
 and the voltage $V_0 = 64.7821$ at angle -58.24° V_{rms} .

Find the average and reactive power for the voltage source V_g .

$$S_g = -1611.3 + j 705.04 \text{ VA}$$

“+” = absorbed and “-” = delivered

Numeric Answer

$$S_g = -1,611.5346 + j 705.0451 \text{ VA}$$

Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 5.00 out of 5.00

Q6b

What is the phase sequence of each of the following sets of voltages?

$$v_a = 820 \cos(\omega t - 46^\circ) \text{ V} \quad v_b = 820 \cos(\omega t + 74^\circ) \text{ V} \quad v_c = 820 \sin(\omega t - 76^\circ) \text{ V}$$

acb – Negative Phase Sequence: ▼ ✓

Correct answer is acb – Negative Phase Sequence


Correct

Marks for this submission: 5.00/5.00.

Question 7

Correct

Mark 15.00 out of 15.00

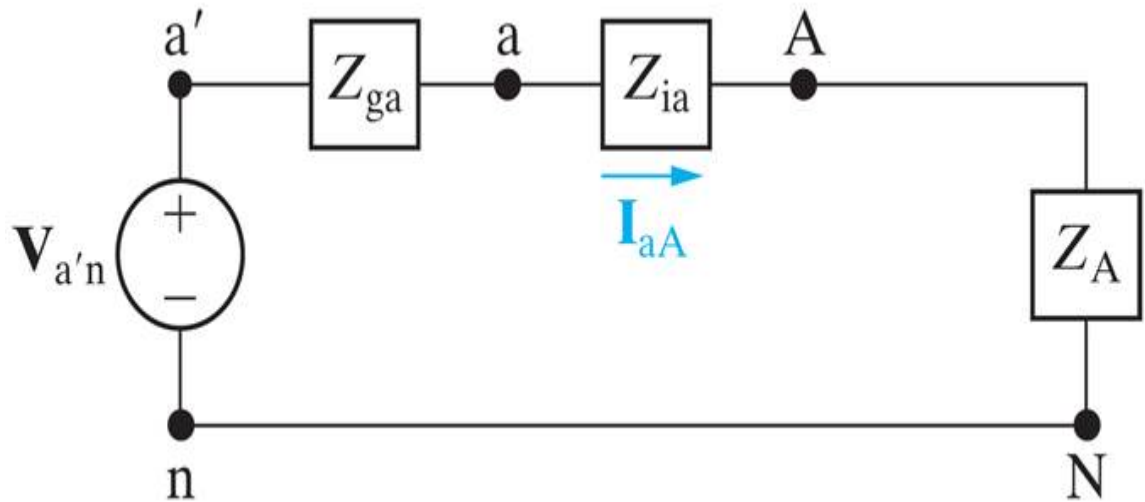

Q7c

Given: $V_{a'n} = 160$ at angle 20° V_{rms} in a balanced three phase system with a positive phase sequence.

The source and load are Y connected.

$$Z_{ga} = 1 + j 15 \Omega \quad Z_{ia} = 20 + j 6 \Omega \quad Z_A = 9 + j 9 \Omega$$

Calculate the single phase equivalent line currents I_{aA} , I_{bB} and I_{cC} .

$$I_{aA} = 3.77 \text{ at angle } -25^\circ \text{ (Degrees) } A_{\text{rms}}$$

$$I_{bB} = 3.77 \text{ at angle } -145^\circ \text{ (Degrees) } A_{\text{rms}}$$

$$I_{cC} = 3.77 \text{ at angle } 95^\circ \text{ (Degrees) } A_{\text{rms}}$$

Calculate the line to line voltages V_{AB} , V_{BC} , and V_{CA} .

$$V_{AB} = 83.12 \text{ at angle } 50^\circ \text{ (Degrees) } V_{\text{rms}}$$

$$V_{BC} = 83.12 \text{ at angle } -70^\circ \text{ (Degrees) } V_{\text{rms}}$$

$$V_{CA} = 83.12 \text{ at angle } 170^\circ \text{ (Degrees) } V_{\text{rms}}$$

$$I_{aA} = 3.7712 \text{ at angle } -25^\circ A_{\text{rms}}$$

$$I_{bB} = 3.7712 \text{ at angle } -145^\circ A_{\text{rms}}$$

$$I_{cC} = 3.7712 \text{ at angle } 95^\circ A_{\text{rms}}$$

$$V_{AB} = 83.1384 \text{ at angle } 50^\circ V_{\text{rms}}$$

$$V_{BC} = 83.1384 \text{ at angle } -70^\circ V_{\text{rms}}$$

$$V_{CA} = 83.1384 \text{ at angle } 170^\circ V_{\text{rms}}$$

Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

Mark 15.00 out of
15.00

Q8c

The total apparent power supplied in a balanced three-phase Y-Δ (wye to delta) system is 3,600 VA. The source line to neutral voltage is $240 \text{ V}_{\text{rms}}$. The line impedance is negligible and the power factor angle of the load is 25° leading.

Determine the impedance of each phase of the delta-connected load.

$$Z_{\Delta, \text{load}} = 130.5 + j -60.86 \text{ } \Omega \text{ (Ohms)}$$

$$Z_{\Delta, \text{load}} = 130.5083 - j 60.8570 \text{ } \Omega \text{ (Ohms)}$$

Correct

Marks for this submission: 15.00/15.00.

◀ Quiz 3 - Chapter 10

Jump to... ▼

Quiz 4 - Chapter 12 ►