

Started on Saturday, 9 September 2017, 2:43 PM

State Finished

Completed on Saturday, 9 September 2017, 3:25 PM

Time taken 42 mins 23 secs

Grade 10.0 out of 10.0 (100%)

Question 1

Correct

Mark 1.0 out of 1.0

If a $42.8\text{k}\Omega$ resistor has 0.23mA flowing through it, then what is the value of the voltage across this resistor in volts?

Answer: ✓

The correct answer is: 9.84

Correct

Marks for this submission: 1.0/1.0.

Question 2

Correct

Mark 1.0 out of 1.0

If a 9.7mA current source is applied to a $1.8\text{k}\Omega$ resistor connected in parallel with a $27.0\text{k}\Omega$ resistor, then what is the current through the $1.8\text{k}\Omega$ resistor in milliamps?

Answer: ✓

The correct answer is: 9.09


Correct

Marks for this submission: 1.0/1.0.

Question 3

Correct

Mark 1.0 out of 1.0

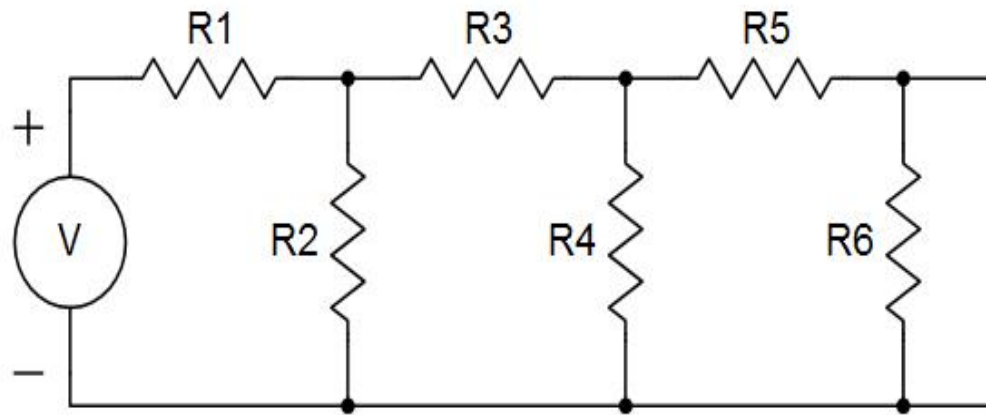

Through repeated applications of Thevenin's Theorem, find the value of the open circuit output voltage for the circuit shown in volts. Use: $V = 6.9\text{V}$, $R_1 = 9.1\text{k}\Omega$, $R_2 = 50.0\text{k}\Omega$, $R_3 = 15.1\text{k}\Omega$, $R_4 = 36.3\text{k}\Omega$, $R_5 = 14.7\text{k}\Omega$ and $R_6 = 23.8\text{k}\Omega$.

Answer: 1.63



The correct answer is: 1.63


Correct

Marks for this submission: 1.0/1.0.

Question 4

Correct

Mark 1.0 out of 1.0

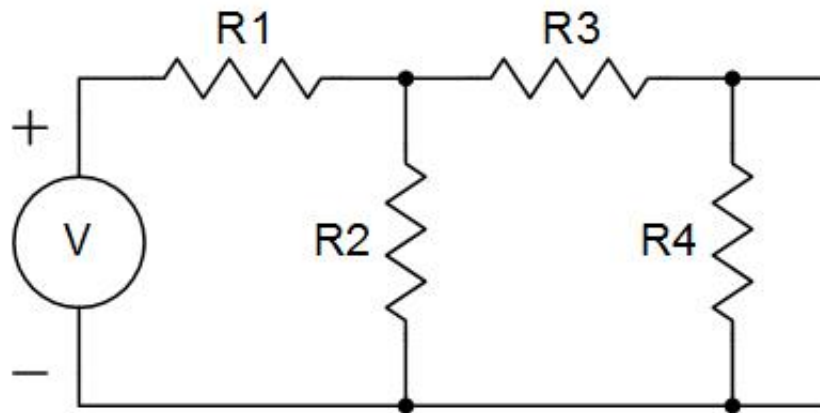

Through repeated applications of Thevenin's Theorem, find the value of the Thevenin equivalent resistance for the circuit shown in kilohms. Use: $V = 7.8\text{V}$, $R1 = 19.2\text{k}\Omega$, $R2 = 26.1\text{k}\Omega$, $R3 = 29.7\text{k}\Omega$ and $R4 = 17.2\text{k}\Omega$.

Answer: 12.1



The correct answer is: 12.10

Correct

Marks for this submission: 1.0/1.0.

Question 5

Correct

Mark 1.0 out of 1.0

Which of the following circuit elements looks like an open circuit at very high frequencies?

Select one:

- ☒ a. Inductors ✓
- ☐ b. Capacitors
- ☐ c. All of these
- ☐ d. None of these
- ☐ e. Resistors

The correct answer is: Inductors

Correct

Marks for this submission: 1.0/1.0.

Question 6

Correct

Mark 1.0 out of 1.0

If the frequency of a constant AC voltage source applied across an ideal capacitor is increased, then the current flowing through the capacitor will :

Select one:

- ☐ a. No way to determine
- ☒ b. Increase ✓
- ☐ c. Decrease
- ☐ d. None of these
- ☐ e. Stay constant

The correct answer is: Increase

Correct

Marks for this submission: 1.0/1.0.

Question 7

Correct

Mark 1.0 out of 1.0

For which of the following circuit elements does the magnitude of the impedance increase as frequency increases?

Select one:

- ☒ a. Inductors ✓
- ☐ b. Resistors
- ☐ c. Capacitors
- ☐ d. All of these
- ☐ e. None of these

The correct answer is: Inductors

Correct

Marks for this submission: 1.0/1.0.

Question 8

Correct

Mark 1.0 out of 1.0

The Norton's equivalent current for a circuit is found by measuring the open circuit output current of the circuit.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 1.0/1.0.

Question 9

Correct

Mark 1.0 out of 1.0

The Thevenin's equivalent resistance for a circuit is found by measuring the resistance looking into the output terminals of the circuit while all dependent voltage and current sources are set equal to zero.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 1.0/1.0.

Question 10

Correct

Mark 1.0 out of 1.0

An inductor looks like a open circuit at very high frequencies.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 1.0/1.0.