

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY myand IS
PORT ( A, B : IN STD_LOGIC;
      C : OUT STD_LOGIC
);
END myand;
ARCHITECTURE dataflow OF myand IS
BEGIN
    C <= A and B;
END dataflow;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY fa IS
PORT ( A, B, Cin : IN STD_LOGIC;
      Cout, S : OUT STD_LOGIC
);
END fa;
ARCHITECTURE dataflow OF fa IS
signal M: std_logic;
BEGIN
    M <= A xor B;
    S <= M xor Cin;
    Cout <= ( M and Cin ) or ( A and B );
END dataflow;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY rca4 IS
Port ( A, B: in std_logic_vector(3 downto 0);
      Cin: in std_logic;
      Cout: out std_logic;
      S: out std_logic_vector(3 downto 0));
END rca4;
ARCHITECTURE structural OF rca4 IS
component fulladder
PORT (A, B, Cin : IN STD_LOGIC;
      Cout, S : OUT STD_LOGIC
);
end component;
signal CR: STD_LOGIC_VECTOR(3 downto 0);
BEGIN
U0: fulladder port map ( A => A(0), B => B(0),
                        Cin => Cin,
                        Cout=> CR(0), S=> S(0)
);
U1: fulladder port map ( A => A(1), B => B(1),
                        Cin => CR(0),
                        Cout=> CR(1), S=> S(1)
);
U2: fulladder port map ( A => A(2), B => B(2),
                        Cin => CR(1),
                        Cout=> CR(2), S=> S(2)
);
U3: fulladder port map ( A => A(3), B => B(3),
                        Cin => CR(2),
                        Cout=> CR(3), S=> S(3)
);
END structural;

```

```

--Unsigned 8x4-bit Multiplier
module multiplier(A, B, RES);
input [7:0] A;
input [3:0] B;
output [11:0] RES;
assign RES = A * B;
endmodule

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY myand_tb IS
END myand_tb;
ARCHITECTURE beh OF myand_tb IS
component myand
PORT( A, B : IN STD_LOGIC;
      C : OUT STD_LOGIC );
end component;
signal TA, TB : STD_LOGIC;
signal TC: STD_LOGIC;
BEGIN
    uut: myand port map (
        A => TA, B => TB,
        C => TC );
    Process
    Begin
        TA <='0'; TB<='0';
        Wait for 10 ns;
        TA <='0'; TB<='1';
        Wait for 10 ns;
        TA <='1'; TB<='0';
        Wait for 10 ns;
        TA <='1'; TB<='1';
        Wait for 10 ns;
        Wait;
    End process;
END beh;

```

```

Library ieee;
Use ieee.std_logic_1164.all;
Entity dff is
Port ( d, clk: in std_logic;
      q: out std_logic );
End dff;
Architecture beh of dff is
begin
    process( clk )
    begin
        -- if (rising_edge( clk ) ) then
            q <= d;
        end if;
    end process;
End beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY dff_tb IS
END dff_tb;
ARCHITECTURE beh OF dff_tb IS
component dff
PORT (
    d, clk: IN STD_LOGIC;
    q : OUT STD_LOGIC
);
end component;
signal d, clk, q : STD_LOGIC;
BEGIN
    uut: dff port map ( d => d,
                        clk => clk, q => q );
    Process
    Begin
        clk <= '0'; Wait for 10 ns;
        Clk <= '1'; Wait for 10 ns;
    End process;
    Process
    Begin
        d <='0'; Wait for 8 ns;
        d <='1'; Wait for 20 ns;
        d <='0'; Wait for 8 ns;
        Wait;
    End process;

```

```

Process
Begin
    clk <= '0'; Wait for 10 ns;
    Clk <= '1'; Wait for 10 ns;
End process;
Process
Begin
    d <='0'; Wait for 8 ns;
    d <='1'; Wait for 20 ns;
    d <='0'; Wait for 8 ns;
    Wait;
End process;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY shiftreg IS
PORT ( Din, clk, clr : IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(3 downto 0)
);
END shiftreg;
ARCHITECTURE beh OF shiftreg IS
signal W: std_logic_vector(3 downto 0);
BEGIN
    process( clk, clr )
    begin
        if (clr = '1') then
            W <= "0000";
        elsif (rising_edge( clk)) then
            W(3) <= Din;
            W(2) <= W(3);
            W(1) <= W(2);
            W(0) <= W(1);
        end if;
    end process;
    Q <= W;
END beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY mux IS
PORT( A, B,C,D : IN STD_LOGIC;
      SEL: IN STD_LOGIC_VECTOR(1 downto 0);
      DOUT : OUT STD_LOGIC
);
END mux;
ARCHITECTURE design OF mux IS
BEGIN
    DOUT <= A WHEN SEL = "00" ELSE
           B WHEN SEL = "01" ELSE
           C WHEN SEL = "10" ELSE
           D;
END design;

```

```

/library ieee;
use ieee.std_logic_1164.all;
package MY_PACK is
function PARITY (X : std_logic_vector)
return std_logic;
end MY_PACK;
package body MY_PACK is
function PARITY (X : std_logic_vector)
return std_logic is
variable TMP : std_logic;
begin
    --TMP:= '0';
    TMP := X(0);
    --for J in X'range loop
    for J in 1 to X'high loop
        TMP := TMP xor X(J);
    end loop;
    -- works for any size X
    return TMP;
end PARITY;
end MY_PACK;

```

```

library ieee;
use ieee.std_logic_1164.all;
use work.MY_PACK.all;

entity PAR is
port( db: in std_logic_vector(7 downto 0);
      dw: in std_logic_vector(15 downto 0);
      pb, pw: out std_logic);
end PAR;

architecture ARCH1 of PAR is
begin
    pb <= PARITY(db);
    pw <= PARITY(dw);
end ARCH1;

```

Even Parity and Odd Parity

Examples

even

ab_parity (f_even)

00_0

01_1

10_1

11_0

f_even = a xor b

odd

ab_parity (f_odd)

00_1

01_0

10_0

11_1

f_odd = not (a xor b);

ADD/SUBTRACT

Modulo 2 uses XOR

0 ± 0 = 0;

0 ± 1 = 1;

1 ± 0 = 1;

1 ± 1 = 0

MULTIPLICATION

```

  1 0 1 1
x 0 1 0 1
-----
  1 0 1 1
 0 0 0 0
 0 0 0 0
0 1 0 0 1 1 1


```

DIVISION

```

      1 0 0 0 1 rem. 1 0 1
1 0 0 1 1 | 1 0 0 1 0 0 1 1 0
      1 0 0 1 1
      -----
            1 0 1 1 0
            1 0 0 1 1
            -----
                  1 0 1
                  1 rem. 1 0 1 0
1 1 0 0 1 | 1 0 0 1 1
            1 1 0 0 1
            -----
                  1 0 1 0
                  1 rem. 1 0 1 0
1 0 0 1 1 | 1 0 0 1
            1 0 0 1 1
            -----
                  1 0 1 0

```

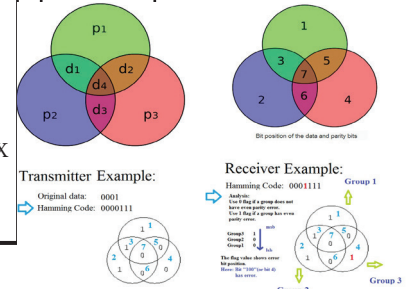

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity hamming is
Port ( hamdin: in std_logic_vector(3 downto 0);
      hamout: out std_logic_vector(7 downto 1) );
end hamming;
architecture Behavioral of hamming is
signal p: std_logic_vector(4 downto 1);
begin
    p(1) <= hamdin(3) xor hamdin(1) xor hamdin(0);
    p(2) <= hamdin(3) xor hamdin(2) xor hamdin(0);
    p(4) <= hamdin(3) xor hamdin(2) xor hamdin(1);
    hamout <= p(1) & p(2) & hamdin(3) & p(4) & ham-
din(2) & hamdin(1) & hamdin(0);
end Behavioral;

```

```


LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY moorefsm IS
PORT
    ( reset, a, clk : IN STD_LOGIC;
      y: OUT STD_LOGIC
    );
END moorefsm;
ARCHITECTURE beh OF moorefsm IS
type state_type is (S0, S1);
signal cs, ns: state_type;
BEGIN
    Process(reset, clk)
    Begin
        If (reset = '1') then
            cs <= S0;
        elsif (rising_edge(clk)) then
            cs <= ns;
        end if;
    End process;
    Process(cs, a)
    Begin
        Case (cs) is
            When S0 => y <= '0';
                If (a='1') then
                    ns <= S1;
                else
                    ns <= S0;
                end if;
            When S1 => y <= '1';
                If (a='1') then
                    ns <= S1;
                else
                    ns <= S0;
                end if;
            When others=> y <= '0'; ns <= S0;
        end case;
    end process;
END beh;

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY moorefsm_tb IS
END moorefsm_tb;
ARCHITECTURE beh OF moorefsm_tb IS
component moorefsm
PORT (
    reset, a, clk : IN STD_LOGIC;
    y: OUT STD_LOGIC
);
end component;
signal reset, a, clk : STD_LOGIC;
signal y: STD_LOGIC;
BEGIN
    Uut: moorefsm port map ( reset => reset,
                                a => a, clk => clk,
                                y => y );
    reset <= '1', '0' after 5 ns, '0' after 100 ns;
    clk <= '0', '1' after 10 ns, '0' after 20 ns,
        '0' after 30 ns, '1' after 40 ns,
        '0' after 50 ns, '1' after 60 ns,
        '0' after 70 ns, '1' after 80 ns,
        '0' after 90 ns, '1' after 100 ns;
    a <= '0', '1' after 12 ns, '0' after 56 ns;
END beh;


```

 

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY mealyfsm IS PORT
    ( reset, a, clk : IN STD_LOGIC;
      y: OUT STD_LOGIC
    );
END mealyfsm;
ARCHITECTURE beh OF mealyfsm IS
type state_type is (S0,S1);
signal cs, ns: state_type;
BEGIN
    Process(reset, clk)
    Begin
        If(reset = '1') then
            cs <= S0;
        elsif (rising_edge(clk)) then
            cs <= ns;
        end if;
    End process;
    Process(cs, a)
    Begin
        Case (cs) is
            When S0 => If (a='1') then
                ns <= S1; y <= '1';
            else
                ns <= S0; y <= '0';
            end if;
            When S1 => If (a='1') then
                ns <= S1; y <= '0';
            else
                ns <= S0; y <= '1';
            end if;
            When others=> y <= '0'; ns <= S0;
        end case;
    end process;
END beh;


```

 

```

library IEEE;
use IEEE.std_logic_1164.all;
entity fsm is
port ( clk, reset, x1 : IN std_logic;
      outp : OUT std_logic
    );
end entity;
architecture beh1 of fsm is
type state_type is (s1,s2,s3,s4);
signal state, next_state: state_type;
begin
    process1: process (clk, reset)
    begin
        if (reset = '1') then
            state <= s1;
        elsif (clk = '1' and clk'Event) then
            state <= next_state;
        end if;
    end process process1;
    process2 : process (state, x1)
    begin
        case state is
            when s1 =>
                if x1='1' then
                    next_state <= s2;
                else
                    next_state <= s3;
                end if;
            when s2 => next_state <= s4;
            when s3 => next_state <= s4;
            when s4 => next_state <= s1;
        end case;
    end process process2;
    process3 : process (state)
    begin
        case state is
            when s1 => outp <= '1';
            when s2 => outp <= '1';
            when s3 => outp <= '0';
            when s4 => outp <= '0';
        end case;
    end process process3;
end beh1;

```

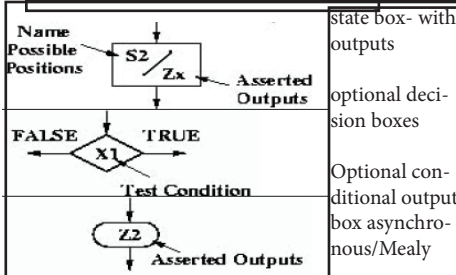

Library ieee;

```


Use ieee.std_logic_1164.all;
entity prob1 is
port (a, b, reset: in std_logic;
      q1, q2: out std_logic);
end prob1;
architecture circuit of prob1 is
    signal clk, m, d1, t1, t2: std_logic;
begin
    clk <= a nand m;
    m <= b nand clk;
    d1 <= not t2;
    process ( clk , reset)
    begin
        if (reset= '1') then t1 <= '0';
        elsif (rising_edge(clk)) then
            t1 <= d1;
        end if;
    end process;
    process ( clk , reset)
    begin
        if (reset= '1') then t2 <= '0';
        elsif (falling_edge(clk)) then
            t2 <= t1;
        end if;
    end process;
    q1 <= t1; q2 <= t2;
end circuit;

```

```

Library ieee; --tb for that circuit
Use ieee.std_logic_1164.all;
entity prob1_tb
is
architecture beh of prob1_tb is
    signal a, b, reset: std_logic;
    signal q1, q2: std_logic;
    component prob1 (a, b, reset: in std_logic;
                    q1, q2: out std_logic);
    end component;
begin
    uut: prob1 port map ( a=> a, b=> b,
                        reset=>reset, q1=>q1, q2=>q2 );
    process
    begin
        reset <= '1';
        wait for 5 ns;
        reset <= '0';
        wait for 100 ns;
        wait;
    end process;
    b <= not a;
    process
    begin
        a <= '1'; wait for 10 ns;
        a <= '0'; wait for 5 ns;
        a <= '1'; wait for 5 ns;
        a <= '0'; wait for 5 ns;
        a <= '1'; wait for 5 ns;
        a <= '0'; wait for 5 ns;
        wait;
    end process;
end beh;

```

 

```

Use ieee.std_logic_1164.all;
entity prob2_fsm is
port ( w, Reset, Clk: in std_logic;
      M, N: out std_logic );
end prob2_fsm;
Architecture beh of prob2_fsm is
type st is ( SA, SB, SC );
signal cs, ns: st;
begin
    process ( w , cs )
    begin
        case (cs)
            when SA=> if (w = '0') then
                ns <= SA ;
            else
                ns <= SB ;
            end if;
            when SB=> if(w='0') then
                ns <= SA ;
            else
                ns <= SC ;
            end if;
            when SC=> if (w = '0') then
                ns <= SA ;
            else
                ns <= SC ;
            end if;
            when others=> ns <= SA;
        end case;
    end process;
end beh;

```

```

Library ieee;
Use ieee.std_logic_1164.all;
entity prob2_fsm_tb
is
architecture beh of prob2_fsm_tb is
    signal w, Reset, Clk: std_logic;
    signal M, N: std_logic;
    component prob2_fsm ( w, Reset,
                        Clk: in std_logic;
                        M, N: out std_logic );
    end component;
begin
    uut: prob2_fsm port map ( w,
                        Reset, Clk, M, N);
    reset <= '1', '0' after 15 ns;
    w <= '0', '1' after 35 ns;
    process
    begin
        Clk <= '1'; wait for 10 ns;
        Clk <= '0'; wait for 10 ns;
    end process;
    process ( Clk , Reset)
    begin
        if( Reset = '1') then
            cs <= SA ;
        elsif (rising_edge(Clk)) then
            cs <= ns ;
        end if;
    end process;
    M <= '1' when (cs=SC) else '0';
    N <= w when (cs=SB) else '0';
end beh;

```

5. CRC Error Detection

Message = 110101
Generating Polynomial = 101

```

11010100... 101 * 11101
101
111
101
100
101
110
101
110
101
11

```

Quotient (has no function in CRC calculations)

Remainder = CRC checksum

Message with CRC = 11010111

```


LIBRARY IEEE; --LFSR
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY lfsr IS
PORT ( reset, clk: IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(4 downto 1)
      );
END lfsr;
ARCHITECTURE beh OF lfsr IS
signal W: std_logic_vector(4 downto 1);
BEGIN
process( clk, reset )
begin
if (reset='1') then
W <= ( 1=>'1', others => '0' );
elsif (rising_edge( clk)) then
W <= W(3 downto 2) & ( W(1) xor W(4) ) & W(4);
end if;
end process;
Q <= W;
END beh;

```

```

LIBRARY IEEE; --lfsr tb
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY lfsr_tb IS
End lfsr_tb;
ARCHITECTURE beh OF lfsr_tb IS
Component lfsr
PORT ( reset, clk: IN STD_LOGIC;
      Q : OUT STD_LOGIC_VECTOR(4 downto 1)
      );
END Component;
signal reset, clk: std_logic;
signal Q: std_logic_vector(4 downto 1);
BEGIN
out: lfsr port map( reset=>reset, clk=>clk, Q=>Q );
Process
Begin
Clk <= '0';
Wait for 10 ns;
Clk <= '1';
Wait for 10 ns;
End process;
Process
Begin
reset <= '1';
Wait for 6 ns;
reset <= '0';
Wait for 40 ns;
Wait;
End process;
END beh;

```

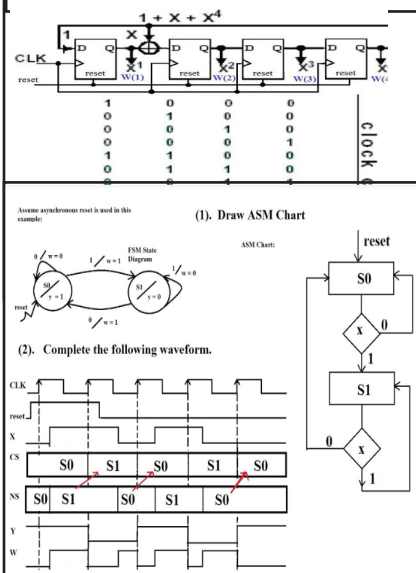

```

library ieee; --Clock division
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity display_counter_vhd is
Port( clk: in std_logic;
      load: in std_logic;
      updown: in std_logic;
      din: in std_logic_vector (3 downto 0);
      cntout: out std_logic_vector (3 downto 0);
      led: out std_logic_vector (3 downto 0);
      clkout: out std_logic
      );
end display_counter_vhd;
architecture behavioral of display_counter_vhd is
signal cnt_div: std_logic_vector (9 downto 0);
signal cnt: std_logic_vector (3 downto 0);
signal clk2: std_logic;
begin
process(clk)
begin
if rising_edge( clk) then
if(cnt_div = 999) then --(N-1), here N=1000
cnt_div <= (others => '0');
clk2 <= '1';
elsif (cnt_div < 499) then --(N/2 - 1)
cnt_div <= cnt_div + 1;
clk2 <= '1';
else
cnt_div <= cnt_div + 1;
clk2 <= '0';
end if;
end if;
end process;
process( clk2, load, updown)
--process active on event of clk2,load, or updown
begin
if(load = '1') then
cnt <= din;
elsif rising_edge( clk2) then
if(updown = '1') then
cnt <= cnt + 1;
else
cnt <= cnt - 1;
end if;
end if;
end process;
cnt_out <= cnt; --output count
clkout <= clk2; --output clk
led <= cnt; --led output value
end behavioral;

```

```

library ieee;
use ieee.std_logic_1164.all;
entity mytt is
port( A, B: in std_logic_vector(5 downto 0);
      Y: out std_logic_vector(11 downto 0));
end mytt;
architecture arch_tt of mytt is
constant C: std_logic_vector(2 downto 0) := "100";
begin
process(A,B)
begin
Y(2 downto 0) <= A(2 downto 0);
Y(3) <= A(3) and B(3);
Y(5 downto 4) <= (A(5) and B(5)) & (A(4) or B(4));
Y(8 downto 6) <= B(2 downto 0);
Y(11 downto 9) <= C;
end process;
end arch_tt;

```

```

library ieee; --pos edge dff
use ieee.std_logic_1164.all;
entity flop is
port( CLK, D : in std_logic;
      Q : out std_logic
      );
end flop;
architecture archi of flop is
begin
process( CLK)
begin
if (rising_edge(CLK)) then
Q <= D;
end if;
end process;
end archi;

```

```

library ieee; --p.edge sync set
use ieee.std_logic_1164.all;
entity flop is
port( C, D, S : in std_logic;
      Q : out std_logic );
end flop;
architecture archi of flop is
begin
process( C)
begin
if (C'event and C='1') then
if (S='1') then
Q <= '1';
else
Q <= D;
end if;
end if;
end process;
end archi;

```

```


library ieee; --4b p.edge clk, asy set, clk en
use ieee.std_logic_1164.all;
entity flop is
port( C, CE, PRE : in std_logic;
      D: in std_logic_vector(3 downto 0);
      Q : out std_logic_vector (3 downto 0)
      );
end flop;
architecture archi of flop is
begin
process( C, PRE)
begin
if (PRE='1') then
Q <= "1111";
elsif (C'event and C='1') then
if (CE='1') then
Q <= D;
end if;
end if;
end process;
end archi;

```

```

library ieee; --tristate
use ieee.std_logic_1164.all;
entity three_st is
port( T, I : in std_logic;
      O : out std_logic
      );
end three_st;
architecture archi of three_st is
begin
process( I, T)
begin
if (T='0') then
O <= I;
else
O <= 'Z';
end if;
end process;
end archi;

```

 

c	a	f
0	0	Z
0	1	1
1	0	0
1	1	1

<pre> library ieee; --4b up/down counter, asy. reset use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity counter is port(C, CLR, UP_DOWN : in std_logic; Q: out std_logic_vector(3 downto 0)); end counter; architecture archi of counter is signal tmp: std_logic_vector(3 downto 0); begin process (C, CLR) begin if (CLR='1') then tmp <= "0000"; elsif (C'event and C='1') then if (UP_DOWN='1') then tmp <= tmp + 1; else tmp <= tmp - 1; end if; end if; end process; Q <= tmp; end archi; </pre>	<pre> library ieee; -- 8b Sft-L Reg, Pedg Clk, Asy CLR, S I/O use ieee.std_logic_1164.all; entity shift is port(C, SI, CLR : in std_logic; SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C, CLR) begin if (CLR='1') then tmp <= (others => '0'); elsif (C'event and C='1') then tmp <= tmp(6 downto 0) & SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --decoder use ieee.std_logic_1164.all; entity dec is port (sel: in std_logic_vector (2 downto 0); res: out std_logic_vector (7 downto 0)); end dec; architecture archi of dec is begin res <= "00000001" when sel = "000" else "00000010" when sel = "001" else "00000100" when sel = "010" else "00001000" when sel = "011" else "00010000" when sel = "100" else "00100000" when sel = "101" else "01000000" when sel = "110" else "10000000"; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity my_block is port(I1 : in std_logic; I2 : in std_logic; O : out std_logic); end my_block; architecture arch1 of my_block is ... end arch1; library ieee; use ieee.std_logic_1164.all; entity top is port(DI_1, DI_2, DI_3, DI_4 : in std_logic; DOUT1, DOUT2 : out std_logic); end top; architecture top_arch of top is component my_block port (I1 : in std_logic; I2 : in std_logic; O : out std_logic); end component; begin inst1: my_block port map (I1=>DI_1, I2=>DI_2, O=>DOUT1); inst2: my_block port map (DI_3, DI_4, DOUT2); end top; </pre>
<pre> library ieee; --8b Sft L Reg, P.Edg Clk, S.i/O use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity shift is port(C, SI : in std_logic; SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C) begin if (C'event and C='1') then for i in 0 to 6 loop tmp(i+1) <= tmp(i); end loop; tmp(0) <= SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --8b Sft L Reg, P.Edg Clk, Asy use ieee.std_logic_1164.all; entity shift is port(C, SI, ALOAD : in std_logic; D : in std_logic_vector(7 downto 0); SO : out std_logic); end shift; architecture archi of shift is signal tmp: std_logic_vector(7 downto 0); begin process (C, ALOAD, D) begin if (ALOAD='1') then tmp <= D; elsif (C'event and C='1') then tmp <= tmp(6 downto 0) & SI; end if; end process; SO <= tmp(7); end archi; </pre>	<pre> library ieee; --decoder use ieee.std_logic_1164.all; entity dec is port (sel: in std_logic_vector (2 downto 0); res: out std_logic_vector (7 downto 0)); end dec; architecture archi of dec is begin with sel select res <= "00000001" when "000", "00000010" when "001", "00000100" when "010", "00001000" when "011", "00010000" when "100", "00100000" when "101", "01000000" when "110", "10000000" when others; end archi; </pre>	<pre> library ieee; --priority encoder use ieee.std_logic_1164.all; entity priority is port (sel : in std_logic_vector (7 downto 0); code :out std_logic_vector (2 downto 0)); end priority; architecture archi of priority is begin code <= "000" when sel(0) = '1' else "001" when sel(1) = '1' else "010" when sel(2) = '1' else "011" when sel(3) = '1' else "100" when sel(4) = '1' else "101" when sel(5) = '1' else "110" when sel(6) = '1' else "111" when sel(7) = '1' else "000"; end archi; </pre>
<pre> library ieee; --unsigned 8b adder/subtractor use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; use ieee.std_logic_arith.all; entity addsub is port(A, B : in std_logic_vector(7 downto 0); OPER : in std_logic; RES : out std_logic_vector(7 downto 0)); end addsub; architecture archi of addsub is begin RES <= A + B when OPER='0' else A - B; end archi; </pre>	<pre> library ieee; --4-1 mux if statement use ieee.std_logic_1164.all; entity mux is port (a, b, c, d : in std_logic; s : in std_logic_vector (1 downto 0); o : out std_logic); end mux; architecture archi of mux is begin process (a, b, c, d, s) begin if (s = "00") then o <= a; elsif (s = "01") then o <= b; elsif (s = "10") then o <= c; else o <= d; end if; end process; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; entity mux is port (a, b, c, d : in std_logic; s : in std_logic_vector (1 downto 0); o : out std_logic); end mux; architecture archi of mux is begin process (a, b, c, d, s) begin case s is when "00" => o <= a; when "01" => o <= b; when "10" => o <= c; when others => o <= d; end case; end process; end archi; </pre>	<pre> library ieee; use ieee.std_logic_1164.all; use ieee.std_logic_arith.all; use ieee.std_logic_unsigned.all; entity adder is port(A, B : in std_logic_vector(7 downto 0); SUM : out std_logic_vector(7 downto 0); CO : out std_logic); end adder; architecture archi of adder is signal tmp: std_logic_vector(8 downto 0); begin tmp <= conv_std_logic_vector((conv_integer(A) + conv_integer(B)),9); SUM <= tmp(7 downto 0); CO <= tmp(8); end archi; -- Or: Res <= ("0" & A) + ("0" & B); </pre>
<pre> library ieee; --Concatenation use ieee.std_logic_1164.all; entity mytt2 is port(A, B : in std_logic_vector(2 downto 0); Y: out std_logic_vector(14 downto 0)); end mytt2; architecture arch_t of mytt2 is constant C: std_logic_vector(2 downto 0) := "100"; begin Y <= A & B & C & C & "110"; end arch_t; </pre>	<pre> library ieee; --comparator use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; entity compar is port(A, B : in std_logic_vector(7 downto 0); CMP : out std_logic); end compar; architecture archi of compar is begin CMP <= '1' when A >= B else '0'; end archi; </pre>		