
Started on Thursday, 12 October 2017, 1:11 PM

State Finished

Completed on Thursday, 12 October 2017, 3:51 PM

Time taken 2 hours 40 mins

Grade 10.0 out of 10.0 (100%)

Question 1

Correct

Mark 2.0 out of 2.0

Which of the following would cause the ripple voltage at the output of a power supply to increase?

Select one:

- ☐ a. Reducing the amplitude of the input voltage
- ☒ b. None of these ✓
- ☐ c. Increasing the size of the load resistance
- ☐ d. Increasing the size of the filter capacitor
- ☐ e. Increasing the frequency of the input voltage

The correct answer is: None of these

Correct

Marks for this submission: 2.0/2.0.

Question 2

Correct

Mark 2.0 out of 2.0

One of the most useful applications for diodes is in DC power supplies, which convert an AC input voltage into a DC output voltage.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.


Correct

Marks for this submission: 2.0/2.0.

Question 3

Correct

Mark 2.0 out of 2.0

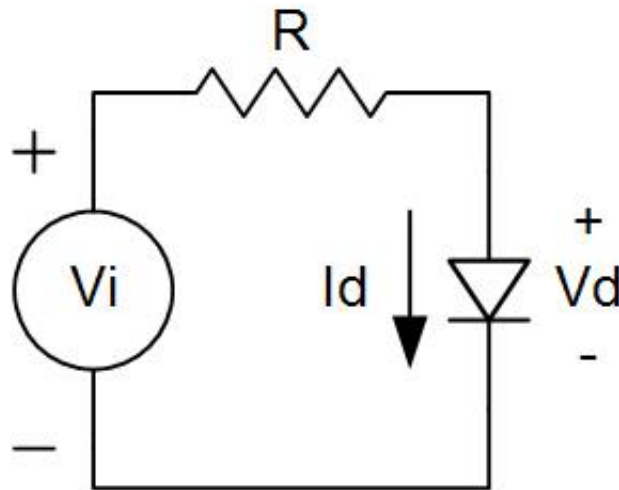

For the diode circuit shown, what will the small-signal resistance of the diode be in Ohms? To find the bias point needed for your small signal analysis use the constant voltage model for the diode with $V_d = 789\text{mV}$. Also use $V_i = 11.4\text{V}$, $R = 6.9\text{k}\Omega$ and $V_t = kt/q = 26\text{mV}$.

Answer: 16.91



The correct answer is: 16.9

Correct

Marks for this submission: 2.0/2.0.

Question 4

Correct

Mark 2.0 out of 2.0

Which of the following would cause the ripple voltage at the output of a power supply to increase?

Select one:

- ☒ a. Reducing the frequency of the input voltage ✓
- ☐ b. Increasing the size of the load resistance
- ☐ c. Increasing the size of the filter capacitor
- ☐ d. Reducing the amplitude of the input voltage
- ☐ e. All of these

The correct answer is: Reducing the frequency of the input voltage

Correct

Marks for this submission: 2.0/2.0.

Question 5

Correct

Mark 2.0 out of 2.0

Once a Zener diode breaks down in the reverse direction, the current through it only changes slightly as the voltage across it varies.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.0/2.0.