

[Home](#) ► [Electrical Engineering](#) ► [Engr17-2016F-Tatro](#) ► [Exams and Quizzes](#) ► [Quiz 6 - Using Matlab](#)

Started on	Wednesday, 19 October 2016, 11:29 AM
-------------------	--------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 19 October 2016, 11:52 AM
---------------------	--------------------------------------

Time taken	22 mins 35 secs
-------------------	-----------------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 100.00 out of
100.00

Quiz 6c

Given this set of linear equations.

$$\frac{V_1 - (100 + j0)}{j40\Omega} + \frac{V_1}{40\Omega} + \frac{V_1 - V_0}{60\Omega} = 0$$

$$\frac{V_0 - V_1}{60\Omega} + \frac{V_0}{j20\Omega} = 0$$

Use Matlab (or other software) to find:

$$V_0 = 15 + j 5 \text{ Volts}$$

$$V_1 = 30 + j -40 \text{ Volts}$$

Express these two results in polar form with a positive valued angle which is less than 180° .

$$V_0 = 15.81 \text{ at angle } 18.43^\circ \text{ (Degree) Volts}$$

$$V_1 = 50 \text{ at angle } 306.87^\circ \text{ (Degree) Volts}$$

Numeric Answer

$$V_0 = 15.0 + j 5.0 \text{ V} = 15.811 \text{ at angle } 18.43^\circ \text{ V}$$

$$V_1 = 30 - j 40 \text{ V} = -50 \text{ at angle } 126.87^\circ \text{ V}$$

Correct

Marks for this submission: 75.00/100.00.

Comment:

Student picked largest positive angle.