

Home ► My courses ► EEE117-2019S-Sec1 ► Homework ► Homework 13 - Chapter 15 and 16

**Started on** Tuesday, 23 April 2019, 11:25 PM

**State** Finished

**Completed on** Tuesday, 23 April 2019, 11:25 PM


**Time taken** 40 secs

**Grade** 100.00 out of 100.00

### Question 1

Correct

Mark 13.00 out of 13.00

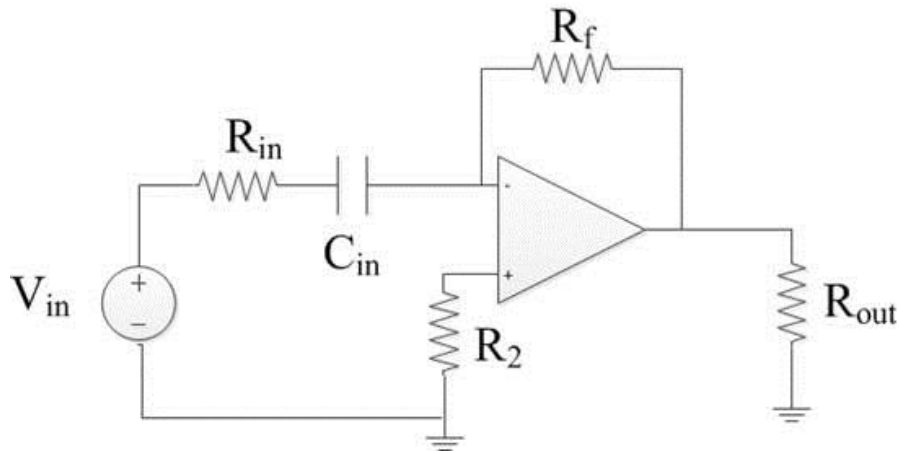

P15.1T

Given:  $R_{in} = 10 \text{ k}\Omega$  (kilo Ohm)  $C_{in} = 0.1 \text{ }\mu\text{F}$  (micro F)  $R_2 = 10 \text{ }\Omega$  (Ohm)

$R_{out} = 1 \text{ k}\Omega$  (kilo Ohm)  $R_f = 10 \text{ k}\Omega$  (kilo Ohm)

$V_{in} = 20 \cos(\omega t)$  Volts

The opamp is not ideal and can only deliver up to 15 mA at the output.

The opamp has power input rails at +15V and -15V.

Determine the radian frequency  $\omega$  where the opamp just begins saturation.

$\omega_{\text{saturation}} = 1133 \checkmark \text{ rad/sec}$

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.


**Correct**

Marks for this submission: 13.00/13.00.

**Question 2**

Correct

Mark 14.00 out of 14.00

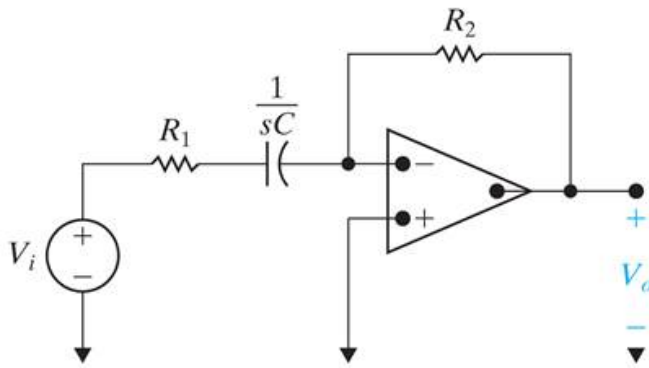

P15.11\_10ed

Given:  $R_1 = 159 \, \Omega$  (Ohm)  $C_{in} = 250 \, \text{nF}$  (nano F)  $R_2 = 1,273 \, \Omega$  (Ohm)

Assume the opamp is ideal.

The input to this high-pass filter is  $v_i(t) = 2.5 \cos(\omega t)$  Volts.

The opamp has power input rails at +20V and -20V.

For the steady-state condition and letting the output voltage magnitude be negative:

a) Find the output voltage when the input frequency  $\omega = \omega_c$ . ( $\omega = \text{omega}$ )

$$v_o(t) = \boxed{-14.1} \checkmark \cos(\boxed{8007} \checkmark \pi t + \boxed{45} \checkmark ^\circ) \text{ (Degrees) Volts}$$

b) Find the output voltage when the input frequency  $\omega = 0.125 \, \omega_c$ .

$$v_o(t) = \boxed{-2.48} \checkmark \cos(\boxed{1000} \checkmark \pi t + \boxed{82.87} \checkmark ^\circ) \text{ (Degrees) Volts}$$

c) Find the output voltage when the input frequency  $\omega = 8 \, \omega_c$ .

$$v_o(t) = \boxed{-19.8} \checkmark \cos(\boxed{64062} \checkmark \pi t + \boxed{7.125} \checkmark ^\circ) \text{ (Degrees) Volts}$$

After you get a numeric answer, create a PSpice simulation and compare your answer with the simulation results.


**Correct**

Marks for this submission: 14.00/14.00.

**Question 3**

Correct

Mark 14.00 out of 14.00

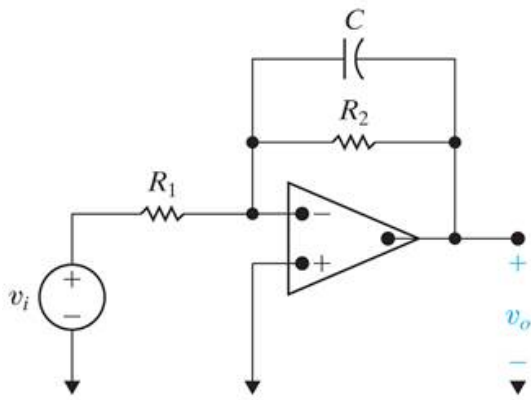

P15.1\_10ed

Given:  $R_1 = ?? \, \Omega$  (Ohm)  $C_{in} = 750 \, \text{nF}$  (nano F)  $R_2 = ?? \, \Omega$  (Ohm)

Assume the opamp is ideal.

Design a low-pass filter with a passband gain of 10 dB and a cutoff frequency of 1 kHz.

$$R_1 = \boxed{67} \, \Omega \text{ (Ohm)}$$

$$R_2 = \boxed{212} \, \Omega \text{ (Ohm)}$$

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.


**Correct**

Marks for this submission: 14.00/14.00.

**Question 4**

Correct

Mark 14.00 out of 14.00

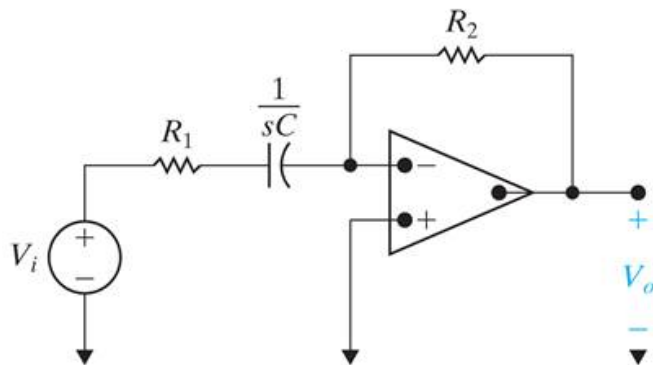

P15.8\_10ed

Given:  $R_1 = ?? \, \Omega$  (Ohm)  $C_{in} = 3.9 \, \text{nF}$  (nano F)  $R_2 = ?? \, \Omega$  (Ohm)

Assume the opamp is ideal.

Design a high-pass filter with a passband gain of 14 dB and a cutoff frequency of 8 kHz.

$$R_1 = \boxed{5100} \, \Omega \text{ (Ohm)}$$

$$R_2 = \boxed{25560} \, \Omega \text{ (Ohm)}$$

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.


**Correct**

Marks for this submission: 14.00/14.00.

**Question 5**

Correct

Mark 15.00 out of 15.00

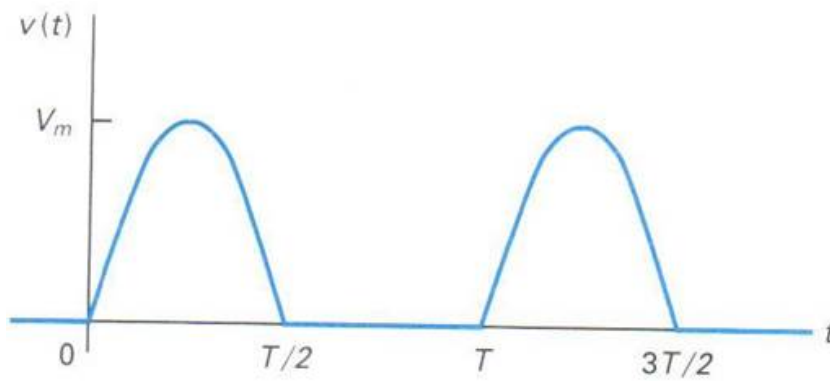

P16.03c\_6ed

Find the Fourier series coefficients for this periodic waveform which is a half-wave rectified sine wave where  $v(t) = V_m \sin(2\pi t/T)$  for  $0 \leq t \leq T/2$ .

Also given  $V_m = 12$  V.

a) Find  $a_v$ .

$a_v = 3.82$  ✓ Volts

b) Find  $a_k$ .

$a_k = 7.64$  ✓ /  $(1 - k^2)$  Volts for all even

c) Find  $b_k$ .

$b_k = 0$  ✓ for  $k$  even and for  $k$  odd  $> 1$ .


$b_1 = 6$  ✓  $\sin(\omega_0 t)$  Volts

**Correct**

Marks for this submission: 15.00/15.00.

**Question 6**

Correct

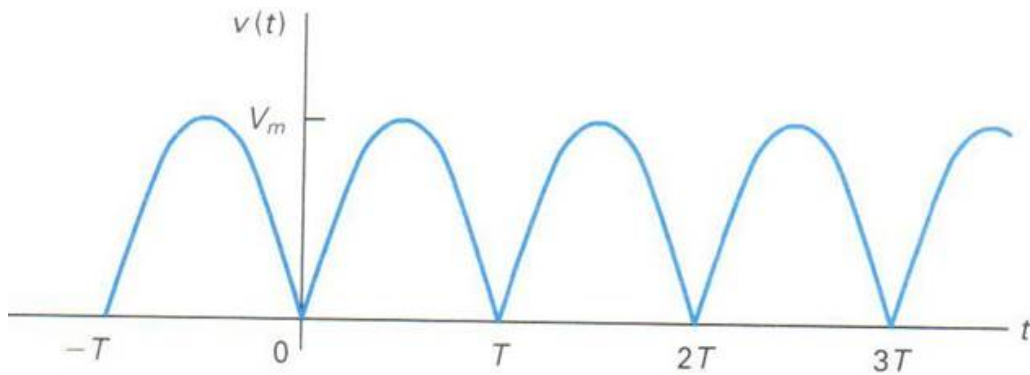Mark 15.00 out of  
15.00

P16.03b\_6ed

Find the Fourier series coefficients for this periodic waveform which is a full-wave rectified sine wave where  $v(t) = V_m \sin(\pi t/T)$  for  $0 \leq t \leq T$ .

a) Find  $a_v$ .

$$a_v = 2 \checkmark V_m / \pi$$

b) Find  $a_k$ .

$$a_k = 4 \checkmark V_m / [\pi (1 - 4 \checkmark k^2)] \text{ for all } k$$

c) Find  $b_k$ .


$$b_k = 0 \checkmark$$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 7**

Correct

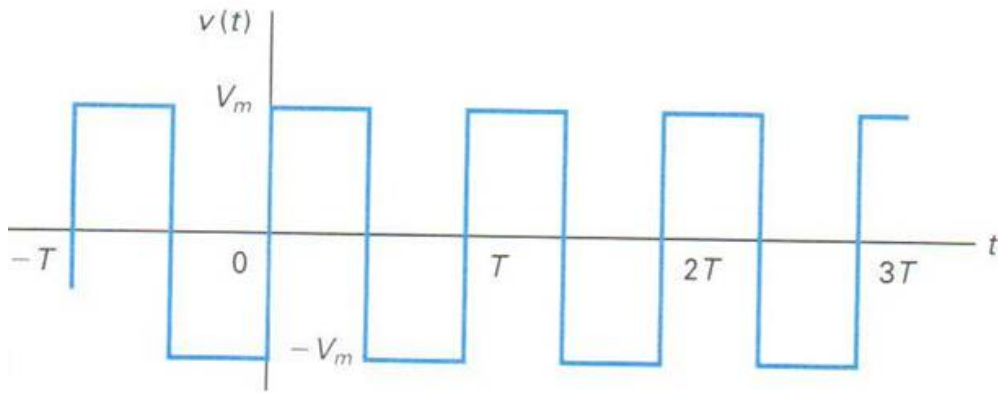Mark 15.00 out of  
15.00

AP16.5\_10ed

Find the Fourier series coefficients for this periodic waveform.

a) Find  $a_v$ .

$$a_v = 0 \quad \checkmark$$

b) Find  $a_k$ .

$$a_k = 0 \quad \checkmark$$

c) Find  $b_k$ .

$$b_k = 4 \quad \checkmark \quad V_m / \pi k \quad \text{for } k \quad \text{Odd} \quad \checkmark$$

**Correct**

Marks for this submission: 15.00/15.00.

◀ Homework 12 - Chapter 14

Jump to...

Homework 14 - Chapter 16 ▶