

Started on Wednesday, 26 October 2016, 11:42 AM

State Finished

Completed on Sunday, 30 October 2016, 4:14 PM


Time taken 4 days 4 hours

Grade 93.3 out of 100.0

Question 1

Correct

Mark 5.0 out of 5.0

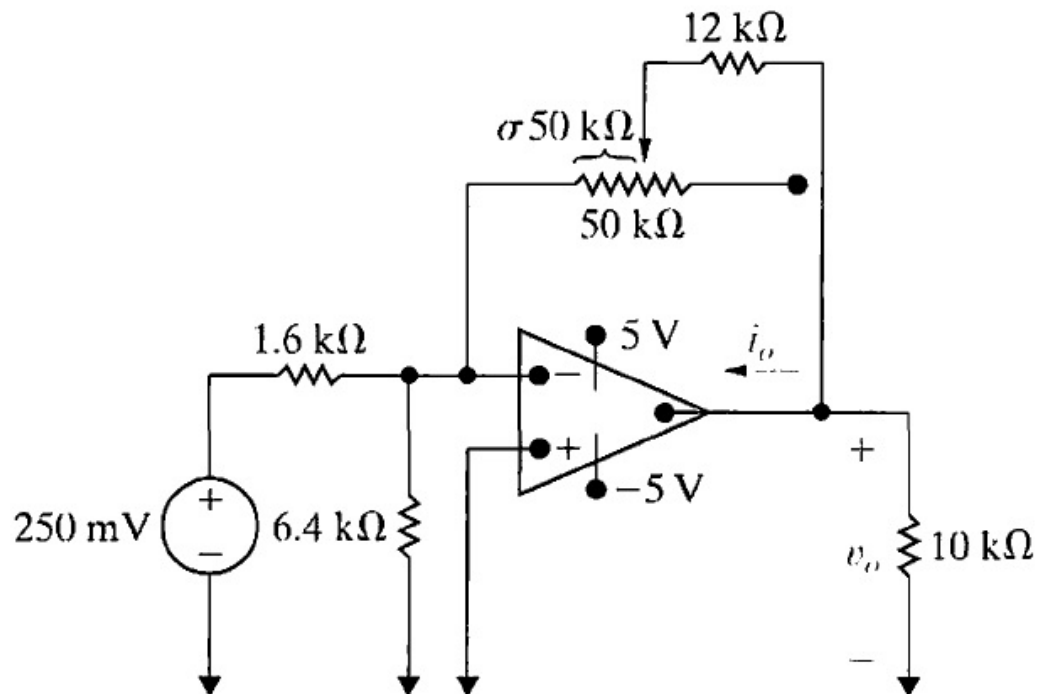

P5.09_9ed

Find the range of values for σ in which the op amp does not saturate. Assume the op amp is ideal

✓ ≤ σ ≤ ✓

Numeric Answer

$0 \leq \sigma \leq 0.40$


Correct

Marks for this submission: 5.0/5.0.

Question 2

Not answered

Mark 0.0 out of 5.0

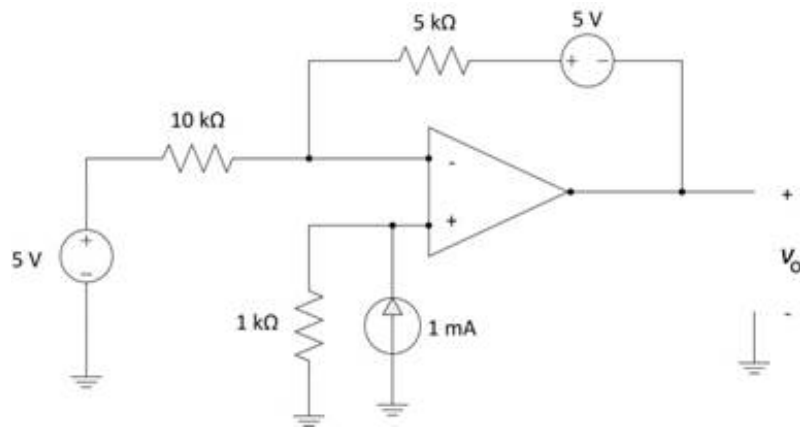


AS5.2

Find v_o . $v_o =$ $\times \text{ V}$ **Numeric Answer** $v_o = -6\text{ V}$

Question 3

Correct

Mark 5.0 out of 5.0

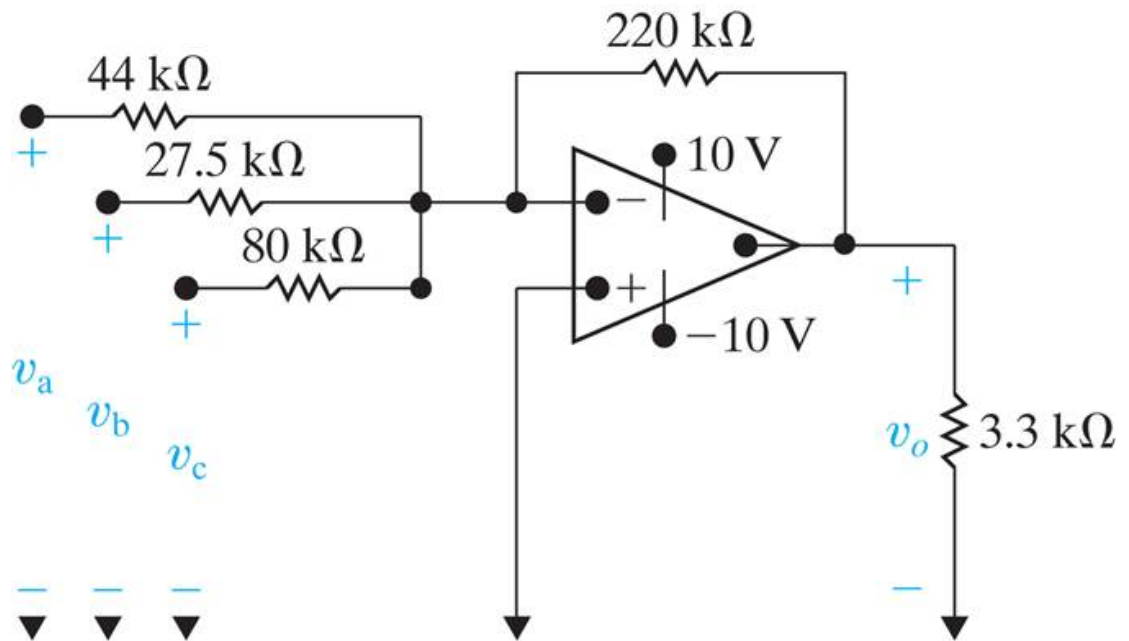

P5.12_10ed

Assume the op amp is ideal.


Find v_o if $v_a = 1$ V, $v_b = 1.5$ V, $v_c = -4$ V. $v_o =$ \checkmark V**Numeric Answer** $v_o = -6$ V**Correct**

Marks for this submission: 5.0/5.0.

Question 4

Correct

Mark 5.0 out of 5.0

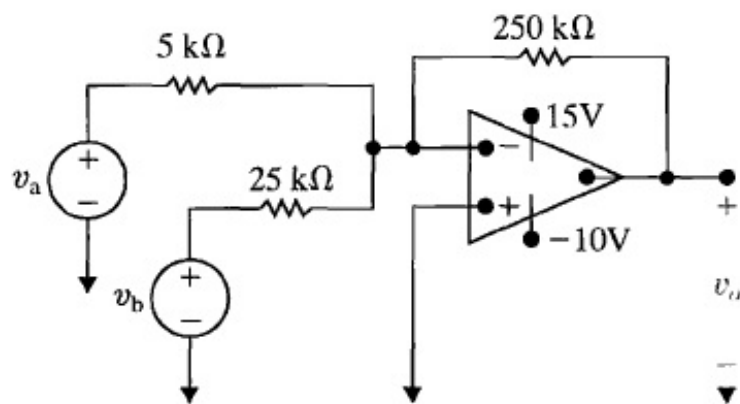

AP5.03_9ed

Assume the op amp is ideal.

a) Find v_o in the circuit shown if $v_a = 0.1$ V and $v_b = 0.25$ V.

$$v_o = -7.5 \text{ V}$$

b) If $v_b = 0.25$ V, how large can v_a be before the op amp saturates?

$$v_a = 0.15 \text{ V}$$


Numeric Answera) $v_o = -7.5$ Vb) $v_a = 0.15$ V**Correct**

Marks for this submission: 5.0/5.0.

Question 5

Correct

Mark 5.0 out of 5.0

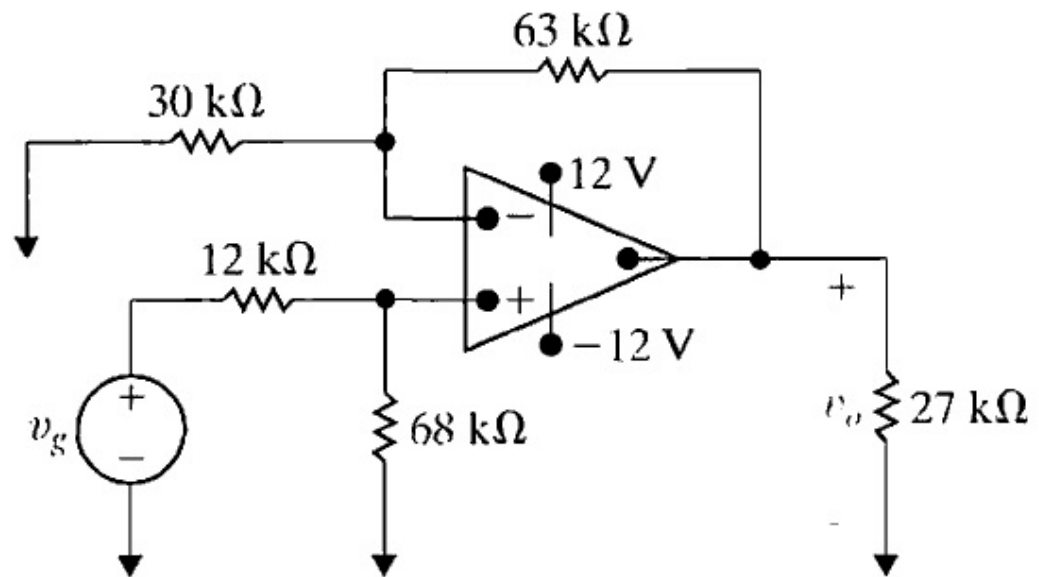

P5.18_9ed

Specify the range of values of v_g so that the op amp operates in a linear mode

$$\boxed{-4.55} \checkmark \leq v_g \leq \boxed{4.55} \checkmark \text{ V}$$

Numeric Answer

$$-4.554 \leq v_g \leq 4.554 \text{ V}$$


Correct

Marks for this submission: 5.0/5.0.

Question 6

Correct

Mark 5.0 out of 5.0

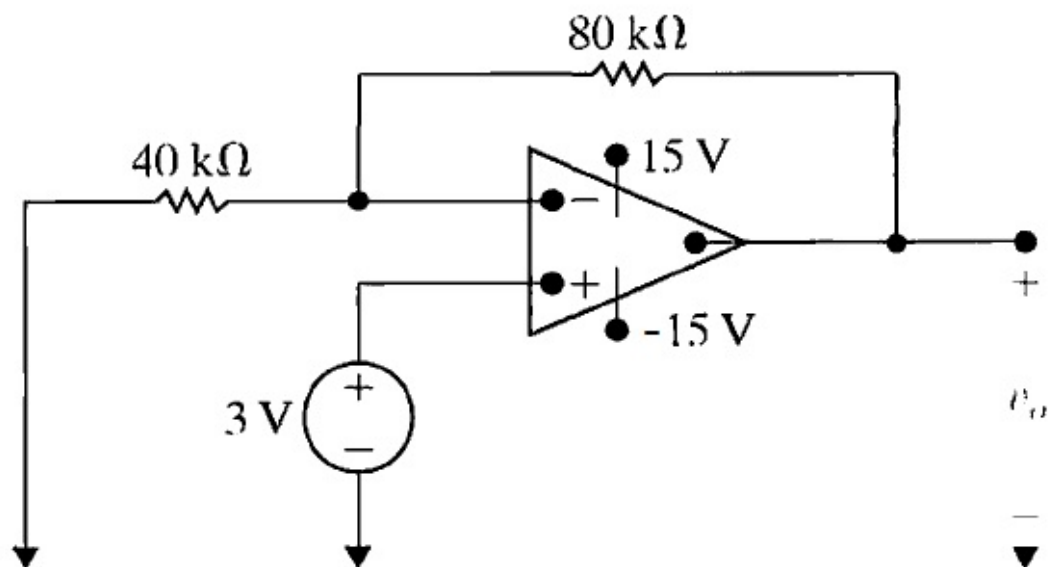

P5.16_9ed

Calculate v_o for this circuit.

$$v_o = \boxed{9} \text{ V}$$

Numeric Answer

$$v_o = 9 \text{ V}$$


Correct

Marks for this submission: 5.0/5.0.

Question 7

Correct

Mark 5.0 out of 5.0

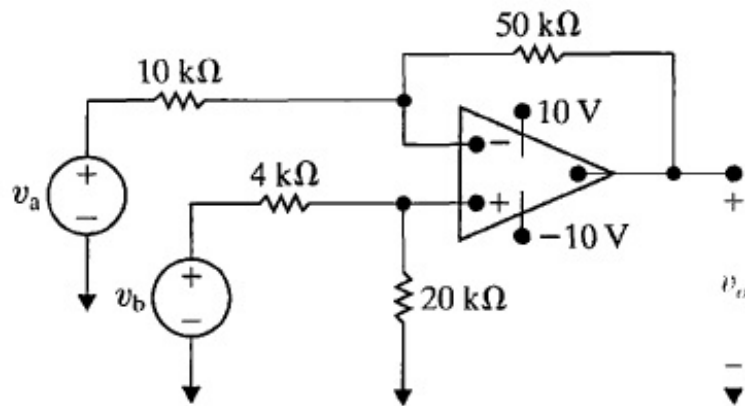

AP5.05_9ed

In the difference amplifier shown, $v_b = 4.0$ V.What range of values for v_a will result in linear operation?

$$2 \leq v_a \leq 6 \text{ V}$$

Numeric Answer

$$2 \text{ V} \leq v_a \leq 6 \text{ V}$$


Correct

Marks for this submission: 5.0/5.0.

Question 8

Correct

Mark 5.0 out of 5.0

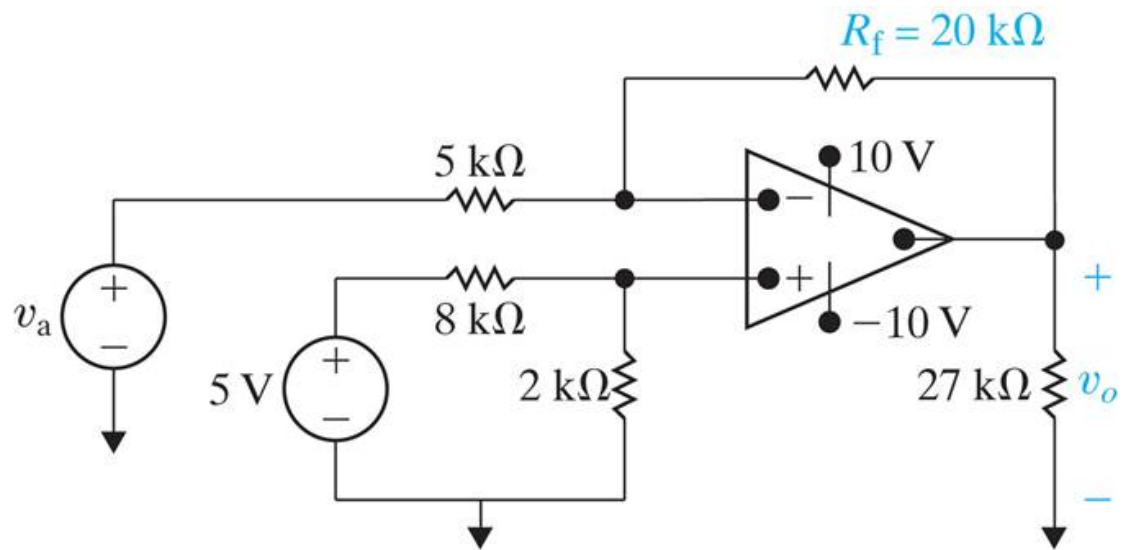

P5.26_10ed

Given: $v_a = 2\text{V}$ Find v_o . $v_o =$ $\checkmark \text{ V}$ **Numeric Answer** $v_o = -3\text{V}$ **Correct**

Marks for this submission: 5.0/5.0.

Question 9

Correct

Mark 5.0 out of 5.0

P6.02_9ed

The current in a 50 μH (micro Henry) inductor is $i_L = 18 t e^{-10t}$ A for $t \geq 0$.

a) Find the voltage across the inductor for $t > 0$.

b) Find the power (in microwatts) at the terminals of the inductor when $t = 200$ ms (milli sec).

Select one:

- ☒ a. $v_L = 900 e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = -59.34$ μW (micro Watts) delivering ✓
- ☐ b. $v_L = -900 e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = +59.34$ μW (micro Watts) absorbing
- ☐ c. $v_L = 90 e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = -5.934$ μW (micro Watts) delivering
- ☐ d. $v_L = 59.34 e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = -900$ μW (micro Watts) delivering

Your answer is correct.

Multiple choice

$v_L = 900e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = -59.34$ μW (micro Watts) delivering

The correct answer is: $v_L = 900 e^{-10t} (1-10t)$ μV (micro Volts)
 $p_L = -59.34$ μW (micro Watts) delivering


Correct

Marks for this submission: 5.0/5.0.

Question 10

Correct

Mark 5.0 out of 5.0

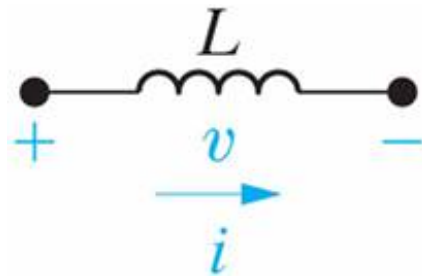

CQ6.09

Given:

 $L = 15 \text{ mH}$ (milli Henry)

At an instant of time the inductor has a current of 9.2 Amps which is increasing by 6.8 Amps/ms.

What is the power absorbed/delivered by the inductor at that instant of time?

 $P_L = ?? \text{ Watts}$ Answer: **Calculated Question**

The correct answer is: 938.400


Correct

Marks for this submission: 5.0/5.0.

Question 11

Correct

Mark 5.0 out of 5.0

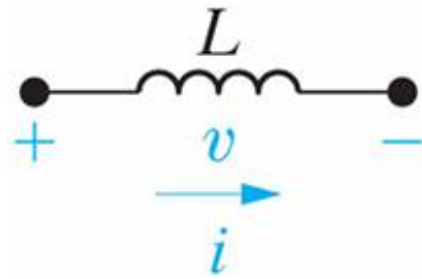

CQ6.07

Given:

 $L = 11 \text{ mH (milli H)}$ The inductor current i changes 9.6 A/ms (Amps per milli sec) for a short while.

What is the voltage across the inductor during this period?

$$V_L = ?? \text{ V}$$

Answer: **Calculated Question**

The correct answer is: 105.600

Correct

Marks for this submission: 5.0/5.0.

Question 12

Correct

Mark 5.0 out of 5.0

P6.13_10ed

The voltage across a 5 μF (micro F) capacitor is $v_c = 500 t e^{-2,500 t}$ V for $t \geq 0$.

Find the current “through” the capacitor for $t > 0$.

Find the power at the terminals of the capacitor when $t = 80 \mu\text{s}$ (micro sec).

Select one:

- ☒ a. $i_c = 2.5 e^{-2500t}$ (1-2500 t) mV (milli Volts)
 $p_c = 53.626 \mu\text{W}$ (micro Watts) absorbing ✓
- ☐ b. $i_c = 2.5 e^{-2500t}$ (1-2500 t) V
 $p_c = 53.626 \text{ W}$ absorbing
- ☐ c. $i_c = 5.3 e^{-5000t}$ (1-2500 t) mV (milli Volts)
 $p_c = -53.626 \mu\text{W}$ (micro Watts) delivering
- ☐ d. $i_c = 0.5 e^{-2500t}$ (1-2500 t) mV (milli Volts)
 $p_c = 13.626 \text{ mW}$ (milli Watts) absorbing

Your answer is correct.

Multiple choice

$i_c = 2.5 e^{-2500t}$ (1-2500 t) mV (milli Volts)
 $p_c = 53.626 \mu\text{W}$ (micro Watts) absorbing

The correct answer is: $i_c = 2.5 e^{-2500t}$ (1-2500 t) mV (milli Volts)
 $p_c = 53.626 \mu\text{W}$ (micro Watts) absorbing


Correct

Marks for this submission: 5.0/5.0.

Question 13

Correct

Mark 5.0 out of 5.0

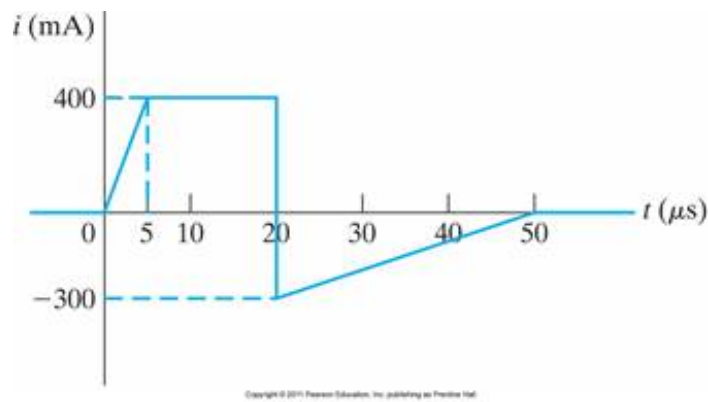

P6.14_9ed

The current shown in the figure is applied to a $0.25 \mu\text{F}$ (micro F) capacitor.

The initial voltage across the capacitor is zero.

Find the charge on the capacitor at $t = 15 \mu\text{s}$ (micro sec).

$$Q_{15\text{ms}} = 5 \mu\text{C (micro C)}$$

Find the voltage across the capacitor at $t = 15 \mu\text{s}$ (micro sec).

$$V_{15\text{ms}} = 20 \text{ V}$$

Numeric Answer

$$Q_{15\text{ms}} = 5 \mu\text{C (micro Coulombs)}$$

$$V_{15\text{ms}} = 20 \text{ Volts}$$


Correct

Marks for this submission: 5.0/5.0.

Question 14

Correct

Mark 5.0 out of 5.0

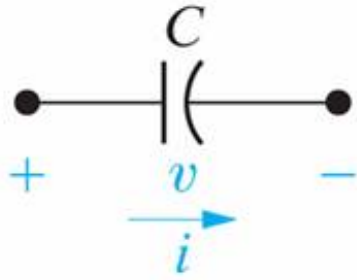

CQ6.10

Given:

 $C = 38 \mu\text{F}$ (micro Farad)The capacitor voltage v changes at $2 \text{ V}/\mu\text{s}$ (Volts per micro sec) for a short while.

What is the current displaced around the capacitor during this period?

 $i_C = ??$ AmpsAnswer: **Calculated Question**

The correct answer is: 76.000


Correct

Marks for this submission: 5.0/5.0.

Question 15

Correct

Mark 5.0 out of 5.0

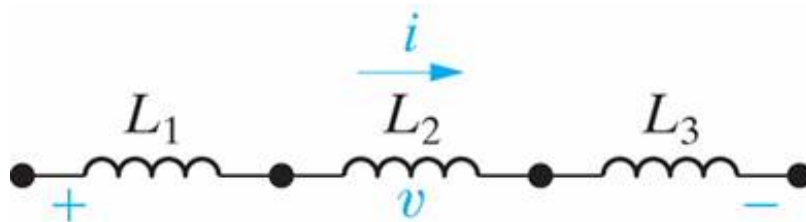

CQ6.04

Given:

 $L_1 = 1.5 \text{ mH (milli Henry)}$ $L_2 = 6.8 \text{ mH (milli Henry)}$ $L_3 = 5.6 \text{ mH (milli Henry)}$ Find the equivalent inductance L_{Eq} . $L_{\text{Eq}} = ?? \text{ mH (milli Henry)}$

Answer: 13.9

**Calculated Question**

The correct answer is: 13.900


Correct

Marks for this submission: 5.0/5.0.

Question 16

Correct

Mark 5.0 out of 5.0

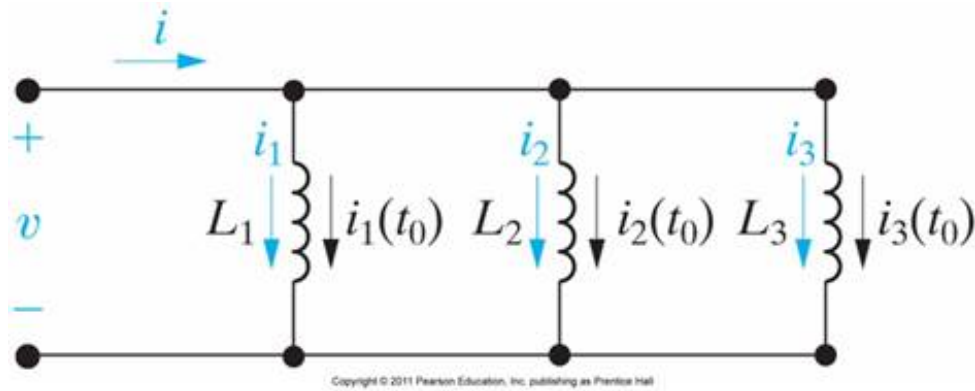

CQ6.05

Given:

 $L_1 = 2.8 \text{ mH (milli Henry)}$ $L_2 = 6.3 \text{ mH (milli Henry)}$ $L_3 = 7.3 \text{ mH (milli Henry)}$ Find the equivalent inductance L_{Eq} . $L_{\text{Eq}} = ?? \text{ mH (milli Henry)}$ Answer: **Calculated Question**

The correct answer is: 1.532


Correct

Marks for this submission: 5.0/5.0.

Question 17

Correct

Mark 5.0 out of 5.0

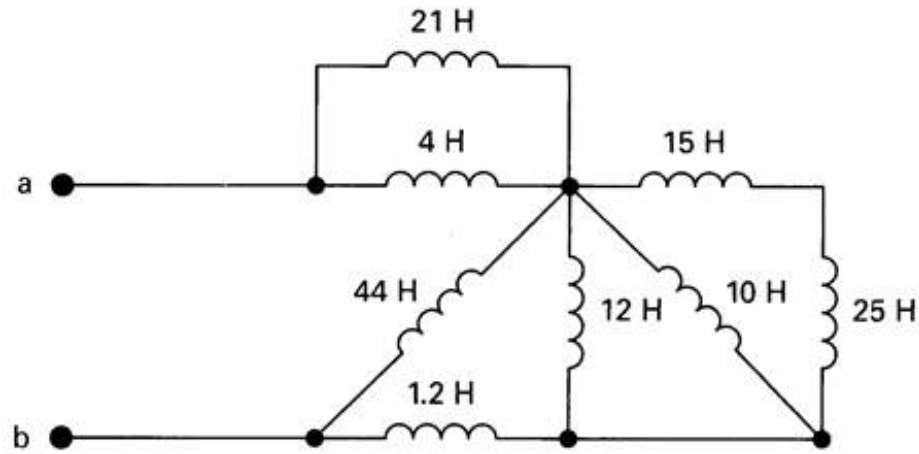

P6.20_6ed

Find the equivalent inductance with respect to the terminals a,b.

$$L_{\text{Eq}} = 8.6 \text{ H}$$

Numeric Answer

$$L_{\text{Eq}} = 8.64 \text{ H}$$


Correct

Marks for this submission: 5.0/5.0.

Question 18

Correct

Mark 5.0 out of 5.0

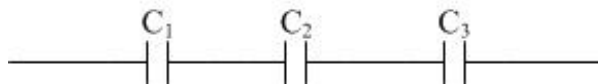

CQ6.01

Given:

$$C_1 = 2.3 \text{ } \mu\text{F (micro Farad)}$$

$$C_2 = 6.8 \text{ } \mu\text{F (micro Farad)}$$

$$C_3 = 1.8 \text{ } \mu\text{F (micro Farad)}$$

Find the equivalent capacitance C_{Eq} .

$$C_{\text{Eq}} = ?? \text{ } \mu\text{F (micro Farad)}$$

Answer: .88

The correct answer is: 0.879


Correct

Marks for this submission: 5.0/5.0.

Question 19

Correct

Mark 5.0 out of 5.0

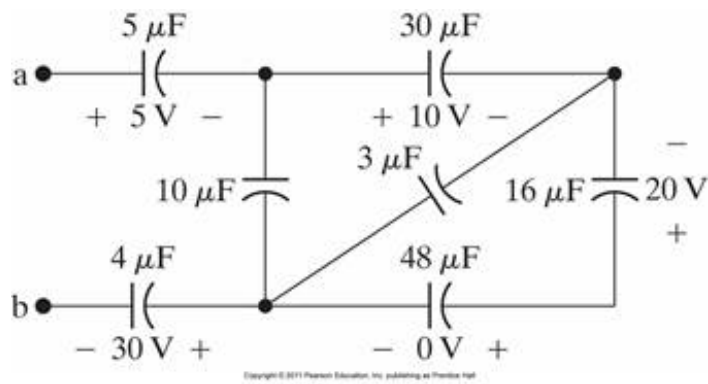

P6.26_9ed

Find the equivalent capacitance with respect to the terminals a,b.

$$C_{\text{Eq}} = \boxed{2} \checkmark \mu\text{F} \text{ (micro F)}$$

And find the initial voltage across the equivalent capacitance.

$$V_{\text{Ceq}} = \boxed{25} \checkmark \text{ V}$$

Numeric Answer

$$C_{\text{Eq}} = 2\ \mu\text{F} \text{ (micro F)}$$

$$V_{\text{Ceq}} = 25\text{ V}$$


Correct

Marks for this submission: 5.0/5.0.

Question 20

Correct

Mark 3.3 out of 5.0

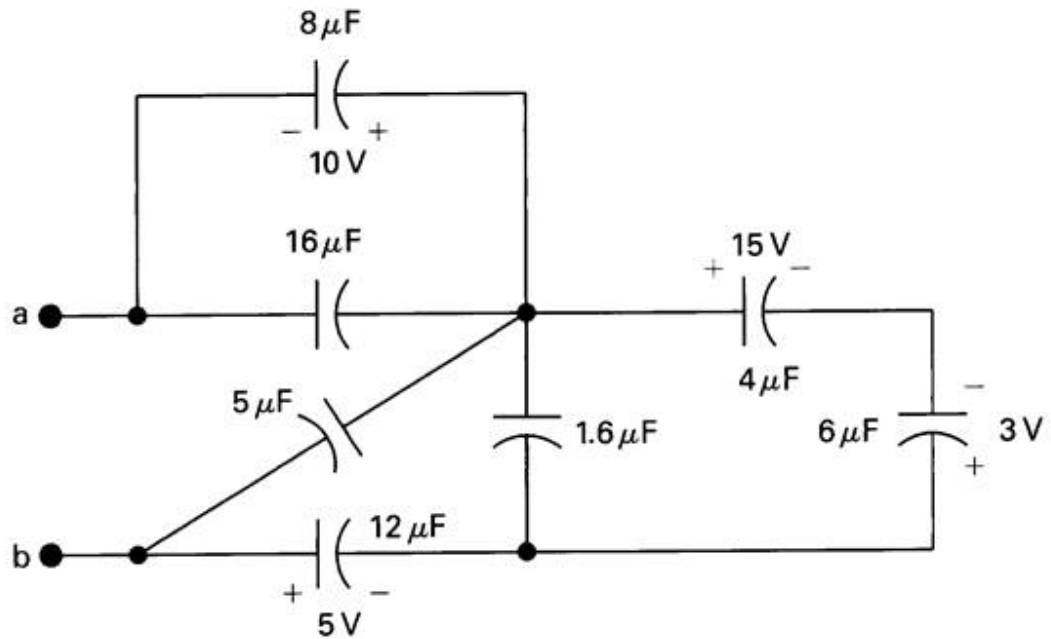

P6.24_6ed

Find the equivalent capacitance with respect to the terminals a,b.

$$C_{\text{Eq}} = \boxed{6} \checkmark \mu\text{F} \quad (\text{micro F})$$

And find the initial voltage across the equivalent capacitance.

$$V_{\text{ab}} = V_{\text{Ceq}} = \boxed{-3} \checkmark \text{V}$$

Numeric Answer

$$C_{\text{Eq}} = 6 \mu\text{F} \text{ (micro F)}$$

$$V_{\text{Ceq}} = -3 \text{ V}$$

CorrectMarks for this submission: 5.0/5.0. Accounting for previous tries, this gives **3.3/5.0**.