


Home ► My courses ► EEE117-2017S-Tatro ► Exams and Quizzes ► Quiz 9 - Chapter 14

<b>Started on</b>	Wednesday, 19 April 2017, 5:22 PM
<b>State</b>	Finished
<b>Completed on</b>	Wednesday, 19 April 2017, 6:30 PM
<b>Time taken</b>	1 hour 7 mins
<b>Overdue</b>	7 mins 16 secs
<b>Grade</b>	<b>100.00</b> out of 100.00

**Question 1**

Correct

Mark 100.00 out of 100.00

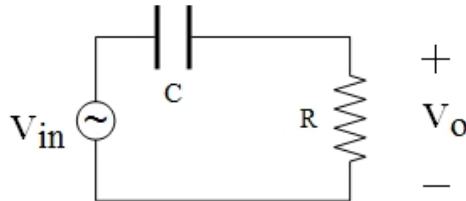

Quiz 9d

Given:  $C = 12 \text{ nF}$  (nano F)       $R = 125 \text{ k}\Omega$  (kilo Ohm)

a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$f_c = 106.1$  ✓

Hz

b) Find the  $H(j\omega)$  for  $H(j\omega = 0.2\omega_c)$ .

$H(j\omega = 0.2\omega_c) = .196$  ✓

at angle  $78.7$  ✓ ° (Degrees)

c) Find the  $H(j\omega)$  for  $H(j\omega = \omega_c)$ .

$H(j\omega = \omega_c) = .707$  ✓

at angle  $45$  ✓ ° (Degrees)

d) Find the  $H(j\omega)$  for  $H(j\omega = 5\omega_c)$ .

$H(j\omega = 5\omega_c) = .98$  ✓

at angle  $11.31$  ✓ ° (Degrees)

**Numeric Answer**

a)  $f_c = 106.1033 \text{ Hz}$

b)  $H(j\omega = 0.2\omega_c) = 0.1961$  at angle  $78.69^\circ$

c)  $H(j\omega = \omega_c) = 0.7071$  at angle  $45^\circ$

d)  $H(j\omega = 5\omega_c) = 0.9806$  at angle  $11.31^\circ$

**Correct**

Marks for this submission: 100.00/100.00.

