

**Started on** Sunday, 23 October 2016, 8:04 PM

**State** Finished

**Completed on** Monday, 24 October 2016, 5:15 AM


**Time taken** 9 hours 10 mins

**Grade** 75.00 out of 100.00

### Question 1

Incorrect

Mark 0.00 out of 10.00

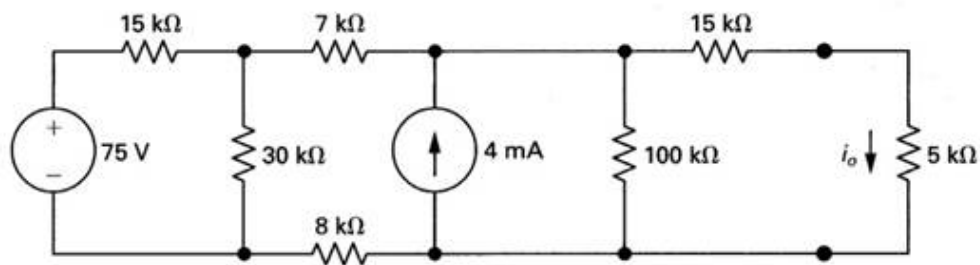

P4.51\_6ed

Use source transformations to:

a) Find the current  $i_o$  through the 5 kΩ (kilo Ohm) resistor.

$i_o =$   ✗ mA (milli Amp)

b) Find the power absorbed/delivered by the 75V voltage source.

$P_{75V} =$   ✗ mW (milli Watt)

### Numeric Answer

a)  $i_o = 3.0$  mA


b)  $P_{75V} = -105$  mW delivering

**Incorrect**

Marks for this submission: 0.00/10.00.

**Question 2**

Correct

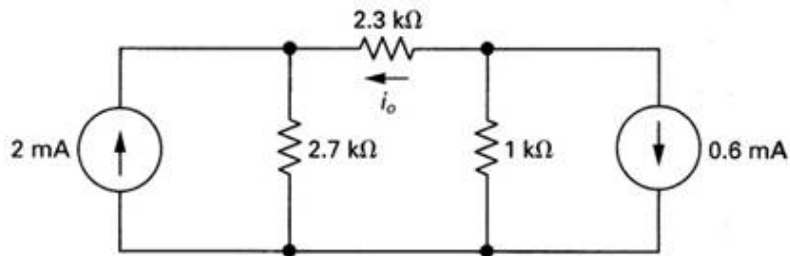Mark 10.00 out of  
10.00

P4.52\_6ed

Use source transformations to:

a) Use Find the current  $i_o$  through the  $2.3 \text{ k}\Omega$  (kilo Ohm) resistor.

$$i_o = \{-1.020|-0.980\} \text{ } \boxed{-1} \text{ } \checkmark \text{ mA (milli Amp)}$$

b) Find the power absorbed/delivered by the  $0.6 \text{ mA}$  current source.

$$P_{0.6\text{mA}} = \boxed{240} \text{ } \checkmark \text{ } \mu\text{W (micro Watt)}$$

**Numeric Answers**

a)  $i_o = -1.0 \text{ mA}$


b)  $P_{0.6\text{mA}} = 240 \text{ } \mu\text{W (micro Watt) absorbing}$

**Correct**

Marks for this submission: 10.00/10.00.


**Question 3**

Correct

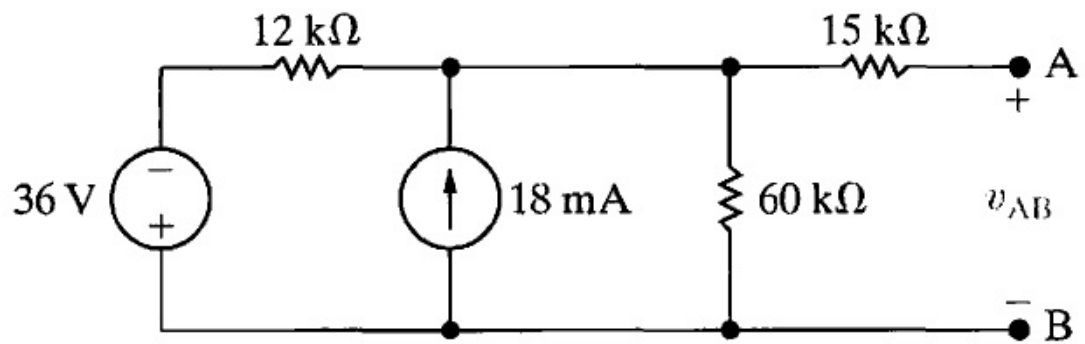Mark 10.00 out of  
10.00

AP4.18\_9ed

A voltmeter with an internal resistance of  $100\text{ k}\Omega$  (kilo Ohm) is used to measure the voltage  $v_{AB}$  in the circuit shown.

What is the voltmeter reading?  $v_{AB} =$    V

**Numeric Answer**


$v_{AB}$  = Voltmeter Reading = 120V

**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

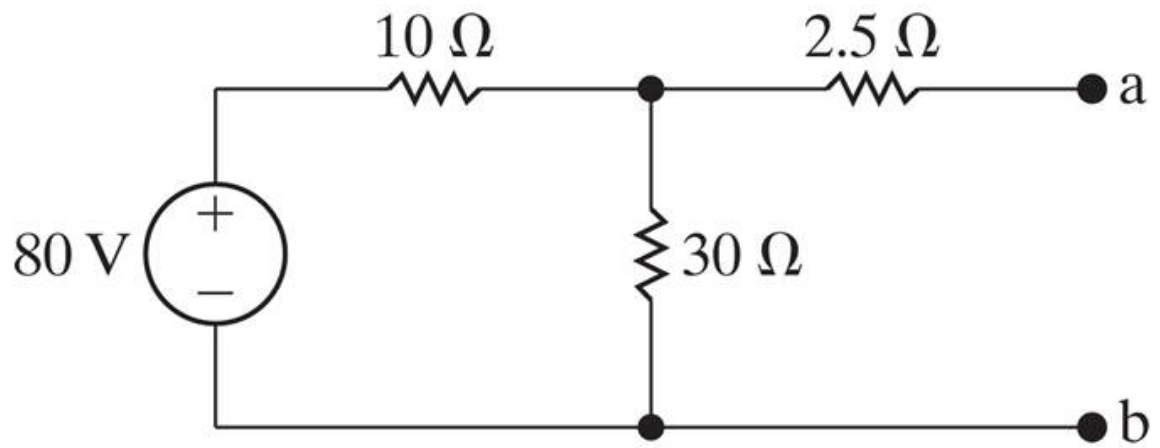Mark 10.00 out of  
10.00

Copyright ©2015 Pearson Education, All Rights Reserved.

P4.64\_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 60 \text{ V}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$V_{Th} = 60 \text{ V}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

Mark 10.00 out of 10.00

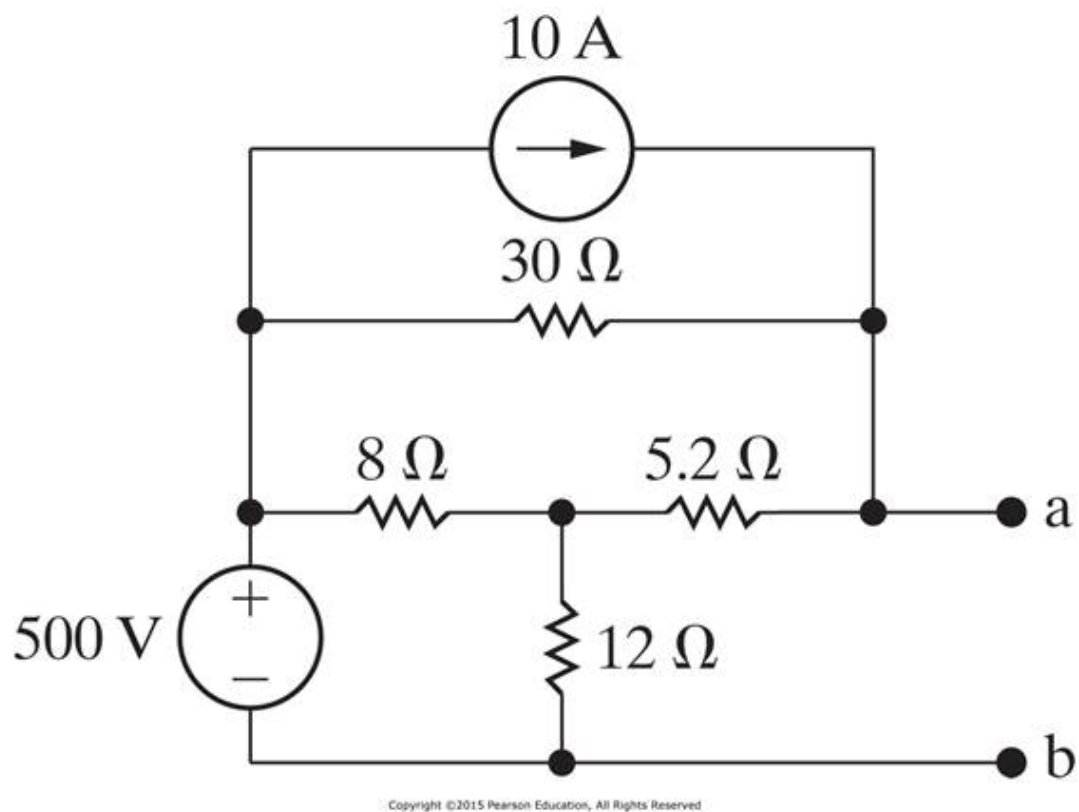

P4.67\_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 425 \text{ V}$$

$$R_{Th} = 7.5 \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$V_{Th} = 425 \text{ V}$$


$$R_{Th} = 7.5 \text{ } \Omega \text{ (Ohm)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Incorrect

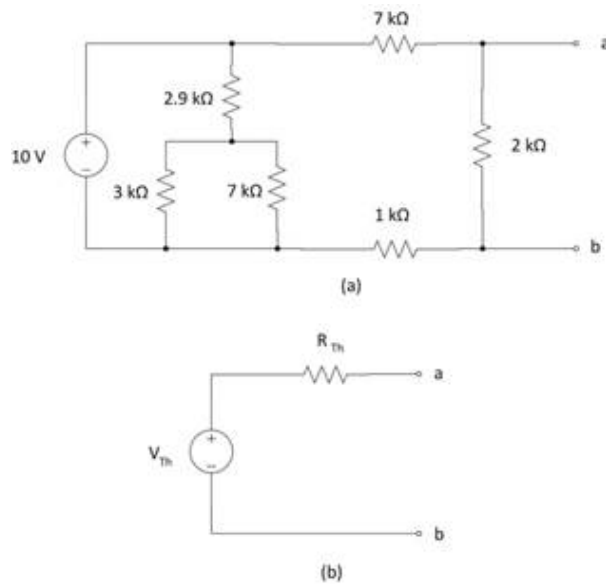Mark 0.00 out of  
10.00

AS4-02

The circuit in figure (a) is simplified to its Thévenin equivalent shown in (b).

Find the numerical values for  $V_{Th}$  and  $R_{Th}$

$$V_{Th} = 60 \text{ V}$$

$$R_{Th} = 20 \text{ k}\Omega \text{ (kilo Ohm)}$$

**Numeric Answer**

$$V_{Th} = 2 \text{ V}$$


$$R_{Th} = 1.6 \text{ k}\Omega$$

**Incorrect**

Marks for this submission: 0.00/10.00.

**Question 7**

Correct

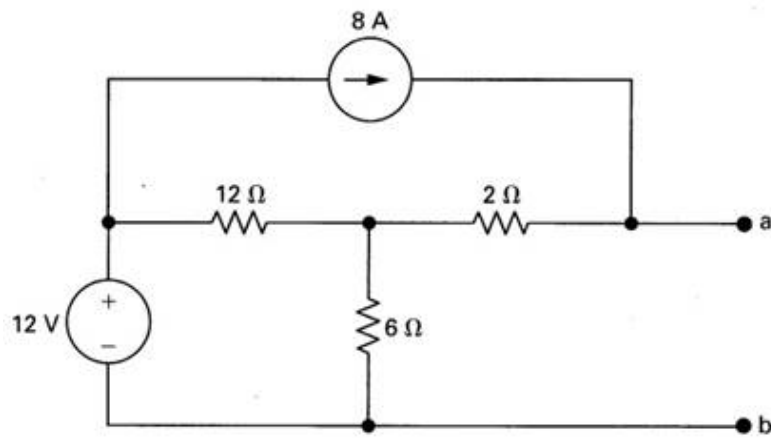Mark 10.00 out of  
10.00

P4.59\_6ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 52 \text{ V}$$

$$R_{Th} = 6 \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$V_{Th} = 52 \text{ V}$$


$$R_{Th} = 6 \text{ } \Omega \text{ (Ohm)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 8**

Correct

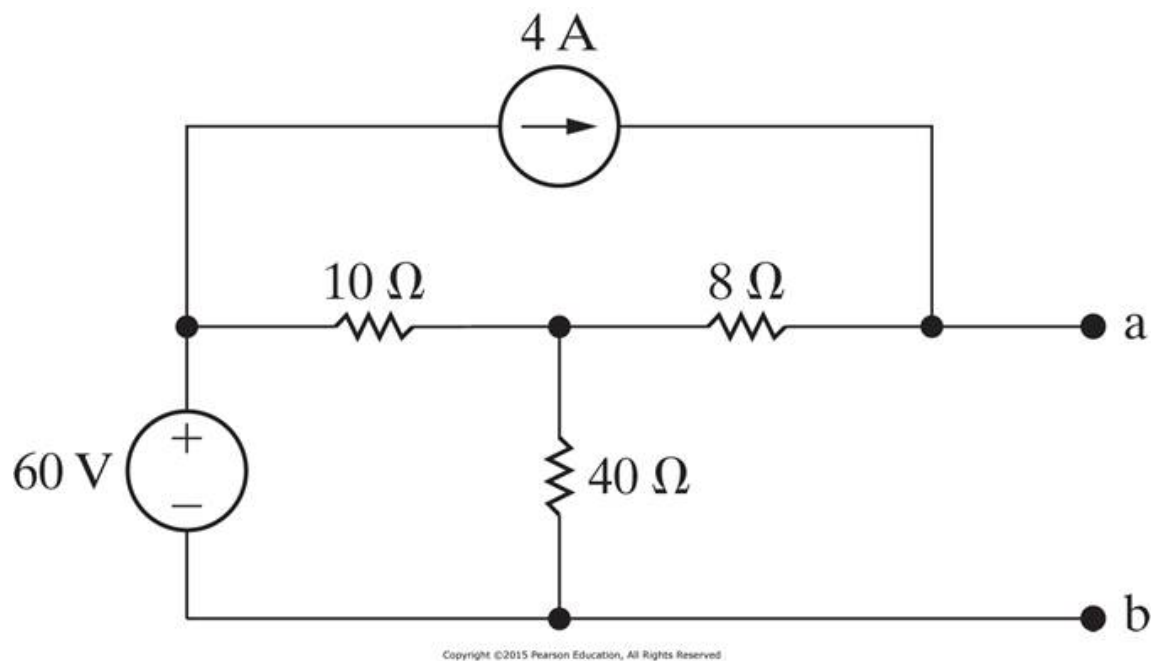Mark 10.00 out of  
10.00

P4.66\_10ed

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit.

$$I_N = 7 \text{ A}$$

$$R_{Th} = 16 \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$I_N = 7 \text{ A}$$

$$R_{Th} = 16 \text{ } \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.



**Question 9**

Correct

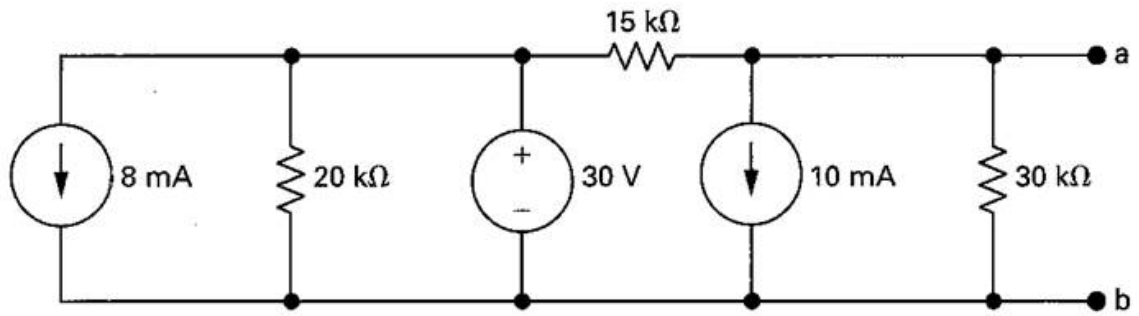Mark 10.00 out of  
10.00

P4.62\_6ed

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit. The Norton equivalent current should “point up”.

$$I_N = -8 \text{ mA (milli Amp)}$$

$$R_{Th} = 10 \text{ k}\Omega \text{ (kilo Ohm)}$$

**Numeric Answer**

$$I_N = -8 \text{ mA}$$

$$R_{Th} = 10 \text{ k}\Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 10**

Partially correct

Mark 5.00 out of 10.00

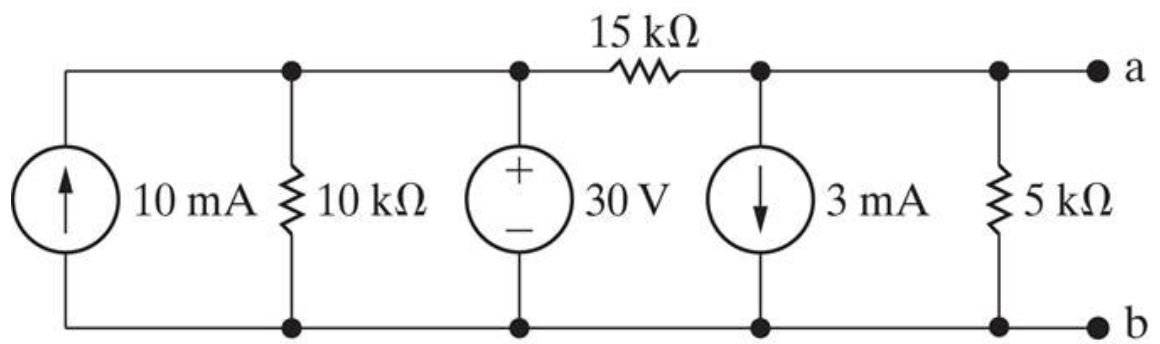

Copyright ©2015 Pearson Education, All Rights Reserved

P4.68\_10ed

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit.

$$I_N = \boxed{-1} \text{ mA}$$

$$R_{Th} = \boxed{3750} \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$I_N = -1 \text{ mA}$$

$$R_{Th} = 3.75 \text{ k}\Omega \text{ (Ohm)}$$

**Partially correct**

Marks for this submission: 5.00/10.00.