

Started on Wednesday, 22 February 2017, 10:57 AM**State** Finished**Completed on** Wednesday, 22 February 2017, 11:51 AM**Time taken** 54 mins 7 secs**Grade** 100.00 out of 100.00**Question 1**

Correct

Mark 15.00 out of 15.00

Q1bConsider the sinusoidal voltage $v(t) = 100 \cos(240 \pi t + 45^\circ) \text{ V}_{\text{rms}}$.

a) What is the maximum amplitude of the voltage?

$$V_m = 141.42 \checkmark \text{ V}$$

b) What is the frequency of $v(t)$ in hertz?

$$f = 120 \checkmark \text{ Hz}$$

c) What is the frequency of $v(t)$ in radians per second?

$$\omega = 753.6 \checkmark \text{ rad/sec}$$

d) What is the phase angle in radians?

$$\phi \text{ (phi)} = .785 \checkmark \text{ radians}$$

e) What is the period in milliseconds?

$$T = 8.3 \checkmark \text{ ms (milli sec)}$$

Correct

Marks for this submission: 15.00/15.00.

Question 2

Correct

Mark 5.00 out of 5.00

Q2aGiven: $x(t) = 100 \cos(300 t + 45^\circ) + 500 \cos(300 t - 60^\circ)$ Use the concept of the phasor to combine this sinusoidal function into a single trigonometric expression in the form similar to $x(t) = A \cos(\omega t + \theta^\circ)$.

$$\text{Magnitude } A \text{ of } x(t) = 483.85 \checkmark$$


$$\text{Angle } \theta \text{ of } x(t) = -48.48 \checkmark^\circ \text{ (Degree)}$$

Correct

Marks for this submission: 5.00/5.00.

Question 3

Correct

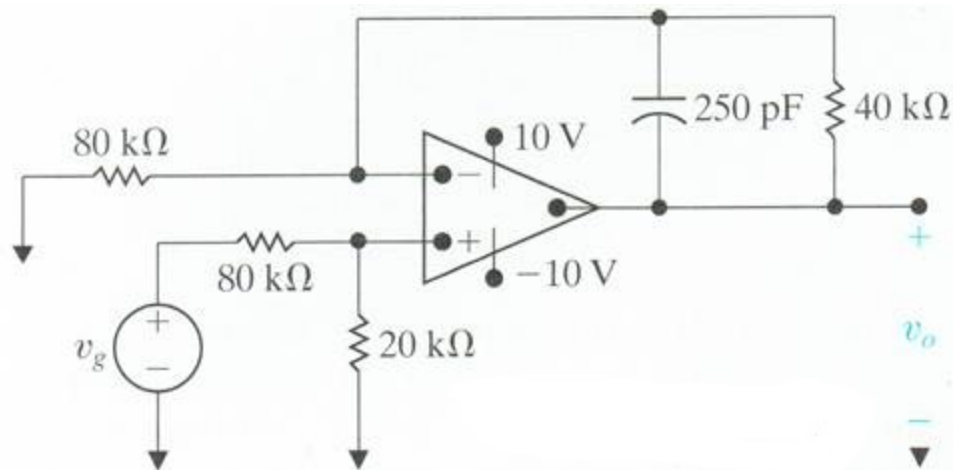Mark 15.00 out of
15.00

Q3c

Assume the operational amplifier is ideal.

Given $v_g(t) = -38.0$ V (a constant voltage)Find the steady-state output $v_o(t)$.

$$v_o(t) = \boxed{-10} \text{ Volts}$$


Correct

Marks for this submission: 15.00/15.00.

Question 4

Correct

Mark 10.00 out of 10.00

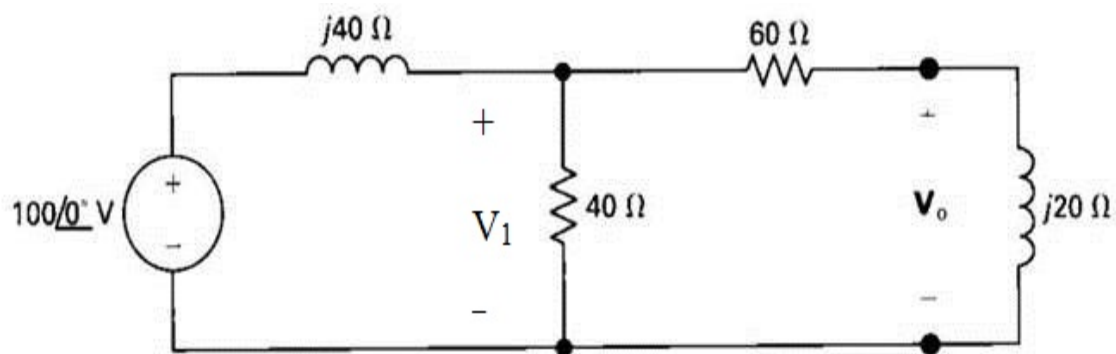

Q4a

Find the phasor voltages V_0 and V_1 . I suggest you use the Node Method. $V_0 = 15.8$ ✓ at angle 18.4 ✓ ° (Degrees) Volts $V_1 = 49.9$ ✓ at angle -53.1 ✓ ° (Degrees) Volts

Express your answer as a positive magnitude and then the angle in the appropriate quadrant.


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 15.00 out of 15.00

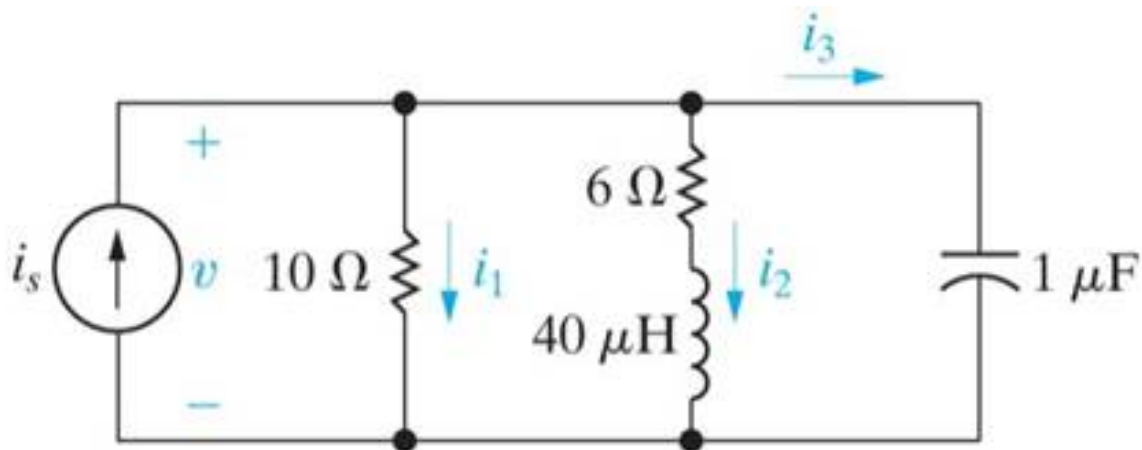

Q5b


Given $i_s = 20 \cos(100,000 t + 6.12^\circ)$ AmpsThe equivalent admittance of the circuit is $Y_{Eq} = 0.2166$ at angle 6.12° (Degrees) SiemensCalculate the average power absorbed/delivered by the 6Ω (Ohm) resistor. $P_{6\Omega} = 491.8033$ ✓ W “+” = absorbed “-” = delivered**Correct**

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 10.00 out of 10.00

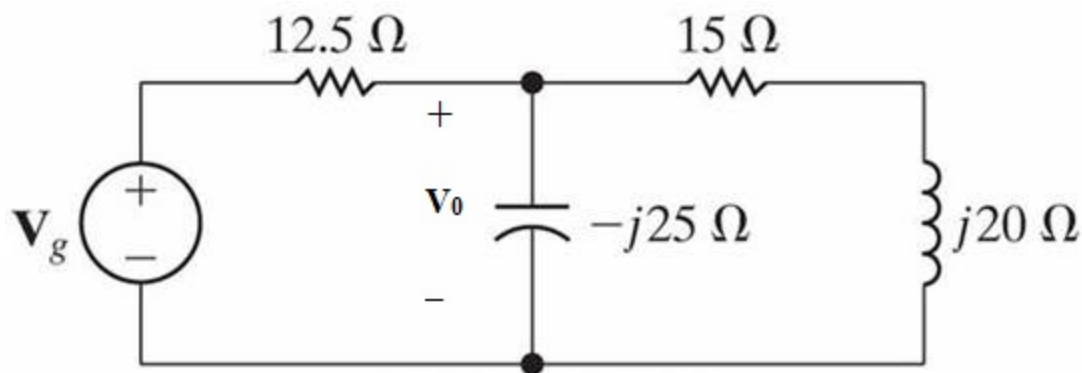

Q6a

Given:

The voltage source $V_g = 160$ at angle 0° V_{rms} and the voltage $V_0 = 122.714$ at angle -4.40° V_{rms} Find the average and reactive power for the voltage source V_g .

$$S_g = -481.2 + j 120.24 \text{ VA}$$

“+” = absorbed and “-” = delivered

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 5.00 out of 5.00

Q7d

Given that a balanced three-phase set of voltages is in the negative phase sequence where

$$v_a = 240 \cos(\omega t - 41^\circ) \text{ V.}$$

Find the other two phase voltages.

$$v_b = 240 \cos(\omega t + 79^\circ) \text{ V}$$

$$v_c = 240 \cos(\omega t - 161^\circ) \text{ V}$$


Correct

Marks for this submission: 5.00/5.00.

Question 8

Correct

Mark 15.00 out of 15.00

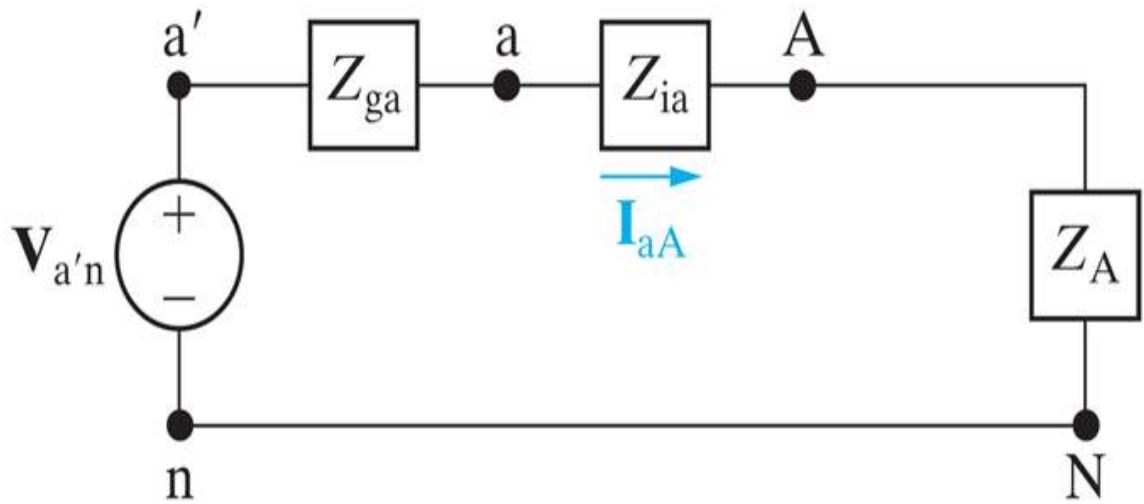

Q8a

Given: $V_{a'n} = 120$ at angle 0° V_{rms} in a balanced three phase system with a positive phase sequence.

The source and load are Y connected.

$$Z_{ga} = 1 + j15 \, \Omega \quad Z_{ia} = 19 + j5 \, \Omega \quad Z_A = 20 + j20 \, \Omega$$

Calculate the single phase equivalent line currents I_{aA} , I_{bB} and I_{cC} .

$$I_{aA} = 2.12 \checkmark \text{ at angle } -45 \checkmark^\circ \text{ (Degrees)} A_{\text{rms}}$$

$$I_{bB} = 2.12 \checkmark \text{ at angle } -165 \checkmark^\circ \text{ (Degrees)} A_{\text{rms}}$$

$$I_{cC} = 2.12 \checkmark \text{ at angle } 75 \checkmark^\circ \text{ (Degrees)} A_{\text{rms}}$$

Calculate the line to line voltages V_{AB} , V_{BC} , and V_{CA} .

$$V_{AB} = 103.92 \checkmark \text{ at angle } 30 \checkmark^\circ \text{ (Degrees)} V_{\text{rms}}$$

$$V_{BC} = 103.92 \checkmark \text{ at angle } -90 \checkmark^\circ \text{ (Degrees)} V_{\text{rms}}$$

$$V_{CA} = 103.92 \checkmark \text{ at angle } 150 \checkmark^\circ \text{ (Degrees)} V_{\text{rms}}$$

Correct

Marks for this submission: 15.00/15.00.

Question 9

Correct

Mark 10.00 out of
10.00

Q9a

The total apparent power supplied in a balanced three-phase Y-D system is 3,600 VA. The source line to neutral voltage is $240 \text{ V}_{\text{rms}}$. The line impedance is negligible and the power factor angle of the load is 35° lagging.

Determine the impedance of the load.

$$Z_{\Delta, \text{load}} = \boxed{39.32} \checkmark + j \boxed{27.5} \checkmark \Omega \text{ (Ohms)}$$

Correct

Marks for this submission: 10.00/10.00.