

---

**Started on** Tuesday, 6 September 2016, 2:06 PM

---

**State** Finished

---

**Completed on** Tuesday, 6 September 2016, 3:29 PM

---

**Time taken** 1 hour 23 mins

---

**Grade** 100.00 out of 100.00

---

**Question 1**

Correct

Mark 10.00 out of  
10.00

SI-05

In a science fiction show, an hour is  $\frac{1}{10}$  of a day and a minute is  $\frac{1}{100}$  of an hour (Centons). How many Centons are in two days of this science fiction show?

✓ Centons

**Question 2**

Correct

Mark 10.00 out of  
10.00


SI-04

A political rally in 1995 known as the "Million Man March" occurred on the National Mall. Assume the Washington DC subway was the sole means of transport. A subway train arrives every 1 minute (not really - just for this problem) and delivered 1,000 men each time. How long in minutes did it take for all the million men to arrive?

Arrival time period:  ✓ minutes.

**Question 3**

Correct

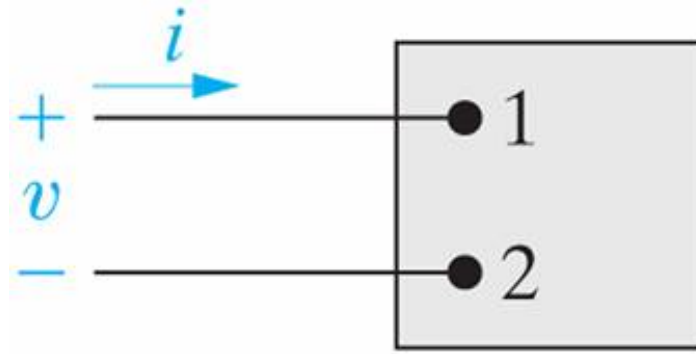Mark 10.00 out of  
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Inc.

P1.07\_10ed

There is no charge at the upper terminal of the ideal element in the above figure for  $t < 0$ .

At  $t = 0$  a current of  $125 e^{-2,500t}$  mA enters the upper terminal and will accumulate at the upper terminal.

a) Be able to derive the expression for the charge that accumulates at the upper terminal for  $t \geq 0$ .

$$q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$$

b) Find the total charge that accumulates at the upper terminal, i.e. let  $t \rightarrow \infty$ .

$$q(t \rightarrow \infty) = 50(1 - e^{(-2500t)}) \mu\text{C} \text{ (micro Coulomb)}$$

c) If the current is abruptly stopped at  $t = 0.5$  ms, how much charge has accumulated at the upper terminal?

$$q(t \rightarrow 0.5\text{ms}) = 35(1 - e^{-2500t}) \mu\text{C} \text{ (micro Coulomb)}$$

Coulomb)

**Numeric Answer**


a)  $q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$

b)  $q(t \rightarrow \infty) = 50 \mu\text{C} \text{ (micro Coulomb)}$

c)  $q(t \rightarrow 0.5\text{ms}) = 35.674 \mu\text{C} \text{ (micro Coulomb)}$

**Question 4**

Correct

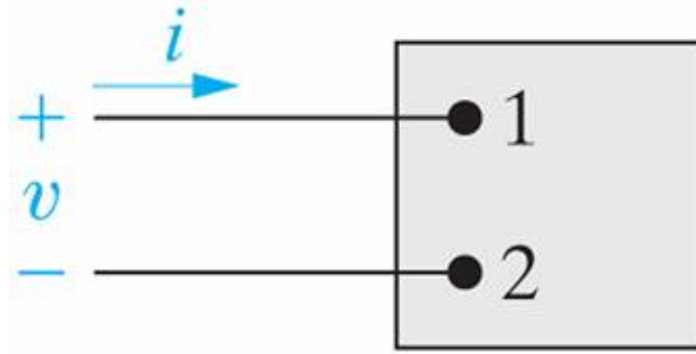Mark 10.00 out of  
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Inc.

P1.07\_10ed

There is no charge at the upper terminal of the ideal element in the above figure for  $t < 0$ .

At  $t = 0$  a current of  $125 e^{-2,500t}$  mA enters the upper terminal and will accumulate at the upper terminal.

a) Be able to derive the expression for the charge that accumulates at the upper terminal for  $t \geq 0$ .

$$q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$$

b) Find the total charge that accumulates at the upper terminal, i.e. let  $t \rightarrow \infty$ .

$$q(t \rightarrow \infty) = 50(1 - e^{(-2500t)}) \mu\text{C} \text{ (micro Coulomb)}$$

c) If the current is abruptly stopped at  $t = 0.5$  ms, how much charge has accumulated at the upper terminal?

$$q(t \rightarrow 0.5\text{ms}) = 35(1 - e^{-2500t}) \mu\text{C} \text{ (micro Coulomb)}$$

Coulomb)

**Numeric Answer**


a)  $q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$

b)  $q(t \rightarrow \infty) = 50 \mu\text{C} \text{ (micro Coulomb)}$

c)  $q(t \rightarrow 0.5\text{ms}) = 35.674 \mu\text{C} \text{ (micro Coulomb)}$

**Question 5**

Correct

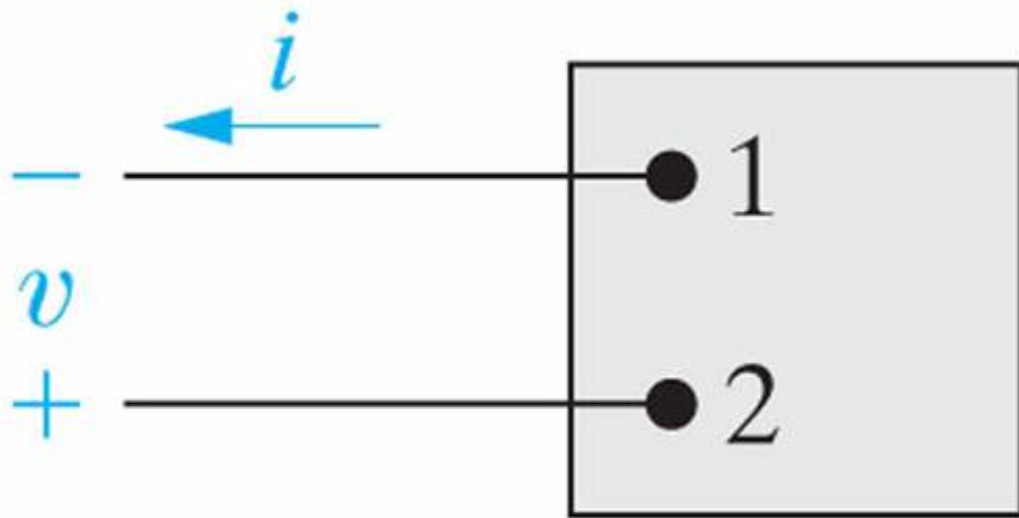Mark 10.00 out of  
10.00

PSS-1

Select the correct expression for power at the terminals 1,2 of the figure.

Select one:

- ☒ A.  $p = (+) v i$  ✓ Great! Current in the direction of voltage drop.
- ☐ B.  $p = (-) v i$


Your answer is correct.

A.  $p = (+) v i$ The correct answer is:  $p = (+) v i$

### Question 6

Correct

Mark 10.00 out of 10.00

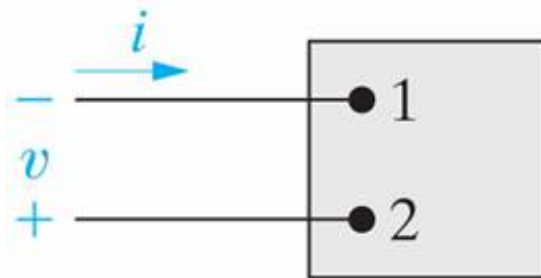

PSS-1

Select the correct expression for power at the terminals 1,2 of the figure.

Select one:

☐ A.  $p = (+) v i$

☒ B.  $p = (-) v i$  ✓

Great! You noticed that current is in the direction of voltage rise.

Your answer is correct.

A.  $p = (-) v i$

The correct answer is:  $p = (-) v i$

### Question 7

Correct

Mark 10.00 out of 10.00

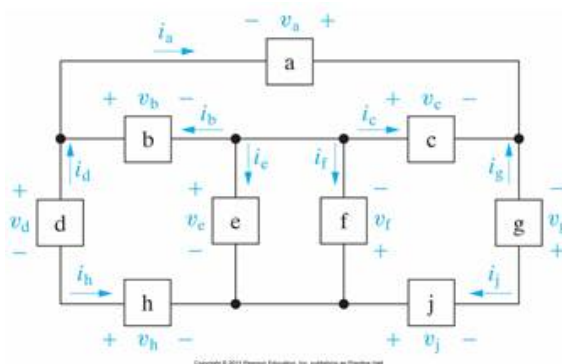


TABLE P1.30

Element	Voltage (V)	Current (mA)
a	1.6	80
b	2.6	60
c	-4.2	-50
d	1.2	20
e	1.8	30
f	-1.8	-40
g	-3.6	-30
h	3.2	-20
j	-2.4	30

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P1.30\_9ed

To be valid, the total power delivered in a complete circuit MUST equal the power absorbed by the circuit.

$P_{\text{abs}} + P_{\text{del}} = \text{zero}$  In other words, all energy is accounted for.

Use the circuit diagram and table to prove the circuit obeys this conservation-of-energy principle.

$$p_a = -128 \text{ mW}$$

$$p_b = -156 \text{ mW}$$

$$p_c = 210 \text{ mW}$$

$$p_d = -24 \text{ mW}$$

$$p_e = 54 \text{ mW}$$

$$p_f = -72 \text{ mW}$$

$$p_g = 108 \text{ mW}$$

$$p_h = -64 \text{ mW}$$

$$p_j = 72 \text{ mW}$$

### Solution

$$p_a = -v_a i_a = -(1.6)(0.080) = -128 \text{ mW}$$

$$p_b = -v_b i_b = -(2.6)(0.060) = -156 \text{ mW}$$

$$p_c = v_c i_c = (-4.2)(-0.050) = 210 \text{ mW}$$

$$p_d = -v_d i_d = -(1.2)(0.020) = -24 \text{ mW}$$

$$p_e = v_e i_e = (1.8)(0.030) = 54 \text{ mW}$$

$$p_f = -v_f i_f = -(-1.8)(-0.040) = -72 \text{ mW}$$

$$p_g = v_g i_g = (-3.6)(-0.030) = 108 \text{ mW}$$

$$p_h = v_h i_h = (3.2)(-0.020) = -64 \text{ mW}$$

$$p_j = -v_j i_j = -(-2.4)(0.030) = 72 \text{ mW}$$

### Question 8

Correct

Mark 10.00 out of  
10.00


### P1.12\_9ed

One 12V battery supplies 100 mA to a music player.  
How much energy does the battery supply in 4 hours?

$$W = 17280 \text{ J}$$

**Question 9**

Correct

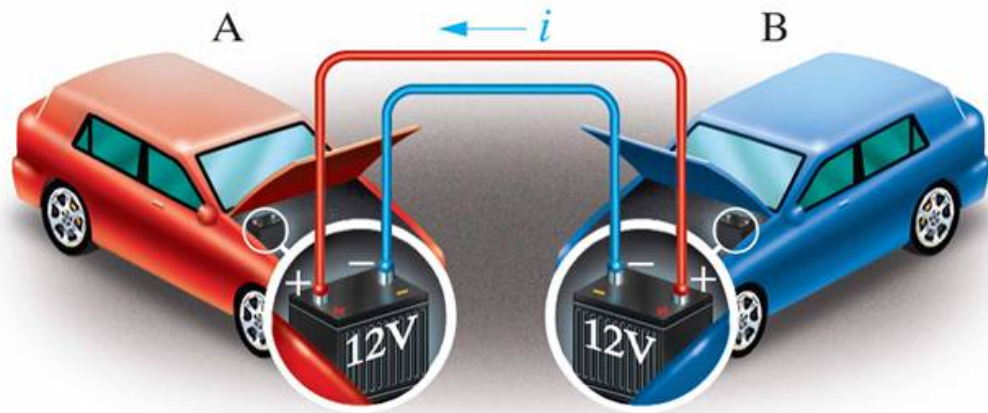Mark 10.00 out of  
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P1.11a\_9ed

You find out that your car's battery is dead. A friend "jumps" your battery as shown in the figure.

What is the color of your car? {Red} Red or Blue?

Select one:

☒ A. Red - Car A ✓

You correctly noted that the current is flowing into battery A and is thus receiving energy (i.e. being charged).

☐ B. Blue - Car B

☐ C. Not enough information shown.

Your answer is correct.

**Correct answer text**

Car A - red.

The correct answer is: Red - Car A

**Question 10**

Correct

Mark 10.00 out of  
10.00

P1.12\_9ed

One 12V battery supplies 100 mA to a music player.

How much energy does the battery supply in 4 hours?

W =  ✓ J