

Sam Lee
CPE 166 – 03
Advanced Logic Design Lab
Wednesday: 5PM -7:50 PM
Lecture Professor: Jing Pang
Lab Professor: Eric Carmi
Lab #2 Report

Contents	
Introduction	3
Part 1:8-Bit Carry Select Adder Design	3
Design Purpose	3
Engineering Data:	3
Source Code.....	8
Simulation Waveforms	13
Results Discussion.....	15
Part 2: 4 By 4 Binary Sequential Multiplier Design	16
Design Purpose	16
Engineering Data	16
Source Code.....	20
User Constraint File.....	28
Simulation Waveforms	29
Results Discussion.....	31
Part 3: Character Displays On 8-Digit Multiplexed Seven Segment Displays	32
Design Purpose	32
Engineering Data	33
Source Code.....	33
User Constraint File.....	35
Results Discussion.....	36
Conclusion	37

Introduction

This lab was a three part lab that served as an introduction to hierarchical design in Verilog. We were tasked with designing an 8-bit carry select adder, 4x4 binary sequential multiplier design, using multiplexed seven segment displays to display out initials and CPE 166 on the NEXYS4 DDR board. In this lab we learned hierarchical design strategy using VHDL, carry select adder designed, sequential shift/add multiplication algorithm, how to use multiplexed seven segment display, simulate a Verilog design, and learn to use a NEXYS4 DDR FPGA board. We are doing this lab because while Lab 1 introduced us to Verilog and VIVADO, we did not explore how to design FPGAs so in Lab 2 we explore how to do these via the concepts in this lab, which is a carry select adder, learn to create a sequential shift binary multiplier and a multiplexed seven segment display. These concepts are important because they explore many elements of circuit design and how to create a hierarchical design like combinational and sequential logic, creating a finite state machine, etc.

Part 1: 8-Bit Carry Select Adder Design

Design Purpose:

In order to create an 8 bit adder, I first built 2 half adders that consist of an XOR and an AND gate. Half adders can add two 1-bit together. Then, by calling on 2 half adders, I was able to create a full adder which can add two 2 bits variable. Next, I built a 4 bit ripple carry adder using 4 full adders in order to add two variable of 4-bits. Lastly, Lastly, I moved on to build a multiplexer which is essentially a switch that output 1 of two input depending on an extra input. Finally, I built the 8-bit ripple carry adder with the modules connected.

Engineering Data:

Figure 1: Half Adder Truth Table, Schematic, and Symbol

A half adder adds two 1-bit binary inputs and generates two 1-bit outputs, in which includes 1-bit carry out.

Table 2-1. Half adder truth table

Inputs		Outputs	
a	b	cout	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
Logic equations:			
$\text{cout} = a \cdot b$			
$\text{sum} = a \oplus b$			

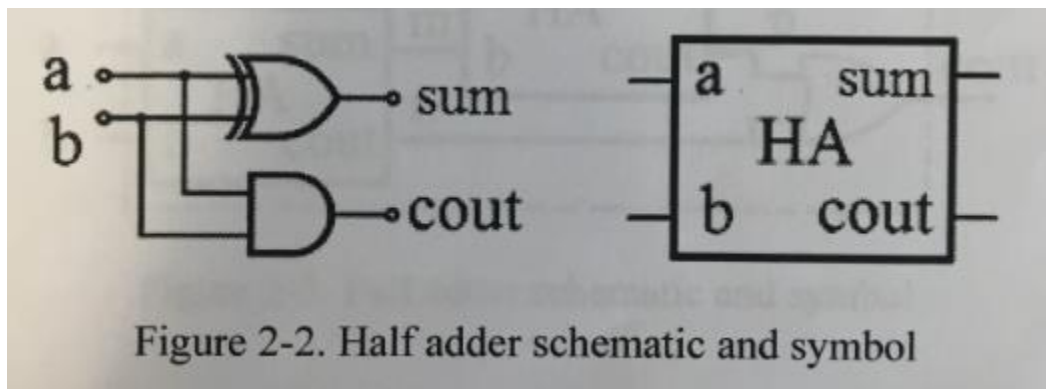


Figure 3: Full Adder Truth Table, Schematic, and Symbol

A full adder is a logical circuit that performs an addition operation on three one-bit binary numbers. The full adder produces a sum of the three inputs and carry value.

Table 2-2. Full adder truth table

Inputs			Outputs	
a	b	cin	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
Logic equations: $\text{sum} = a \oplus b \oplus \text{cin}$ $\text{cout} = (a \oplus b) \text{cin} + a b$				

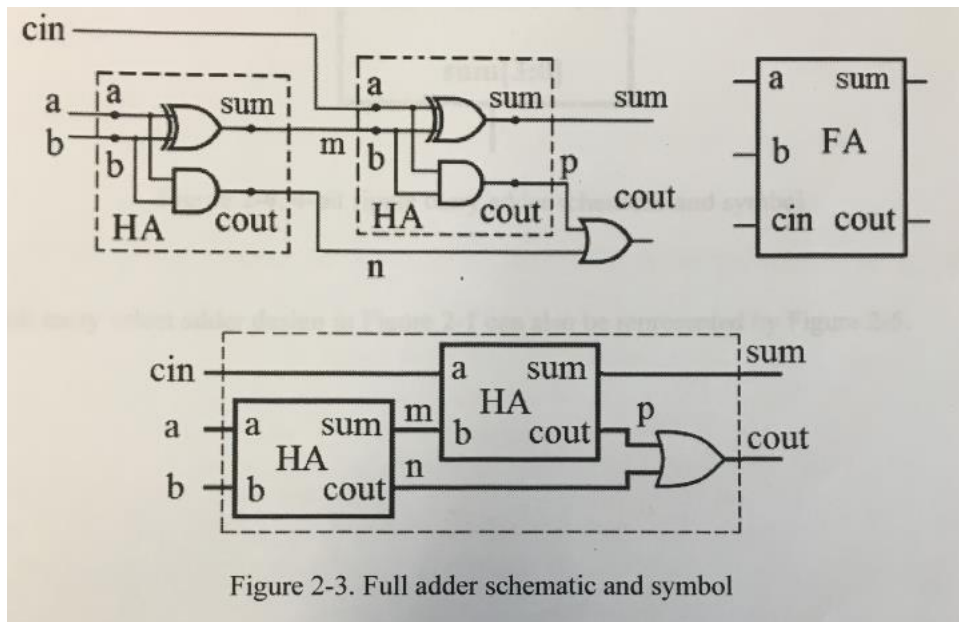


Figure 2-3. Full adder schematic and symbol

Figure 5: 4-Bit Ripple Carry Adder Schematic

In a ripple carry adder, the sum and carry out bits of any half adder stage is not valid until the carry in of that stage occurs. Propagation delays inside the logic circuitry is the reason behind this. Propagation delay is time elapsed between the application of an input and occurrence of the corresponding output. Consider a NOT gate, When the input is “0” the output will be “1” and vice versa. The time taken for the NOT gate’s output to become “0” after the application of logic “1” to the NOT gate’s input is the propagation delay here. Similarly, the carry propagation delay is the time elapsed between the application of the carry in signal and the occurrence of the carry out (Cout) signal. Circuit diagram of a 4-bit ripple carry adder is shown below.

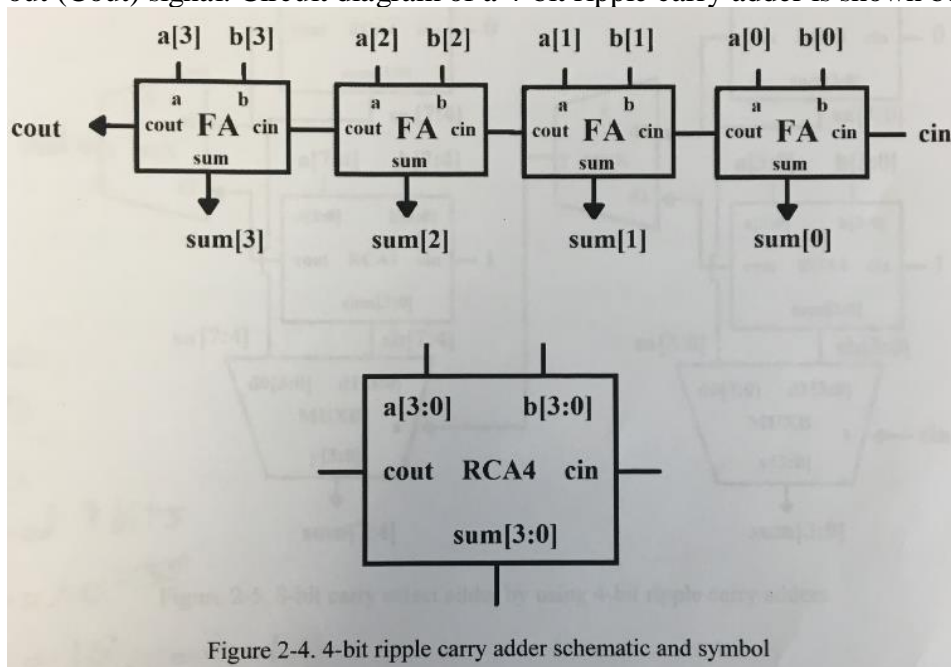


Figure 2-4. 4-bit ripple carry adder schematic and symbol

Figure 6: MUX and MUXB Truth Table and Schematic

A multiplexer (or mux) is a common digital circuit used to mix a lot of signals into just one. If you want multiple sources of data to share a single, common data line, you'd use a multiplexer to run them into that line. Multiplexers come in all sorts of shapes and sizes, but they're all made out of logic gates. Every multiplexer has at least one select line, which is used to select which input signal gets relayed to the output. In a 2-to-1 multiplexer, there's just one select line. More inputs means more select lines: a 4-to-1 multiplexer would have 2 select lines, an 8-to-1 has 3, and so on (2^n inputs requires n select lines). Think of a mux as a "digital switch". The select line is the throw on the switch, it chooses which of the many inputs get to be the output.

Table 2-3. MUX truth table

Input	Output
s	y
0	d0
1	d1

Table 2-4. MUXB truth table

Input	Output
s	y[3:0]
0	d0[3:0]
1	d1[3:0]

 


Figure 8: 8-Bit Carry Select Adder By Using 4-Bit Ripple Carry Adders

To wrap it all up, we will be combining all the previous designs into one (the CSA8). This design includes two of the 4-bit ripple carry adders and two of each multiplexer. Two RCA4 will assume the carry in is 1 and the other two will assume carry in is 0. The multiplexers' role in this is to choose the right sum and carry out based on the carry in value. This method of addition is far faster than an 8-bit ripple carry adder.

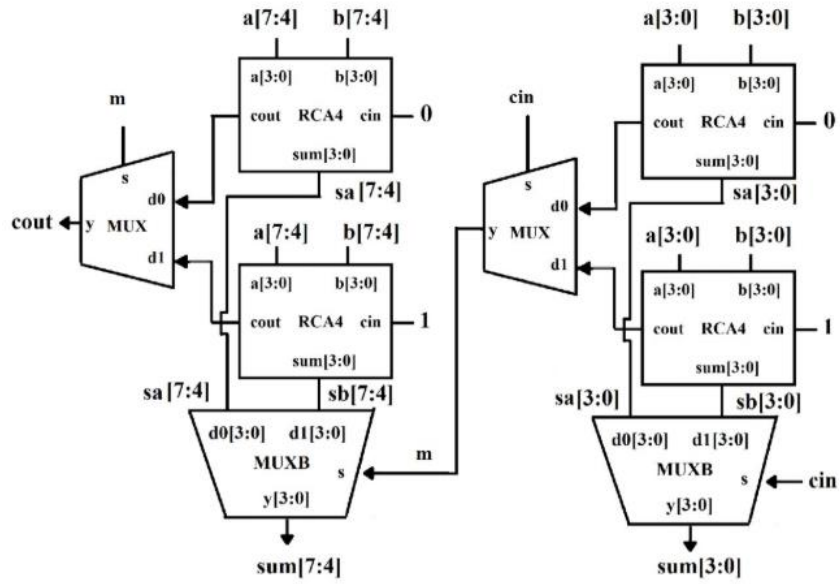


Figure 2-5. 8-bit carry select adder by using 4-bit ripple carry adders

Source Code:

Half Adder Verilog and Test Bench Code:

```
`timescale 1ns / 1ps
```

```
module ha( a, b, cout, sum);
```

```
input  a, b;
```

```
output cout, sum;
```

```
assign cout = a & b;
```

```
assign sum = a ^ b;
```

```
// xor  g1 (sum, a, b);
```

```
// and  g2 (cout, a, b);
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

```
module halfadder_tb;
```

```
reg a, b;
```

```
wire cout, sum;
```

```
ha u1 ( .a(a), .b(b), .cout(cout), .sum(sum) );
```

```
initial begin
```

```
{ a, b } = 2'b00;
```

```
#10
```

```
{ a, b } = 2'b01;
```

```
#10
```

```
{ a, b } = 2'b10;
```

```
#10
```

```
{ a, b } = 2'b11;
```

```
#10
```

```
$stop;
```

```
end
```

```
initial $monitor($time, "ns, a=%b, b=%b, cout=%b, sum=%b", a, b, cout, sum);
```

```
endmodule
```

Full Adder Verilog and Test Bench Code:

```
`timescale 1ns / 1ps
```

```
module fa( a, b, cin, cout, sum);
```

```
input  a, b, cin;
```

```
output cout, sum;
```



```

wire m, n, p;

ha  g1 (.cout(n), .sum(m), .a(a), .b(b) );
ha  g2 (.cout(p), .sum(sum), .a(cin), .b(m) );

assign cout = p | n;

endmodule

module fulladder_tb;

reg    a, b, cin;
wire   cout, sum;

fa u1 ( a, b, cin, cout, sum );

initial begin
    {a, b, cin} = 3'b000;
    #10 {a, b, cin} = 3'b001;
    #10 {a, b, cin} = 3'b010;
    #10 {a, b, cin} = 3'b011;
    #10 {a, b, cin} = 4;
    #10 {a, b, cin} = 5;
    #10 {a, b, cin} = 6;
    #10 {a, b, cin} = 7;
    #10 $stop;
end

initial $monitor($time, "ns, a=%b, b=%b, cin = %b, cout=%b, sum=%b", a, b, cin, cout, sum);

endmodule

4-Bit Ripple Carry Adder Verilog and Test Bench Code:
`timescale 1ns / 1ns
module rca (a, b, cin, cout, sum);
input [3:0] a,b;
input    cin;

output [3:0] sum;
output    cout;

wire [2:0] m;

```

```

fa    h1(.cout(m[0]), .sum(sum[0]), .a(a[0]), .b(b[0]), .cin(cin));
fa    h2(.cout(m[1]), .sum(sum[1]), .a(a[1]), .b(b[1]), .cin(m[0]));
fa    h3(.cout(m[2]), .sum(sum[2]), .a(a[2]), .b(b[2]), .cin(m[1]));
fa    h4(.cout(cout), .sum(sum[3]), .a(a[3]), .b(b[3]), .cin(m[2]));

endmodule

`timescale 1ns / 1ns
module rca_tb;

reg [3:0]    a, b;
reg         cin;
wire [3:0]   sum;
wire        cout;
wire [3:0]   res;

assign res = { cout, sum};

rca u1 ( a, b, cin, cout, sum);

initial begin
a = 2; b = 4; cin = 0;
    #10 a = 3; b = 3; cin = 1;
    #10 a = 5; b = 6; cin = 1;
    #10 a = 7; b = 7; cin = 1;

    #10 $stop;
end

initial $monitor($time, "ns, a=%d, b=%d, cin = %d, addition result = %d", a, b, cin, res);

endmodule

```

MUX Verilog and Test Bench Code:

```

`timescale 1ns / 1ns
module mux2to1(d1, d0, s, y);
input  d1, d0, s;
output y;
reg    y;

always@(d1 or d0 or s)
begin
    if (s) y = d1;
    else  y = d0;
end

```

```
endmodule
```

```
`timescale 1ns / 1ns
module mux2to1_tb;
reg    d1, d0, s;
wire   y;
```

```
mux2to1  u1 (d1, d0, s, y);
initial begin
    d1 = 0; d0 = 0; s = 0;
    #10 d1 = 0; d0 = 0; s = 1;
    #10 d1 = 0; d0 = 1; s = 0;
    #10 d1 = 0; d0 = 1; s = 1;
    #10 d1 = 1; d0 = 0; s = 0;
    #10 d1 = 1; d0 = 0; s = 1;
    #10 d1 = 1; d0 = 1; s = 0;
    #10 d1 = 1; d0 = 1; s = 1;
    #10 $stop;
end
```

```
initial $monitor($time, "ns, d1=%b, d0=%b, s = %b, y=%b", d1, d0, s, y);
```

```
endmodule
```

MUXB Verilog and Test Bench Code:

```
`timescale 1ns / 1ns
module muxb(d1, d0, s, y);
input [3:0] d1, d0;
input      s;
output [3:0] y;
reg  [3:0] y;
```

```
always@(d1 or d0 or s)
begin
    if (s) y = d1;
    else  y = d0;
end
```

```
endmodule
```

```
`timescale 1ns / 1ns
module muxb_tb;

reg [3:0] d1,d0;
reg s;
wire [3:0] y;
```

```
muxb k1(d1, d0, s, y);
```

```
initial begin
```

```
    d1 = 4'b0000; d0 = 4'b0000; s = 0;
```

```
    #10 d1 = 4'b0001; d0 = 4'b0000; s = 0;
```

```
    #10 d1 = 4'b0001; d0 = 4'b0010; s = 0;
```

```
    #10 d1 = 4'b1001; d0 = 4'b0000; s = 1;
```

```
    #10 d1 = 4'b1001; d0 = 4'b1000; s = 1;
```

```
    #10 d1 = 4'b0001; d0 = 4'b1100; s = 1;
```

```
    #10 $stop;
```

```
end
```

```
initial $monitor($time, "ns, d1=%b, d0=%b, s = %b, y= %b", d1, d0, s, y);
```

```
endmodule
```

8-Bit Carry Select Adder Verilog and Test Bench Code:

```
`timescale 1ns / 1ps
```

```
module CSA8(a , b, cin, cout, sa, sb, sum);
```

```
    input [7:0] a, b;
```

```
    input cin;
```

```
    output [7:0] sa, sb, sum;
```

```
    output cout;
```

```
    wire c1, c2, c3, c4, m;
```

```
    rca r1(.a(a[3:0]), .b(b[3:0]), .cin(0), .cout(c1), .sum(sa[3:0]));
```

```
    rca r2(.a(a[3:0]), .b(b[3:0]), .cin(1), .cout(c2), .sum(sb[3:0]));
```

```
    muxb mb1(.d1(sb[3:0]), .d0(sa[3:0]), .s(cin), .y(sum[3:0]));
```

```
    mux2to1 m1(.d1(c2), .d0(c1), .s(cin), .y(m));
```

```
    rca r3(.a(a[7:4]), .b(b[7:4]), .cin(0), .cout(c3), .sum(sa[7:4]));
```

```
    rca r4(.a(a[7:4]), .b(b[7:4]), .cin(1), .cout(c4), .sum(sb[7:4]));
```

```
    muxb mb2(.d1(sb[7:4]), .d0(sa[7:4]), .s(m), .y(sum[7:4]));
```

```
    mux2to1 m2(.d1(c4), .d0(c3), .s(m), .y(cout));
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

```

module CSA8_tb;
    reg cin;
    reg [7:0] a,b;

    wire cout;
    wire [7:0] sum;

    CSA8 u1(a, b, cin, cout, sa, sb, sum);

    initial begin
        cin = 1'b0; a = 8'b0000_1000; b = 8'b1001_1100;
        #10;
        cin = 1'b1; a = 8'b0000_1001; b = 8'b1101_1100;
        #10;
        cin = 1'b0; a = 8'b0000_1001; b = 8'b1001_1100;
        #10;
        cin = 1'b1; a = 8'b0100_1000; b = 8'b1001_1100;
        #10;
        cin = 1'b0; a = 8'b0010_1000; b = 8'b1001_1100;
        #10;
        cin = 1'b0; a = 8'b0100_1000; b = 8'b1001_1100;
        #10;
        cin = 1'b0; a = 8'b0100_1000; b = 8'b1001_1100;
        #10 $stop;
    end
endmodule

```

Simulation Waveforms:

 


Figure 1: This figure above is the half adder simulation. A half adder adds the two values without CIN and this waveform shows that.

 


Figure 2: This figure above is the full adder simulation. A full adder is a half adder with cin, this waveform shows this to be the case.

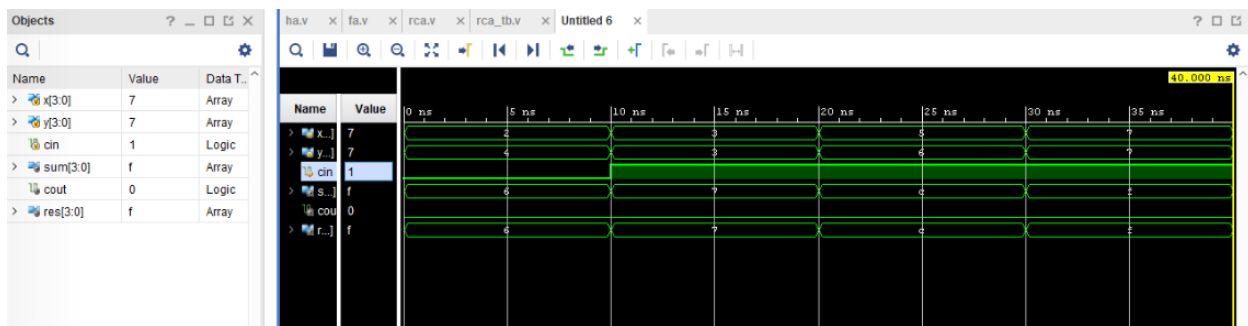


Figure 3: This figure above is the 4-bit ripple carry adder simulation. RCA4 is full bit adders feeding into each other, allowing you to add 4 bit numbers. This waveform shows this to be the case

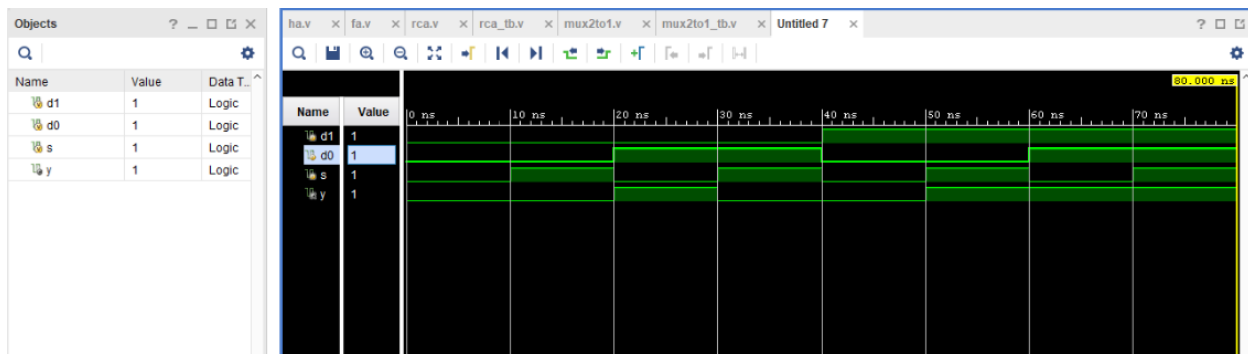


Figure 4: This figure above is the MUX simulation. A multiplexer selects from the two, this waveform shows a multiplexer in action.

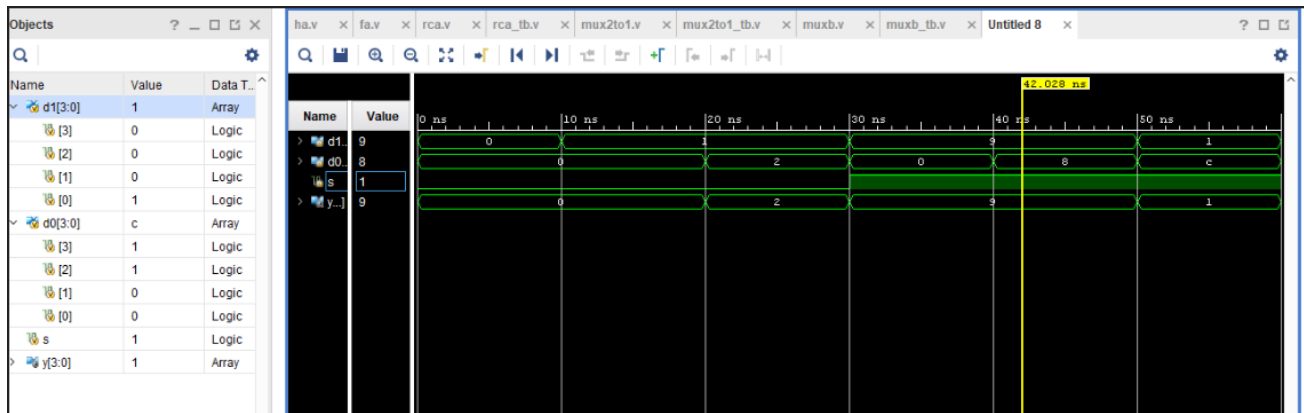


Figure 5: This figure above is the MUXB simulation. MUXB is a 4 bit multiplexer, this shows that it selects properly.

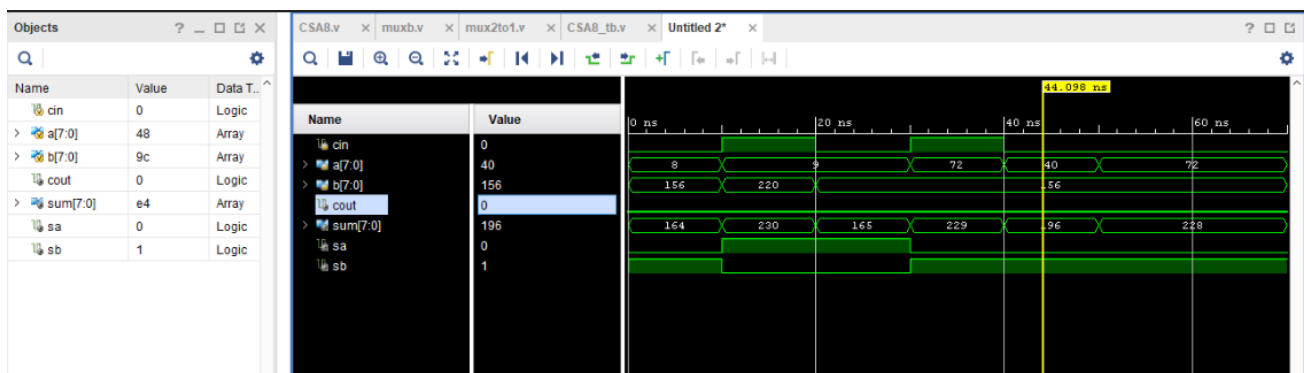


Figure 6: This figure above is the 8-bit carry select adder simulation. CSA8 is an 8 bit adder - this waveform shows that CSA8 adds properly.

Results Discussion:

The results of this part of the lab met the expectations, which was the CSA8 adds two 8 bit numbers properly and all the other Verilog files were correct. I had issues creating the CSA8, but by putting all files together but after some time I figured it out with the help of learning how to read the schematic diagram. The key findings of this part of the lab were how to use combinational logic via making a 4 bit RCA4, and putting it together with multiplexers to create an 8 bit carry adder and it went well.

Part 2: 4 By 4 Binary Sequential Multiplier Design


Design Purpose:

The purpose of this lab is to create a 4 bit binary shift multiplier with an FSM controlling it. This part of the lab consists of 7 modules - 2 four bit shift registers with one acting as a loader and one actually shifting, a multiplexer which emulates binary emulation, a 4 bit adder, a 8 bit shift register which stores the current product, a mult module which contains the elements that the FSM controls, the FSM itself and a TOP module which includes everything.

Engineering Data:

Overall Design:

A 4 by 4 sequential multiplier uses shift and add algorithm. At every clock cycle, the multiplier is shifted right by one bit and its value is tested. If the value is zero, a zero value is added to the accumulator, and the result is shifted right by one bit. If the value is one, the multiplicand value is added to the accumulator and the result is shifted right by one bit. The result is obtained when all the values have been tested.

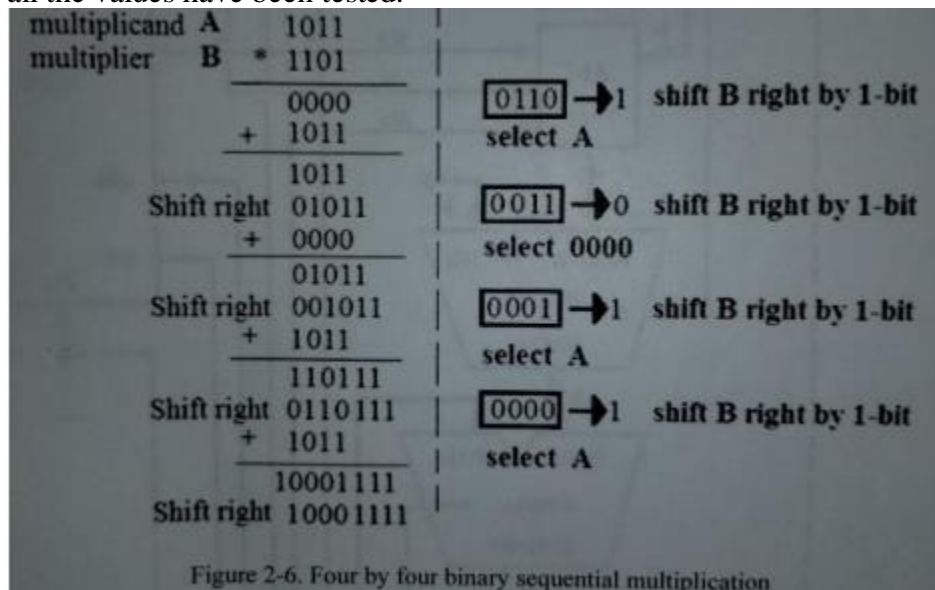

0011

0001

0000

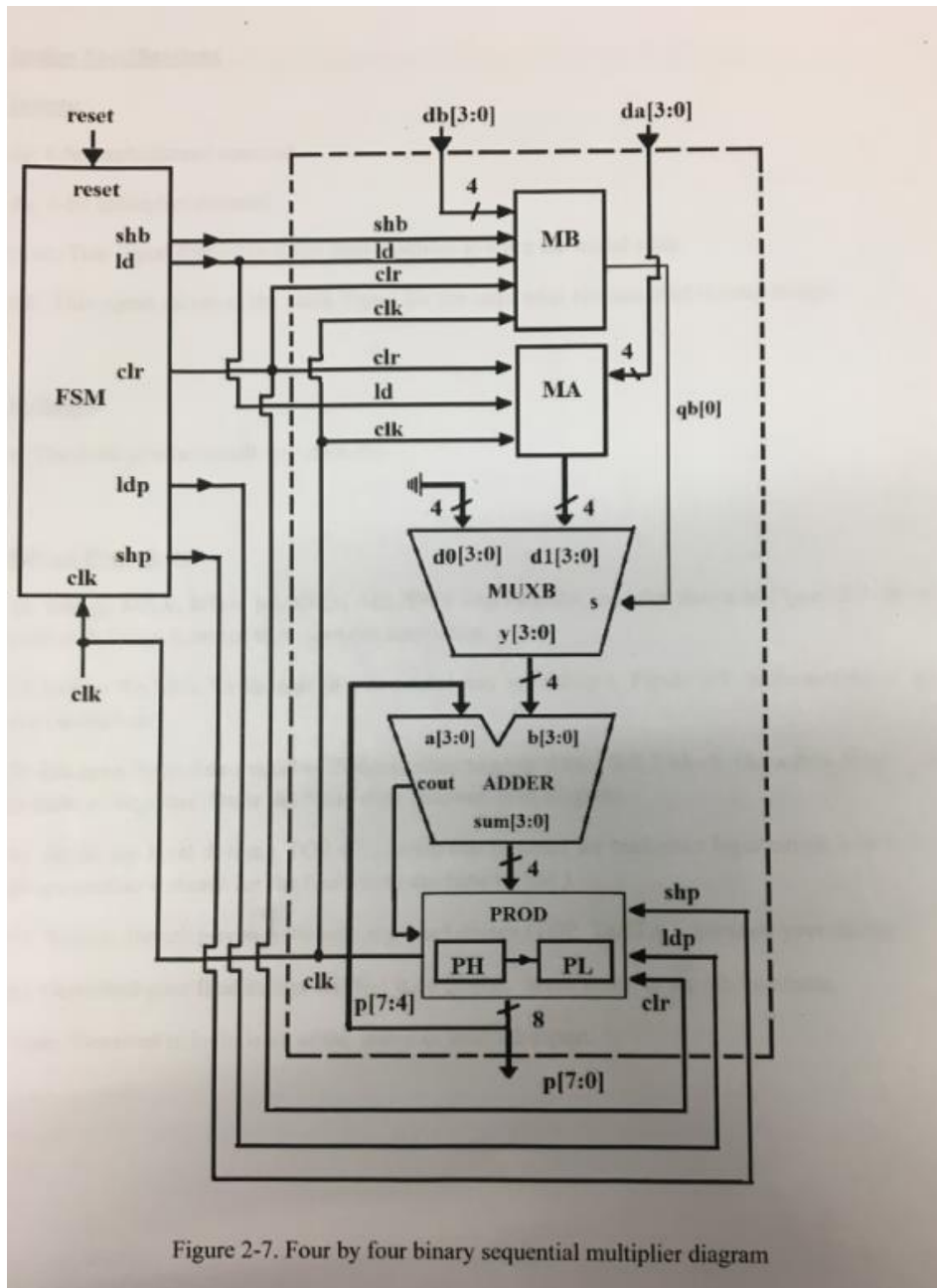


Figure 2-7. Four by four binary sequential multiplier diagram

Figure 1: The figure below is the MA and MB. MA is a shift register that doesn't shift (takes data in) and MB shifts

 


Figure 2: The figure below is the MUXB. MUXB is a 4 bit multiplexer.

 


Table 2-4. MUXB truth table

Input	Output
s	y[3:0]
0	d0[3:0]
1	d1[3:0]

Figure 3: The figure below is the ADDER. The adder adds 2 4-bit numbers together.

 


Figure 4: The figure below is the PROD. PROD is an 8 bit shift register split in half - PH is the first half and loads Cin and SUM, PL gets from PH.

 


Figure 5: This figure below is the MULT.


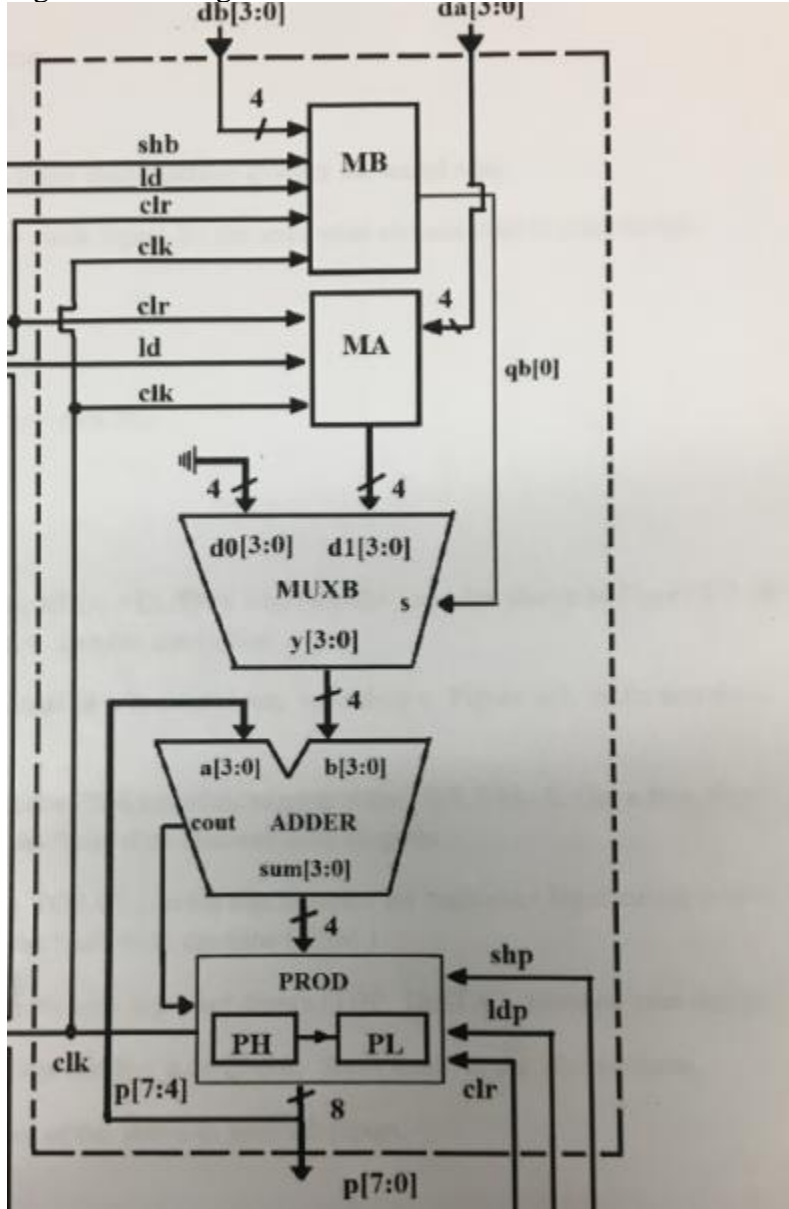


Figure 6: The figure is below is the FSM.

 

Source Code:

MA and MB Verilog and Test Bench Code:

```

`timescale 1ns / 1ps
module MA(clk, clr, ld, da, qa);
  input  clk, clr, ld;
  input [3:0] da;
  output [3:0] qa;

  reg [3:0] qa;

  always@(posedge clr or posedge clk)
  begin
    if(clr) qa <= 0;
    else if (ld)
      qa <= da;
    end
endmodule

`timescale 1ns / 1ps
module MA_tb;
  reg  clk, clr, ld;
  reg [3:0] da;

  wire [3:0] qa;

  MA uut(.clk(clk), .clr(clr), .ld(ld), .da(da), .qa(qa));

  initial clk = 0;

  always #10 clk = ~clk;

  initial
  begin
    clr = 1;
    da = 4'b1011;
  end
endmodule

```

```

        #24 clr = 0; ld = 1;
        #24 ld = 0;

        #60 $stop;
    end

endmodule

`timescale 1ns / 1ps
module MB(clk, clr, ld, shb, db, qb);
    input    clk, clr, ld, shb;
    input [3:0] db;
    output [3:0] qb;

    reg [3:0] qb;

    always@(posedge clr or posedge clk)
    begin
        if(clr) qb <= 0;
        else if (ld)
            qb <= db;
        else if (shb)
            qb <= { 1'b0, qb[3:1] };

        // qb[3] <= 1'b0;
        // qb[2] <= qb[3];
        // qb[1] <= qb[2];
        // qb[0] <= qb[1];

    end
endmodule

`timescale 1ns / 1ps
module MB_tb;
    reg    clk, clr, ld, shb;
    reg [3:0] db;
    wire [3:0] qb;

    MB uut (clk, clr, ld, shb, db, qb);

    initial clk = 0;
    always #10 clk = ~ clk;

    initial
    begin

```

```

        clr = 1; ld = 0; shb = 0; db = 4'b1011;
        #22    ld = 1;
        #20 shb = 1;
        #60 $stop;
    end
endmodule

```

ADDER Verilog and Test Bench Code:

```

`timescale 1ns / 1ps
module ADDER(a, b, sum, cout);
    input [3:0] a, b;

    output [3:0] sum;
    output cout;

    assign {cout,sum} = a + b;

endmodule

`timescale 1ns / 1ps
module ADDER_tb;
    reg [3:0] a,b;

    wire [3:0] sum;
    wire cout;

    ADDER g1(.a(a), .b(b), .sum(sum), .cout(cout));

    initial begin
        a = 4'b0000; b = 4'b0001;
        #10
        a = 4'b1000; b = 4'b0101;
        #10
        a = 4'b0011; b = 4'b0101;
        #10
        a = 4'b1010; b = 4'b0101;
        #10 $stop;
    end
endmodule

```

PROD Verilog and Test Bench Code:

```

`timescale 1ns / 1ps
module PROD(sum, shp, ldp, clr, clk, cout, p);
    input [3:0] sum;
    input shp, ldp, clr, clk, cout;

```

```

output [7:0] p;
reg [7:0] p;

always@(posedge clr or posedge clk)
begin
    if(clr) p <= 0;
    else if(ldp) p[7:3] <= {cout, sum};
    else if(shp) begin
        p[7:3] <= {1'b0, p[7:4]};
        p[2:0] <= {p[3], p[2:1]};
    end
end
endmodule

`timescale 1ns / 1ps
module PROD_tb;
reg cin, shp, ldp, clr, clk;
reg [3:0] sum;
wire [7:0] p;

PROD uu1PROD(sum, shp, ldp, clr, clk, p, cin);

initial clk = 0;
always #10 clk = ~clk;

initial
begin
    sum = 4'b1011; cin = 1; shp = 0; ldp = 0; clr = 1;
    #10
    clr = 0;
    #10;
    shp = 1;
    #10
    ldp = 1;
    #10
    ldp = 0;
    #60 $stop;
end
endmodule

```

MULT Verilog and Test Bench Code:

```

`timescale 1ns / 1ns
module MULT(da, db, p, ld, shb, clr, clk, shp, ldp);

input [3:0] db , da;
input ld, ldp, shb, shp, clk, clr;

```

```

output [7:0] p;

wire [3:0] null, a, qa, mux_out, add_out, qb;
wire cout;

assign null = 4'b0000;

MB g1 (.clk(clk), .clr(clr), .ld(ld), .shb(shb), .db(db), .qb(qb));

MA g2 (.clk(clk), .clr(clr), .ld(ld), .da(da), .qa(qa));

MUXB g3 (.d1(qa), .d0(null), .s(qb[0]), .y(mux_out));

ADDER g4 (.a(p[6:3]), .b(mux_out), .sum(add_out), .cout(cout));

PROD g5 (.sum(add_out), .cout(cout), .shp(shp), .ldp(ldp), .clr(clr), .p(p), .clk(clk));

endmodule

`timescale 1ns / 1ns
module MULT_tb;
reg [3:0] da, db;
reg ld, shb, clr, clk, shp, ldp;
wire [7:0] p;

MULT g1(da, db, p, ld, shb, clr, clk, shp, ldp);

initial clk = 0;
always #10 clk = ~clk;

initial begin
    da = 4'b1011; db = 4'b1101; ld = 0; shb = 0; clr = 1; shp = 0; ldp = 0;
    #20 clr = 0;
    #20 ld = 1;
    #20 ld = 0;

    #20 ldp = 1;
    #20 ldp = 0;

    #20 shb = 1;
    #20 shb = 0;

    #20 shp = 1;
    #20 shp = 0;

```



```

#20 ldp = 1;
#20 ldp = 0;

#20 shb = 1;
#20 shb = 0;

#20 shp = 1;
#20 shp = 0;

#20 ldp = 1;
#20 ldp = 0;

#20 shb = 1;
#20 shb = 0;

#20 shp = 1;
#20 shp = 0;

#20 ldp = 1;
#20 ldp = 0;

#20 $stop;

end
endmodule

FSM Verilog Code:
`timescale 1ns / 1ns
module FSM(reset, clk, shb, ld, clr, ldp, shp );

    input clk, reset;

    output shb, ld, clr, ldp, shp;
    reg shb, ld, clr, ldp, shp;

    reg [3:0] cs, ns;
    parameter s0 = 0, s1 = 1, s2 = 2, s3 = 3, s4 = 4, s5 = 5,
    s6 = 6, s7 = 7, s8 = 8, s9 = 9, s10 = 10, s11 = 11, s12 = 12,
    s13 = 13;

    always @(posedge clk or posedge reset ) begin
        if(reset)
            cs <= s0;
        else
            cs <= ns;

```

end

```
always @(cs)
begin
  case(cs)
    s0: ns = s1;
    s1: ns = s2;
    s2: ns = s3;
    s3: ns = s4;
    s4: ns = s5;
    s5: ns = s6;
    s6: ns = s7;
    s7: ns = s8;
    s8: ns = s9;
    s9: ns = s10;
    s10: ns = s11;
    s11: ns = s12;
    s12: ns <= s12;
    //s13: ns <= s13;
    default: ns <= s0;
  endcase
end
```

```
always @(cs)
begin
  case (cs)
    s0:begin
      clr = 1;ld = 0; shp = 0; shb = 0; ldp = 0;
    end

    s1:begin
      clr = 0;ld = 1; shp = 0; shb = 0; ldp = 0;
    end
    //-----
    s2:begin
      clr = 0;ld = 0; shp = 0; shb = 0; ldp = 1;
    end
    //-----
    s3:begin
      clr = 0;ld = 0; shp = 1; shb = 0; ldp = 0;
    end

    s4:begin
      clr = 0;ld = 0; shp = 0; shb = 1; ldp = 0;
    end
```

```

s5:begin
clr = 0;ld = 0; shp = 0; shb = 0; ldp = 1;
end
//-----
s6:begin
clr = 0;ld = 0; shp = 1; shb = 0; ldp = 0;
end

s7:begin
clr = 0;ld = 0; shp = 0;shb = 1; ldp = 0;
end

s8:begin
clr = 0;ld = 0; shp = 0; shb = 0; ldp = 1;
end
//-----
s9:begin
clr = 0;ld = 0; shp = 1; shb = 0; ldp = 0;
end

s10:begin
clr = 0;ld = 0; shp = 0; shb = 1; ldp = 0;
end

s11:begin
clr = 0;ld = 0; shp = 0; shb = 0; ldp = 1;
end
//-----
s12:begin
clr = 0;ld = 0; shp = 0; shb = 0; ldp = 0;
end

default: begin
clr = 0;ld = 0; shp = 0;shb = 0; ldp = 0;
end
endcase
end
endmodule

```

TOP Verilog Code and Test Bench Code:

```

`timescale 1ns / 1ps
module TOP(reset,clk,db,da,p);
input reset,clk;
input [3:0] db,da;
output[7:0] p;

```

```

wire shb,ld,clr,ldp,shp;
MULT g1(.da(da), .db(db), .p(p), .ld(ld), .shb(shb), .clr(clr), .clk(clk), .shp(shp), .ldp(ldp));
FSM g2(.reset(reset), .clk(clk), .shb(shb), .ld(ld),.clr(clr), .ldp(ldp), .shp(shp));

endmodule

```

```

`timescale 1ns / 1ps
module TOP_tb;
reg [3:0] da,db;
reg reset, clk;
wire [7:0] p;

TOP g1(reset,clk,db,da,p);

initial clk =0;
always #10 clk = ~clk;

initial begin
    //da = 4'b1011; db = 4'b1101; reset = 1;
    //da = 4'b1010; db = 4'b1010; reset = 1;
    da = 4'b1011; db = 4'b1101; reset = 1;
    #20 reset = 0;
    #400 $stop;
end
endmodule

```

User Constraints File:

```

set_property -dict { PACKAGE_PIN E3 IOSTANDARD LVCMOS33 } [get_ports clk];
create_clock -period 10.000 -name sys_clk_pin -waveform {0 5} -add [get_ports clk];

```

```

set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { da[0]
}]; #IO_L24N_T3_RS0_15 Sch=sw[0]
set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { da[1]
}]; #IO_L3N_T0_DQS_EMCCCLK_14 Sch=sw[1]
set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { da[2]
}]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { da[3]
}]; #IO_L13N_T2_MRCC_14 Sch=sw[3]

```

```

set_property -dict { PACKAGE_PIN R17 IOSTANDARD LVCMOS33 } [get_ports { db[0]
}]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
set_property -dict { PACKAGE_PIN T18 IOSTANDARD LVCMOS33 } [get_ports { db[1]
}]; #IO_L7N_T1_D10_14 Sch=sw[5]
set_property -dict { PACKAGE_PIN U18 IOSTANDARD LVCMOS33 } [get_ports { db[2]
}]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]

```

```

set_property -dict { PACKAGE_PIN R13  IOSTANDARD LVCMOS33 } [get_ports { db[3]
}]; #IO_L5N_T0_D07_14 Sch=sw[7]

#set_property -dict { PACKAGE_PIN T8  IOSTANDARD LVCMOS18 } [get_ports {
SW[8] }]; #IO_L24N_T3_34 Sch=sw[8]
#set_property -dict { PACKAGE_PIN U8  IOSTANDARD LVCMOS18 } [get_ports {
SW[9] }]; #IO_25_34 Sch=sw[9]
#set_property -dict { PACKAGE_PIN R16  IOSTANDARD LVCMOS33 } [get_ports {
SW[10] }]; #IO_L15P_T2_DQS_RDWR_B_14 Sch=sw[10]
#set_property -dict { PACKAGE_PIN T13  IOSTANDARD LVCMOS33 } [get_ports {
SW[11] }]; #IO_L23P_T3_A03_D19_14 Sch=sw[11]
#set_property -dict { PACKAGE_PIN H6  IOSTANDARD LVCMOS33 } [get_ports {
SW[12] }]; #IO_L24P_T3_35 Sch=sw[12]
#set_property -dict { PACKAGE_PIN U12  IOSTANDARD LVCMOS33 } [get_ports {
SW[13] }]; #IO_L20P_T3_A08_D24_14 Sch=sw[13]
#set_property -dict { PACKAGE_PIN U11  IOSTANDARD LVCMOS33 } [get_ports {
SW[14] }]; #IO_L19N_T3_A09_D25_VREF_14 Sch=sw[14]

set_property -dict { PACKAGE_PIN V10  IOSTANDARD LVCMOS33 } [get_ports { reset
}]; #IO_L21P_T3_DQS_14 Sch=sw[15]


set_property -dict { PACKAGE_PIN H17  IOSTANDARD LVCMOS33 } [get_ports { p[0]
}]; #IO_L18P_T2_A24_15 Sch=led[0]
set_property -dict { PACKAGE_PIN K15  IOSTANDARD LVCMOS33 } [get_ports { p[1]
}]; #IO_L24P_T3_RS1_15 Sch=led[1]
set_property -dict { PACKAGE_PIN J13  IOSTANDARD LVCMOS33 } [get_ports { p[2]
}]; #IO_L17N_T2_A25_15 Sch=led[2]
set_property -dict { PACKAGE_PIN N14  IOSTANDARD LVCMOS33 } [get_ports { p[3]
}]; #IO_L8P_T1_D11_14 Sch=led[3]
set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports { p[4]
}]; #IO_L7P_T1_D09_14 Sch=led[4]
set_property -dict { PACKAGE_PIN V17  IOSTANDARD LVCMOS33 } [get_ports { p[5]
}]; #IO_L18N_T2_A11_D27_14 Sch=led[5]
set_property -dict { PACKAGE_PIN U17  IOSTANDARD LVCMOS33 } [get_ports { p[6]
}]; #IO_L17P_T2_A14_D30_14 Sch=led[6]
set_property -dict { PACKAGE_PIN U16  IOSTANDARD LVCMOS33 } [get_ports { p[7] }];
#IO_L18P_T2_A12_D28_14 Sch=led[7]

```

Simulation Waveforms:

Figure 1: This figure below is the simulation of MA and MB. MA loads data in, this shows this to be true. MB is a shift register which outputs the carry, this waveform shows that MB is working properly.

MA:

 

MB:

 


Figure 2: This figure below is the simulation of the MUXB. MUXB is a four bit multiplier, this waveform shows it is selecting properly.

 


Figure 3: This figure below is the simulation of the ADDER. ADDER adds the two values together, this shows it is adding properly.

 


Figure 4: This figure below is the simulation of the PROD. The PROD is an 8 bit shift register, this waveform shows it loads values properly and shifts them over properly.

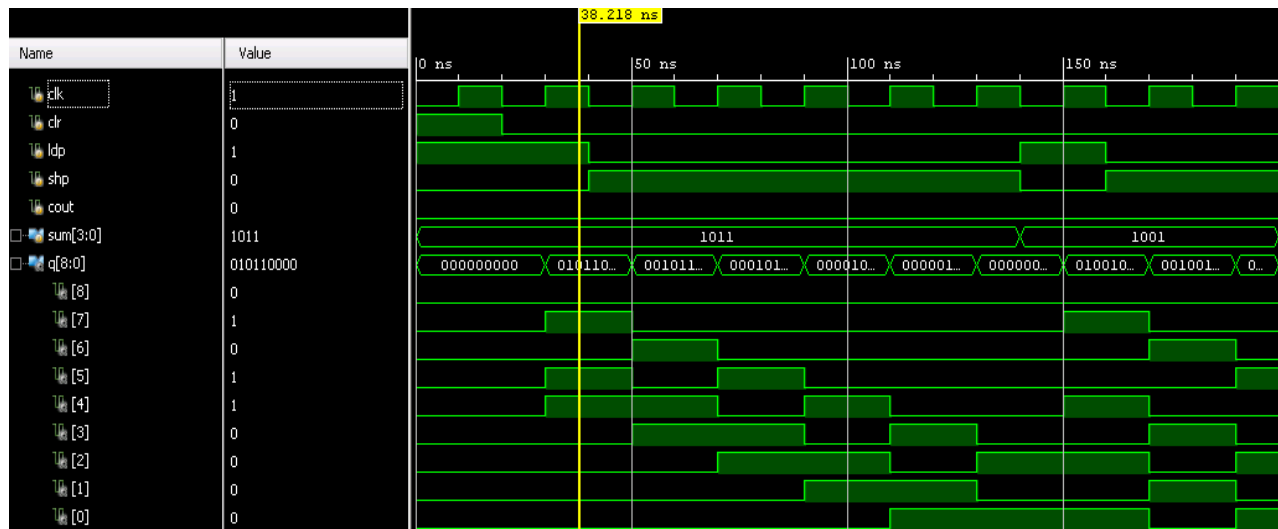


Figure 5: This figure below is the simulation of the MULT. MULT is a module that contains everything FSM controls. This test bench shows that each component works properly together in the way that it should. It loads, it does the operations, it shifts properly.


 


Figure 6: This figure below is the simulation for the TOP. TOP is the result of the multiplier, the values in display should be multiplied values of da and db at the end, this waveform shows that TOP, and everything in TOP is working properly.

 


Results Discussion:

The results of this part of the lab met the expectations - the 4 binary segmental multiplier multiplies values properly. I had issues mainly with PROD and MULT - I was trying to make prod with two 4-bit shift registers but was having issues loading it in, I resolved them by making PROD an 8 bit shift register, and MULT was having issues getting things loading properly and I fixed it with troubleshooting skills. The key findings of this part of the lab were how to put these components together and use sequential logic with the FSM to control all of these components, I had a lot of issues during the process of this lab but figured out the elements in the end. In this

part of the lab we figured out how to create shift registers and FSM and got complex circuits to work together, in the end though we had a multiplier on the FPGA that produces correct values. This part of the lab taught us a lot about how Verilog, Vivado and the NEXYS board works and while it was challenging it was very rewarding in the end.

Figure 1: This figure below is the result of multiplying 1011 and 1101 together.

 

Part 3: Character Displays On 8-Digit Multiplexed Seven Segment Displays

Design Purpose:

For this final part of the lab, I was expected to display “CPE 166” and my initials “SL”. This required me to understand how to access each cathode and each segment in each cathode in order to turn the segments on in a pattern that is recognizable as a number or letter. In order to do this, I must first understand the common Anode which allows you to understand which letter to turn high in order to activate a certain part of 1 segment display. By turning on the correct segments of each display, I was able to turn the segments into a recognizable letter or number. I also had to understand which pins to connect in order to access each cathode.

Engineering Data:

Figure 1: This figure is a common anode seven segment display device.

The schematic of the internal structure of one common anode seven segment display device is shown in Figure 2-8.

 


Figure 2-8. Internal schematic of one common anode seven segment display device

Figure 2: This figure below is the 8-digit seven segment displays on the NEXXYS4 DDR FPGA board.

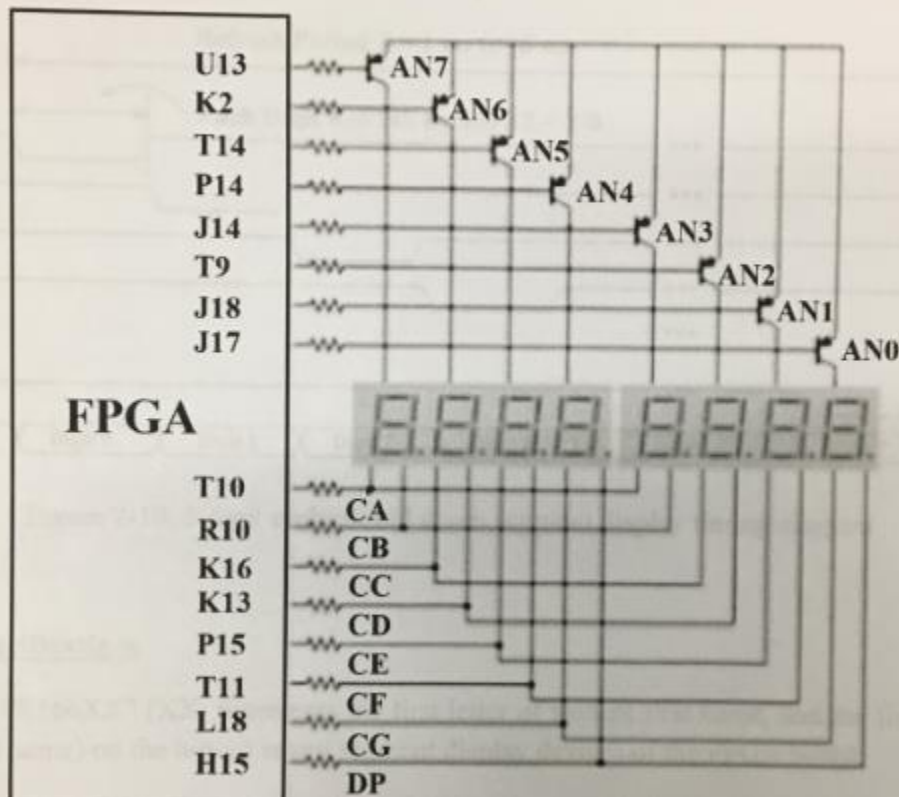


Figure 2-9. 8-digit seven segment displays on the NEXXYS4 DDR FPGA board

Source Code:
``timescale 1ns / 1ps`

```
module fpga_fun( clk, seg, dig);
```

```
input    clk;
output [7:0] seg;
output [7:0] dig;
```

```
parameter N = 18;
```

```
reg [N-1:0] count;
reg [3:0]  dd;
reg [7:0]  seg;
reg [7:0]  an;
```

```
always @ (posedge clk)
```

```
begin
    count <= count + 1;
```

```
    case(count[N-1:N-3])
    3'b000 :
        begin
            dd = 4'd7;
            an = 8'b11111110;
        end
```

```
    3'b001:
        begin
            dd = 4'd6;
            an = 8'b11111101;
        end
```

```
    3'b010:
        begin
            dd = 4'd5;
            an = 8'b11111011;
        end
```

```
    3'b011:
        begin
            dd = 4'd4;
            an = 8'b11110111;
        end
```

```
    3'b100 :
        begin
            dd = 4'd3;
            an = 8'b11101111;
```

```

        end

3'b101:
    begin
        dd = 4'd2;
        an = 8'b11011111;
    end

3'b110:
    begin
        dd = 4'd1;
        an = 8'b10111111;
    end

3'b111:
    begin
        dd = 4'd0;
        an = 8'b01111111;
    end
endcase
end
assign dig = an;

always @ (dd)
begin
    seg[7] = 1'b1;
    case(dd)
        4'd0 : seg[6:0] = 7'b1000110; //to display C
        4'd1 : seg[6:0] = 7'b0001100; //to display P
        4'd2 : seg[6:0] = 7'b0000110; //to display E
        4'd3 : seg[6:0] = 7'b1111001; //to display 1
        4'd4 : seg[6:0] = 7'b0000010; //to display 6
        4'd5 : seg[6:0] = 7'b0000010; //to display 6
        4'd6 : seg[6:0] = 7'b0010010; //to display S
        4'd7 : seg[6:0] = 7'b1000111; //to display L
        default : seg[6:0] = 7'b1111111; //blank
    endcase
end

endmodule

```

User Constraints File:

```

set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 } [get_ports { clk }];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz

```

```

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports { clk }];

set_property -dict { PACKAGE_PIN T10  IOSTANDARD LVCMOS33 } [get_ports { seg[0]
}]; #IO_L24N_T3_A00_D16_14 Sch=ca
set_property -dict { PACKAGE_PIN R10  IOSTANDARD LVCMOS33 } [get_ports { seg[1]
}]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16  IOSTANDARD LVCMOS33 } [get_ports { seg[2]
}]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13  IOSTANDARD LVCMOS33 } [get_ports { seg[3]
}]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports { seg[4]
}]; #IO_L13P_T2_MRCC_14 Sch=ce
set_property -dict { PACKAGE_PIN T11  IOSTANDARD LVCMOS33 } [get_ports { seg[5]
}]; #IO_L19P_T3_A10_D26_14 Sch=cf
set_property -dict { PACKAGE_PIN L18  IOSTANDARD LVCMOS33 } [get_ports { seg[6]
}]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15  IOSTANDARD LVCMOS33 } [get_ports { seg[7]
}]; #IO_L19N_T3_A21_VREF_15 Sch=dp


set_property -dict { PACKAGE_PIN J17  IOSTANDARD LVCMOS33 } [get_ports { dig[0]
}]; #IO_L23P_T3_FOE_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN J18  IOSTANDARD LVCMOS33 } [get_ports { dig[1]
}]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9   IOSTANDARD LVCMOS33 } [get_ports { dig[2] }];
#IO_L24P_T3_A01_D17_14 Sch=an[2]
set_property -dict { PACKAGE_PIN J14  IOSTANDARD LVCMOS33 } [get_ports { dig[3]
}]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14  IOSTANDARD LVCMOS33 } [get_ports { dig[4]
}]; #IO_L8N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14  IOSTANDARD LVCMOS33 } [get_ports { dig[5]
}]; #IO_L14P_T2_SRCC_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2   IOSTANDARD LVCMOS33 } [get_ports { dig[6]
}]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13  IOSTANDARD LVCMOS33 } [get_ports { dig[7]
}]; #IO_L23N_T3_A02_D18_14 Sch=an[7]

```

Results Discussion:

The results of this part of the lab met the expectations - we managed to manipulate the 7-segment display. This lab was pretty much smooth sailing with no major issues. The key findings of this part of the lab were how to use write constraint files as well as how the anodes and diodes work with the seven-segment display to show values, and things went smoothly. This part of the lab taught us a lot about how the seven-segment display works as well as constraint works, and it went smoothly.

Figure 1: This figure below is CPE166SI on the board.

 

Conclusion:

Overall, this lab helped me learn more about Verilog, taught me how to use the NEXYS4 board/VIVADO and how combinational and sequential logic works. Part 1 introduced us to hierarchical design by breaking the design into several components. We then used these parts to learn how to create a carry select adder. Part 2 then introduced us to sequential design with the FSM and we had to create a sequential shift/add multiplication algorithm/circuit. Part 3 taught us how to use a multiplexed seven segment display. Throughout the process of both part 1 and 2 we learned how to write test benches and create waveform simulations, while part 2 and 3 showed us how to use constraint files to download a program into the NEXYS4 FPGA board. After this lab I have a better understanding of hierarchical, combinational and sequential design, as well as a better understanding of Verilog, VIVADO, and the NEXYS4 Board. Overall the lab was challenging but went well and I learned a lot from the lab.

