

Quiz - 3

For CpE 151, 5 lowest grade questions will be dropped. For EEE234 2 questions will be dropped.

Name: _____

✓ 1. DC Analysis is used to evaluate which of the following information?

- a. Noise Analysis
- b. Band width
- c. Slew-Rate
- ☒ d. Bias Conditions/Operating point

X 2. AC Analysis is used to evaluate which of the following information?

- ☒ a. Noise Analysis
- ☒ b. Band width
- ☒ c. Slew-Rate
- d. Bias Conditions/Operating point

✓ 3. Transient Analysis is used to evaluate which of the following information?

- a. Noise Analysis
- b. Band width
- ☒ c. Slew-Rate
- d. Bias Conditions/Operating point

X 4. RC delay model approximates a transistor as a switch in series with a resistor.

X 5. A unit nMOS transistor (M1) with L_{\min} and W_{\min} dimensions has a resistance of R and a Capacitance of C . What would be the resistance of an pMOS (M2) with twice the width of M1? $\frac{2R}{R}$.

✓ 6. What would be the diffusion cap of a pMOS (M3) with k -times the width of M1? kC .

✓ 7. The Capacitance of a MOS transistor is directly (directly/inversely) proportional to its width.

✓ 8. The Capacitance of a MOS transistor is directly (directly/inversely) proportional to its length.

9. By increasing the W of a MOS transistor, its resistance is decreased (increased/decreased)?

10. In Elmore-delay estimation, the effect of the largest Resistance is felt closest to the source/load?
Load

11. The Figure – 1 shown below, represents a fanout-of-1 inverter. What is its total delay in terms of R and C defined in problem 5? $3RC + 3RC$.

 


Figure – 1. Fanout – of – 1 inverter

12. In figure – 1: if the fanout of the first inverter is 4 instead of 1, what would be its delay? $15RC$.

$$12RC + 3RC = 15RC$$

13. In figure – 1, what percentage of the delay is from self-loading (parasitic and internal capacitances) of a fanout – of – 1 inverter? 50% (25%/50%/75%/100%)

14. What is the relationship between t_{pd} and t_{cd} ? $t_{pd} \geq t_{cd}$.

15. In linear delay model, the relationship between d , g , h and p is given by $d = gh + p$, where:

d : delay (Normalized to units of delay of a parasitic free fanout-of-1 inverter)

f : effort component of the delay

p : parasitic component of the delay

g : logical effort

h : fanout (electrical effort)