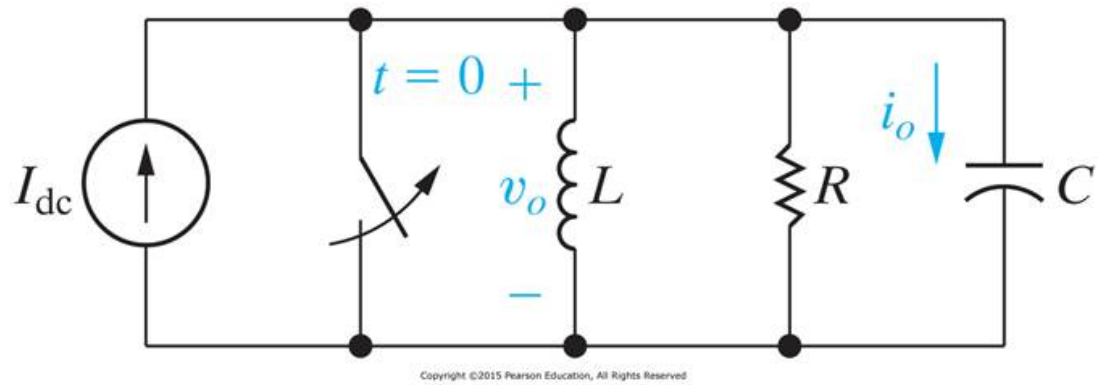


[Home](#) ► [My courses](#) ► [EEE117-2017S-Tatro](#) ► [Homework](#) ► [Homework 8 - Chapter 12](#)

<b>Started on</b>	Tuesday, 7 March 2017, 10:05 PM
<b>State</b>	Finished
<b>Completed on</b>	Tuesday, 7 March 2017, 10:10 PM
<b>Time taken</b>	4 mins 35 secs
<b>Marks</b>	100.00/100.00
<b>Grade</b>	<b>10.00</b> out of 10.00 ( <b>100%</b> )

**Question 1**

Correct

Mark 20.00 out of  
20.00

P12.47\_10ed

Given:  $I_{DC} = 3$  AmpsThe Laplace Transform of  $v_o(t)$  and  $i_o(t)$  are

$$V_0(s) = \frac{\frac{I_{DC}}{C}}{s^2 + s\frac{1}{RC} + \frac{1}{LC}}$$

$$I_0(s) = \frac{s I_{DC}}{s^2 + s\frac{1}{RC} + \frac{1}{LC}}$$

a) Use the initial-value theorem to find the initial value of  $v_o(t = 0^+)$ .

$$v_o(t = 0^+) = \boxed{0} \text{ V}$$

b) Use the final-value theorem to find the final value of  $v_o(t = \infty)$ . ( $\infty$  is infinity)

$$v_o(t = \infty) = \boxed{0} \text{ V}$$

c) Use the initial-value theorem to find the initial value of  $i_o(t = 0^+)$ .

$$i_o(t = 0^+) = \boxed{3} \text{ A}$$

d) Use the final-value theorem to find the final value of  $i_o(t = \infty)$ . ( $\infty$  is infinity)


$$i_o(t = \infty) = \boxed{0} \text{ A}$$

**Correct**

Marks for this submission: 20.00/20.00.

**Question 2**

Correct

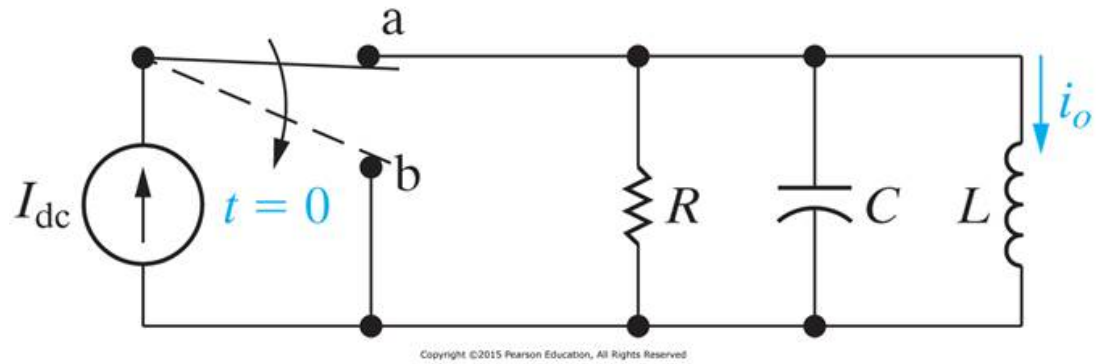Mark 20.00 out of  
20.00

P12.48\_10ed

The switch moves from position a to position b at  $t = 0$ .Given:  $I_{DC} = 5$  Amps

The Laplace Transform of  $i_0(t)$  is 
$$I_0(s) = \frac{I_{DC} \left[ s + \frac{1}{RC} \right]}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

a) Use the initial-value theorem to find the initial value of  $i_0(t = 0^+)$ .

$$i_0(t = 0^+) = \boxed{5} \checkmark \text{ A}$$

b) Use the final-value theorem to find the final value of  $i_0(t \rightarrow \infty)$ . ( $\infty$  is infinity)


$$i_0(t \rightarrow \infty) = \boxed{0} \checkmark \text{ A}$$

**Correct**

Marks for this submission: 20.00/20.00.

**Question 3**

Correct

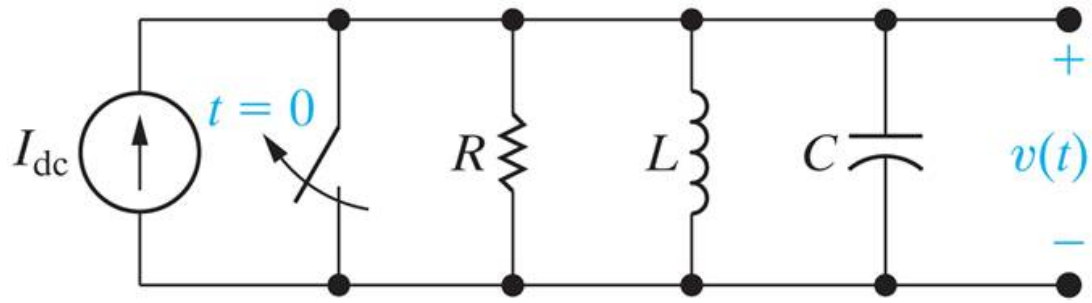Mark 20.00 out of  
20.00

P12.46\_10ed

The DC current source is replaced with a sinusoidal current source  $i(t) = 5 \cos(20t)$  A.

Given:  $R = 1.25 \, \Omega$  (Ohm)    $C = 50 \, \text{mF}$  (milli F)    $L = 200 \, \text{mH}$  (milli H)

With these given values the Laplace Transform of  $v(t)$  is

$$V(s) = \frac{100s^2}{(s^2 + 16s + 100)(s^2 + 400)} = \frac{100s^2}{(s + 8 - j6)(s + 8 + j6)(s + 0 - j20)(s + 0 + j20)}$$

a) Use the initial-value theorem to find the initial value of  $v(t=0)$ .

$v(t) =$    $\checkmark \text{ V}$

b) Can we use the final-value theorem on this Laplace function?


$\checkmark$

**Correct**

Marks for this submission: 20.00/20.00.

**Question 4**

Correct

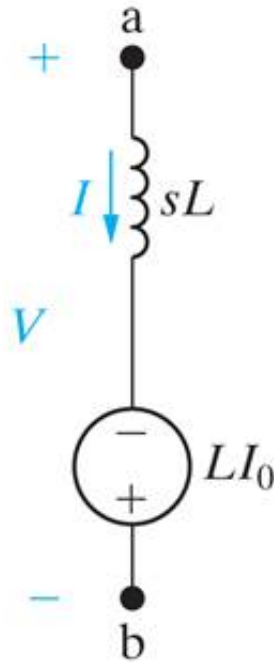Mark 20.00 out of  
20.00

Copyright ©2015 Pearson Education, All Rights Reserved

P13.03\_10ed

Find the Norton Equivalent of this circuit.

Select one:


- ☒ a.  $I_N = I_{ab} = -I_0/s$      $Z_{Th} = sL$  ✓
- ☐ b.  $I_N = I_{ab} = I_0/s$      $Z_{Th} = sL$
- ☐ c.  $I_N = I_{ab} = -I_0$      $Z_{Th} = sL$
- ☐ d.  $I_N = I_{ab} = -I_0/s$      $Z_{Th} = 1/(sL)$

**Correct**

Marks for this submission: 20.00/20.00.

**Question 5**

Correct

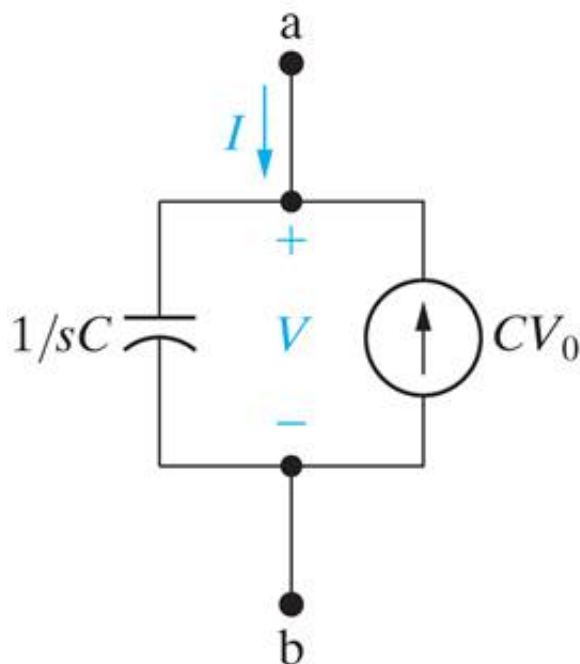Mark 20.00 out of  
20.00

P13.02\_10ed

Find the Thévenin Equivalent of this circuit.

Select one:

- ☒ a.  $V_{Th} = V_{ab} = V_0/s$      $Z_{Th} = 1/(sC)$  ✓
- ☐ b.  $V_{Th} = V_{ab} = V_0/s$      $Z_{Th} = sC$
- ☐ c.  $V_{Th} = V_{ab} = V_0$      $Z_{Th} = sC$
- ☐ d.  $V_{Th} = V_{ab} = 1/s$      $Z_{Th} = V_0/(sC)$

**Correct**

Marks for this submission: 20.00/20.00.