

Home ► My courses ► **EEE 108\_f17** ► Chapter 7 - BJT and MOS amplifiers ►  
Quiz 7 - BJT and MOS biasing, and small-signal models


<b>Started on</b>	Saturday, 25 November 2017, 9:23 PM
<b>State</b>	Finished
<b>Completed on</b>	Saturday, 25 November 2017, 10:03 PM
<b>Time taken</b>	39 mins 17 secs
<b>Grade</b>	<b>10.00</b> out of 10.00 ( <b>100%</b> )

**Question 1**

Correct

Mark 2.00 out of 2.00

For the MOSFET bias circuit shown, what is the source current,  $I_S$ , in milliamps? Assume that the transistor is in the saturation region, and use:  $V_{DD} = 14V$ ,  $R_{G1} = 51.5k\Omega$ ,  $R_{G2} = 49.9k\Omega$ ,  $R_D = 3.1k\Omega$ ,  $R_S = 4.9k\Omega$ ,  $V_t = 0.7V$ , and  $V_{on} = 0.26$ . (Remember that  $V_{on} = V_{ov} = V_{gs} - V_t$ ) Neglect the effect of channel-length modulation and body effect.

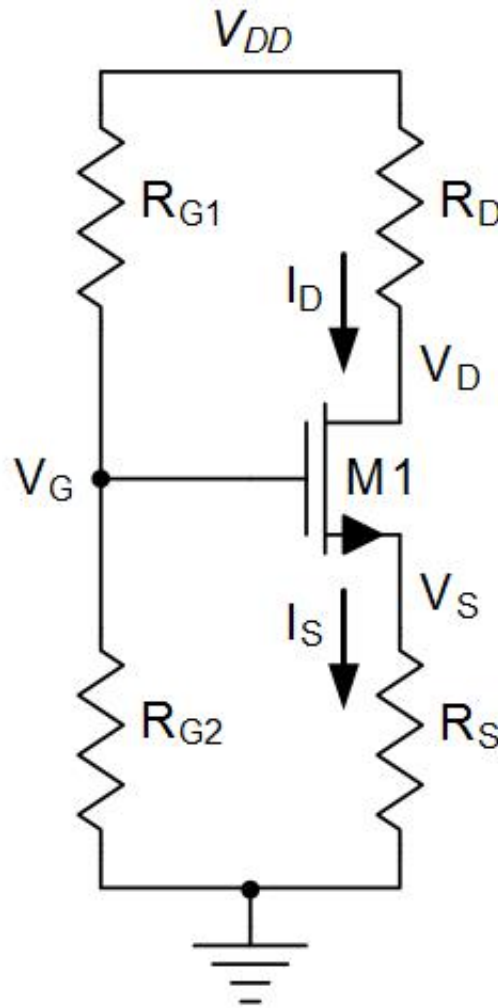

Answer: 1.185



The correct answer is: 1.21

**Correct**


Marks for this submission: 2.00/2.00.

**Question 2**

Correct

Mark 2.00 out of 2.00

For the BJT bias circuit shown, what is the base current,  $I_B$ , in microamps? Use  $V_{CC} = 10V$ ,  $V_{EE} = -6V$ ,  $V_B = -1.6V$ ,  $R_C = 3.3k\Omega$ , and  $R_E = 9.4k\Omega$ . Assume that the transistor is in the forward-active region, with  $\beta = 32$  and  $|V_{BE(on)}| = 0.7V$ . Neglect the effects of base-width modulation.

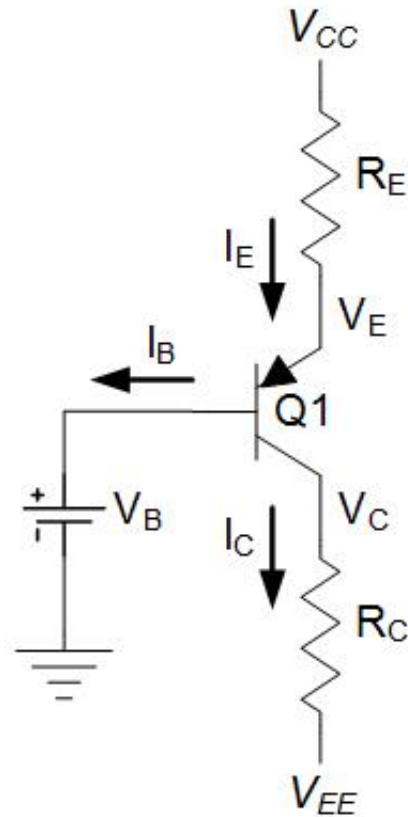

Answer: 35.1386



The correct answer is: 35.1

**Correct**

Marks for this submission: 2.00/2.00.

**Question 3**

Correct

Mark 2.00 out of 2.00

MOSFET amplifiers use DC bias circuits to keep the transistors “on” so they can respond to small variations in the input signal.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

**Correct**

Marks for this submission: 2.00/2.00.

**Question 4**

Correct

Mark 2.00 out of 2.00

What is the gate-to-source capacitance,  $C_{gs}$ , in fF for an NMOS FET operating in triode with  $W = 57\mu\text{m}$ ,  $L = 0.39\mu\text{m}$  and  $t_{ox} = 29$  angstroms?

Answer:  ✓

The correct answer is: 132.35

**Correct**

Marks for this submission: 2.00/2.00.

**Question 5**

Correct

Mark 2.00 out of 2.00

What is the transconductance,  $g_m$ , in mA/V for an PNP BJT operating in the forward-active region at  $27^\circ\text{C}$  with  $I_c = 369\mu\text{A}$ ? Use  $V_t = kT/q = 26\text{mV}$ .

Answer:  ✓

The correct answer is: 14.19

**Correct**

Marks for this submission: 2.00/2.00.