

**Started on** Tuesday, 15 November 2016, 3:18 PM

**State** Finished

**Completed on** Tuesday, 15 November 2016, 3:18 PM


**Time taken** 5 secs

**Grade** 90.00 out of 100.00

**Question 1**

Correct

Mark 10.00 out of 10.00

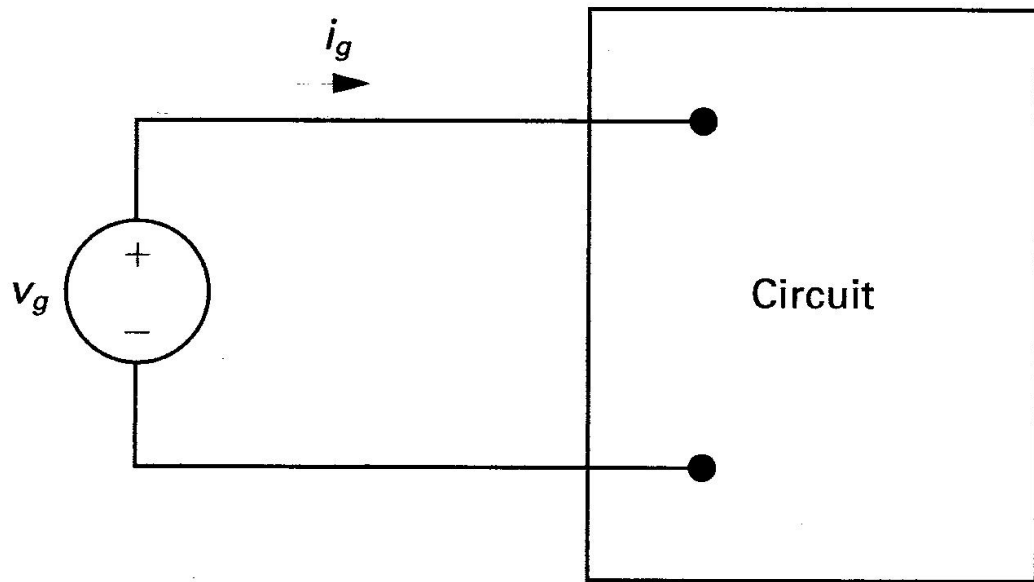

P9.29\_6ed

Given:

$$v_g = 150 \cos(8,000 \pi t + 20^\circ) \text{ V}$$

$$i_g = 30 \sin(8,000 \pi t + 38^\circ) \text{ A}$$

a) What is the impedance seen by the source?

$$Z_{\text{circuit}} = \text{Mag } \boxed{5} \checkmark \text{ with Angle } \boxed{72} \checkmark^\circ \text{ (Degrees) } \Omega \text{ (Ohm)}$$

b) By how many microseconds is the current out of phase with the voltage?

$$t_{\text{phase}} = \boxed{50} \checkmark \mu\text{s (micro sec)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

Mark 10.00 out of 10.00

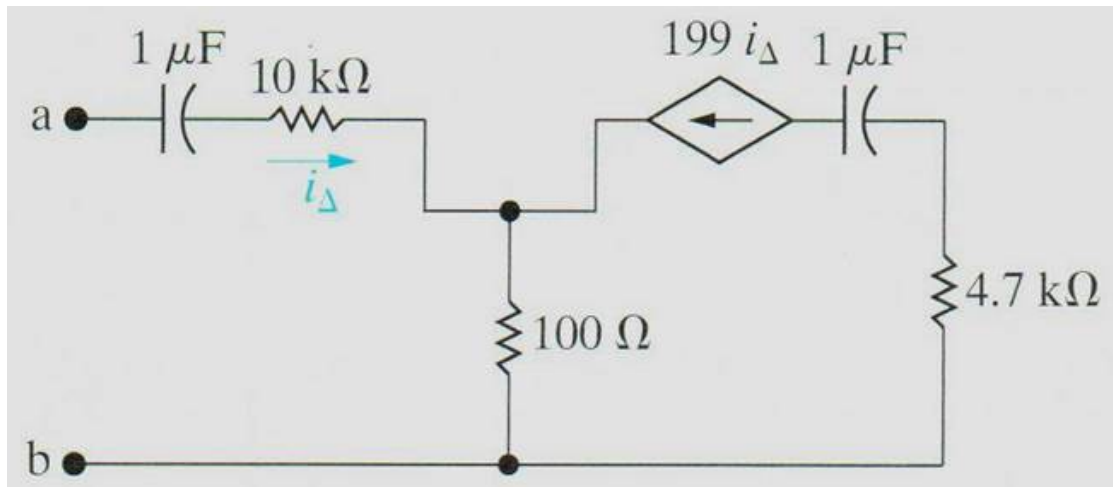

P9.46\_7ed

The frequency of operation is 400 rad/sec.

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

$$Z_{Th} = 30000 \checkmark + j -2500 \checkmark \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 3**

Correct

Mark 10.00 out of 10.00

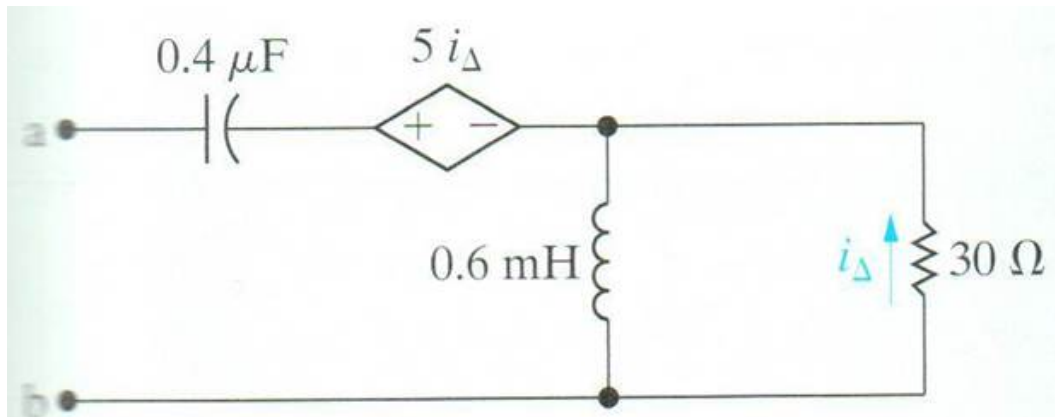

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

The frequency of operation is 100 krad/sec (kilo rad/sec).

$$Z_{Th} = 20 \checkmark + j -15 \checkmark \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

Mark 10.00 out of 10.00

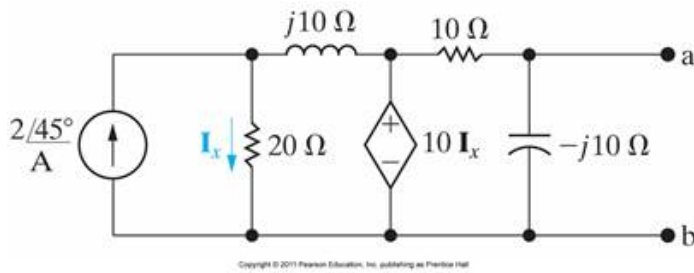

AP9.11\_9ed

Find the Thévenin equivalent with respect to terminals a,b.

 $V_{Th}$  = Magnitude  ✓ with Angle  ✓° (Degrees) Volts


 $Z_{Th}$  = Magnitude  ✓ with Angle  ✓° (Degrees) Ω (Ohm)
**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

Mark 10.00 out of 10.00

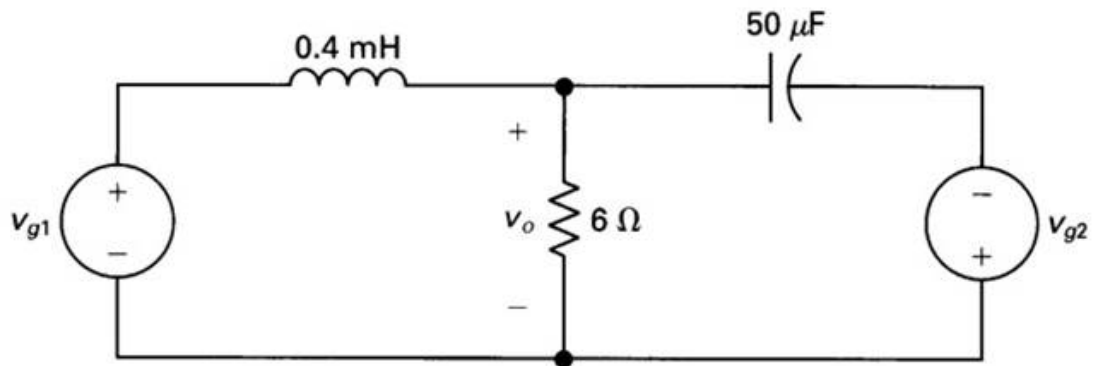

P9.49\_6ed

Given:

$$v_{g1} = 10 \cos(5,000 t + 53.13^\circ) \text{ V}$$

$$v_{g2} = 8 \sin(5,000 t) \text{ V}$$


Find the steady-state time domain expression for  $v_o(t)$  of this circuit.
 $v_o(t) =$   ✓  $\cos(5,000t +$   ✓° (Degrees) Volts
**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

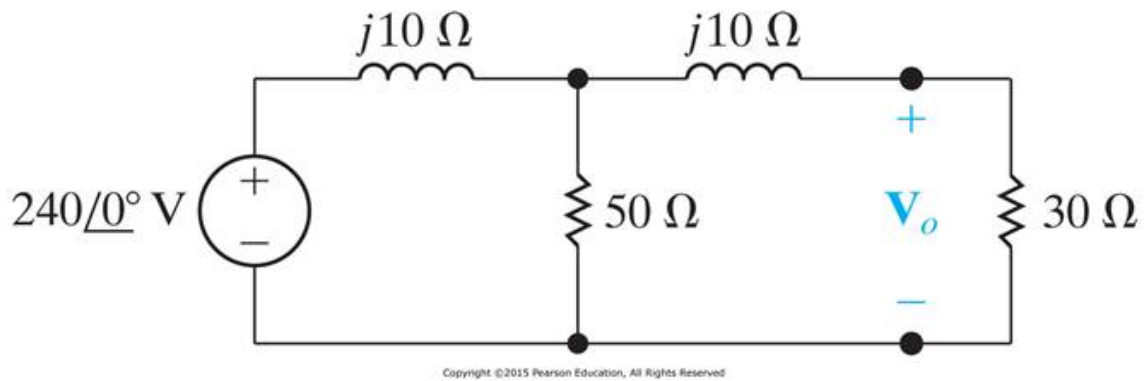

P9.54\_10ed


Use the node-voltage method to find  $V_o$ .
 $V_o$  = Magnitude  ✓ with Angle  ✓° (Degrees) Volts
**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Incorrect

Mark 0.00 out of 10.00

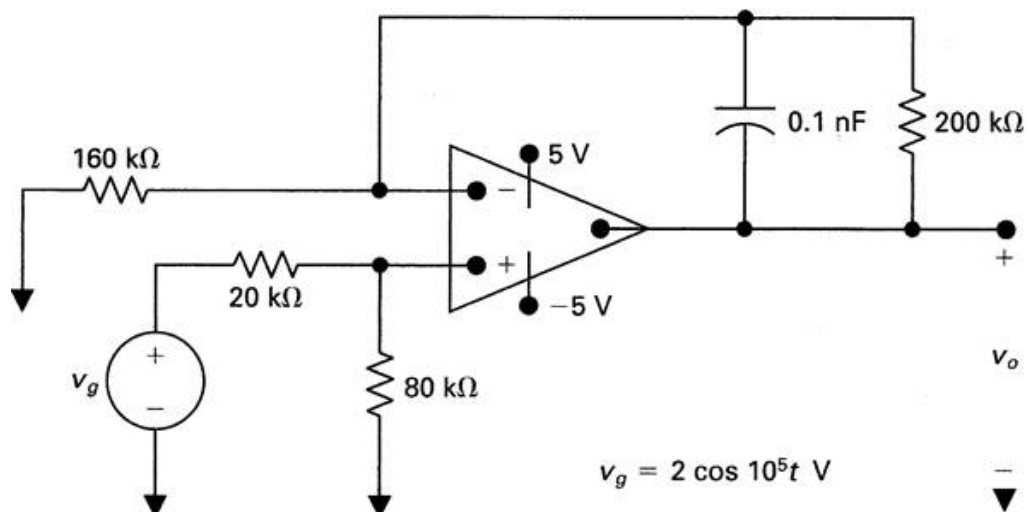

P9.72\_6ed

The operational amplifier is ideal.


Given  $v_g(t) = 2 \cos(100,000 t) \text{ V}$ a) Find the steady-state output  $v_o(t)$ .
 $v_o(t) =$   ✗  $\cos(100,000 t +$   ✗  $^\circ) \text{ Volts}$ 
b) How large can the amplitude of  $v_g(t)$  be before the amplifier saturates?
 $|v_o(t)|_{\max} \leq$   ✗  $\text{ Volts (less than or equal to)}$ 
**Incorrect**

Marks for this submission: 0.00/10.00.

**Question 8**

Correct

Mark 10.00 out of 10.00

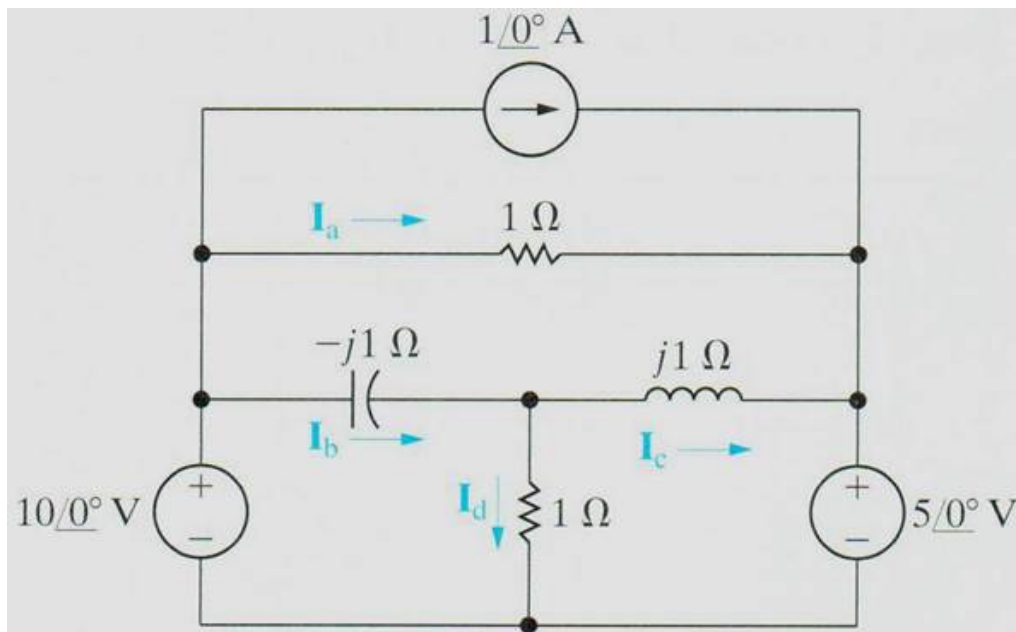

P9.62\_7ed

Use the Mesh method and find the following currents:


 $I_a$  = Magnitude  ✓ with Angle  ✓° (Degrees) Amps $I_b$  = Magnitude  ✓ with Angle  ✓° (Degrees) Amps $I_c$  = Magnitude  ✓ with Angle  ✓° (Degrees) Amps $I_d$  = Magnitude  ✓ with Angle  ✓° (Degrees) Amps**Correct**

Marks for this submission: 10.00/10.00.

**Question 9**

Correct

Mark 10.00 out of 10.00

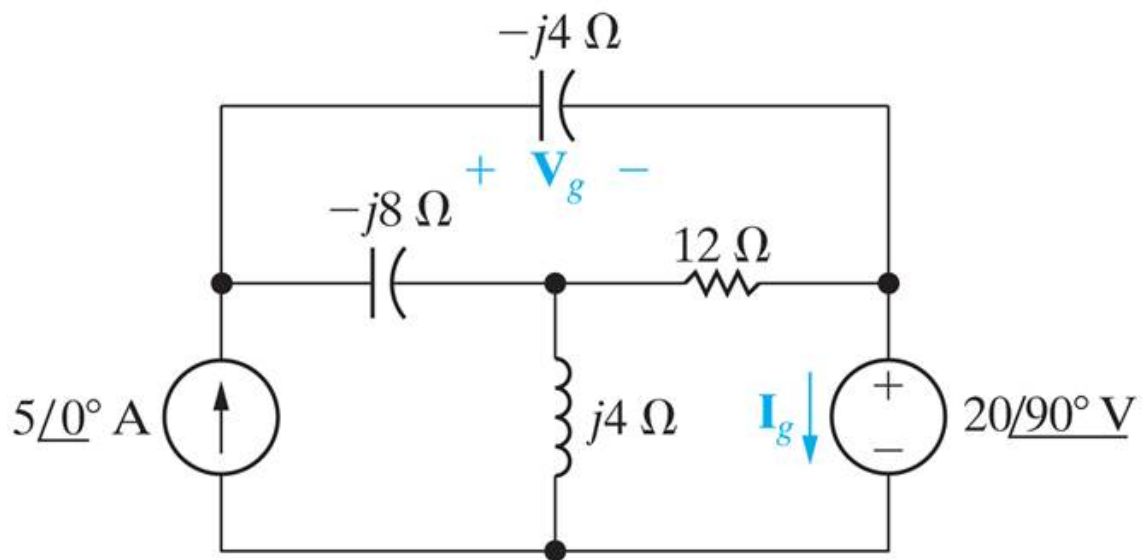

P9.60\_10ed

Use the mesh-current method to find  $\mathbf{I}_g$ .

$$\mathbf{I}_g = \boxed{4} \checkmark + j \boxed{-2} \checkmark \text{ A}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 10**

Correct

Mark 10.00 out of 10.00

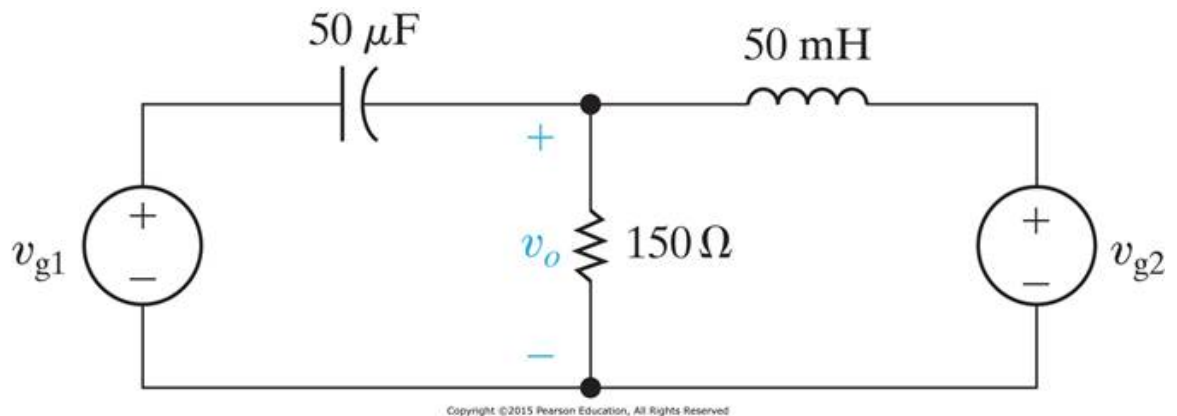

P9.61\_10ed

Given:  $v_{g1} = 25 \sin(400t + 143.12^\circ) \text{ V}$  and  $v_{g2} = 18.03 \cos(400t + 33.69^\circ) \text{ V}$ Use the mesh-current method to find the steady-state voltage of  $v_o(t)$ .

$$v_o(t) = \boxed{15} \checkmark \cos(400t + \boxed{0} \checkmark^\circ) \text{ (Degrees) V}$$

**Correct**

Marks for this submission: 10.00/10.00.