

Home ► My courses ► EEE117-2017S-Tatro ► Exams and Quizzes ► Exam 2 - Chapter 12 and 13

<b>Started on</b>	Wednesday, 5 April 2017, 11:03 AM
<b>State</b>	Finished
<b>Completed on</b>	Wednesday, 5 April 2017, 11:42 AM
<b>Time taken</b>	38 mins 48 secs
<b>Grade</b>	100.00 out of 100.00

**Question 1**

Correct

Mark 5.00 out of 5.00

Q1d

Find the Laplace Transform of  $\left\{ \frac{d}{dt}[e^{-at} \cos(\omega t)] \right\} \Leftrightarrow$

Select one:

- ☒ a.  $-\frac{a(s+a)+\omega^2}{(s+a)^2+\omega^2}$  ✓
- ☐ b.  $\frac{\omega^2}{(s+a)^2+\omega^2}$
- ☐ c.  $\frac{-s^2}{(s+a)^2+\omega^2}$
- ☐ d.  $\frac{s(s+a)^2}{(s+a)^2+\omega^2}$

Your answer is correct.

$$-\frac{a(s+a)+\omega^2}{(s+a)^2+\omega^2}$$

The correct answer is:  $-\frac{a(s+a)+\omega^2}{(s+a)^2+\omega^2}$

**Correct**

Marks for this submission: 5.00/5.00.

**Question 2**

Correct

Mark 15.00 out of 15.00

Q2a

Given  $F(s) = \frac{100(s^2+69)}{(s+10)(s^2+10s+169)} = \frac{100(s^2+69)}{(s+10)(s+5-j12)(s+5+j12)}$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

f(t) = [   $e^{-10t}$  +   $e^{-5t} \cos(12t + 90^\circ)$  ] u(t)

$$f(t) = [100e^{-10t} + 83.33e^{-5t} \cos(12t + 90^\circ)] u(t)$$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 3**

Correct

Mark 10.00 out of 10.00

Q3b

Given:  $F(s) = \frac{10(s^2+40)}{(s+8)(s^2+12s+136)}$  which has an inverse transform f(t).

a) Find the initial value of f(t = 0).

f(t = 0) =

b) Find the final value of f(t → ∞)

f(t → ∞) =

**Numeric Answer**

a) f(t = 0) = 10

b) f(t → ∞) = 0


**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

Mark 10.00 out of 10.00

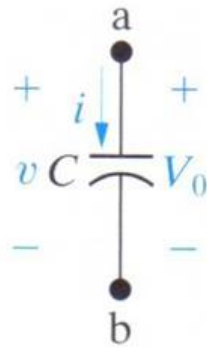

Q4b

Given: This capacitor has a value of  $1\ \mu\text{F}$  (micro F) and has an initial voltage of  $45\ \text{V}$  at  $t = 0^-$ .

Identify the Frequency Domain series form of the capacitor.

Select one:

- ☐ a.  $V = \frac{1}{s(1 \times 10^{-3})} + \frac{45}{s}$
- ☐ b.  $I = s(1 \times 10^{-3})V - 45 \times 10^{-3}$
- ☐ c.  $I = s(1 \times 10^{-6})V - 45 \times 10^{-6}$
- ☒ d.  $V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$  ✓

Your answer is correct.

$$V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$$

The correct answer is:  $V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

Mark 15.00 out of 15.00

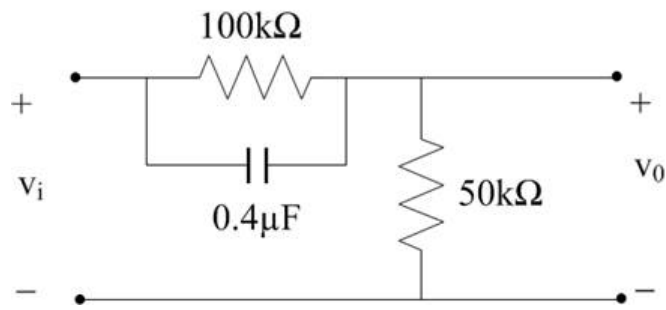

Q5b

Find the s domain transfer function  $H(s) = V_o/V_i$  for this circuit.

$$H(s) = (s + 25) / (s + 75)$$

$$H(s) = \frac{s+25}{s+75}$$


Correct

Marks for this submission: 15.00/15.00.

**Question 6**

Correct

Mark 15.00 out of 15.00

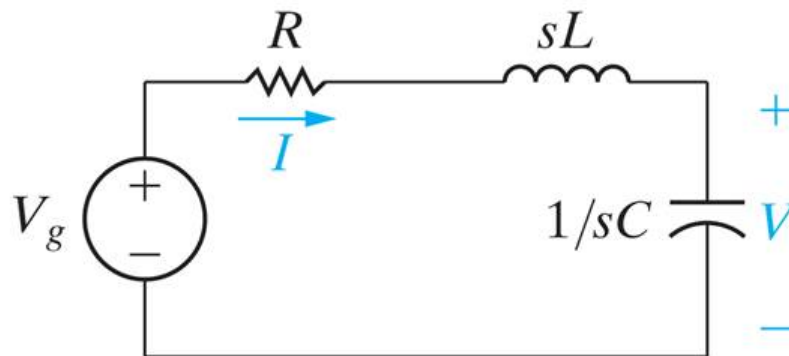

Q6d

Given: There is no energy stored in this circuit prior to  $t = 0$ .The voltage source  $V_g = 25$  V for  $t \geq 0^+$ . $R = 250 \Omega$  (Ohm) $L = 1$  H $C = 2$  mF (milli F)Find the defined current  $I$  in the s domain.

$$I(s) = 25 / (s^2 + 250s + 500)$$

$$I = \frac{25}{s^2 + 250s + 500}$$

Correct

Marks for this submission: 15.00/15.00.

**Question 7**

Correct

Mark 15.00 out of 15.00

Q7d

Given:  $F(s) = \frac{8(s^2 - 5s + 50)}{s(s + 10)}$

Find the partial fraction expansion of this transfer function.

$$F(s) = \frac{40}{s} + \frac{-160}{s + 10}$$

$$/s + \frac{-160}{s + 10}$$

$$F(s) = \frac{8(s^2 - 5s + 50)}{s(s + 10)} = \frac{40}{s} + \frac{-160}{s + 10}$$


**Correct**

Marks for this submission: 15.00/15.00.

**Question 8**

Correct

Mark 15.00 out of 15.00

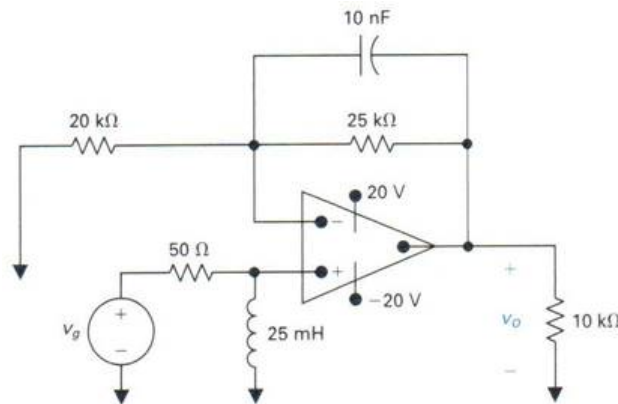

Q8c

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s + 9,000)}{(s + 2,000)(s + 4,000)}$$

Find the steady-state response when the input  $v_g(t) = 12 \cos(10,000 t)$  V.

$$v_o(t)_{\text{steady-state}} = [14.69 \cos(10000 t - 8.88^\circ)] u(t) \text{ V}$$

$$\cos(10000 t - 8.88^\circ) u(t) \text{ V}$$

**Numeric Answer**

$$v_o(t)_{\text{steady-state}} = 14.6980 \cos(10,000 t - 8.86^\circ) u(t) \text{ V}$$

**Correct**

Marks for this submission: 15.00/15.00.