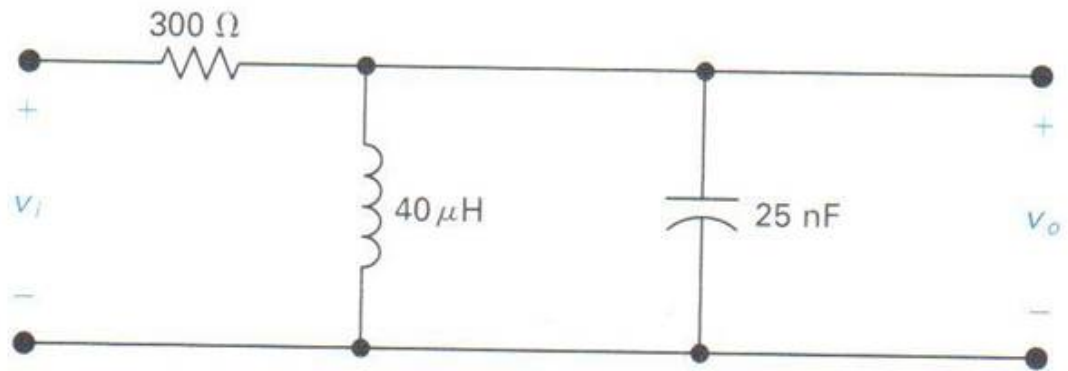


[Home](#) ► [My courses](#) ► [EEE117-2017S-Tatro](#) ► [Homework](#) ► [Homework 12 - Chapter 14](#)

<b>Started on</b>	Friday, 14 April 2017, 2:34 PM
<b>State</b>	Finished
<b>Completed on</b>	Saturday, 22 April 2017, 6:38 PM
<b>Time taken</b>	8 days 4 hours
<b>Grade</b>	<b>100.00</b> out of 100.00

**Question 1**

Correct

Mark 25.00 out of  
25.00

P14.12\_6ed

For this bandpass filter circuit, find the following values.

a) Find  $\omega_0$ .

$$\omega_0 = 1000 \checkmark \text{ krad/sec (kilo rad/sec)}$$

b) Find  $f_0$ .

$$f_0 = 159.155 \checkmark \text{ kHz (kilo Hz)}$$

c) Find  $Q$ .

$$Q = 7.5 \checkmark$$

d) Find  $\omega_{c1}$ .

$$\omega_{c1} = 935.55 \checkmark \text{ krad/sec}$$

e) Find  $\omega_{c2}$ .

$$\omega_{c2} = 1068.88 \checkmark \text{ krad/sec}$$

f) Find  $\beta$  (Beta).


$$\beta = 133.33 \checkmark \text{ krad/sec}$$

**Correct**

Marks for this submission: 25.00/25.00.

**Question 2**

Correct

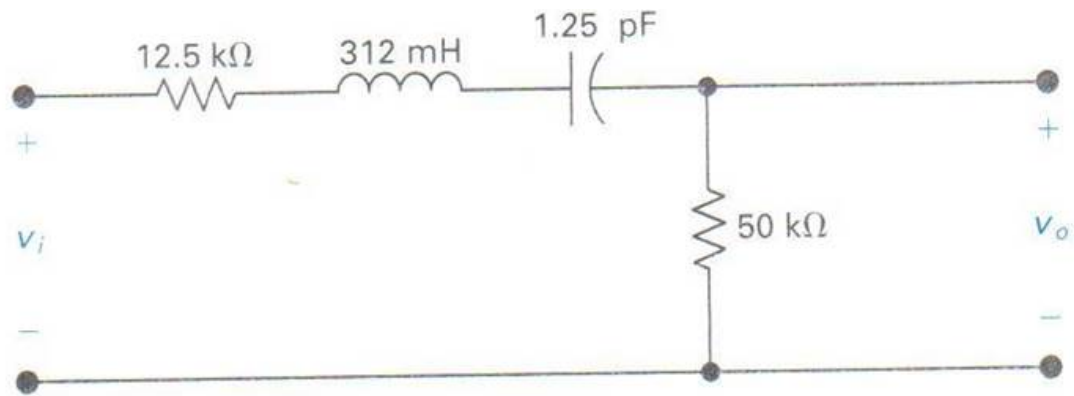Mark 25.00 out of  
25.00

P14.13\_6ed

Given: 
$$H(s) = \frac{\frac{R_0}{L}s}{s^2 + \left(\frac{R_0 + R_{in}}{L}\right)s + \frac{1}{LC}}$$

Where  $R_0 = 50\text{ k}\Omega$  (kilo Ohm) and  $R_{in} = 12.5\text{ k}\Omega$  (kilo Ohm)

a) Find  $f_0$ .

$f_0 = 254.64$  ✓ kHz (kilo Hz)

b) Find  $Q$ .

$Q = 7.98$  ✓

c) Find  $f_{c1}$ .

$f_{c1} = 239.41$  ✓ kHz (kilo Hz)

d) Find  $f_{c2}$ .

$f_{c2} = 271.29$  ✓ kHz (kilo Hz)

e) Find  $\beta$  (Beta).

$\beta = (R + R_i)/L = 31.88$  ✓ kHz (kilo Hz)


**Correct**

Marks for this submission: 25.00/25.00.

**Question 3**

Correct

Mark 25.00 out of 25.00

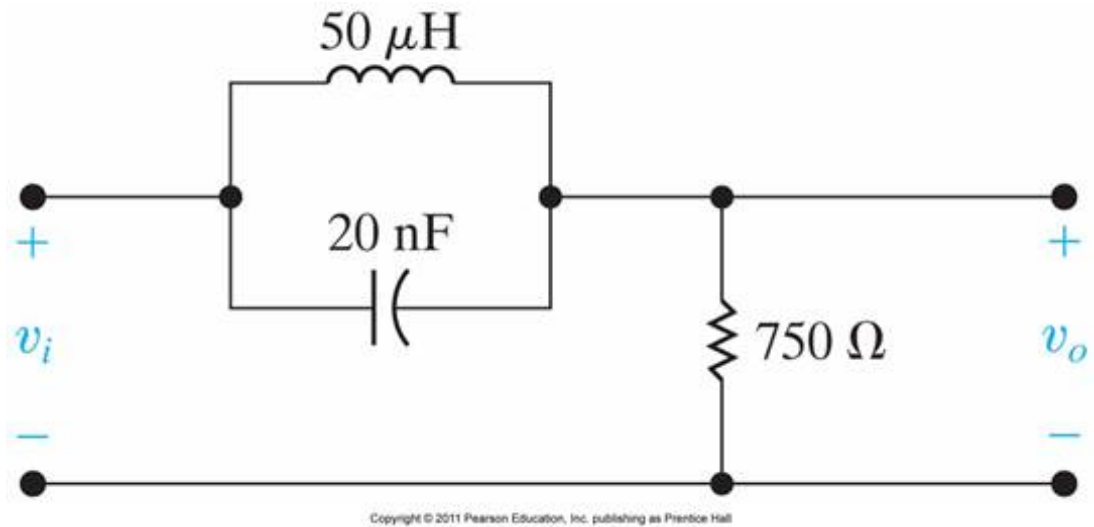

P14.35\_9ed

Given: 
$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

For this bandreject filter:

a) Calculate  $\omega_0$ .

$$\omega_0 = 1000 \checkmark \text{ krad/sec (kilo rad/sec)}$$

b) Calculate  $f_0$ .

$$f_0 = 159.16 \checkmark \text{ kHz (kilo Hz)}$$

c) Find Q.

$$Q = 15 \checkmark$$

d) Find  $\omega_{c1}$ .

$$\omega_{c1} = 967.22 \checkmark \text{ krad/sec (kilo rad/sec)}$$

e) Find  $\omega_{c2}$ .

$$\omega_{c2} = 1033.88 \checkmark \text{ krad/sec (kilo rad/sec)}$$

f) Find  $\beta$  (Beta).

$$\beta = 10.61 \checkmark \text{ kHz (kilo Hz)}$$


**Correct**

Marks for this submission: 25.00/25.00.

**Question 4**

Correct

Mark 25.00 out of 25.00

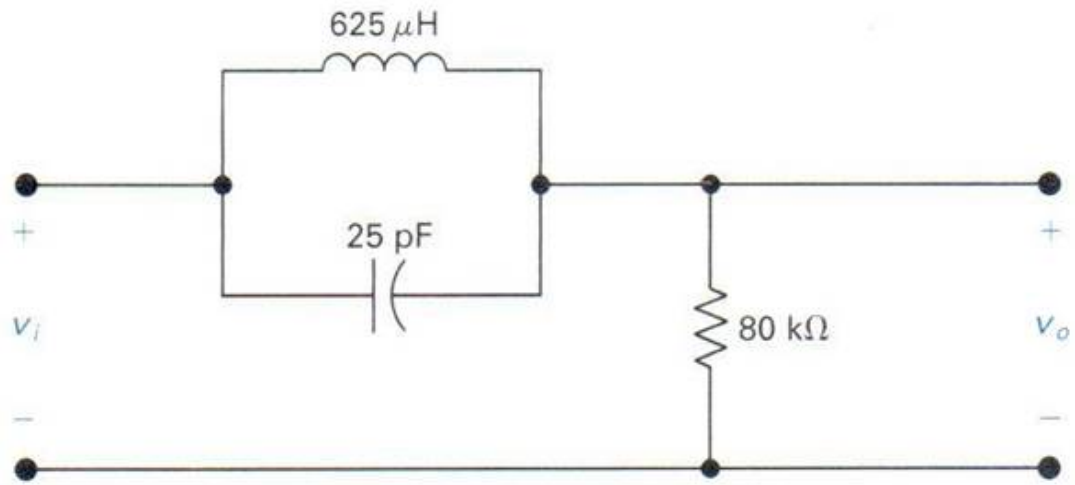

P14.27\_6ed

Given: 
$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

For this bandreject filter:

a) Calculate  $\omega_0$ .

$$\omega_0 = 8000 \checkmark \text{ krad/sec (kilo rad/sec)}$$

b) Calculate  $f_0$ .

$$f_0 = 1273.24 \checkmark \text{ kHz (kilo Hz)}$$

c) Find Q.

$$Q = 16 \checkmark$$

d) Find  $\omega_{c1}$ .

$$\omega_{c1} = 7753.91 \checkmark \text{ krad/sec (kilo rad/sec)}$$

e) Find  $\omega_{c2}$ .

$$\omega_{c2} = 8253.91 \checkmark \text{ krad/sec (kilo rad/sec)}$$

f) Find  $\beta$  (Beta).

$$\beta = 79.58 \checkmark \text{ kHz (kilo Hz)}$$

**Correct**

Marks for this submission: 25.00/25.00.