

Started on Wednesday, 29 March 2017, 5:36 PM

State Finished

Completed on Wednesday, 29 March 2017, 6:45 PM

Time taken 1 hour 8 mins


Overdue 8 mins 12 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 100.00 out of 100.00

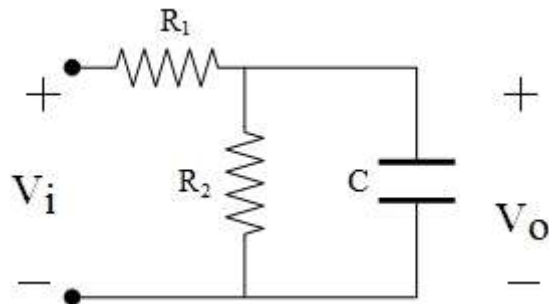

Quiz 7f

Given: $R_1 = 200 \text{ k}\Omega$ (kilo Ohm) $R_2 = 40 \text{ k}\Omega$ (kilo Ohm) $C = 0.4 \text{ }\mu\text{F}$ (micro F)

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$H(s) =$ ✓ $/ (s +$ ✓ $)$

$$H(s) = \frac{12.5}{s+75}$$

Correct

Marks for this submission: 100.00/100.00.