

Started on Tuesday, 22 November 2016, 3:14 PM

State Finished

Completed on Tuesday, 22 November 2016, 4:04 PM


Time taken 49 mins 56 secs

Grade 0.00 out of 100.00

Question 1

Incorrect

Mark 0.00 out of 100.00

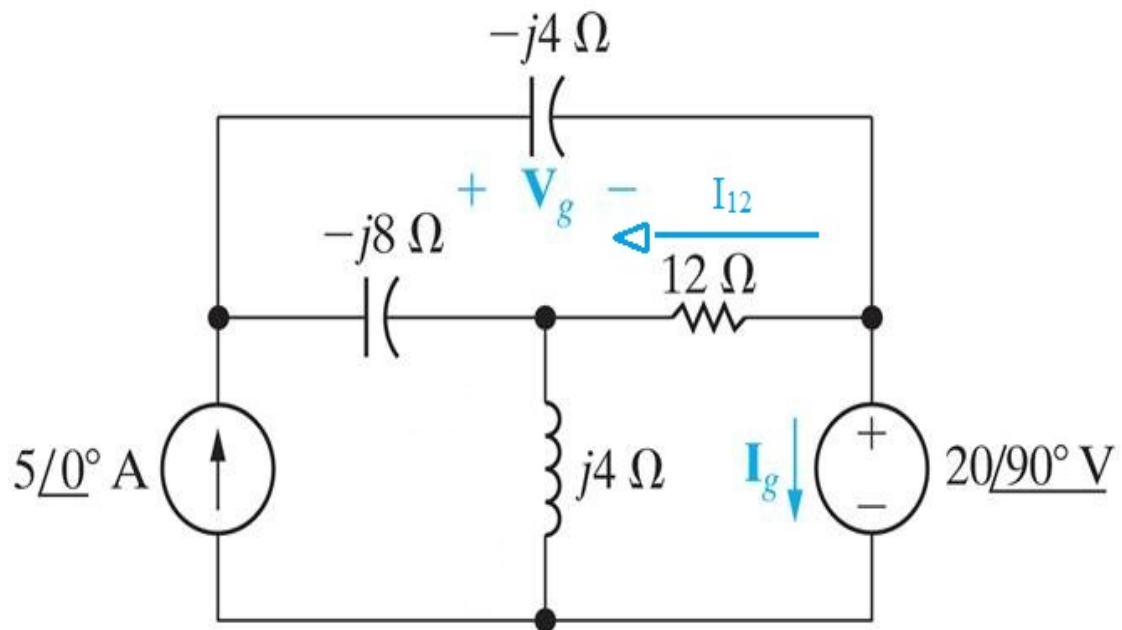

Copyright ©2015 Pearson Education, All Rights Reserved

Quiz 10c

Use the node-voltage method to find the phasor current I_{12} through the $12\ \Omega$ (Ohm) resistor.

$I_{12} =$ $\times + j$ \times Amps

Numeric answer

$I_{12} = 0.6667 + j1.3333\text{ A} = 1.4907\text{ at angle }63.43^\circ\text{ A}$

Incorrect

Marks for this submission: 0.00/100.00.