 


- This circuit takes 4-bit binary input and has a 7-bit binary output. From the basic analysis, it seems like it has a 7-segment display. This circuit is known as **BCD (Binary Coded Decimals) to 7-segment display**. It lights up each LED segment whenever the output is '1' and it gives out the decimal value. BCD: 4-bits to 16-bits ( $2^4 = 16$ ), used for the 10 digits 0 to 9 to be displayed.

Display	D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	1
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1



Example: Decimal value 0 has output abcdef 'HIGH'.

HIGH = LED ONE

LOW = LED OFF

Although the output is recorded in binary, the 7-segment display shows decimal value.

- Circuit A is a JK Flip Flop. It functions like a SR Flip Flop except when all the inputs are HIGH. SR Flip Flop is best expressed using **OR gates** whereas JK Flip Flop is best described using **AND gate**
  - DFF has one input (data) and 2 possible combo
    - When a positive rising edge, the value remembered by the FF becomes the value of the D input
  - JKFF has 2 inputs and 4 possible combo
    - When positive rising edge:
      - the value remembered by the FF toggles when  $J = 1$  &  $K = 1$ .
      - the value remains the same when  $J$  &  $K = 0$ .
      - the value equals to K or J when  $J = 1$  &  $K = 0$  or  $K = 1$  &  $J = 0$
  - TFF functions with JKFF with same inputs
    - When the positive rising edge, the value remembered by FF either toggles or remains the same depending on whether the T inputs is 1 or 0

Truth Table for SR Flip Flop

clk	S	R	Output	
0	0	0	Memory	
1	0	0	Memory	
1	1	0	$Q = 1$	$\bar{Q} = 0$
1	0	1	$Q = 0$	$\bar{Q} = 1$
1	1	1	Not in use	

Truth table for JK Flip Flop

clk	J	K	Output	
0	0	0	Memory	
1	0	0	Memory	
1	1	0	$Q = 1$	$\bar{Q} = 0$
1	0	1	$Q = 0$	$\bar{Q} = 1$
1	1	1	Toggles	

Notice the first 4 inputs to be similar! The difference occurs when all inputs are HIGH. JK Flip Flop, toggles its output

Truth Table for T Flip Flop




clk	T	Output
-----	---	--------

Display	X <sub>1</sub>	X <sub>2</sub>	X <sub>3</sub>	X <sub>4</sub>	a	b	c	d	e	f	g
0 0 X Memory	0	0	0	0	1	1	1	1	1	1	0
1 1 0 Memory	0	0	1	0	0	1	1	0	0	0	0
1 2 1 Toggles	0	1	0	1	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	1	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	1
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
A	1	0	1	0	1	1	1	0	1	1	1
b	1	0	1	1	0	0	1	1	1	1	1
C	1	1	0	0	1	0	0	1	1	1	0
d	1	1	0	1	0	1	1	1	1	0	1
E	1	1	1	0	1	0	0	1	1	1	1
F	1	1	1	1	1	0	0	1	1	1	1


the 7 segment display

TFF uses a **XOR gate**  
It is implemented using a JKFF – or at least it functions similarly as it.  
The output will depend on previous states.


3. Truth table for

   

 
$$A = X_1\overline{X_2}\overline{X_3} + \overline{X_1}X_2X_4 + \overline{X_2}X_4 + \overline{X_1}X_3 + X_1\overline{X_4}$$



 
$$B = \overline{X_1}X_3X_4 + \overline{X_1}X_3\overline{X_4} + X_1\overline{X_3}X_4 + \overline{X_1}X_2 + \overline{X_2}X_4$$


 
$$C = \overline{X_1}X_3 + \overline{X_1}X_4 + \overline{X_3}X_4 + \overline{X_1}X_2 + X_1\overline{X_2}$$




 
$$D = \overline{X_1}X_2\overline{X_4} + X_1\overline{X_3}\overline{X_4} + \overline{X_2}X_3X_4 + X_2\overline{X_3}X_4 + X_2X_3\overline{X_4}$$




$$E = \overline{X}_2\overline{X}_4 + X_1X_3 + X_1X_2$$
  
$$F = \overline{X}_1X_2\overline{X}_3 + \overline{X}_3\overline{X}_4 + X_1\overline{X}_2 + X_1X_3$$


 
$$G = \overline{X}_1X_2 + X_1\overline{X}_2 + X_2X_4 + X_3$$



This was the closest PLA Design I could find that is an replica of each Boolean expression.