

[Home](#) ► [Electrical Engineering](#) ► [Engr17-2016F-Tatro](#) ► [Exams and Quizzes](#) ► [Quiz 4 - Chap 4](#)

Started on	Wednesday, 5 October 2016, 12:56 PM
-------------------	-------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 5 October 2016, 1:15 PM
---------------------	------------------------------------


Time taken	18 mins 36 secs
-------------------	-----------------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 100.00 out of 100.00

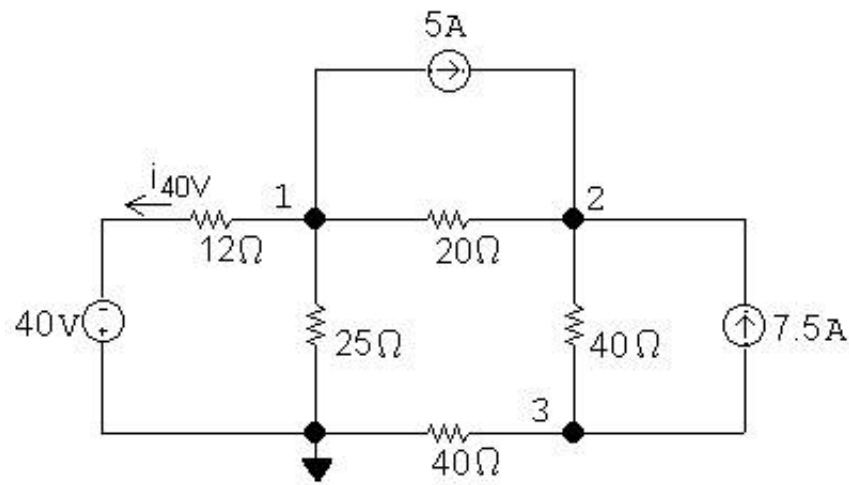

Quiz 4d

Practice using the node-voltage method and ...

Find the three node voltages V_1 , V_2 and V_3 and the current i_{40V} .

$$V_1 = -10 \text{ V}$$

$$V_2 = 132 \text{ V}$$

$$V_3 = -84 \text{ V}$$

$$i_{40V} = 2.5 \text{ A}$$

Numeric Answer

$$V_1 = -10 \text{ V}$$

$$V_2 = 132 \text{ V}$$

$$V_3 = -84 \text{ V}$$

$$i_{40V} = 2.5 \text{ A}$$

Correct

Marks for this submission: 100.00/100.00.