

Started on Wednesday, 21 September 2016, 11:17 AM

State Finished

Completed on Wednesday, 21 September 2016, 11:18 AM


Time taken 1 min 44 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 40.00 out of 40.00

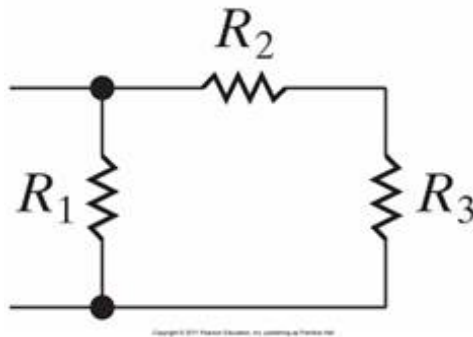

Q3a

Given: $R_1 = 523 \, \Omega$ (Ohms) $R_2 = 6087 \, \Omega$ (Ohms) $R_3 = 4095 \, \Omega$ (Ohms)

Find the equivalent resistance R_{Eq} .


Answer: 497.45 ✓

Calculated question

The correct answer is: 497.45

Question 2

Correct

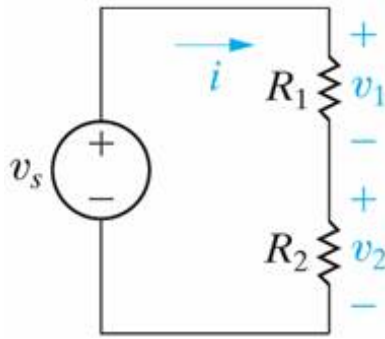Mark 60.00 out of
60.00

Quiz 3-2d

Given:

$$v_s = 60 \text{ Volts} \quad R_1 = 300 \, \Omega \text{ (Ohms)} \quad R_2 = 500 \, \Omega \text{ (Ohms)}$$

a) Find the voltage v_1 . $v_1 =$ ✓ Volts

b) Find the voltage v_2 . $v_2 =$ ✓ Volts

c) Find the current i . $i =$ ✓ mA (milli Amp)

Numeric Answer

a) $v_1 = 22.50$ Volts

b) $v_2 = 37.50$ Volts

c) $i = 75.0$ mA (milli Amp)