

Engr 17 - CSUS

Instructor – Russ Tatro


Chapter 10 Sinusoidal Steady-State Power Calculations

James W. Nilsson and Susan A. Riedel, *Electric Circuits*, 6th Edition, 2001

Lecture Notes

Please see your textbook for the figures and problems cited in the lectures.

Chap 10 - sinusoidal steady-state Power

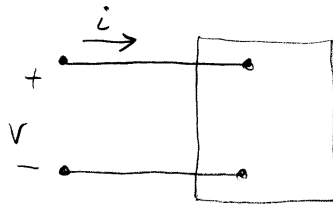

Instantaneous Power

$$P = v i = v_m \cos(\omega t + \theta_{\text{voltage}}) \cdot I_m \cos(\omega t + \theta_i)$$

For convenience we write this as (current passing thru maximum)

$$P = v_m \cos(\omega t + \theta_v - \theta_i) \cdot I_m \cos(\omega t)$$

$$= v_m I_m \cos(\omega t + \theta_v - \theta_i) \cos \omega t$$

Now use the trig identity

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$\text{let } \alpha = \omega t + \theta_v - \theta_i$$

$$\text{let } \beta = \omega t$$

re-write Power as

$$P = \frac{v_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{v_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

Now let's expand the 2nd term by Trig Identities again

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\begin{aligned}
 P = & \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_P \\
 & + \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_P \cos 2\omega t \\
 & - \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)}_Q \sin 2\omega t
 \end{aligned}$$

So the Power can have a "DC" component (1st Term)
 & the freq of the instantaneous power is twice that
 of the input current & voltage.

Negative Power indicates energy is being extracted
 (from capacitor and/or inductor) for that instant

See fig 10.2 on page 491

Sec 10.2 Average Power

From the above eqn we see that

$$\text{power} = P + P \cos 2\omega t - Q \sin 2\omega t$$

where $P =$ the average power - delivers work

$Q \triangleq$ the reactive power

Recall the average is given by $P = \int_{t_0}^{t_0+T} p \, dt$

as well, but easier to use Trig form above.

Power for Purely resistive circuit

voltage & current are in phase

that is $\theta_v = \theta_i$

$$\text{so } \cos(\theta_v - \theta_i) = 1$$

$$\sin(\theta_v - \theta_i) = 0$$

$$p = P + P \cos 2\omega t = \text{instantaneous real power in watts}$$

see fig 10.3 \rightarrow real power is always positive since no energy can be extracted from a purely resistive network (all energy dissipated as heat)

Power for Purely Inductive circuit

current lags voltage by exactly 90°

$$\theta_i = \theta_v - 90^\circ \text{ or } \theta_v - \theta_i = 90^\circ$$

$$\text{thus } \cos(\theta_v - \theta_i) = 0$$

$$\sin(\theta_v - \theta_i) = 1$$

thus

$$\text{power} = -Q \sin 2\omega t \quad \text{reactive power in "VAR"}$$

volt-amp reactive

Power is continually exchanged between the inductor's magnetic field & the source.

$$\text{average power} = 0$$

Inductors "demand" (absorb) magnetizing VARs

Power for Purely Capacitive Circuits

current leads the voltage

$$\theta_i = \theta_v + 90^\circ \Rightarrow \theta_v - \theta_i = -90^\circ$$

$\cos -90^\circ = 0$ $\sin -90^\circ = -1$ so negatives cancel
thus power = $Q \sin 2\omega t$

$$\text{avg power} = 0$$

energy is continually exchanged between the source & the capacitor's electric field.

Capacitors "furnish" (deliver) magnetizing VARs

The Power Factor

the angle $\theta_v - \theta_i$ is called the "Power factor Angle"

$$pf = \cos(\theta_v - \theta_i) \triangleq \text{Power Factor} \quad \text{abbrev. } pf$$


$$rf = \sin(\theta_v - \theta_i) \triangleq \text{Reactive Factor} \quad \text{abbrev. } rf$$

we add "lagging" power factor for inductive load
(current lags voltage)

& "leading" power factor for capacitive load
(current leads voltage)

Ex 10.1 pg 494

for our block diagram

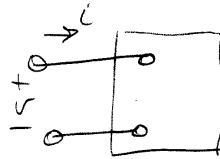

$$V = 100 \cos(\omega t + 15^\circ) \text{ Volts}$$

$$i = 4 \sin(\omega t - 15^\circ) \text{ Amps}$$

$$= 4 \cos(\omega t - 15^\circ - 90^\circ) = 4 \cos(\omega t - 105^\circ) \text{ A}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_V - \theta_i) = \frac{100 \cdot 4}{2} \cos[15 - (-105)]$$

$$= 200 \cos 120^\circ = -100 \text{ watts delivering power}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_V - \theta_i) = \frac{100 \cdot 4}{2} \sin 120^\circ = 173.21 \text{ VAR}$$

absorbing magnetizing VARs

D.E. 10.2 pg 495

Find the power factor for the ex 10.1

we shift to $-i$ to keep pf positive so

$$180^\circ - 105^\circ = 75^\circ$$

$$\text{pf} = \cos(15 - 75) = \cos(-60) = 0.5 \text{ lagging}$$

$$\text{pf} = \sin(-60) = -0.866$$

read section on appliance ratings on your own.

recall that $P_{\text{effective}} = V_{\text{rms}} I_{\text{rms}}$

so if computer takes $300\text{W} = P_{\text{eff}}$

$$\text{then } I_{\text{eff}} = \frac{P_{\text{eff}}}{V_{\text{rms}}} = \frac{300\text{W}}{115 V_{\text{rms}}} = 2.6 \text{ Amps}$$

Plug in a laser printer (my HP 3100) takes 135W

$$\text{so } I_{\text{eff}} = \frac{135\text{W}}{115 V_{\text{rms}}} = 1.2 \text{ Amp}$$

Combined = 3.8 Amp

Notes on O.E. 10.2 (Text answers are wrong!)


Voltage is $+15^\circ$ & current is -15°

so Voltage peaks 30° before the current

so current is lagging

$$\begin{aligned} pf &= 0.5 \text{ lagging} \\ pf &= -0.866 \end{aligned} \left. \vphantom{\begin{aligned} pf &= 0.5 \text{ lagging} \\ pf &= -0.866 \end{aligned}} \right\} \text{ as given in class}$$

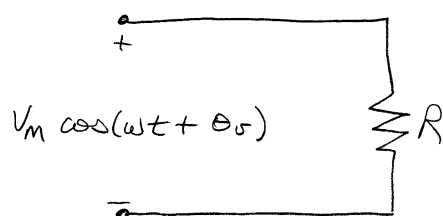Sec 10.3 The RMS Value & Power calculations



Find the average Power delivered to the resistor

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \theta_v)}{R} dt \\ &= \frac{1}{R} \left[V_{rms}^2 \right] \end{aligned}$$

It also directly follows that

$$P_{avg} = I_{rms}^2 R$$

rms is often called the "effective value" of the sinusoidal voltage or current.

The Avg Power found by the rms is equal to a DC source at the rms value over the same time interval.

$$\begin{aligned}
 P_{avg} &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\
 &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\
 &= V_{eff} I_{eff} \cos(\theta_v - \theta_i)
 \end{aligned}$$

$$\text{Reactive Power } Q = V_{eff} I_{eff} \sin(\theta_v - \theta_i)$$

Ex 10.3 pg 499

$$V_m = 625V \quad \text{sinusoidal voltage}$$

a) find avg power delivered to 50 Ω load.

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{625V}{\sqrt{2}} = 441.94V$$

$$P = \frac{V_{rms}^2}{R} = \frac{(441.94V)^2}{50\Omega} = 3906.25 \text{ Watt}$$


b) repeat by calculating current I_m

$$I_m = \frac{V_m}{R} = \frac{625V}{50\Omega} = 12.5A$$

$$I_{rms} = \frac{12.5}{\sqrt{2}} = 8.84A$$

$$P = I_{rms}^2 R = (8.84A)^2 (50\Omega) = 3906.25 \text{ Watt}$$

D.E. 10.5 pg 500

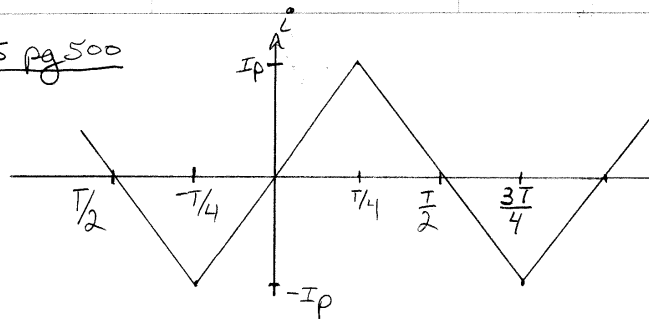

$$I_{\text{peak}} = 180 \text{ mA}$$

Find the average power delivered to a $5 \text{ k}\Omega$ resistor.

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2 dt}$$

$$= \sqrt{\frac{1}{T} 4 \int_0^{T/4} i^2 dt}$$

$$\text{where } i = \frac{4}{T} I_p t \quad \text{for } 0 \leq t \leq \frac{T}{4}$$

$$\text{so } \int_0^{t_0+T} i^2 dt = 4 \int_0^{T/4} \frac{16 I_p^2}{T^2} t^2 dt$$

$$\text{integral} = (4) \frac{16 I_p^2}{T^2} \int_0^{T/4} t^2 dt = \frac{4 \cdot 16 I_p^2}{T^2} \left(\frac{t^3}{3} \right) \Big|_0^{T/4}$$

$$= \frac{4 \cdot 16 I_p^2}{T^2} \left(\frac{T^3}{4^3 \cdot 3} \right) = \frac{I_p^2 T}{3}$$


$$I_{\text{rms}} = \sqrt{\frac{1}{T} \left(\frac{I_p^2 T}{3} \right)} = \frac{I_p}{\sqrt{3}}$$

$$\text{so } I_{\text{eff}} = \frac{.180}{\sqrt{3}} \text{ A}$$

$$P_{\text{avg}} = I_{\text{eff}}^2 R = \left(\frac{.180}{\sqrt{3}} \right)^2 (5 \text{ k}\Omega) = \underline{\underline{54 \text{ watts}}}$$

Sec 10.4 complex Power

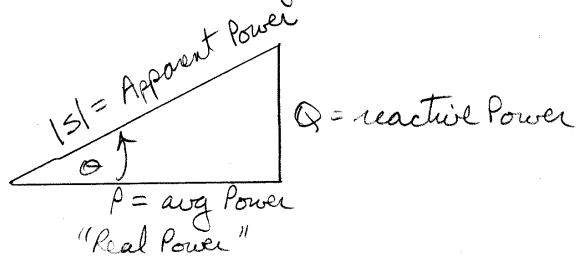complex Power $\stackrel{d}{=} \underline{S} = P + jQ$ V.A (volt Amps)



where $\tan \theta = \frac{Q}{P}$ (from the geometry)

$$\begin{aligned} \text{recall that } \frac{Q}{P} &= \frac{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)}{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)} \\ &= \tan(\theta_v - \theta_i) \end{aligned}$$

Therefore our θ in the right triangle above is equal to $\theta_v - \theta_i$

$$\theta = \theta_v - \theta_i = \text{Power factor angle}$$

so all the right triangle tools apply.

$$\text{Apparent Power } \stackrel{d}{=} |S| = \sqrt{P^2 + Q^2} \text{ in V.A (Volt Amps)}$$

this apparent power is the volt-Amps required to supply the avg power.

When power factor angle $\theta = 0^\circ$

then $pf = 1$ & $rf = 0$

$$pf = \cos \theta \quad rf = \sin \theta$$

So when $\theta > 0^\circ$ you must supply more volt. Amps than the average power used by the device!

Ex 10.4

$$V_{rms} = 240V$$

$$P_{avg} = 8kW$$

$pf = 0.8$ lagging (inductive load)

a) Find the complex power S of the load.

$$S = P + jQ \quad (Q \text{ is positive})$$

$$\cos \theta = 0.8 \quad \text{so} \quad \sin \theta = 0.6 \quad \theta = 36.87^\circ$$

$$P = |S| \cos \theta \Rightarrow |S| = \frac{P}{\cos \theta} = \frac{8kW}{0.8} = 10kVA$$

$$Q = (10kVA) \underbrace{\sin \theta}_{0.6} = 6kVA$$

$$\text{so } \underline{S = 8 + j6 \text{ kVA}}$$

for inductor $= \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$
for capacitor $= \frac{V_m I_m}{2} \sin(\theta_i - \theta_v)$

$\theta_v - \theta_i = +90^\circ$ for inductor so Q positive

b) Now find the impedance of the load.

$$P_{avg}(\text{given}) = 8 \text{ kW}$$

$$= V_{eff} I_{eff} \cos(\theta_v - \theta_i)$$

$$= (240 V_{rms}) I_{eff} (0.8)$$

$$\text{so } I_{eff} = \frac{8 \text{ kW}}{(240 V_{rms})(0.8)} = 41.67 \text{ Amps}$$

θ is positive = 36.87° (inductive load)

$$|Z| = \frac{|V_{eff}|}{|I_{eff}|} = \frac{240}{41.67} = 5.76$$

thus

$$Z = 5.76 \angle 36.87^\circ \Omega = 4.608 + j 3.456 \Omega$$

Next Time - Sec 10.5 Power calculations.

Sec 10.5 Power Calculations

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \quad \text{eqn 10.10}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \quad \text{eqn 10.11}$$

$$S = P + jQ \quad \text{eqn 10.23}$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \angle(\theta_v - \theta_i)$$

$$= \left[\frac{V_m}{\sqrt{2}} \quad \frac{I_m}{\sqrt{2}} \right] \angle(\theta_v - \theta_i)$$

$$= V_{\text{eff}} I_{\text{eff}} \angle(\theta_v - \theta_i)$$

$$= (V_{\text{eff}} e^{j\theta_v}) (I_{\text{eff}} e^{-j\theta_i})$$

$$= V_{\text{eff}} \quad I_{\text{eff}}^* \quad \text{* complex conjugate}$$

Now to prove the last equation.

$$\text{Recall } \cos(-\theta) = \cos \theta$$


$$\sin(-\theta) = -\sin \theta$$

$$\begin{aligned} \text{so } I_{\text{eff}} e^{-j\theta i} &= I_{\text{eff}} \cos(-\theta i) + j I_{\text{eff}} \sin(-\theta i) \\ &= I_{\text{eff}} \cos \theta i - j I_{\text{eff}} \sin \theta i \\ &= I_{\text{eff}}^* \text{ as stated before.} \end{aligned}$$

we can also write S in terms of V_m & I_m

$$S = \frac{1}{2} V I^*$$

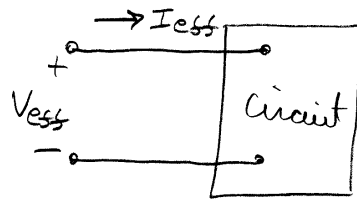All work has been derived by the passive sign convention.



For example

$$\text{Let } V = 100 \angle 15^\circ \text{ Volts}$$

$$I = 4 \angle -105^\circ \text{ Amps}$$

$$\text{so } I^* = 4 \angle +105^\circ \text{ A}$$

$$S = \frac{1}{2} (100 \angle 15^\circ) (4 \angle 105^\circ) = \frac{400}{2} \angle 15^\circ + 105^\circ = 200 \angle 120^\circ \text{ VA}$$

$$= 200 \cos 120^\circ + j 200 \sin 120^\circ$$

$$= -100 + j 173.2 \text{ Volt-Amps}$$

$$= P + jQ$$

$$\text{so } P = -100 \text{ watts}$$

$$Q = 173.2 \text{ VAR}$$

Alternate ways to express complex Power

$$V_{\text{eff}} = Z I_{\text{eff}} \quad \text{Ohm's Law (again)}$$

thus

$$S = V_{\text{eff}} I_{\text{eff}}^* = Z I_{\text{eff}} I_{\text{eff}}^* = Z |I_{\text{eff}}|^2$$

we can write the impedance in terms of the real
& imag parts (reactance)

$$Z = R + jX$$

$$\text{so } S = |I_{\text{eff}}|^2 (R + jX)$$

$$= \underbrace{|I_{\text{eff}}|^2 R}_P + j \underbrace{|I_{\text{eff}}|^2 X}_{+j Q}$$

so

$$P = |I_{\text{eff}}|^2 R = \frac{1}{2} I_m^2 R$$

$$Q = |I_{\text{eff}}|^2 X = \frac{1}{2} I_m^2 X$$

where X is the reactance of either an inductor (positive) or a capacitor (negative)

Second Variation


$$S = V_{\text{eff}} \left(\frac{V_{\text{eff}}}{Z} \right)^* \quad \text{which follows from}$$

$$I_{\text{eff}}^* = \left(\frac{V_{\text{eff}}}{Z} \right)^*$$

$$= \frac{|V_{\text{eff}}|^2}{Z^*}$$

$$= \underbrace{\frac{|V_{\text{eff}}|^2}{R}}_P + j \underbrace{\frac{|V_{\text{eff}}|^2}{X}}_Q$$

Ex 10.5 pg 505

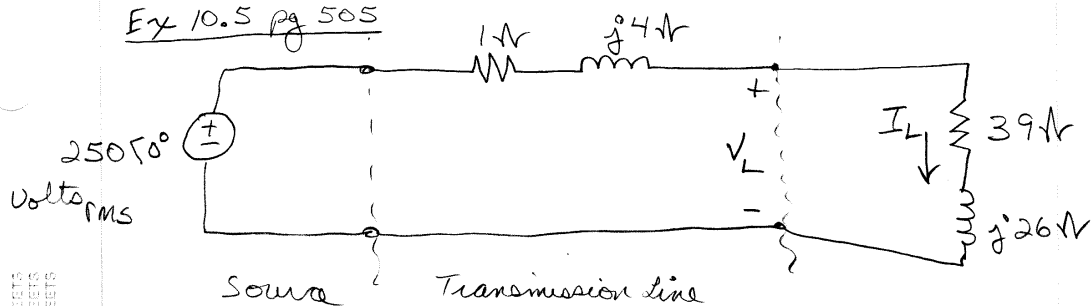a) find load current I_L & voltage V_L

$$Z_{eq} = (1 + j4) + (39 + j26) = 40 + j30 \Omega$$

$$= 50\angle 36.9^\circ \Omega$$

$$I_L = \frac{250\angle 0^\circ V_{rms}}{50\angle 36.9^\circ \Omega} = 5\angle -36.9^\circ A_{rms}$$

$$= 4 - j3 A$$

$$V_L = I_L(rms) Z_L = (4 - j3)(39 + j26) = 234 - j13 V_{rms}$$

$$= 234.36\angle -3.18^\circ V_{rms}$$


b) Pavg & Q for the load

$$S = \sqrt{e_{ss}} I_{e_{ss}}^* = (234 - j13)(4 + j3)^* = \underbrace{975}_{P} + j\underbrace{650}_{Q} VA$$

absorbing both

D.E. 10.6 pg 511

Now add a capacitor shunt to the last exercise

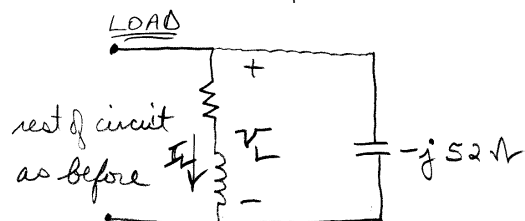a) find the new phasors V_L & I_L (rms)

$$Z_L = (39 + j26) \parallel (-j52) = (\text{much math later}) = 52 \angle -22.62^\circ$$

$$= 48 - j20$$

$$\text{so } Z_{eq} \text{ for the circuit is } = (48 - j20)(1 + j4) = 49 - j16$$

$$= 51.55 \angle -18.08^\circ \Omega$$

$$\underline{I_{\text{Load TOTAL}} = \frac{V_{rms}}{Z_{eq}} = \frac{250 \angle 0^\circ}{51.55 \angle -18.08^\circ} = 4.85 \angle 18.08^\circ \text{ A}_{rms}}$$

(Total for parallel branch)

$$\text{So } V_{\text{Load}} = Z_L \cdot I_{\text{LOAD TOTAL}} = (4.85 \angle 18.08^\circ)(52 \angle -22.62^\circ)$$

$$= 252.20 \angle -4.54^\circ \text{ V}_{rms}$$

$$I_L \text{ (original branch)} = \frac{V_L}{39 + j26} = \frac{252.20 \angle -4.54^\circ}{46.87 \angle 33.69^\circ}$$

$$= 5.38 \angle -38.23^\circ \text{ A}_{rms}$$

b) find the new P & Q for the original load now that the shunt is in place.

$$S_{\text{load}} = \underbrace{(252.2 \angle -4.54)}_{V_L} \underbrace{(5.38 \angle +38.23^\circ)}_{I_L^*}$$


$$= 1357 \angle 33.69^\circ \text{ VA}$$

$$= \underbrace{1129.09}_P - j \underbrace{752.73}_Q \text{ VA}$$

compare without
the shunt $950 + j 650 \text{ VA}$

Next Time sec 10.6 Max Power

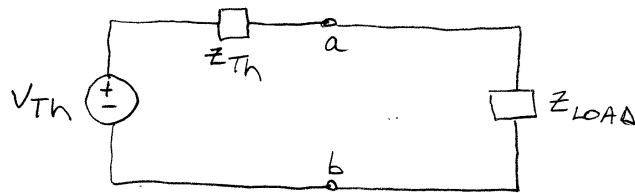

Sec 10.6 Max Power Transfer

we want to find the load impedance Z_L that results in the delivery of the max average power at terminals ab.

we will show max avg transfer occurs when $Z_L = Z_{TH}^*$
 Z_{TH}^* = complex conjugate of the Thevenin impedance.

$$Z_{TH} = R_{TH} + jX_{TH}$$

reactance
positive for inductor

$$Z_L = R_L + jX_L$$

negative for capacitor

Since we are making avg power calculation - we will express V_{TH} as its rms value.

thus

$$I_{rms} = \frac{V_{TH}(rms)}{(R_{TH} + jX_{TH}) + (R_L + jX_L)}$$

$$= \frac{V_{TH}(rms)}{(R_{TH} + R_L) + j(X_{TH} + X_L)}$$

recall Power at the load $P_L = |I|^2 R_L$

recall $|I|^2 = I \cdot I^*$

$$P_L = \frac{|V_{Th}|^2 R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

the 2 independent variables are R_L & X_L (ie can change)
all others are "fixed" by the source Thevenin circuit.

thus max P is when $\frac{\partial P}{\partial R_L} = 0 = \frac{\partial P}{\partial X_L}$

$$\frac{\partial P}{\partial X_L} = \frac{|V_{Th}|^2 R_L (-2)(X_L + X_{Th})}{[(R_L + R_{Th})^2 + (X_L + X_{Th})^2]^2}$$

Be careful with the
quotient rule here!

$$= 0 \quad \text{only when } X_L = -X_{Th}$$

$$\frac{\partial P}{\partial R_L} = \frac{|V_{Th}|^2 [(R_L + R_{Th})^2 + (X_L + X_{Th})^2 - 2R_L(R_L + R_{Th})]}{[(R_L + R_{Th})^2 + (X_L + X_{Th})^2]^2}$$

Product & Quotient
rule here

$$= 0 \quad \text{when } (R_L + R_{Th})^2 + (X_L + X_{Th})^2 - 2R_L(R_L + R_{Th}) = 0$$

shuffle the terms

$$2R_L^2 + 2R_L R_{Th} - (R_L^2 + 2R_L R_{Th} + R_{Th}^2) = (X_L + X_{Th})^2$$

$$R_L^2 = R_{Th}^2 + (X_L + X_{Th})^2$$

$$R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2} \quad \text{when } \frac{\partial P}{\partial R_L} = 0$$

So these two conditions are simultaneously met when

$$Z_L = Z_{Th}^*$$

To verify this let $Z_{Th} = R_{Th} + jX_{Th}$

$$Z_{Th}^* = R_{Th} - jX_{Th}$$

$$\text{and } Z_L = R_L + jX_L$$

thus it directly follows $X_L = -X_{Th}$ as found for $\frac{dP}{dX_L} = 0$

$$\text{and } R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

$$= \sqrt{R_{Th}^2 + (-X_{Th} + X_{Th})^2} = \sqrt{R_{Th}^2}$$

$$= R_{Th} \quad \text{as found by } \frac{dP}{dR_L} = 0$$

Max Power Absorbed

$$\begin{aligned} \text{when } Z_L = Z_{Th}^* \text{ then } I_{LOAD} &= \frac{V_{Th}}{(R_{Th} + jX_{Th})(R_{Th} - jX_{Th})} \\ \text{ie } R_L = R_{Th} \quad &= \frac{V_{Th}}{2R_{Th}} = \frac{V_{Th}}{2R_L} \end{aligned}$$

so max Power is

$$P_{max} = \frac{|V_{Th}|^2 R_L}{4 R_L^2}$$

$$P_{max} = |I|^2 R_L$$

$$= \frac{1}{4} \frac{|V_{Th}|^2}{R_L}$$

$$= \frac{1}{4} \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{R_L} = \frac{1}{8} \frac{V_m^2}{R_L}$$

max Power when $Z_L \neq Z_{Th}^*$

① we want to adjust $X_L \rightarrow -X_{Th}$ near as possible


$$\& R_L \rightarrow \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

② what about when $|Z_L|$ can be varied



but $\angle \theta$ is fixed?

in this case set $|Z_L| \rightarrow |Z_{Th}|$ as close as possible.

Ex 10.8 pg 514

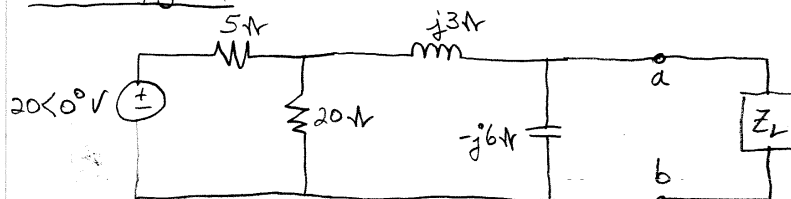

Source Transform

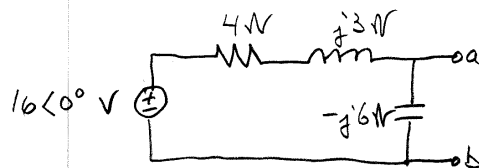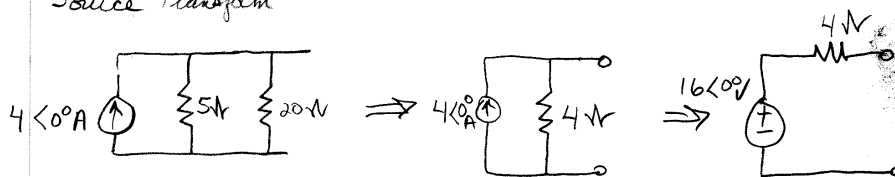

$$Z_{Th} \text{ seen at } ab \Rightarrow Z_{Th} = (4 + j3)\Omega \parallel (-j6\Omega) = \frac{(4 + j3)(-j6)}{-j6 + 4 + j3}$$

$$Z_{Th} = \frac{18 - j24}{4 - j3} \Omega = \frac{144 - j42}{25} \Omega = (5.76 - j1.68) \Omega$$

Thus $Z_L = Z_{Th}^* = 5.76 + j1.68 \Omega$ for max avg power


$$V_{Th} = \frac{(-j6)\Omega}{(4+j3-j6)\Omega} (16\angle 0^\circ \text{ Volts}) = \frac{(18-j24)}{25} (16\angle 0^\circ \text{ V})$$

$$= 11.52 - j15.36 \text{ Volts}$$

$$= 19.2 \angle -53.13^\circ \text{ Volts}$$

$$\text{thus } P_{max} = \frac{1}{8} \frac{V_m^2}{R_L} = \frac{1}{8} \frac{(19.2 \text{ V})^2}{5.76} = \underline{\underline{8 \text{ watts}}}$$

D.E. 10.9 pg 517

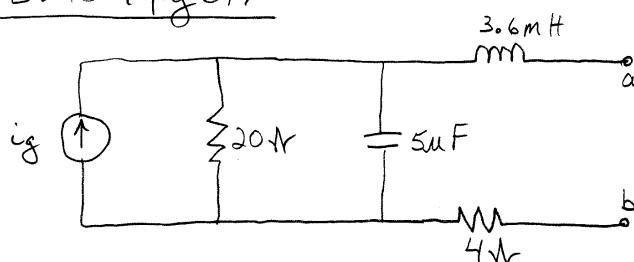


where $i_g = 3 \cos 5000t$ Amps

$$Z_{\text{inductor}} = j\omega L = j(5000)^{\text{rad/s}} (3.6 \text{ mH}) = j18 \Omega$$

$$Z_{\text{cap}} = j\left(\frac{-1}{\omega C}\right) = j\left(\frac{-1}{5000 \cdot 5 \mu\text{F}}\right) = -j40 \Omega$$

so Phasor Domain Equiv Circuit is

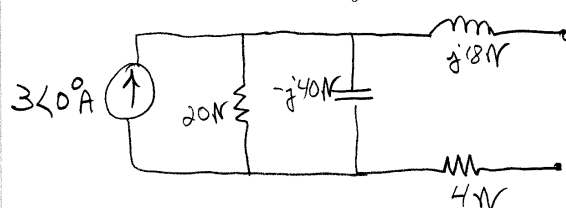

Now find The Thevenin Equivalent.

the impedance seen at terminals ab is

$$\begin{aligned} Z_{Th} &= [20 \Omega \parallel (5 - j40) \Omega] \Omega + j18 \Omega + 4 \Omega \\ &= (16 - j8) \Omega + j18 \Omega + 4 \Omega \\ &= 20 + j10 \Omega \end{aligned}$$

a) so max avg power transfer when $Z_L = Z_{Th}^*$


$$\underline{Z_L = 20 - j10 \Omega}$$

b) what is P_{max} in part a)? ($V = IR$)

$$V_{Th} = \frac{(20 \Omega)(-j40 \Omega)}{20 - j40 \Omega} (3 \text{ Amp}) = (16 - j8 \Omega) (3A) = 48 - j24V$$

already found above
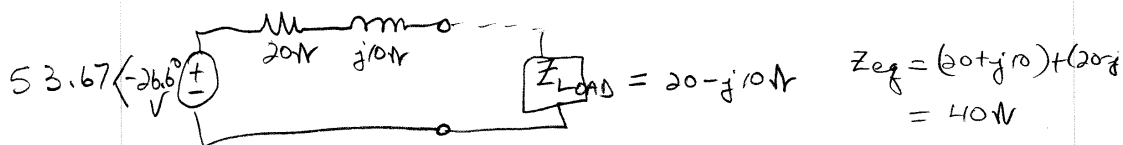
$$= 53.67 \angle -26.57^\circ \text{ Volts}$$



$$I = \frac{V_{Th}}{(20 + 20) \Omega} = 1.34 \angle -26.57^\circ \text{ Amps} \quad I_{rms} = \frac{I}{\sqrt{2}}$$

$$\underline{P_{max} = \left(\frac{|I|}{\sqrt{2}} \right)^2 (20 \Omega) = \frac{1.34^2}{2} (20 \Omega) = 17.956 \text{ watts}}$$

at the load