

Started on Thursday, 14 December 2017, 10:59 AM

State Finished

Completed on Thursday, 14 December 2017, 12:09 PM

Time taken 1 hour 10 mins

Grade 52.00 out of 106.00 (49%)

Question 1

Correct

Mark 1.00 out of 2.00

Which of the following is true for a PNP BJT operating in the forward-active region ?

Select one:

- ☐ a. The collector current consists primarily of holes injected from the collector into the base
- ☒ b. The emitter current consists primarily of holes injected from the emitter into the base ✓
- ☐ c. Some base current flows to replace holes which are lost as electrons diffusing across the base recombine
- ☐ d. All of these
- ☐ e. The base current consists primarily of holes injected from the emitter into the base

The correct answer is: The emitter current consists primarily of holes injected from the emitter into the base

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 2

Correct

Mark 1.00 out of 2.00

Which of the following is true for a PNP BJT ?

Select one:

- ☒ a. None of these ✓
- ☐ b. Current flows when either V_{be} or V_{bc} are positive voltages
- ☐ c. A P-type base is sandwiched between an N-type emitter and an N-type collector
- ☐ d. The base current consists of mostly holes
- ☐ e. Current flows primarily because of electrons injected into the base

The correct answer is: None of these

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 3

Correct

Mark 1.00 out of 2.00

A BJT with its base-emitter junction reverse biased and its base-collector junction reverse biased is in :

Select one:

- ☐ a. Reverse-Active
- ☐ b. Forward-Active
- ☐ c. Saturation
- ☒ d. Cutoff ✓
- ☐ e. None of these

The correct answer is: Cutoff

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 4

Correct

Mark 2.00 out of 2.00

A BJT with its base-emitter junction forward biased and its base-collector junction forward biased is in :

Select one:

- ☐ a. Reverse-Active
- ☐ b. None of these
- ☒ c. Saturation ✓
- ☐ d. Cutoff
- ☐ e. Forward-Active

The correct answer is: Saturation

Correct

Marks for this submission: 2.00/2.00.

Question 5

Correct

Mark 1.00 out of 2.00

As $|V_{ce}|$ increases for a BJT in the forward active region, “base-width modulation” causes :

Select one:

- ☐ a. The width of the base-collector depletion region to decrease
- ☐ b. All of these
- ☐ c. The output resistance, r_o , to increase
- ☒ d. The collector current for the BJT to increase ✓
- ☐ e. The width of the base to increase

The correct answer is: The collector current for the BJT to increase

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 6

Correct

Mark 2.00 out of
2.00

If an NPN BJT at 300°K with a constant collector current of 10 μ A has a V_{be} voltage of 620mV, then what will V_{be} be for this same BJT if the collector current is increased to 1mA?

Select one:

- ☒ a. 740mV ✓
- ☐ b. None of these
- ☐ c. 680mV
- ☐ d. 800mV
- ☐ e. 560mV

The correct answer is: 740mV

Correct

Marks for this submission: 2.00/2.00.

Question 7

Correct

Mark 1.00 out of
2.00

Considering the typical input and output resistances, a BJT common-collector is well suited to be which of the following types of amplifiers ?

Select one:

- ☒ a. Voltage amplifier ✓
- ☐ b. Transconductance amplifier
- ☐ c. None of these
- ☐ d. Current amplifier
- ☐ e. Transresistance amplifier

The correct answer is: Voltage amplifier

CorrectMarks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 8

Correct

Mark 1.00 out of 2.00

For a BJT common-collector amplifier, which of the following is true ?

Select one:

- ☐ a. The input resistance is typically low
- ☒ b. The output resistance is typically low ✓
- ☐ c. The voltage gain is negative
- ☐ d. All of these
- ☐ e. The voltage gain is typically high

The correct answer is: The output resistance is typically low

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 9

Correct

Mark 1.00 out of 2.00

Considering the typical input and output resistances, which of the following MOS amplifier types is well suited to be used as a transresistance amplifier ?

Select one:

- ☐ a. Common-source
- ☐ b. Common-drain
- ☐ c. Source-follower
- ☒ d. None of these ✓
- ☐ e. Common-gate

The correct answer is: None of these

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 10

Correct

Mark 1.00 out of 2.00

For a MOS common-source amplifier, which of the following is true ?

Select one:

- ☒ a. The voltage gain is typically high ✓
- ☐ b. The output resistance is typically low
- ☐ c. The input resistance is typically low
- ☐ d. The voltage gain is positive
- ☐ e. None of these

The correct answer is: The voltage gain is typically high

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 11

Correct

Mark 2.00 out of 2.00

In the forward-active region, current flows out of the base of a PNP BJT.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00.

Question 12

Correct

Mark 2.00 out of 2.00

When the base-emitter and base-collector junctions in a BJT are reverse biased, zero current will flow.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 13

Correct

Mark 2.00 out of 2.00

If the base-emitter junction of a BJT is reverse biased and the base-collector junction is forward biased, then the BJT is operating in the saturation region of operation.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 14

Correct

Mark 2.00 out of 2.00

As the reverse bias across the base-collector junction in a BJT increases, the width of the base increases which causes the collector current to increase.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 15

Correct

Mark 0.00 out of 2.00

The output resistance in a transresistance amplifier model is used to determine the signal lost due to the current division between the load resistance and the output resistance of the amplifier.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

CorrectMarks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 16

Correct

Mark 0.00 out of
2.00

Since most amplifiers are intentionally designed to be bidirectional, the two-port model for an amplifier needs to include a term to model the gain from the output back to the input.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 17

Correct

Mark 0.00 out of
2.00

The base resistance in the BJT hybrid-pi model, r_{π} , increases as the collector current increases.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 18

Correct

Mark 0.00 out of
2.00

The output resistance for a common-collector amplifier is the same as the input resistance for a common-base amplifier.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 19

Correct

Mark 0.00 out of 2.00

Since current normally flows into the source of a PMOS FET, the source is usually drawn pointing up towards the positive power supply.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 20

Correct

Mark 2.00 out of 2.00

All three MOS amplifier types (CS, CG, CD) are identical when the input and output are applied.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 21

Correct

Mark 6.00 out of 6.00

What is the base-to-emitter resistance, r_{π} , in $k\Omega$ for a PNP BJT operating in the forward-active region at 27°C with $I_c = 417\mu\text{A}$? Use: $\beta = 24$ and $V_t = kT/q = 26\text{mV}$.

Answer: ✓

The correct answer is: 1.50

Correct

Marks for this submission: 6.00/6.00.

Question 22

Correct

Mark 6.00 out of 6.00

What is the open-circuit voltage gain, μ_f , in V/V for an NMOS FET operating in saturation with $I_d = 967\mu\text{A}$ and $V_{on} = V_{gs} - V_t = 245\text{mV}$? Use: $\lambda = 0.11$

Answer: 74.211



The correct answer is: 74.21

Correct


Marks for this submission: 6.00/6.00.

Question 23

Not answered

Mark 0.00 out of 6.00

For the BJT bias circuit shown, what is the base current, I_B , in microamps? Use $V_{CC} = 7\text{V}$, $V_{EE} = -8\text{V}$, $V_B = 2.9\text{V}$, $R_C = 1.8\text{k}\Omega$, and $R_E = 6.8\text{k}\Omega$. Assume that the transistor is in the forward-active region, with $\beta = 46$ and $|V_{be(on)}| = 0.7\text{V}$. Neglect the effects of base-width modulation.

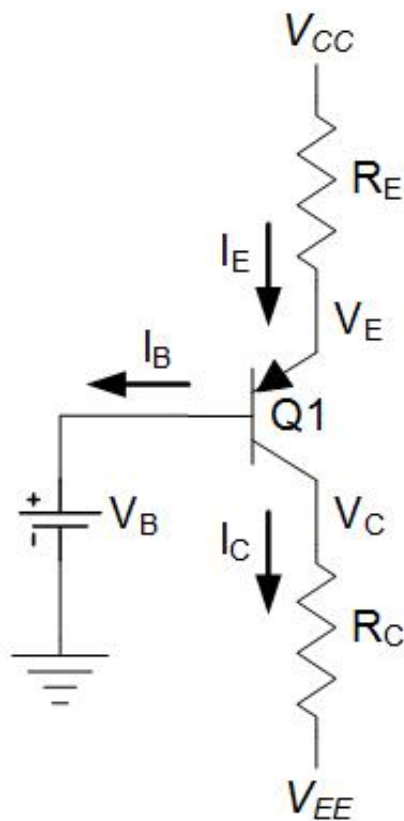

Answer:



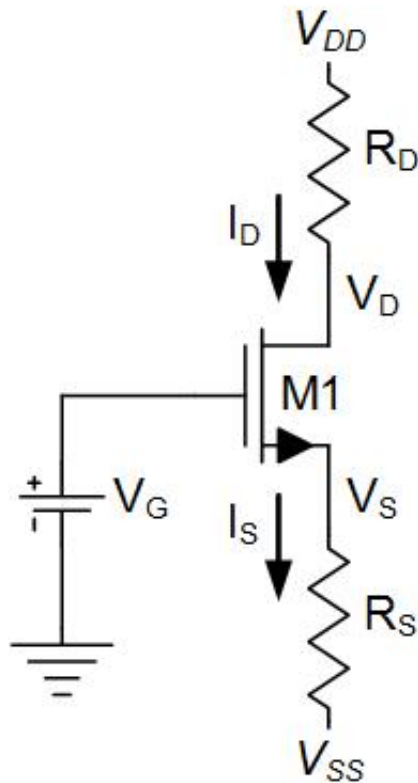
The correct answer is: 10.6

Question 24

Not answered

Mark 0.00 out of
6.00

For the MOSFET bias circuit shown, what value of R_D in kilohms is needed to allow the maximum possible peak-to-peak signal swing on the drain without clipping? Use: $V_{DD} = 8V$, $V_{SS} = -7V$, $V_G = -0.6V$, $R_S = 4.8k\Omega$, $V_t = 0.5V$, and $V_{on} = 0.15$. (Remember that $V_{on} = V_{ov} = V_{gs} - V_t$) Neglect the effect of channel-length modulation and body effect. (Hint: Be sure to keep the MOSFET in saturation!)

Answer: ✖

The correct answer is: 3.8


Question 25

Incorrect

Mark 0.00 out of

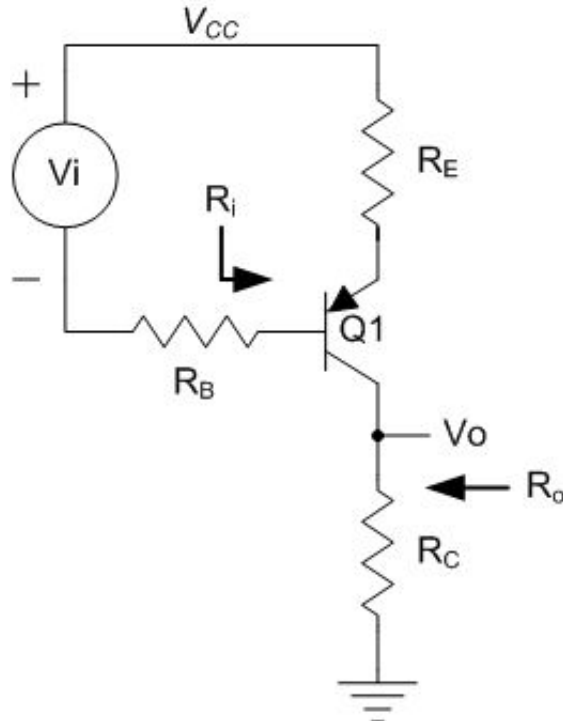6.00

What is the low frequency voltage gain for the amplifier shown at 27°C with $R_C = 36.6\text{k}\Omega$, $R_E = 0.1\text{k}\Omega$ and $R_B = 1.0\text{k}\Omega$? Use: $I_C = 971\mu\text{A}$, $\beta = 44$, and $V_T = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.



Answer: 246.62



The correct answer is: -241.14

Incorrect

Marks for this submission: 0.00/6.00.


Question 26

Incorrect

Mark 0.00 out of

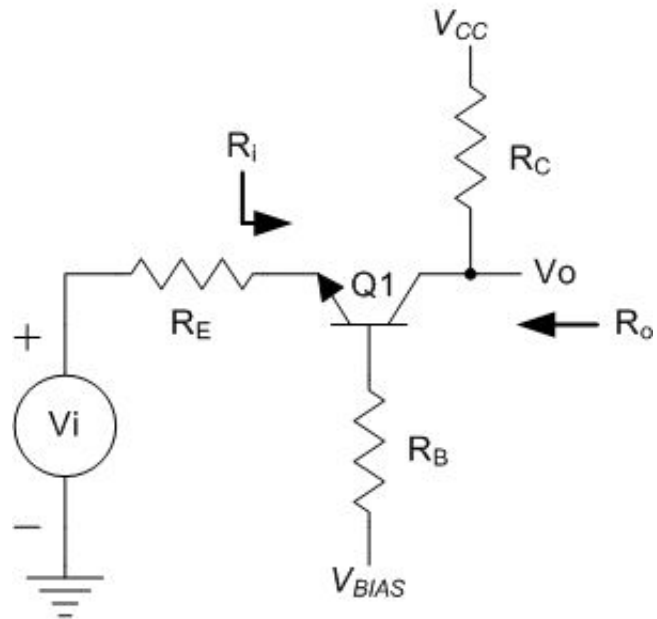6.00

What is the low frequency voltage gain for the amplifier shown at 27°C with $R_C = 40.6\text{k}\Omega$, $R_E = 0.1\text{k}\Omega$ and $R_B = 0.5\text{k}\Omega$? Use: $I_C = 48\mu\text{A}$, $\beta = 197$, and $V_T = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.



Answer: -29.936



The correct answer is: 62.97

Incorrect


Marks for this submission: 0.00/6.00.

Question 27

Correct

Mark 6.00 out of 6.00

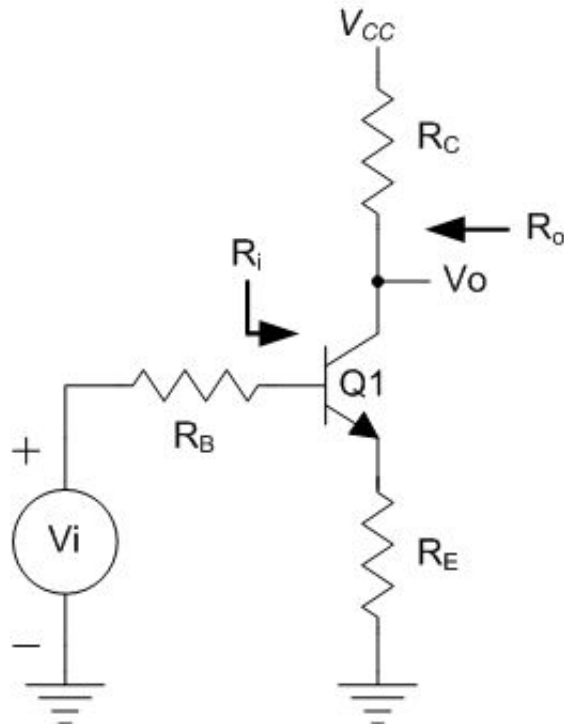What is the low frequency input resistance, R_i , in $k\Omega$ for the amplifier shown at 27°C with $R_C = 10.1k\Omega$, $R_E = 0.2k\Omega$ and $R_B = 0.8k\Omega$? Use: $I_C = 427\mu\text{A}$, $\beta = 146$, and $V_T = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.



Answer: 38.1



The correct answer is: 38.3

Correct


Marks for this submission: 6.00/6.00.

Question 28

Correct

Mark 6.00 out of 6.00

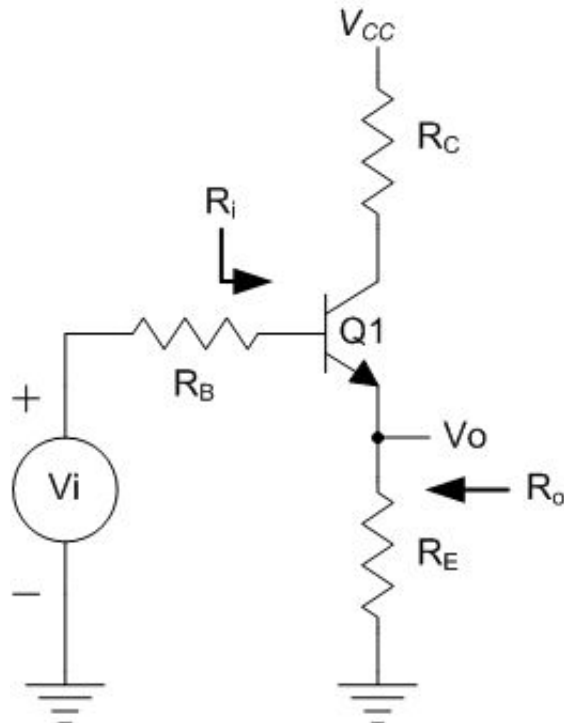What is the low frequency input resistance, R_i , in $k\Omega$ for the amplifier shown at 27°C with $R_C = 13.9k\Omega$, $R_E = 0.4k\Omega$ and $R_B = 1.0k\Omega$? Use: $I_C = 50\mu\text{A}$, $\beta = 98$, and $V_T = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.



Answer: 90.16



The correct answer is: 90.6

Correct


Marks for this submission: 6.00/6.00.

Question 29

Incorrect

Mark 0.00 out of
6.00

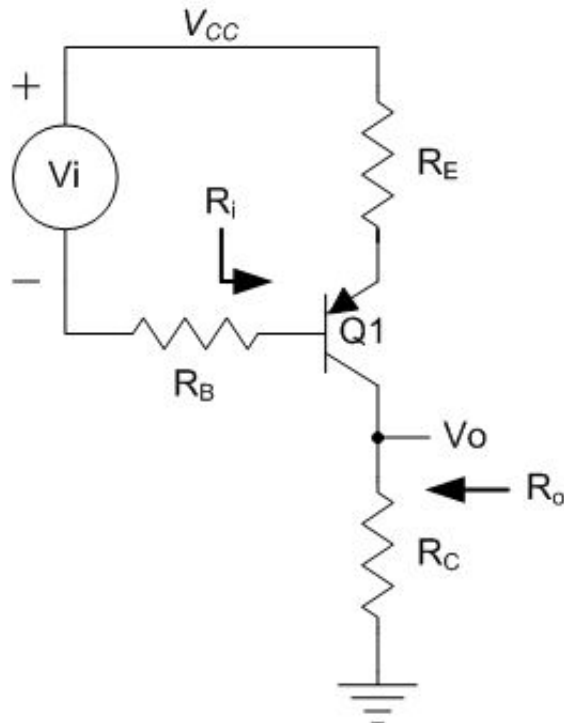What is the low frequency output resistance, R_o , in $k\Omega$ for the amplifier shown at 27°C with $R_c = 62.3k\Omega$, $R_e = 0.9k\Omega$ and $R_b = 0.9k\Omega$? Use: $I_c = 28\mu\text{A}$, $\beta = 22$, $V_A = 10\text{V}$, and $V_t = kT/q = 26\text{mV}$. Use the "short-cut approach" discussed in class.



Answer: 0.456



The correct answer is: 57.2

Incorrect


Marks for this submission: 0.00/6.00.

Question 30

Incorrect

Mark 0.00 out of
6.00

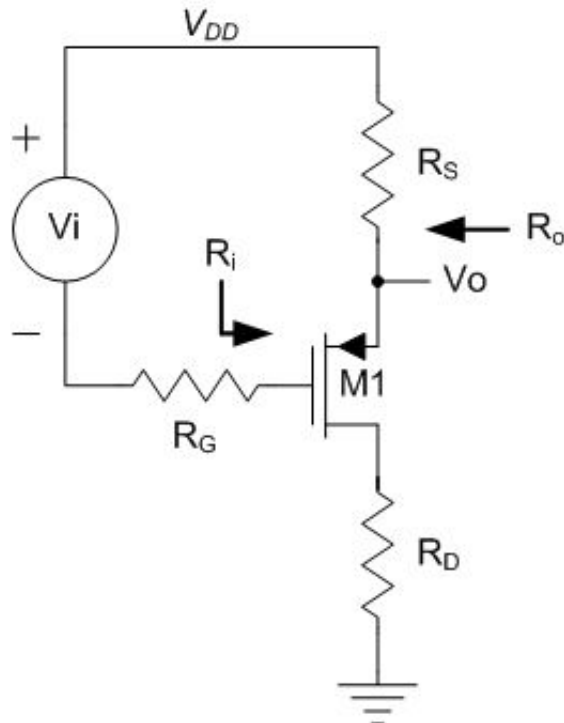What is the low frequency output resistance, R_o , in Ω for the amplifier shown at 27°C with $R_d = 35.2\text{k}\Omega$, $R_s = 0.6\text{k}\Omega$ and $R_g = 9.5\text{k}\Omega$. Use: $W/L = 67$, $I_d = 156\mu\text{A}$, $V_{TP} = -0.5\text{V}$, $k'_p = 40\mu\text{A/V}^2$, $\lambda = 0$ Neglect body effect.



Answer: 35200



The correct answer is: 387.4

Incorrect


Marks for this submission: 0.00/6.00.

Question 31

Correct

Mark 6.00 out of
6.00

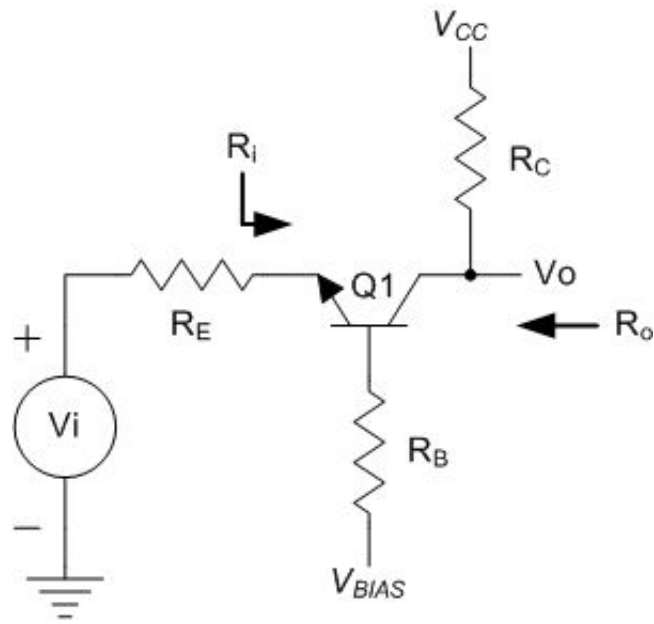Estimate the maximum low frequency voltage gain for the amplifier shown if the bias voltage across R_C is 1693mV and the bias voltage across R_E is 364mV.



Answer: 4.65




The correct answer is: 4.65

Correct

Marks for this submission: 6.00/6.00.

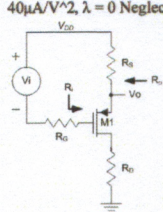
30. What is the low frequency output resistance, R_o , in Ω for the amplifier shown at 27°C with $R_d = 35.2\text{k}\Omega$, $R_s = 0.6\text{k}\Omega$ and $R_g = 9.5\text{k}\Omega$. Use: $W/L = 67$, $I_d = 156\mu\text{A}$, $V_{TP} = -0.5\text{V}$, $k'_p = 40\mu\text{A/V}^2$, $\lambda = 0$. Neglect body effect.



$$g_m = \sqrt{2 \cdot k'_p \cdot (W/L) \cdot I_d} = \sqrt{2 \cdot (40 \times 10^{-6}) \cdot (67) \cdot (156 \times 10^{-6})} = 0.0009144$$

$$R_o = R_s \parallel \frac{1}{g_m} = \frac{1}{\frac{1}{600} + 0.0009144} = \frac{1}{0.002581085} = 387.4\Omega$$

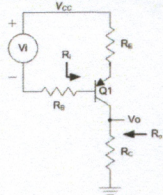29. What is the low frequency output resistance, R_o , in $\text{k}\Omega$ for the amplifier shown at 27°C with $R_c = 62.3\text{k}\Omega$, $R_e = 0.9\text{k}\Omega$ and $R_b = 0.9\text{k}\Omega$? Use: $I_c = 28\mu\text{A}$, $\beta = 22$, $V_A = 10\text{V}$, and $V_t = kT/q = 26\text{mV}$. Use the "short-cut approach" discussed in class.



$$g_m = \frac{I_c}{V_t} = \frac{(28 \times 10^{-6})}{(26 \times 10^{-3})} = 0.001077$$

$$r_{\pi} = \frac{\beta}{g_m} = 20428.57$$


$$r_o = \frac{V_A}{I_c} = \frac{10}{(28 \times 10^{-6})} = 357142.86$$

$$R_{o1} = r_o \left[1 + \frac{\beta R_E}{R_b + R_E + r_{\pi}} \right] + \frac{R_E}{1 + \left(\frac{R_E}{r_{\pi} + R_b} \right)}$$

$$R_o = R_c \parallel R_{o1} = \frac{1}{\frac{1}{62300} + \frac{1}{676129.84}} = \frac{1}{0.00001753} = 57043.86\Omega = 57.04\text{k}\Omega$$

57.2 k Ω (moodle)

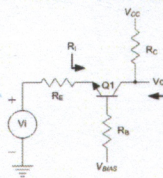26. What is the low frequency voltage gain for the amplifier shown at 27°C with $R_c = 40.6\text{k}\Omega$, $R_e = 0.1\text{k}\Omega$ and $R_b = 0.5\text{k}\Omega$? Use: $I_c = 48\mu\text{A}$, $\beta = 197$, and $V_t = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.



$$g_m = \frac{I_c}{V_t} = \frac{(48 \times 10^{-6})}{(26 \times 10^{-3})} = 0.001846$$


$$V_{BE} = -V_i \cdot \frac{1}{1 + g_m \left(\frac{R_b}{\beta + 1} + R_E \right)}$$

$$V_o = -g_m V_{BE} R_c \rightarrow \frac{V_o}{V_i} = g_m R_c \left(\frac{1}{1 + g_m \left(\frac{R_b}{\beta + 1} + R_E \right)} \right) \Rightarrow \frac{V_o}{V_i} = \frac{g_m R_c}{1 + \frac{g_m R_b}{\beta + 1} + g_m R_E}$$

$$\frac{0.001846 \cdot 40600}{1 + \left(\frac{0.001846 \cdot 500}{197 + 1} \right) + (0.001846 \cdot 100)} =$$

63.02 (calculated)
62.97 (moodle answer)

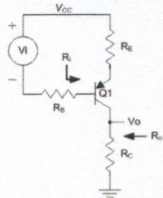25. What is the low frequency voltage gain for the amplifier shown at 27°C with $R_c = 36.6\text{k}\Omega$, $R_e = 0.1\text{k}\Omega$ and $R_b = 1.0\text{k}\Omega$? Use: $I_c = 971\mu\text{A}$, $\beta = 44$, and $V_t = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.




$$g_m = \frac{I_c}{V_t} = \frac{(971 \times 10^{-6})}{(26 \times 10^{-3})} = 0.037346$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{44}{0.037346} = 1178.167$$

$$A_v = \frac{-\beta R_c}{R_b + r_{\pi} + (\beta + 1) R_E} = \frac{(-44)(36600)}{1000 + 1178.167 + (45 \cdot 100)} = -241.14$$

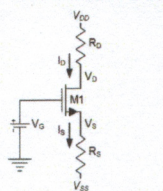24. For the MOSFET bias circuit shown, what value of R_d in kilohms is needed to allow the maximum possible peak-to-peak signal swing on the drain without clipping? Use: $V_{DD} = 8\text{V}$, $V_{SS} = -7\text{V}$, $V_g = -0.6\text{V}$, $R_s = 4.8\text{k}\Omega$, $V_t = 0.5\text{V}$, and $V_{on} = 0.15$. (Remember that $V_{on} = V_{ov} = V_{gs} - V_t$) Neglect the effect of channel-length modulation and body effect. (Hint: Be sure to keep the MOSFET in saturation!)




$$V_{GS} = V_{GN} + V_t = 0.15 + 0.5 = 0.65$$

$$-V_G + V_{GS} + I_S R_s + V_{SS} = 0 \rightarrow -(-0.6) + 0.65 + I_S (4800) + 7 = 0 \rightarrow I_S = \frac{-8.25}{4800} = -0.00172 \quad I_S = I_D$$

$$V_G = V_{GS} - V_t = 0.65 - 0.5 = 0.15\text{V}$$

23. For the BJT bias circuit shown, what is the base current, I_b , in microamps? Use $V_{CC} = 7\text{V}$, $V_{EE} = -8\text{V}$, $V_b = 2.9\text{V}$, $R_c = 1.8\text{k}\Omega$, and $R_e = 6.8\text{k}\Omega$. Assume that the transistor is in the forward-active region, with $\beta = 46$ and $|V_{be(on)}| = 0.7\text{V}$. Neglect the effects of base-width modulation.

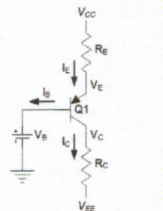

$$V_E = V_{be} + V_b = 0.7 + 2.9 = 3.4$$

$$I_E = \frac{V_{CC} - V_E}{R_E} = \frac{7 - 3.4}{6800} = 0.0005$$

$$I_B = \frac{I_E}{(1 + \beta)} = \frac{0.0005}{(1 + 46)} = 0.000010638\text{A} = 10.6\mu\text{A}$$