

Home ► My courses ► **EEE117-2019S-Sec1** ► Homework ►  
Homework 2 - Chapter 9

---

<b>Started on</b>	Thursday, 24 January 2019, 7:50 AM
-------------------	------------------------------------

---

<b>State</b>	Finished
--------------	----------

---

<b>Completed on</b>	Friday, 1 February 2019, 4:32 PM
---------------------	----------------------------------

---

<b>Time taken</b>	8 days 8 hours
-------------------	----------------

---


<b>Grade</b>	<b>90.83</b> out of 100.00
--------------	----------------------------

---

**Question 1**

Correct

Mark 10.00 out of 10.00

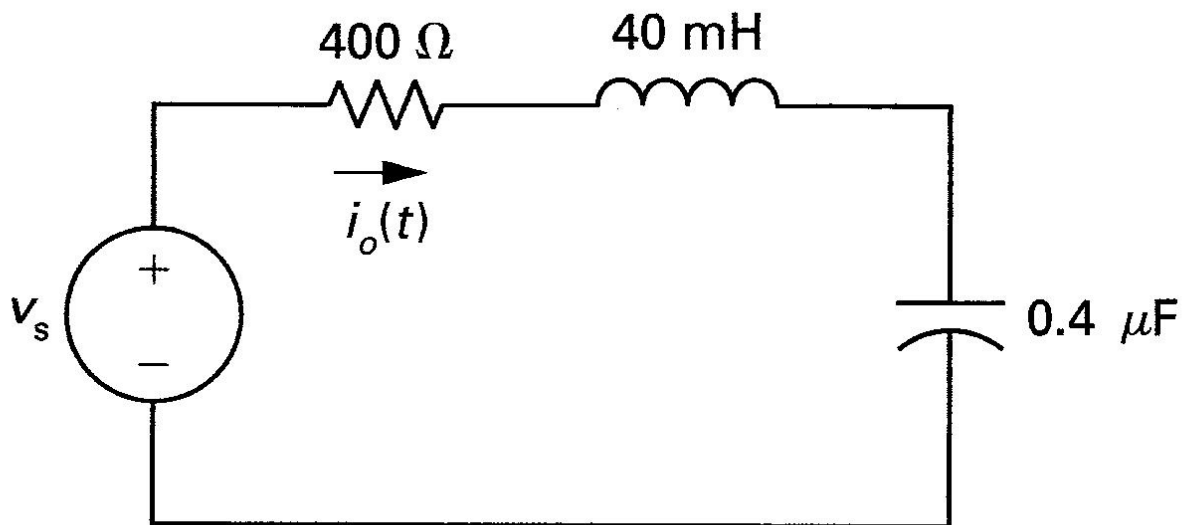

P9.14\_6ed

Given:  $v_s = 750 \cos(5,000t)$  V.Find the time domain current  $i_o(t)$ .

$$i_o(t) = \boxed{1.5} \checkmark \cos(5,000 t + \boxed{36.87} \checkmark ^\circ) \text{ A}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

Mark 6.67 out of 10.00

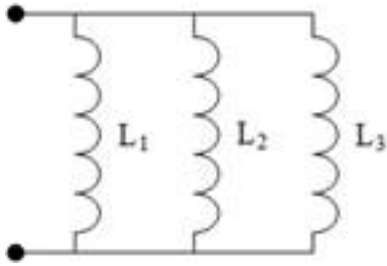

CQ9.11

Given:

$$L_1 = 8.5 \text{ mH (milli H)} \quad L_2 = 10.4 \text{ mH (milli H)} \quad L_3 = 15.2 \text{ mH (milli H)}$$

The radian frequency of the driving source is 61047 rad/sec

Find the equivalent impedance of this parallel combination.  $Z_{Leq} = j \text{ ?? } \Omega$   
(Ohms)


Answer: 218

**Correct**Marks for this submission: 10.00/10.00. Accounting for previous tries, this gives  
**6.67/10.00.**

### Question 3

Correct

Mark 10.00 out of 10.00

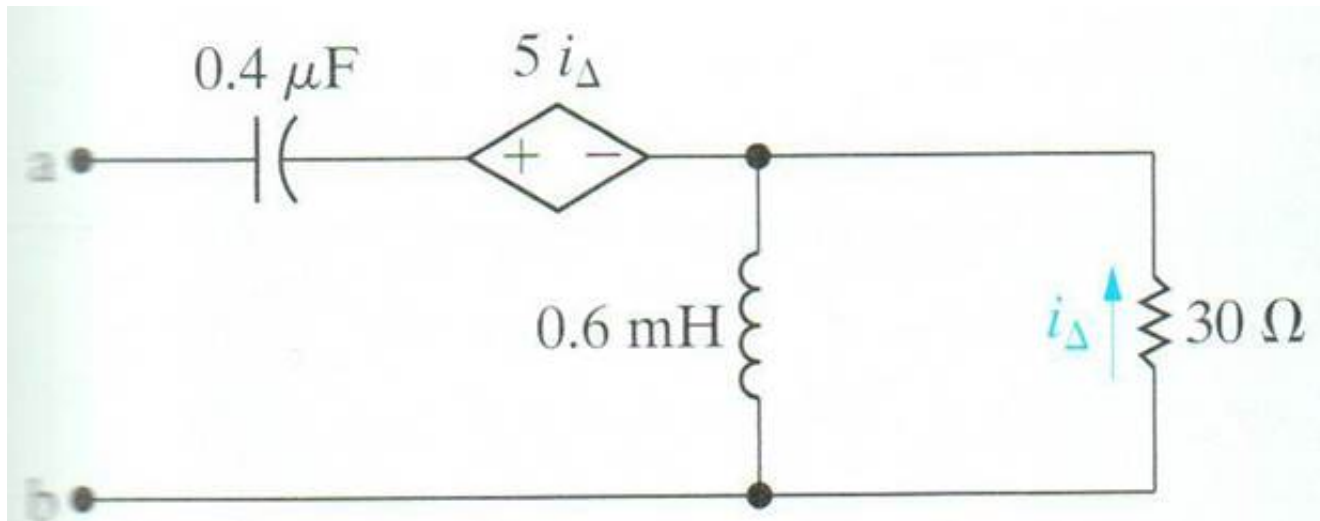

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

The frequency of operation is 100 krad/sec.

$$Z_{\text{Th}} = \boxed{20} \checkmark + j \boxed{-15} \checkmark \Omega (\text{Ohm})$$


**Correct**

Marks for this submission: 10.00/10.00.

#### Question 4

Correct

Mark 10.00 out of 10.00

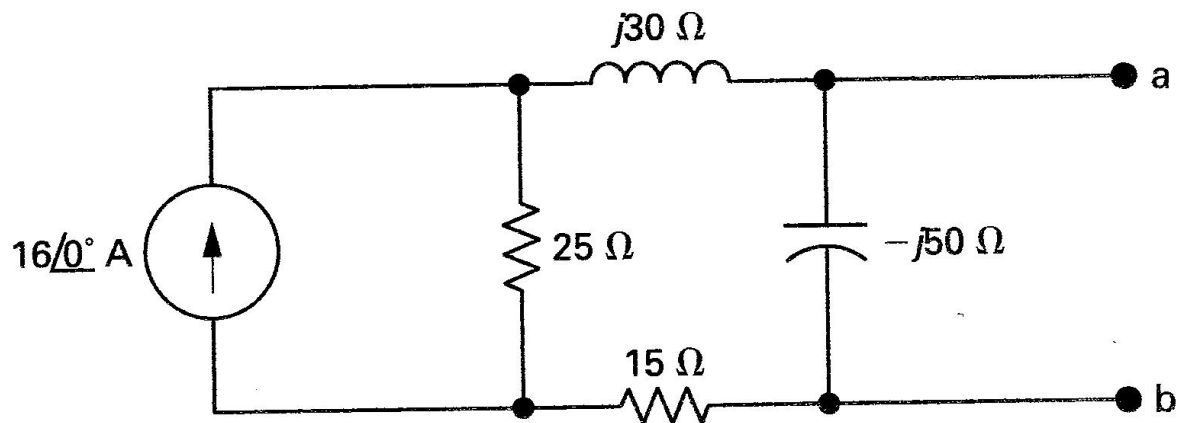

P9.39\_6ed

Find the Norton equivalent circuit with respect to the terminals ab.

$I_N =$   ✓  $+ j$   ✓ A in rectangular form

$Z_{Th} =$   ✓  $+ j$   ✓  $\Omega$  (Ohm) in rectangular form


**Correct**

Marks for this submission: 10.00/10.00.

### Question 5

Correct

Mark 10.00 out of 10.00

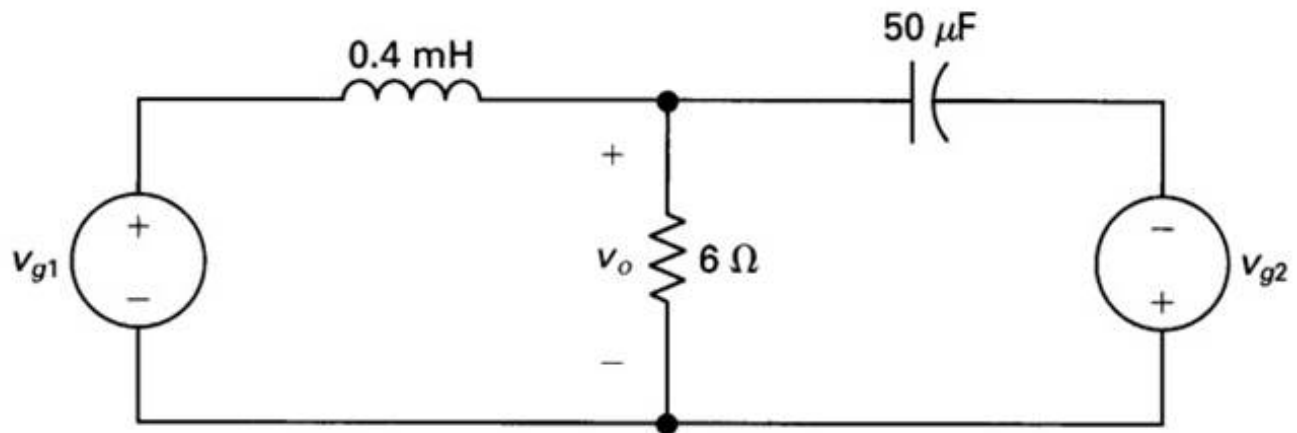

P9.49\_6ed

Given:

$$v_{g1} = 10 \cos(5,000 t + 53.13^\circ) \text{ V}$$

$$v_{g2} = 8 \sin(5,000 t) \text{ V}$$

Find the steady-state time domain expression for  $v_o(t)$  of this circuit.

$$v_o(t) = \boxed{12} \checkmark \cos(5,000t + \boxed{.0001} \checkmark^\circ) \text{ (Degrees) Volts}$$


**Correct**

Marks for this submission: 10.00/10.00.

## Question 6

Correct

Mark 10.00 out of 10.00

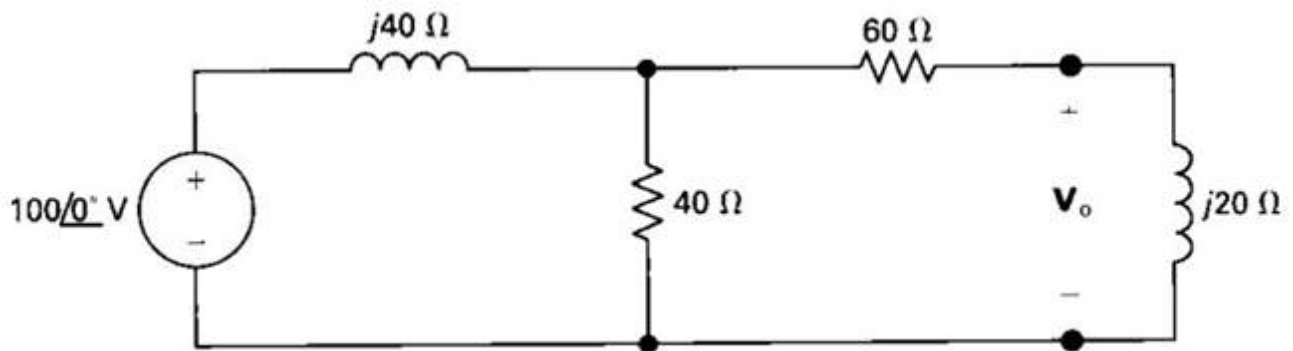

P9.47\_6ed

Find  $V_o$  in this circuit.

$V_o = \text{Mag}$   ✓ with Angle  ✓ Degrees Volts


**Correct**

Marks for this submission: 10.00/10.00.

### Question 7

Correct

Mark 6.67 out of 10.00

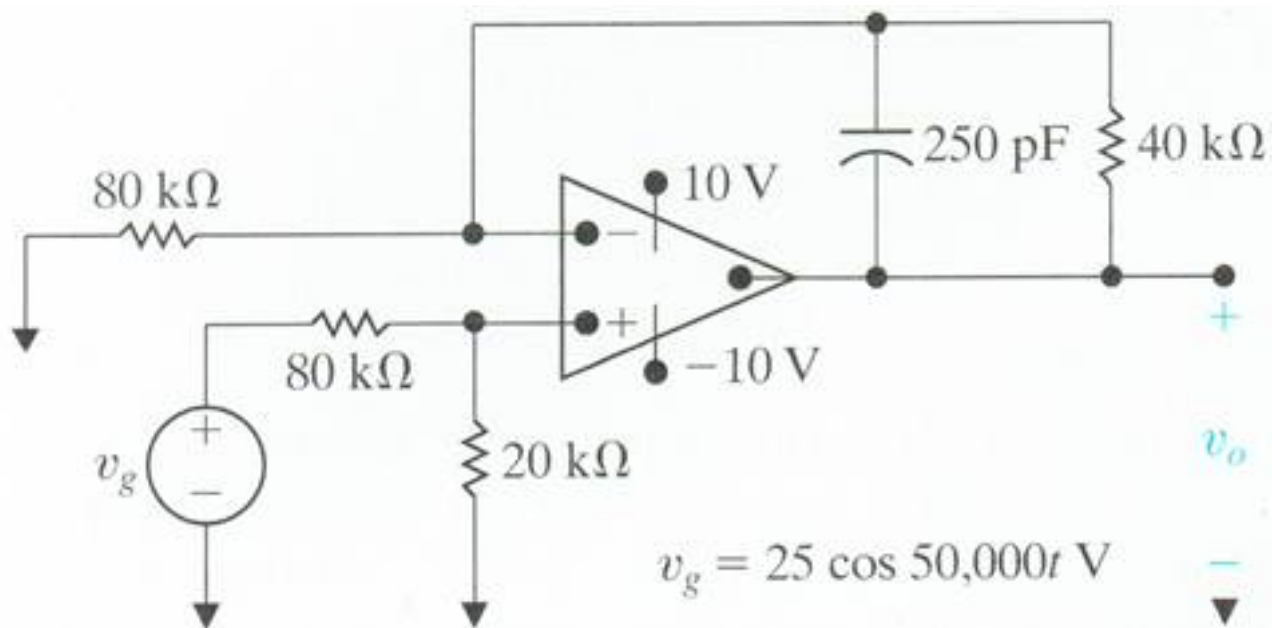

P9.81\_7ed

The operational amplifier is ideal.

Given  $v_g(t) = 25 \cos(50,000 t) \text{ V}$

a) Find the steady-state output  $v_o(t)$ .

$$v_o(t) = 7.07 \cos(50,000 t + -8.13^\circ) \text{ (Degrees)}$$

Volts

b) How large can the amplitude of  $v_g(t)$  be before the amplifier saturates?

$$|v_o(t)_{\max}| \leq 35.3 \text{ Volts (less than or equal to)}$$

**Correct**


Marks for this submission: 10.00/10.00. Accounting for previous tries, this gives **6.67/10.00**.



### Question 8

Correct

Mark 10.00 out of 10.00

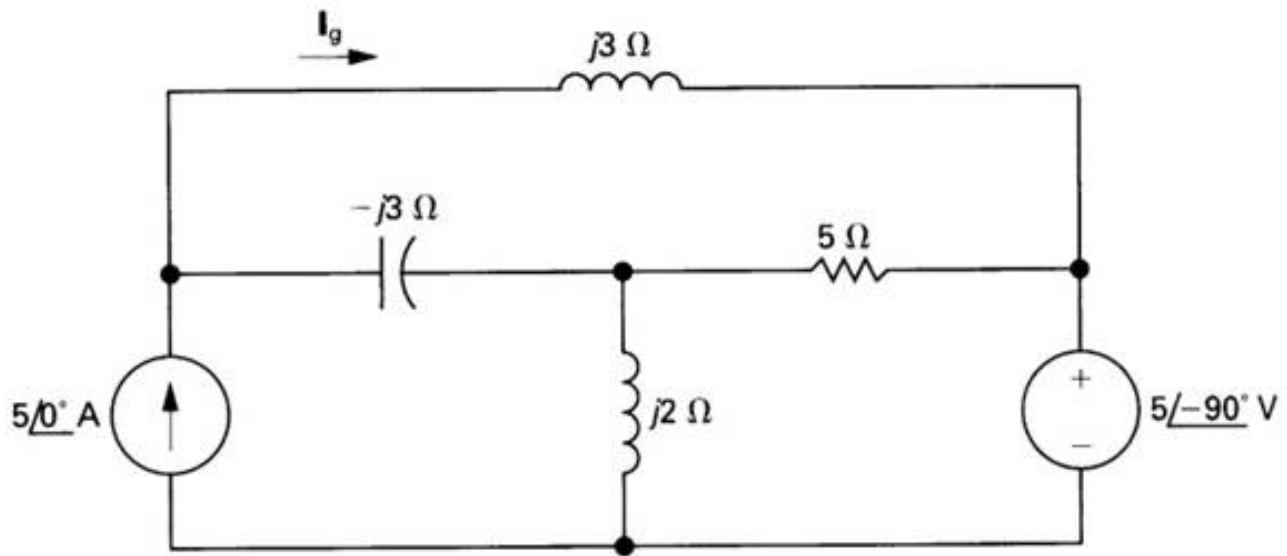

P9.45\_6ed

Use the mesh-current method to find  $I_g$ .

$$I_g = 0 + j -3 \text{ A}$$


**Correct**

Marks for this submission: 10.00/10.00.

### Question 9

Correct

Mark 10.00 out of 10.00

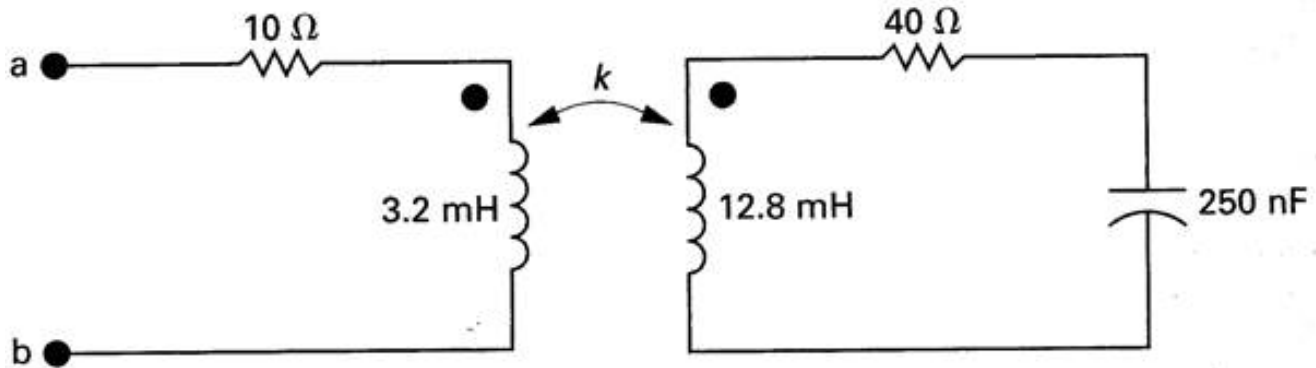

P9.63\_6ed

Given driving source frequency =  $25 \text{ krad/sec}$ .

The coefficient of coupling  $k$  is adjusted so that  $Z_{ab}$  is purely resistive.

Find  $Z_{ab}$  for this condition.

$$Z_{ab} = \boxed{30} \checkmark \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

## Question 10

Correct

Mark 7.50 out of 10.00

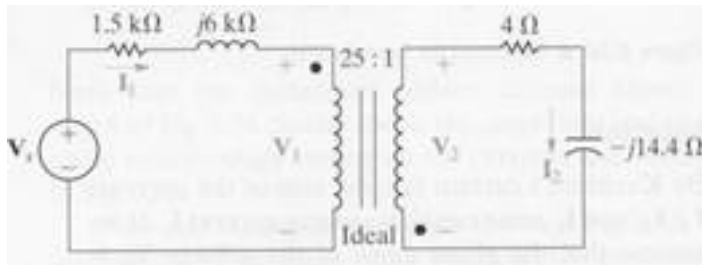

AP9.15\_9ed

The source voltage is  $25 \angle 0^\circ$  kV (kilo Volts).

Find the amplitude and phase angle of  $V_2$  and  $I_2$ .

$|V_2| = 1868$  ✓ Volts      Phase angle  $V_2 = 142$  ✓  $^\circ$

(Degrees)

$|I_2| = 125$  ✓ A      Phase angle  $I_2 = 217$  ✓  $^\circ$  (Degrees)

**Correct**

Marks for this submission: 10.00/10.00. Accounting for previous tries, this gives **7.50/10.00**.

◀ Homework 1 - Chapter 9

Jump to...



Homework 3 - Chapter 10 ▶