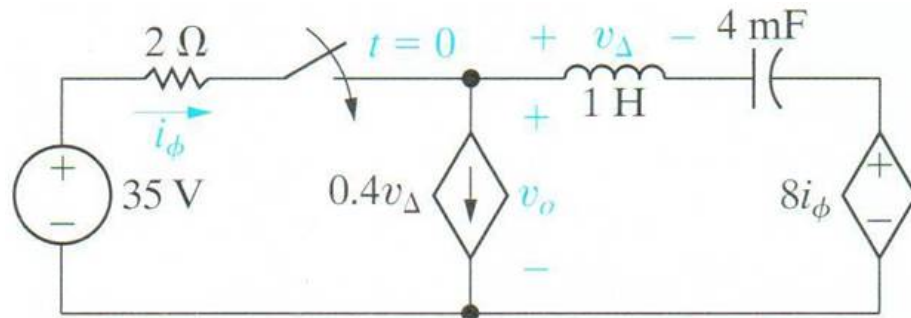


Home ► My courses ► EEE117-2017S-Tatro ► Homework ► Homework 9 - Chapter 13

Started on Sunday, 2 April 2017, 7:55 PM**State** Finished**Completed on** Sunday, 2 April 2017, 11:11 PM**Time taken** 3 hours 15 mins**Grade** 90.57 out of 100.00**Question 1**

Partially correct

Mark 7.00 out of 10.00



P13.13_6ed and P13.15_7ed

Given: No energy is stored in this circuit for $t < 0$.At time $t = 0$, the switch closes (i.e. makes contact).a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V(s) = \boxed{35} \checkmark$$

$$/s + (\text{mag } \boxed{11111} \times \text{Angle } \boxed{167.91} \checkmark) / (s + 1 - j7)$$

$$+ (\text{mag } \boxed{11111} \times \text{Angle } \boxed{11111} \times) / (s + 1 + j7)$$

$$\text{Angle } \boxed{11111} \times) / (s + 1 + j7)$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = \boxed{35} \checkmark$$

$$+ \boxed{5.73} \checkmark \exp(\boxed{-1} \checkmark t) \cos(\boxed{7} \checkmark t + \boxed{168} \checkmark) u(t) \text{ V}$$

$$V_0 = \frac{35}{s} + \frac{2.864 \angle 167.91^\circ}{s+1-j7} + \frac{2.864 \angle [?][?]-167.91^\circ}{s+1+j7}$$

$$v_o(t) = \left[35 + 5.727 e^{-t} \cos(7t + 167.91^\circ) \right] u(t) \text{ Volts}$$


Partially correct

Marks for this submission: 7.00/10.00.

Question 2

Partially correct

Mark 5.00 out of 10.00

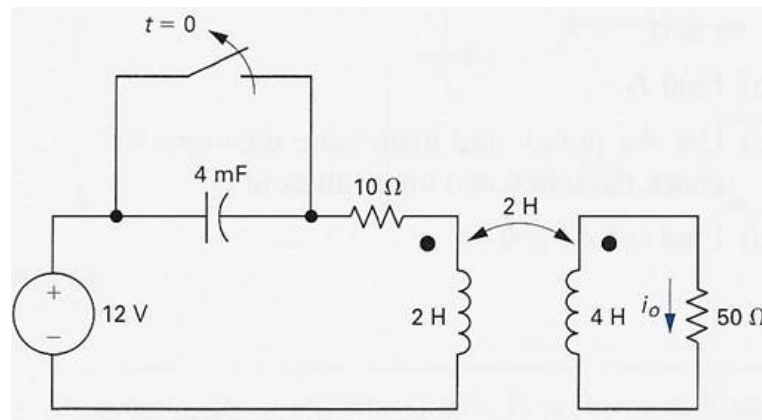

P13.37_6ed

The switch in this circuit has been closed for a long time before opening at $t = 0$.For $t \geq 0$, Find the Laplace form of the voltage $i_0(t)$.

$$i_0(t) = [\text{11111}] \times$$

$$\exp(-25 \checkmark t) + [\text{11111}] \times \exp(-5 \checkmark t) \cos(10 \checkmark t + [\text{111111}] \times \text{°}) u(t)$$

mA (milli A)

$$i_0(t) = \left[-300e^{-25t} + 300\sqrt{5}e^{-5t} \cos(10t + 63.43^\circ) \right] u(t) \text{ m A m p s}$$


Partially correct

Marks for this submission: 5.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

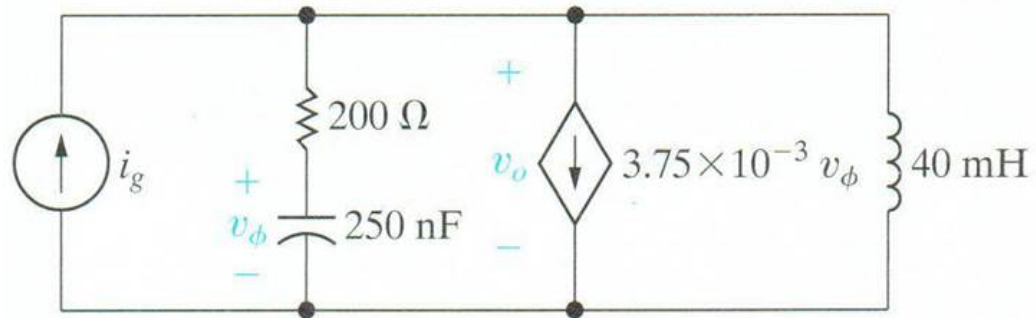

P13.17_7ed

Given: No energy is stored in this circuit for $t < 0$ and $i_g = 5\text{ mA}$ for $t \geq 0$.a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V(s) = (s + 20000)$$

$$) / (s + 10000)^2$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = [10000$$

$$t \exp(-10000 t) + \exp(-10000 t)] u(t) \text{ V}$$

$$V_0(s) = \frac{s + 20,000}{(s + 10,000)^2}$$

$$v_0(t) = [10,000 t e^{-10,000 t} + e^{-10,000 t}] u(t) \text{ Volts}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

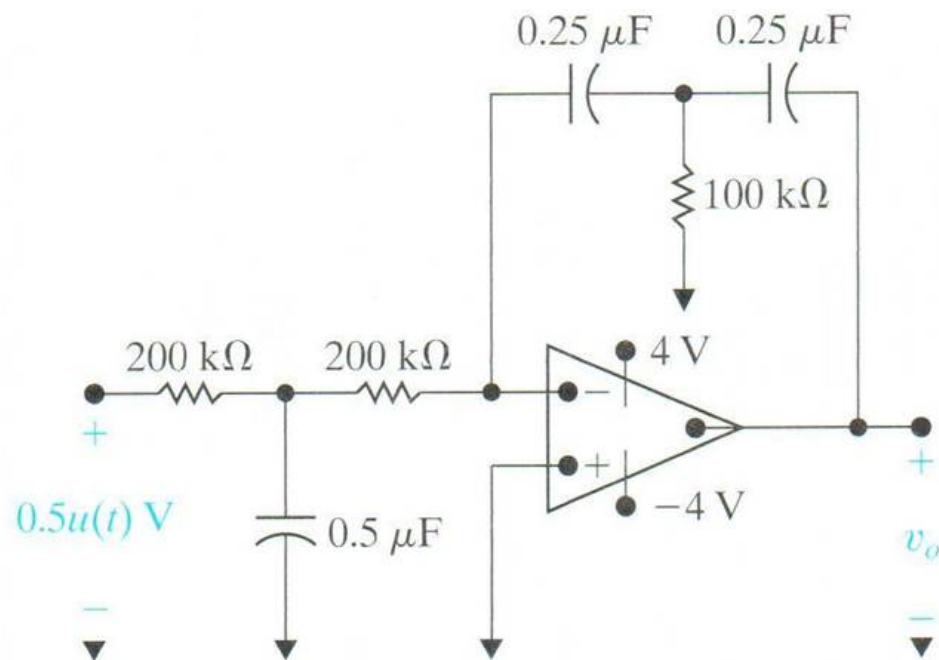

P13.48_7ed

Given: No energy is stored in this circuit for $t < 0$ and you can assume the OpAmp is ideal.a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V_o(s) = \boxed{-200} \checkmark$$

$$/ s^3$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = \boxed{-100} \checkmark$$

$$t^{\boxed{2}} \checkmark u(t) \text{ V}$$

c) Calculate how long in ms (milli sec) until the opamp saturates.

$$t_{\text{saturation}} = \boxed{200} \checkmark$$

ms (milli sec)

$$V_0 = \frac{-200}{s^3}$$

$$v_o(t) = [?][?] - 100t^2 u(t) \text{ Volts}$$


c) $t_{\text{saturation}} = 200 \text{ ms (milli sec)}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

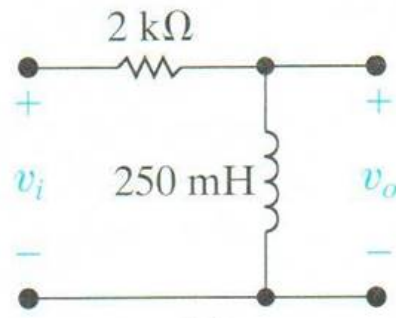

P13.49c_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + 8000)$$

)

$$H(s) = \frac{s}{s + 8,000}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

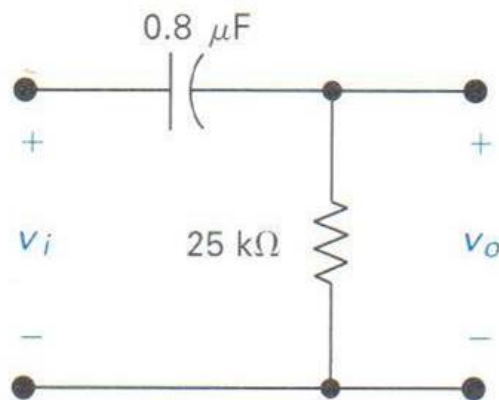

P13.49b_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + 50)$$

)

$$H(s) = \frac{s}{s + 50}$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

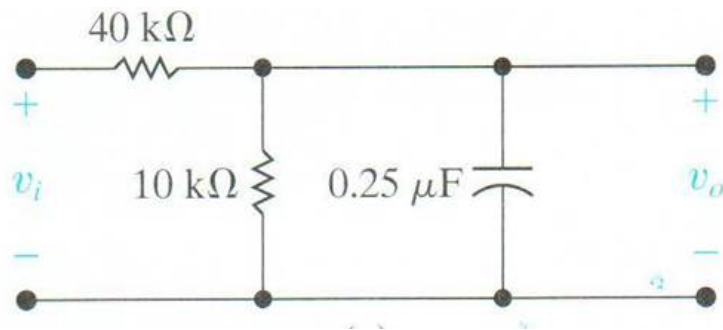

P13.49e_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \frac{100}{s + 500}$$

$$/ (s + 500)$$

$$H(s) = \frac{100}{s + 500}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

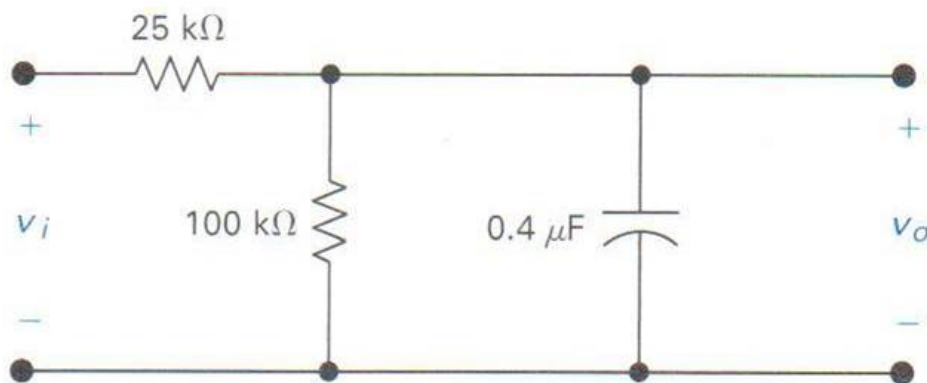

P13.49e_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \frac{100}{s + 125}$$

$$/ (s + 125)$$

$$H(s) = \frac{100}{s + 125}$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Partially correct

Mark 8.57 out of 10.00

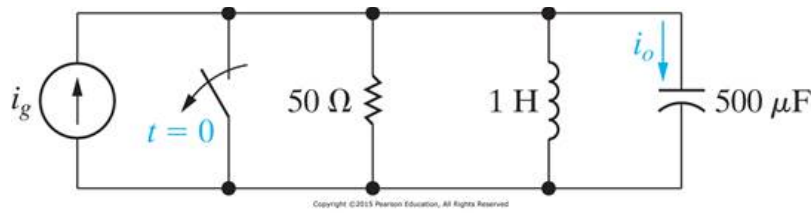

P13.56_10ed

There is no energy stored in this circuit at the time the switch is opened. The sinusoidal current source is generating the signal $25 \cos(200t)$ mA (milli Amp). The desired response signal is the current $i_o(t)$.

a) Find the s domain transfer function $H(s) = I_o/I_g$ for this circuit.

$$H(s) = s^2 / (s^2 + \boxed{40} \checkmark)$$

$$s + \boxed{2000} \checkmark)$$

b) Find the s domain form for $I_o(s)$.

$$I_o(s) = \boxed{.025} \checkmark$$

s^3 / (There are four factors in the denominator – list each one separately)

$$\text{Factor 1: } s + 20 - j \boxed{40} \checkmark$$

$$\text{Factor 2: } s + 20 + j \boxed{40} \checkmark$$

$$\text{Factor 3: } s + 0 - j \boxed{200} \checkmark$$

$$\text{Factor 4: } s + 0 + j \boxed{200} \checkmark$$

c) Find the time domain form $i_o(t)$.

$$i_o(t) = \boxed{111111} \times$$

$$\exp(\boxed{-20} \checkmark t) \cos(\boxed{40} \checkmark t + \boxed{-97.94} \checkmark ^\circ) + \boxed{111111} \times \cos(\boxed{200} \checkmark t + \boxed{11.89} \checkmark ^\circ) u(t) \text{ mA (milli A)}$$

$$H(s) = \frac{I_o}{I_g} = \frac{s^2}{s^2 + 40s + 2,000}$$

$$I_o = \frac{0.025s^3}{(s+20-j40)(s+20+j40)(s+0-j200)(s+0+j200)}$$

$$i_o(t) = [1.4395e^{-20t} \cos(40t - 97.94^\circ) + 25.7514 \cos(200t + 11.89^\circ)] u(t) \text{ mA}$$


Partially correct

Marks for this submission: 8.57/10.00. Accounting for previous tries, this gives **8.57/10.00**.

Question 10

Correct

Mark 10.00 out of 10.00

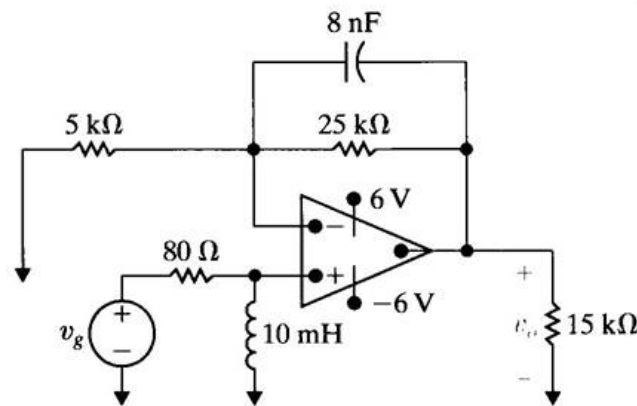

P13.78_7ed and P13.77_10ed

You may assume the opamp is ideal.

a) Find the s domain transfer function $H(s) = V_o/V_g$ for this circuit.

$$H(s) = s * (s + 30000)$$

$$/ [(s + 5,000) * (s + 8000)]$$

b) Find the time domain $v_o(t)$ if $v_g(t) = 600 u(t)$ mV (milli V).

$$v_o(t) = [5$$

$$e^{-5,000t} + -4.4 \exp(-8000 t)] u(t) \text{ V}$$

c) Find the steady-state express for $v_o(t)$ if $v_g(t) = 2 \cos(10,000 t)$ V.

$$v_o(t)_{\text{steady-state}} = [4.42$$

$$\cos(10000 + -6.34^\circ) u(t) \text{ V}$$

$$H(s) = \frac{s(s+30,000)}{(s+5,000)(s+8,000)}$$

$$v_o(t) = [5e^{-5,000t} - 4.4e^{-8,000t}] u(t) \text{ Volts}$$

$$v_o(t)_{\text{steady-state}} = 4.4172 \cos(10,000t - 6.34^\circ) u(t) \text{ Volts}$$

Correct

Marks for this submission: 10.00/10.00.