

**Started on** Thursday, 27 October 2016, 12:48 PM

**State** Finished

**Completed on** Thursday, 27 October 2016, 12:49 PM


**Time taken** 13 secs

**Grade** 88.0 out of 100.0

**Question 1**

Not answered

Mark 0.0 out of 5.0

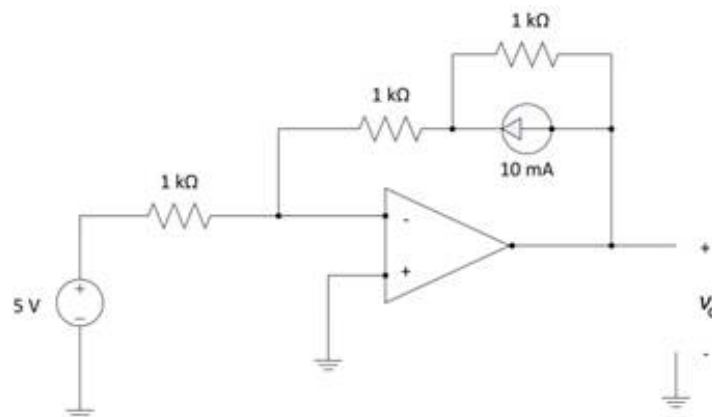

AS5.1

Find  $v_o$ .

$v_o =$    $\times V$


**Numeric Answer**

$v_o = -20 V$

**Question 2**

Correct

Mark 5.0 out of 5.0

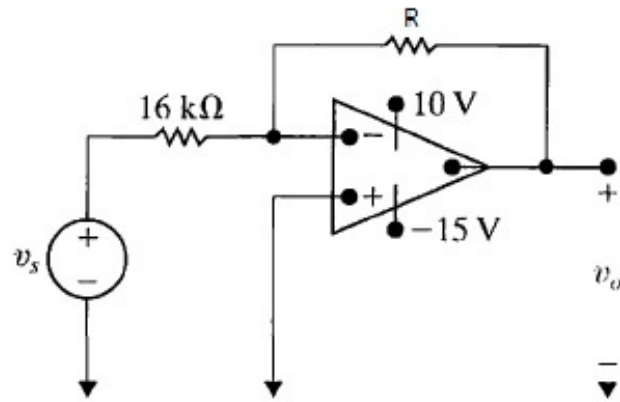

AP5.02\_9ed


The source voltage  $v_s$  in this circuit is  $-640\text{ mV}$ .What range of  $R$  allows the inverting amplifier to operate in its linear region? ✓  $\text{k}\Omega < R <$   ✓  $\text{k}\Omega$  (kilo Ohms)**Numeric Answer** $0\ \Omega \leq R \leq 250\text{ k}\Omega$ **Correct**

Marks for this submission: 5.0/5.0.

**Question 3**

Correct

Mark 5.0 out of 5.0

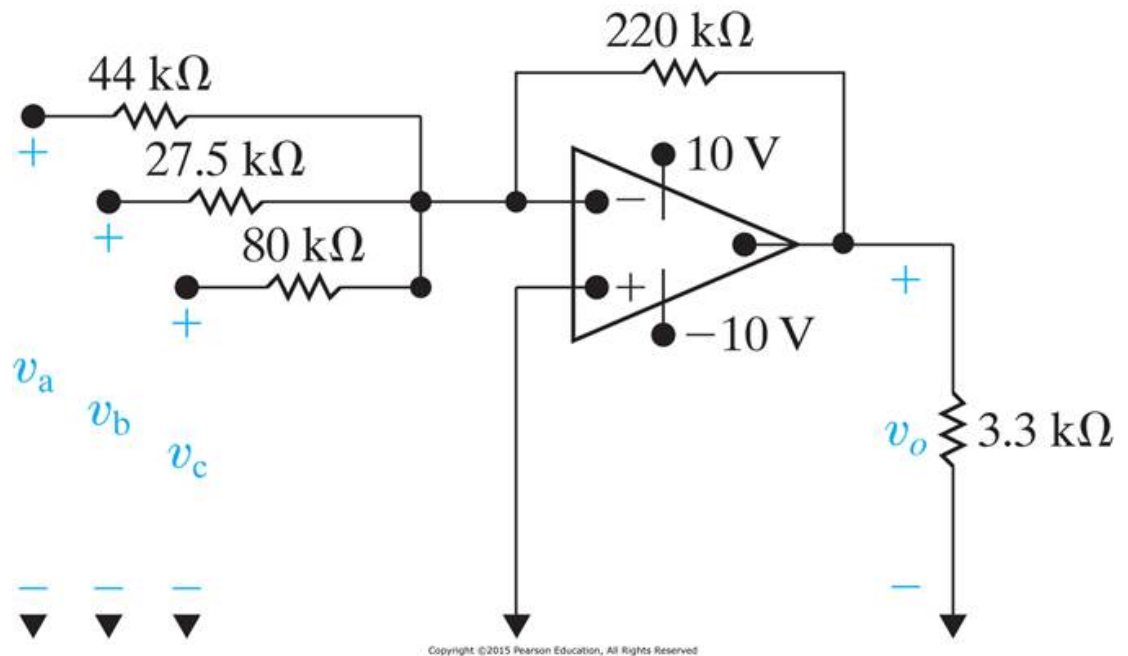

P5.12\_10ed

Assume the op amp is ideal.


Find  $v_o$  if  $v_a = 1\text{ V}$ ,  $v_b = 1.5\text{ V}$ ,  $v_c = -4\text{ V}$ . $v_o =$    $\checkmark\text{ V}$ **Numeric Answer** $v_o = -6\text{ V}$ **Correct**

Marks for this submission: 5.0/5.0.

**Question 4**

Correct

Mark 5.0 out of 5.0

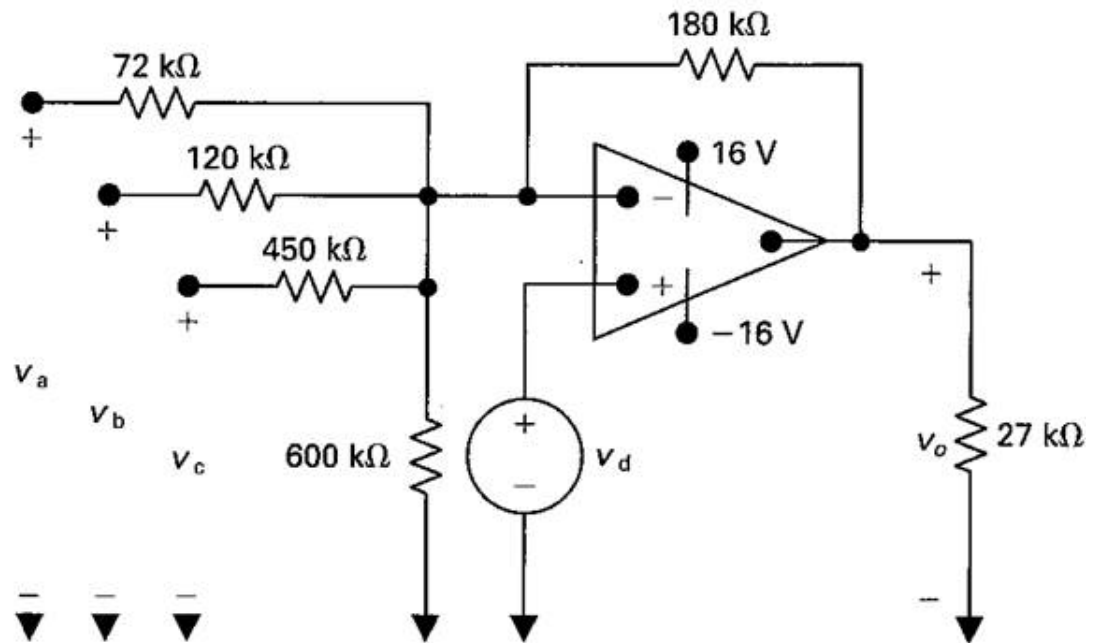

P5.10\_6ed

Assume the op amp is ideal.

Given:

$$V_a = 18\text{V} \quad V_b = 6\text{V} \quad V_c = -15\text{V} \quad V_d = 8\text{V}$$

Find  $V_o$ .

$$V_o = -2.4 \text{ V}$$

**Numeric Answer**

$$V_o = -2.4 \text{ V}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 5**

Correct

Mark 5.0 out of 5.0

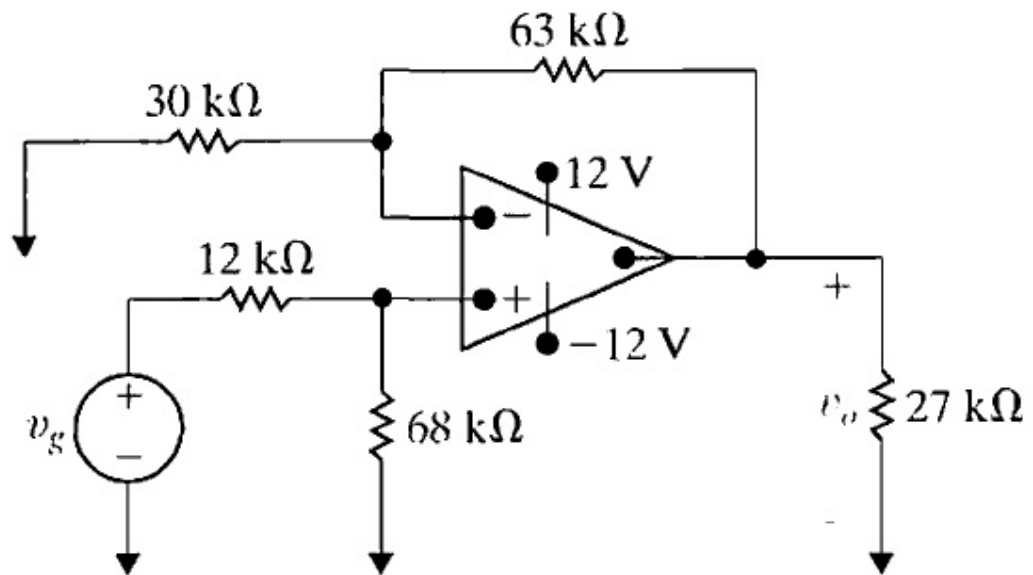

P5.18\_9ed

Specify the range of values of  $v_g$  so that the op amp operates in a linear mode

$$\boxed{-4.55} \checkmark \leq v_g \leq \boxed{4.55} \checkmark \text{ V}$$

**Numeric Answer**

$$-4.554 \leq v_g \leq 4.554 \text{ V}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 6**

Correct

Mark 5.0 out of 5.0

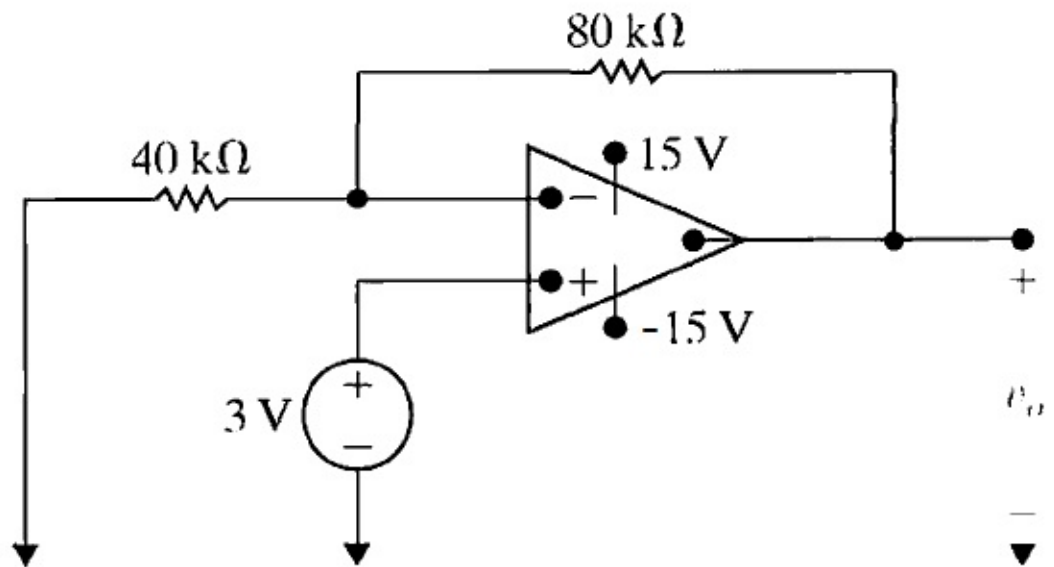

P5.16\_9ed

Calculate  $v_o$  for this circuit.

$$v_o = 9 \text{ V}$$

**Numeric Answer**

$$v_o = 9 \text{ V}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 7**

Correct

Mark 5.0 out of 5.0

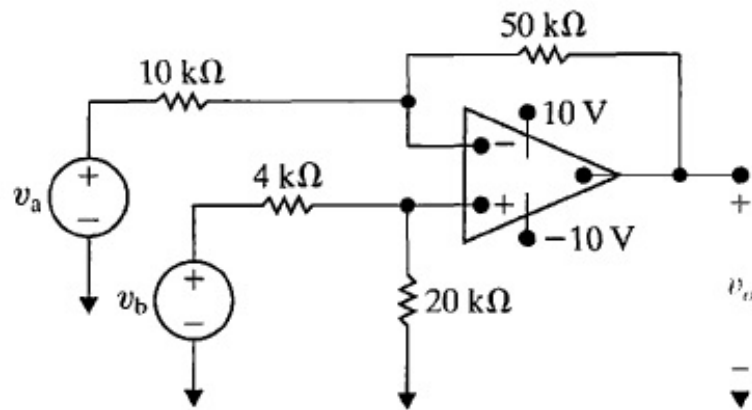

AP5.05\_9ed

In the difference amplifier shown,  $v_b = 4.0\text{ V}$ .

What range of values for  $v_a$  will result in linear operation?

$$2 \leq v_a \leq 6 \text{ V}$$

**Numeric Answer**

$$2\text{ V} \leq v_a \leq 6\text{ V}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 8**

Correct

Mark 5.0 out of 5.0

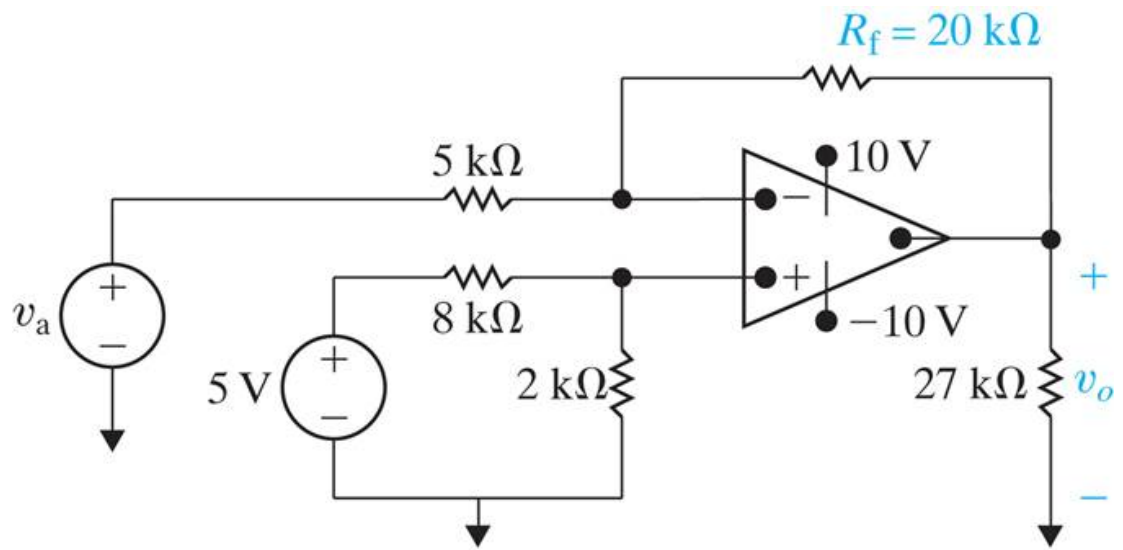

P5.26\_10ed

Given:  $v_a = 2\text{V}$ Find  $v_o$ .

$$v_o = \boxed{-3} \text{ V}$$

**Numeric Answer**

$$v_o = -3\text{V}$$

**Correct**

Marks for this submission: 5.0/5.0.



**Question 9**

Correct

Mark 5.0 out of 5.0

P6.08\_9ed

The current in a 25 mH (milli Henry) inductor is known to be -10A for  $t \leq 0^-$  and  $-(10 \cos 400t + 5 \sin 400t) e^{-200t}$  A for  $t \geq 0^+$ .

At what instant of time is the voltage across the inductor maximum?

$t_{\max} =$    msec (milli second)

What is the maximum voltage?

$V_{\max} =$    V

**Numeric Answer**

$$t_{\max} = 2.77 \text{ ms}$$

$$v_{\max} = 64.27 \text{ V}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 10**

Incorrect

Mark 0.0 out of 5.0

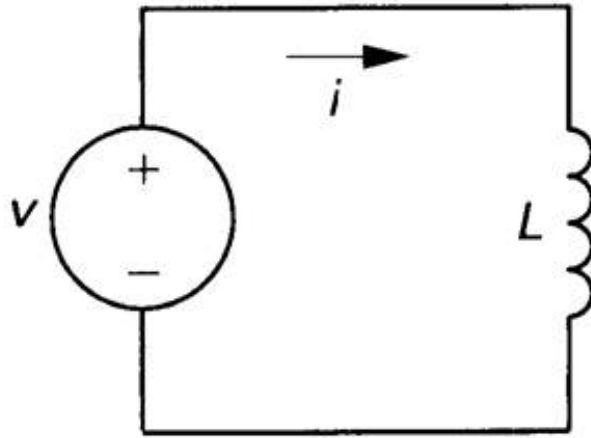

P6.10\_6ed


Given:  $v = 250 \sin(1,000 t)$  Volts for  $t \geq 0$  $L = 50 \text{ mH (milli H)}$        $i(t = 0^-) = -5 \text{ A}$ Find the current  $i(t)$  at  $t = 1 \text{ sec}$ . $i(t = 1 \text{ s}) =$    $\times \text{ A}$ **Numeric Answer** $i(t = 1 \text{ sec}) = -2.812 \text{ A}$ **Incorrect**

Marks for this submission: 0.0/5.0.

**Question 11**

Correct

Mark 5.0 out of 5.0

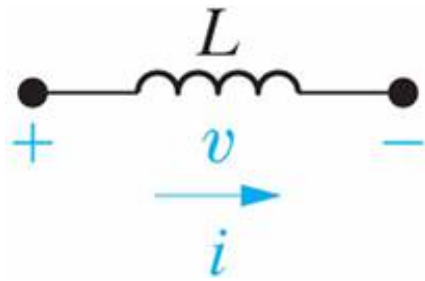

CQ6.08

Given:

 $L = 83 \text{ mH}$  (milli Henry)

The inductor has a constant voltage of 28 V across it for a short while.

What is the change in current per milli sec during this period?

 $di/dt = ?? \text{ Amps/ms}$ Answer: **Calculated Question**

The correct answer is: 0.337

**Correct**

Marks for this submission: 5.0/5.0.

**Question 12**

Partially correct

Mark 3.0 out of 5.0

P6.17\_6ed

The voltage across the terminals of a  $0.40 \mu\text{F}$  (micro F) capacitor is:

$$V_C(t) = 25 \text{ V for } t \leq 0;$$

$$V_C(t) = A_1 t e^{-1,500t} + A_2 e^{-1,500t} \text{ V for } t \geq 0.$$

The initial current in the capacitor is 90 mA (milli Amp).

Assume the passive sign convention (current is in the direction of voltage drop).

a) What is the initial energy stored in the capacitor?

$$w(t = 0) = \boxed{125} \checkmark \text{ mJ (micro J)}$$

b) Find the coefficients  $A_1$  and  $A_2$ .

$$A_1 = \boxed{262500} \checkmark \text{ Volts/Sec}$$

$$A_2 = \boxed{25} \checkmark \text{ Volts/Sec}$$

c) Find the capacitor current at  $t = 0.4 \text{ ms}$  (milli sec).

$$i(t = 0.4 \text{ ms}) = \boxed{-12.62} \times \text{ mA (milli Amp)}$$

d) Find the capacitor current at  $t = 2 \text{ ms}$  (milli sec).

$$i(t = 2 \text{ ms}) = \boxed{-13.69} \times \text{ mA (milli Amp)}$$

**Numeric Answer**

a)  $w(t=0) = 125 \text{ mJ (micro J)}$

b)  $A_1 = 262,500 \text{ Volts/Sec}$        $A_2 = 25 \text{ Volts/sec}$

c)  $i(t = 0.4 \text{ ms}) = 14.818 \text{ mA}$

d)  $i(t = 2 \text{ ms}) = -11.202 \text{ mA}$


**Partially correct**

Marks for this submission: 3.0/5.0.

**Question 13**

Correct

Mark 5.0 out of 5.0

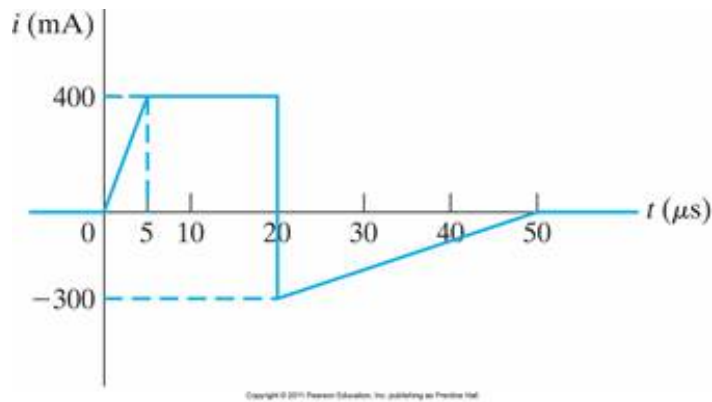

P6.14\_9ed

The current shown in the figure is applied to a  $0.25 \mu F$  (micro F) capacitor.

The initial voltage across the capacitor is zero.

Find the charge on the capacitor at  $t = 15 \mu s$  (micro sec).

$$Q_{15ms} = 5 \mu C \text{ (micro C)}$$

Find the voltage across the capacitor at  $t = 15 \mu s$  (micro sec).

$$V_{15ms} = 20 V$$

**Numeric Answer**

$$Q_{15ms} = 5 \mu C \text{ (micro Coulombs)}$$

$$V_{15ms} = 20 \text{ Volts}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 14**

Correct

Mark 5.0 out of 5.0

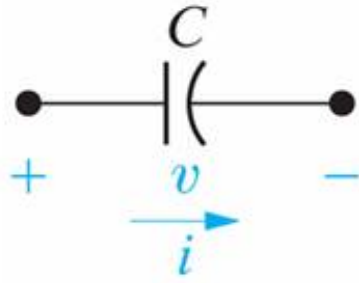

CQ6.11

Given:

 $C = 37 \mu\text{F}$  (micro Farad)

The capacitor has a constant current 88.5 Amps “through” it for a short while.

What is the change in voltage per  $\mu\text{s}$  (micro sec) during this period? $dv/dt = ?? \text{ Volts}/\mu\text{s}$  (Volts per micro sec)Answer: **Calculated Question**

The correct answer is: 2.392


**Correct**

Marks for this submission: 5.0/5.0.

**Question 15**

Correct

Mark 5.0 out of 5.0

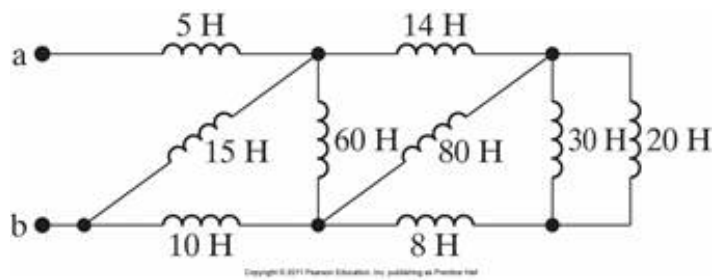

P6.20\_9ed

Find the equivalent inductance with respect to the terminals a,b.

$$L_{\text{Eq}} = 15 \text{ H}$$

**Numeric Answer**

$$L_{\text{Eq}} = 15 \text{ H}$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 16**

Correct

Mark 5.0 out of 5.0

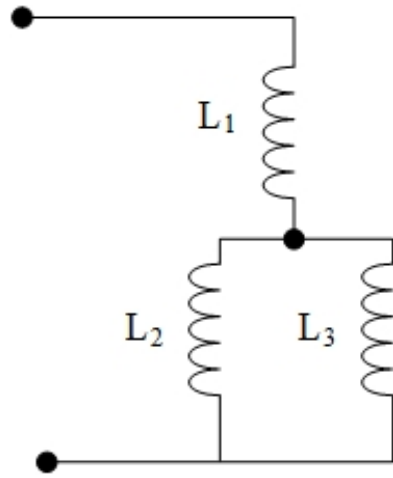

CQ6.06

Given:

 $L_1 = 1.3 \text{ mH (milli Henry)}$      $L_2 = 7.2 \text{ mH (milli Henry)}$  $L_3 = 3.1 \text{ mH (milli Henry)}$ Find the equivalent inductance  $L_{\text{Eq}}$ . $L_{\text{Eq}} = ?? \text{ mH (milli Henry)}$ 

Answer: 3.47

**Calculated Question**

The correct answer is: 3.467

**Correct**


Marks for this submission: 5.0/5.0.



**Question 17**

Correct

Mark 5.0 out of 5.0

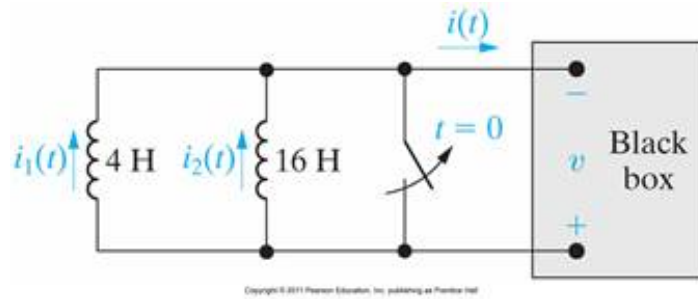

P6.25\_9ed

Given: The voltage  $v$  (across all the parallel elements) is  $64 e^{-4t}$  Volts for  $t > 0$ .  
And at  $t = 0^-$   $i_1 = -10\text{A}$  and  $i_2 = 5\text{A}$

a) Find the equivalent inductance of the two inductors in the figure.

$$L_{\text{Eq}} = \boxed{3.2} \checkmark \text{ H}$$

b) Find  $i(t)$  at  $t = 1\text{sec}$ .

$$i(t = 1\text{s}) = \boxed{-91.58} \checkmark \text{ mA (milli Amp)}$$

**Numeric Answer**

a)  $L_{\text{Eq}} = 3.2 \text{ H}$

b)  $i(t = 1\text{s}) = -92 \text{ mA}$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 18**

Correct

Mark 5.0 out of 5.0

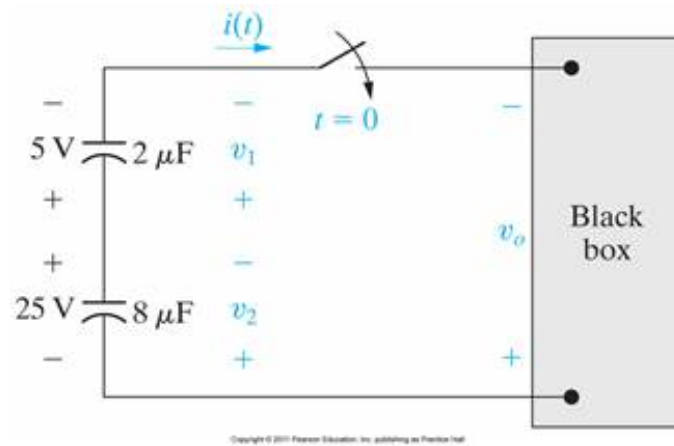

P6.31\_9ed

The current  $i(t)$  is given as  $800 e^{-25t}$   $\mu\text{A}$  (micro Amp) for  $t > 0$  with the initial voltages across the capacitors shown in the figure.

Find the equivalent capacitor of the two capacitors in the figure.

$$C_{\text{Eq}} = \boxed{1.6} \checkmark \mu\text{F (micro F)}$$

Find  $v_o(t)$  for  $t = 1\text{ms}$  (milli sec).

$$v_o(t = 1\text{ms}) = \boxed{-19.5} \checkmark \text{ V}$$

**Numeric Answer**

$$C_{\text{Eq}} = 1.6 \mu\text{F}$$

$$v_o(t = 1\text{ms}) = -19.51\text{V}$$

**Correct**

Marks for this submission: 5.0/5.0.

Correct

Find the equivalent capacitance with respect to the terminals a,b.

Find the initial voltage across the equivalent capacitance.

### Numeric Answer

$$C_{Eq} = 6 \mu F \text{ (micro Farad)}$$

$$V_{Ceq} = -3V$$


**Correct**

Marks for this submission: 5.0/5.0.

**Question 20**

Correct

Mark 5.0 out of 5.0

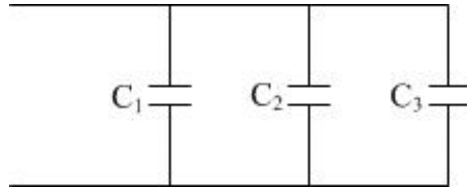

Given:

$$C_1 = 2.3 \mu\text{F (micro F)} \quad C_2 = 6.4 \mu\text{F (micro F)} \quad C_3 = 6.8 \mu\text{F (micro F)}$$

Find the equivalent capacitance  $C_{\text{Eq}}$ .

$$C_{\text{Eq}} = ?? \mu\text{F (micro F)}$$

Answer: 15.5

**Calculated Question**

The correct answer is: 15.500

**Correct**

Marks for this submission: 5.0/5.0.