

Started on Sunday, 20 November 2016, 7:12 PM

State Finished

Completed on Sunday, 20 November 2016, 8:53 PM


Time taken 1 hour 40 mins

Grade 98.75 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

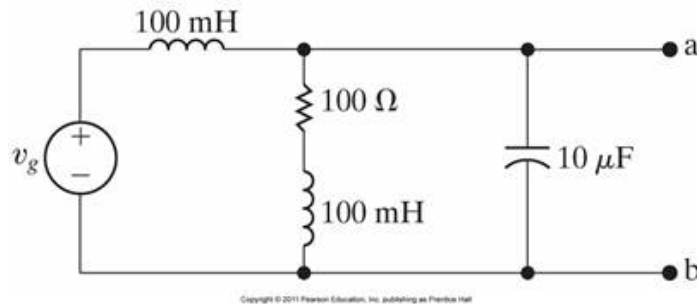

P9.44_9ed

The sinusoidal voltage source in the circuit is developing a voltage equal to $247.49 \cos(1,000 t + 45^\circ) \text{ V}$.

a) Find the Thévenin voltage with respect to the terminals a,b.

$|V_{\text{Th}}| =$ $\checkmark \text{ V}$

Angle = \checkmark° (Degrees)

b) Find the Thévenin impedance with respect to the terminals a,b.

Express your answer in polar form.

$|Z_{\text{ab}}| =$ $\checkmark \Omega$ (Ohm)

Angle = \checkmark° (Degrees)

Numeric Answer

$V_{\text{Th}} = 350$ at angle 0° Volts


$Z_{\text{ab}} = 100 + j 100 \Omega$ (Ohm) = 141.42 at angle $45^\circ \Omega$ (Ohm)

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

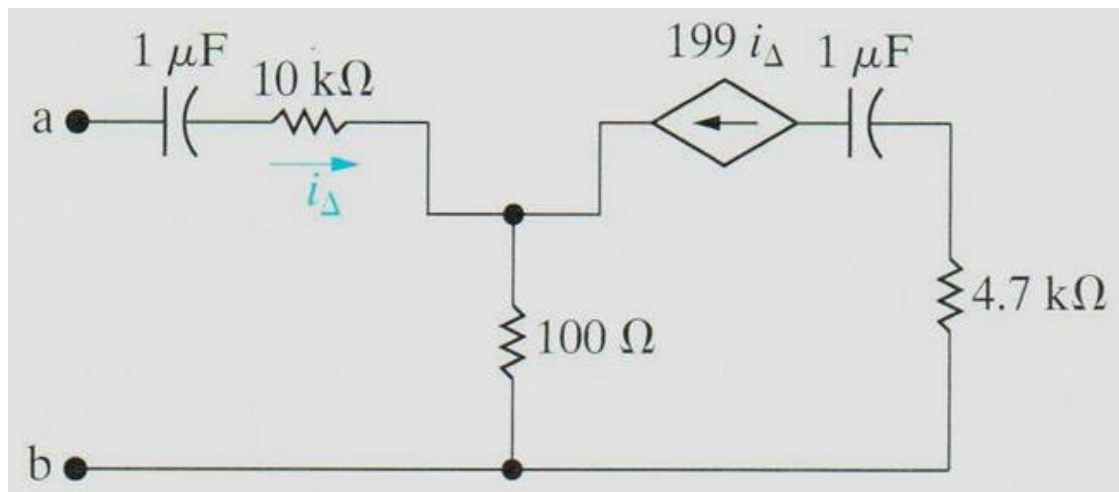Mark 10.00 out of
10.00

P9.46_7ed

The frequency of operation is 400 rad/sec.

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

$$Z_{Th} = 30000 \checkmark + j -2500 \checkmark \Omega \text{ (Ohm)}$$

Numeric Answer


$$Z_{Th} = 30,000 - j 2,500 \Omega \text{ (Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

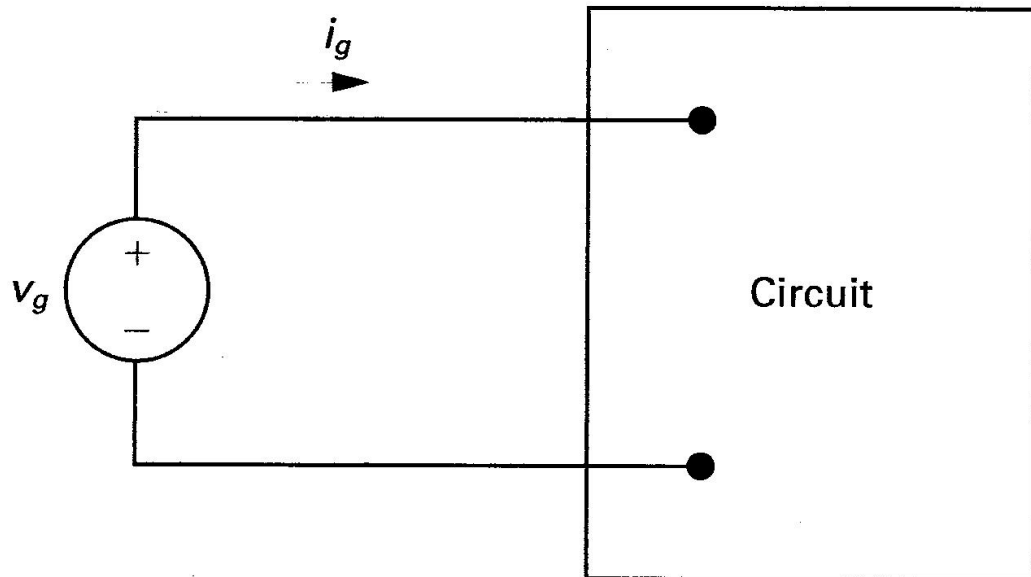Mark 10.00 out of
10.00

P9.29_6ed

Given:

$$v_g = 150 \cos(8,000 \pi t + 20^\circ) \text{ V}$$

$$i_g = 30 \sin(8,000 \pi t + 38^\circ) \text{ A}$$

a) What is the impedance seen by the source?

$$Z_{\text{circuit}} = \text{Mag } \boxed{5} \checkmark \text{ with Angle } \boxed{72} \checkmark^\circ \text{ (Degrees) } \Omega \text{ (Ohm)}$$

b) By how many microseconds is the current out of phase with the voltage?

$$t_{\text{phase}} = \boxed{50} \checkmark \mu\text{s (micro sec)}$$

Numeric Answer

a) $Z_{\text{circuit}} = 5 \text{ at angle } 72^\circ \Omega \text{ (Ohm)}$


b) $t_{\text{phase}} = 50 \mu\text{s (micro sec)}$

Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

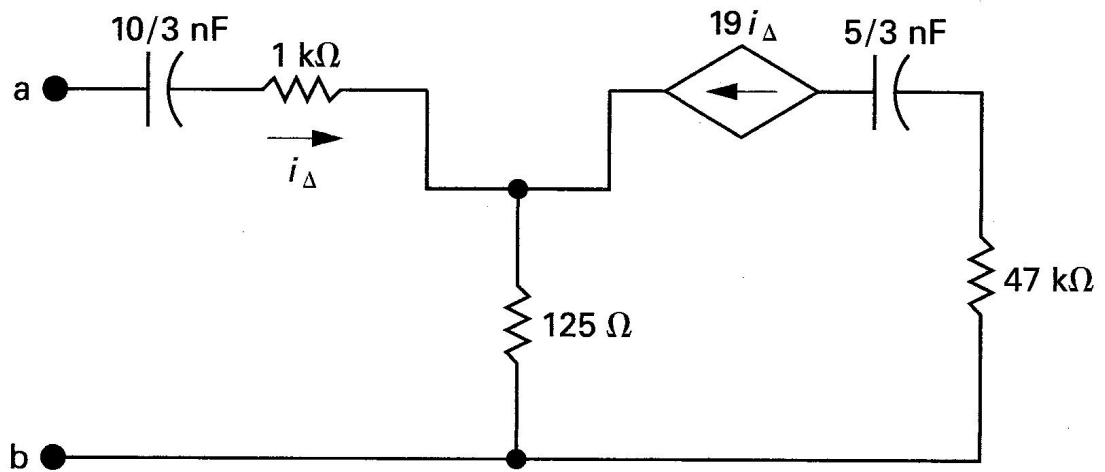Mark 10.00 out of
10.00

P9.36_6ed

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

The frequency of operation is 25 krad/sec (kilo rad/sec).


 $Z_{Th} =$ ✓ $+ j$ ✓ Ω (Ohm) in rectangular form**Numeric Answer** $Z_{Th} = 3,500 - j 12,000 \Omega$ (Ohm)**Correct**

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

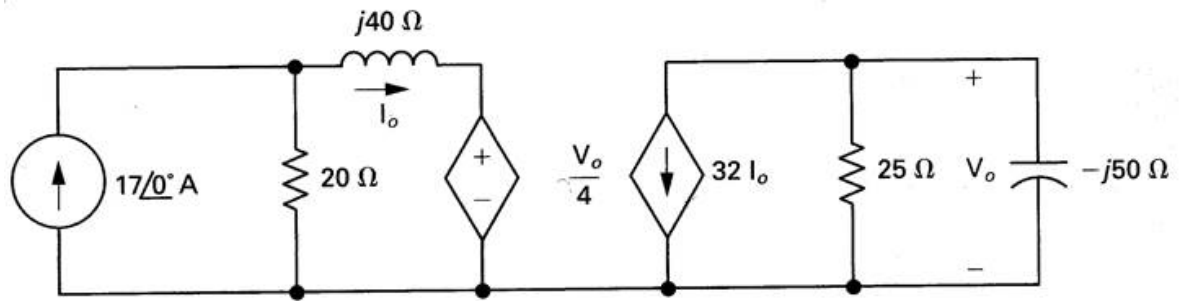

P9.56_6ed

Use the node-voltage method to find the follow phasor values.

$$\mathbf{V}_0 = 1280 + j 320 \text{ Volts}$$

$$\mathbf{I}_0 = -1.4 - j 1.2 \text{ Amps}$$

Numeric answer

$$\mathbf{V}_0 = 1,280 + j 320 \text{ V} = 1319.394 \text{ at angle } 14.04^\circ \text{ V}$$

$$\mathbf{I}_0 = -1.40 - j 1.20 \text{ A} = 1.844 \text{ at angle } -139.40^\circ \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

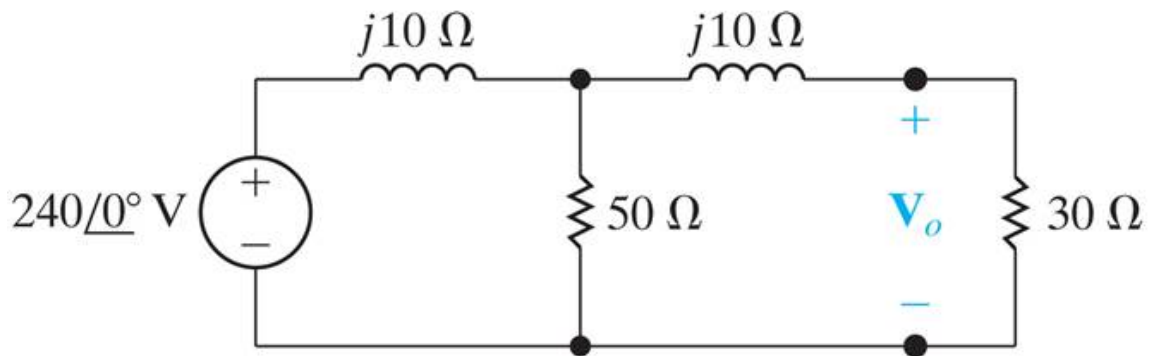

Copyright ©2015 Pearson Education, All Rights Reserved

P9.54_10ed

Use the node-voltage method to find \mathbf{V}_0 .

$$\mathbf{V}_0 = \text{Magnitude } 188.43 \text{ with Angle } -42.88^\circ \text{ (Degrees) Volts}$$

Numeric answer


$$\mathbf{V}_0 = 188.432 \text{ at angle } -42.88^\circ \text{ Volts}$$

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

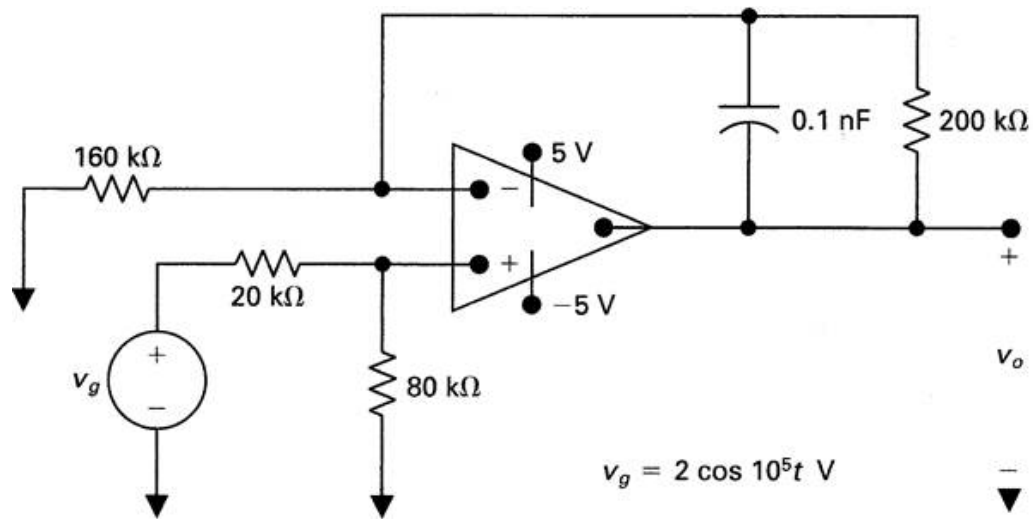Mark 10.00 out of
10.00

P9.72_6ed

The operational amplifier is ideal.

Given $v_g(t) = 2 \cos(100,000 t)$ Va) Find the steady-state output $v_o(t)$.

$$v_o(t) = 2.152 \checkmark \cos(100,000 t + -22.08 \checkmark^\circ) \text{ Volts}$$

b) How large can the amplitude of $v_g(t)$ be before the amplifier saturates?


$$|v_o(t)_{\max}| \leq 4.646 \checkmark \text{ Volts (less than or equal to)}$$

Numeric answera) $v_o(t) = 2.154 \cos(100,000 t - 21.80^\circ)$ Voltsb) $|v_o(t)_{\max}| \leq 4.634$ Volts**Correct**

Marks for this submission: 10.00/10.00.

Question 8

Correct

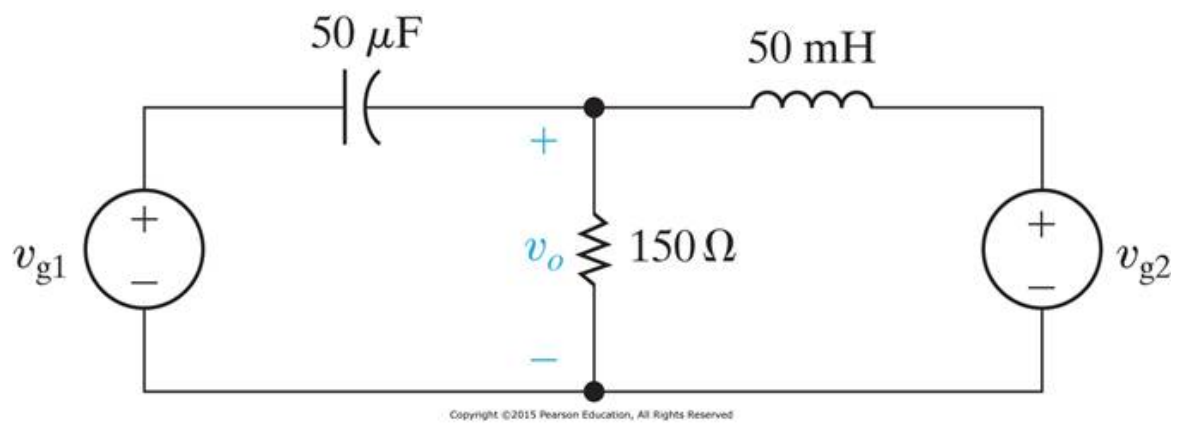Mark 10.00 out of
10.00

P9.61_10ed

Given: $v_{g1} = 25 \sin(400t + 143.12^\circ)$ V and $v_{g2} = 18.03 \cos(400t + 33.69^\circ)$ VUse the mesh-current method to find the steady-state voltage of $v_o(t)$.

$$v_o(t) = \boxed{15} \checkmark \cos(400t + \boxed{0} \checkmark^\circ) \text{ (Degrees) V}$$

Numeric answer


$$v_o(t) = 15 \cos(400t + 0^\circ) \text{ V}$$

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

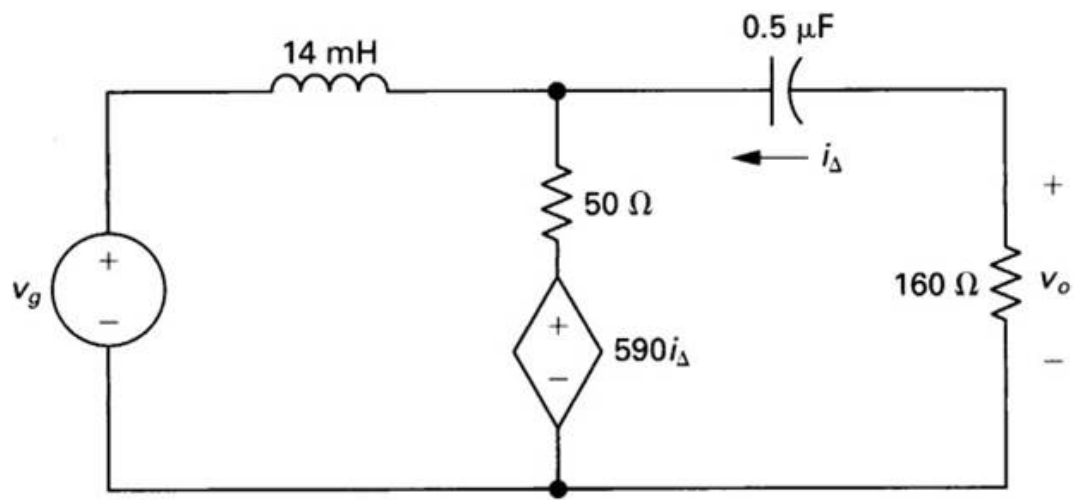Mark 10.00 out of
10.00

P9.48_6ed

Given: $v_g = 72 \cos(5,000t)$ VFind the steady-state expression for $v_o(t)$ in this circuit.

$$v_o(t) = \boxed{11.31} \checkmark \cos(5,000 t + \boxed{-45} \checkmark^\circ) \text{ (Degrees) V}$$

Numeric answer

$$v_o(t) = 11.314 \cos(5,000t - 45^\circ) \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Partially correct

Mark 8.75 out of 10.00

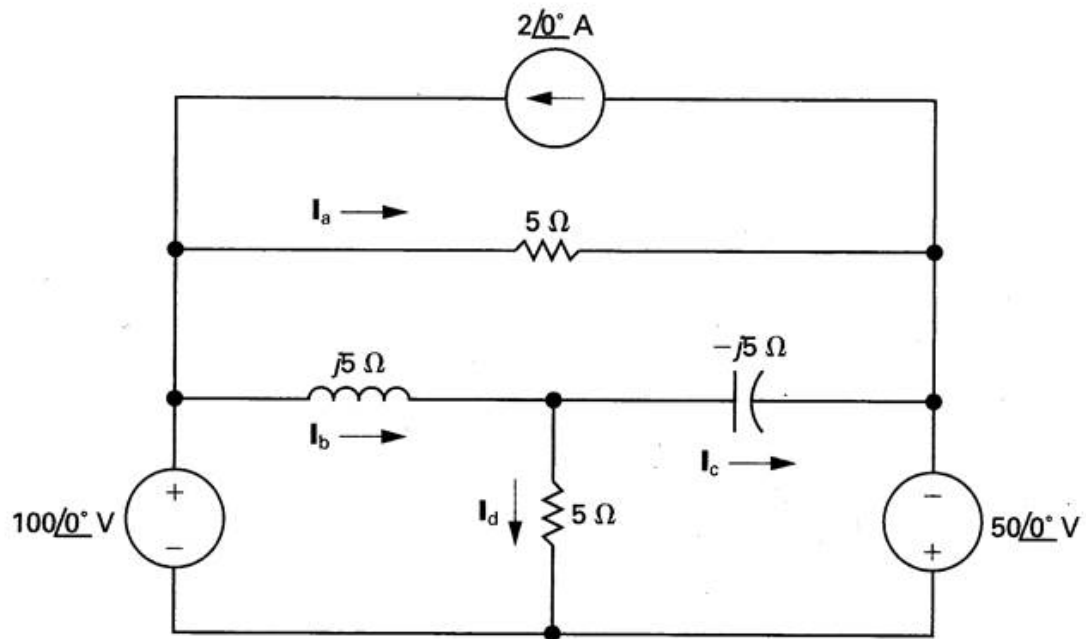

P9.52_6ed

Use the Mesh method and find the following currents:

 I_a = Magnitude ✓ with Angle ✓° (Degrees) Amps I_b = Magnitude ✓ with Angle ✓° (Degrees) Amps I_c = Magnitude ✓ with Angle ✓° (Degrees) Amps I_d = Magnitude ✗ with Angle ✓° (Degrees) Amps**Numeric Answer** I_a = 30 at angle 0° A I_b = 36.056 at angle -33.69° A I_c = 31.623 at angle 18.43° A I_d = 30 at angle -90° A**Partially correct**

Marks for this submission: 8.75/10.00.