

Started on Wednesday, 2 November 2016, 11:55 AM

State Finished

Completed on Wednesday, 2 November 2016, 12:55 PM


Time taken 1 hour

Grade 82.50 out of 100.00

Question 1

Partially correct

Mark 7.50 out of 15.00

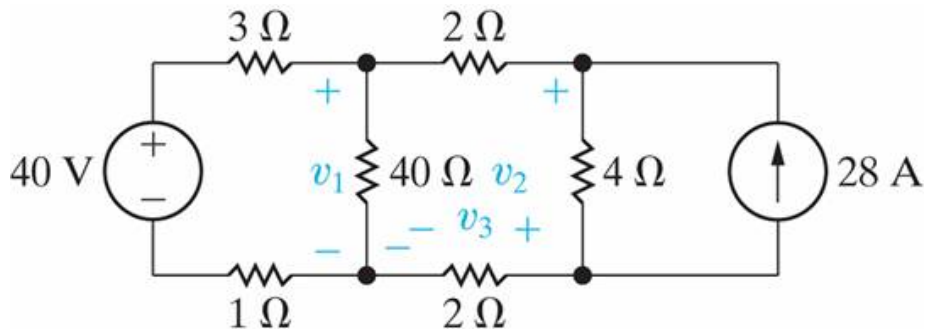

Q1e

a) Find the voltage v_1 .

$v_1 =$ Volts

b) Find the voltage across the 28A current source.

$V_{28A} =$ Volts

Numeric Answer

$v_1 = 60V$

$V_{28A} = 86V$


Partially correct

Marks for this submission: 7.50/15.00.

Question 2

Correct

Mark 15.00 out of 15.00

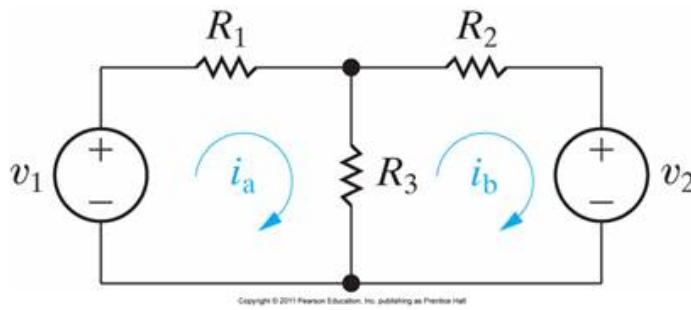

Q2c

Given:

$v_1 = 28 \text{ Volts}$

$v_2 = 14 \text{ Volts}$

$R_1 = 10 \, \Omega \text{ (Ohms)}$

$R_2 = 20 \, \Omega \text{ (Ohms)}$

$R_3 = 40 \, \Omega \text{ (Ohms)}$

Find the currents i_a and i_b .

$i_a = 800 \text{ mA (milli Amp)}$

$i_b = 300 \text{ mA (milli Amp)}$

Numeric Answer

$i_a = 800 \text{ mA}$


$i_b = 300 \text{ mA}$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

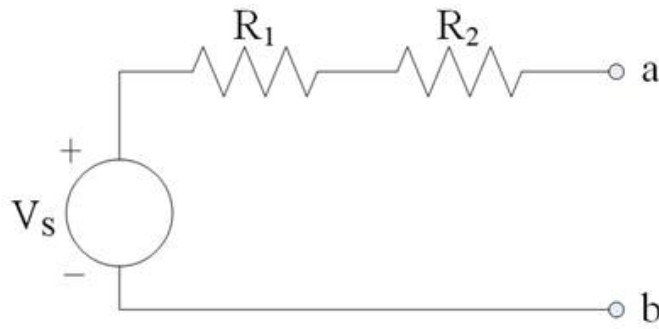Mark 10.00 out of
10.00

Q3a

Given: $V_s = 200$ Volts $R_1 = 100 \, \Omega$ (Ohms) $R_2 = 300 \, \Omega$ (Ohms)

Perform a source transformation and find the current transform equivalent.

$$I_{transform} = .5 \, \text{A}$$

$$R_{transform} = 400 \, \Omega \text{ (Ohm)}$$

Numeric Answer

$$I_{transform} = 0.50 \, \text{A}$$

$$R_{transform} = 400 \, \Omega \text{ (Ohm)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 15.00 out of 15.00

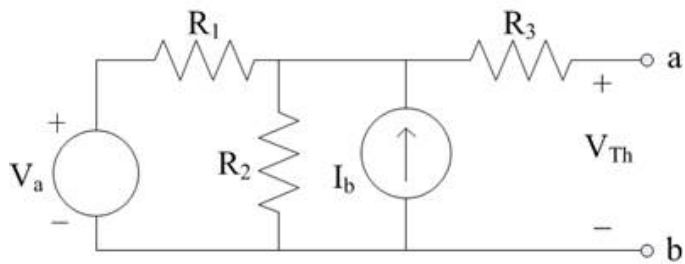

Q4f

Given:

$$V_a = 20 \text{ Volts} \quad I_b = 6 \text{ Amps}$$

$$R_1 = 20 \, \Omega \text{ (Ohm)} \quad R_2 = 60 \, \Omega \text{ (Ohm)} \quad R_3 = 10 \, \Omega \text{ (Ohm)}$$

a) Find the Thévenin equivalent voltage V_{Th} . $V_{Th} =$ ✓ Volts

b) Find the Thévenin equivalent resistance R_{Th} . $R_{Th} =$ ✓ Ω (Ohms)

Numeric Answer

a) $V_{Th} = 105.0$ Volts


b) $R_{Th} = 25.0 \, \Omega$ (Ohms)

Correct

Marks for this submission: 15.00/15.00.

Question 5

Correct

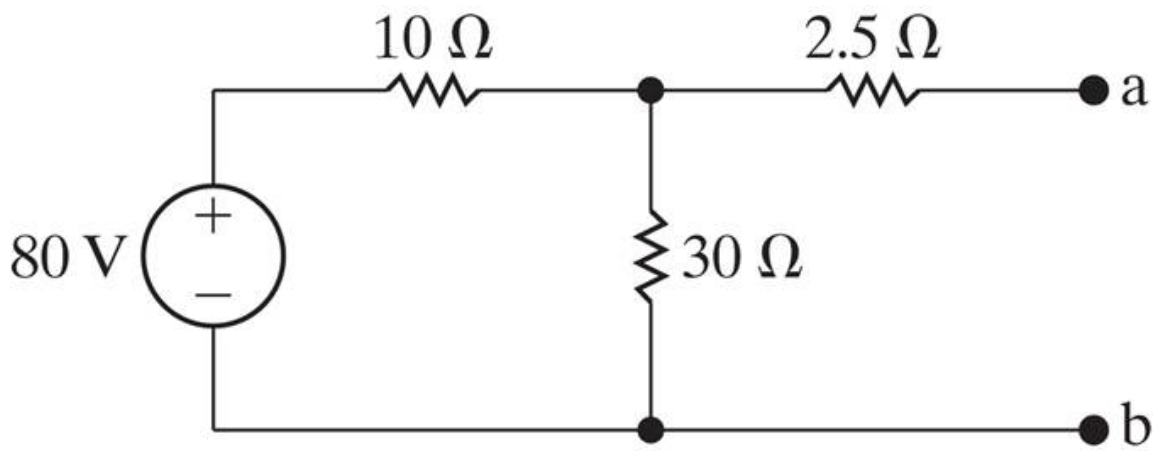Mark 15.00 out of
15.00

Copyright ©2015 Pearson Education, All Rights Reserved

Q5b

Find the Norton equivalent circuit with respect to terminals ab.

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 10.00 out of 10.00

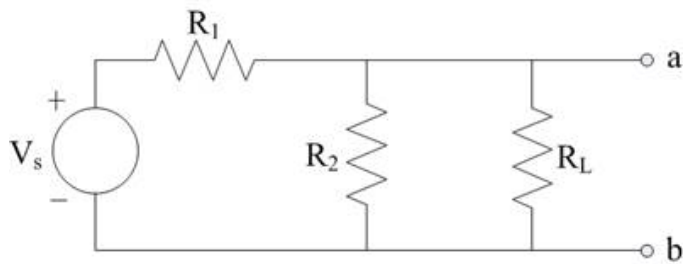

Q6e

Given:

$$V_s = 30 \text{ Volts} \quad R_1 = 140 \, \Omega \text{ (Ohm)} \quad R_2 = 140 \, \Omega \text{ (Ohm)}$$

a) Find the value of R_L that results in maximum power being transferred to R_L .

$$R_{L, \text{max power}} = 70 \, \Omega \text{ (Ohms)}$$

b) Find the maximum power that can be delivered to R_L .

$$P_{R_L, \text{max power}} = .803 \text{ Watts}$$

Numeric Answer

a) $R_{L, \text{max power}} = 70.0 \, \Omega \text{ (Ohms)}$


b) $P_{R_L, \text{max power}} = 0.8036 \text{ Watts}$

Correct

Marks for this submission: 10.00/10.00.

Question 7

Not answered

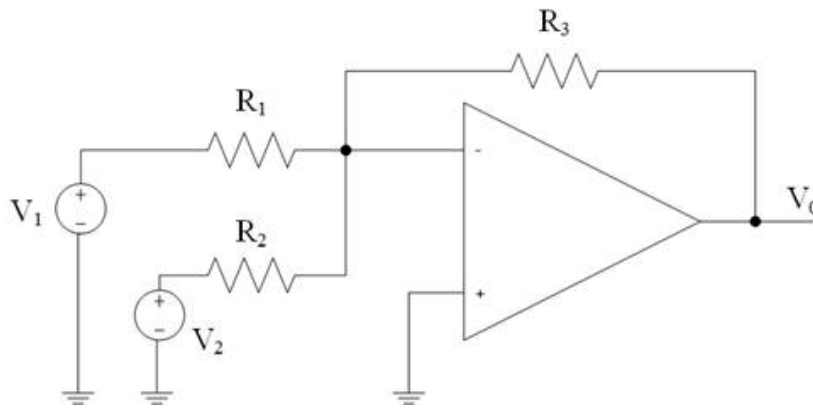Mark 0.00 out of
5.00

Q7k


Assume that the operational amplifier is ideal.

The opamp has two power inputs (not shown) of $+V_{cc} = +15V$ and $-V_{cc} = -15V$.Given: $V_1 = 5$ Volts $V_2 = 8$ Volts $R_1 = 2$ k Ω (kilo Ohm) $R_2 = 3$ k Ω (kilo Ohm) $R_3 = 1.5$ k Ω (kilo Ohm)Determine the voltage v_{out} . $v_{out} =$ \times Volts**Numeric Answer** $v_{out} = -7.75$ Volts

Question 8

Incorrect

Mark 0.00 out of 5.00

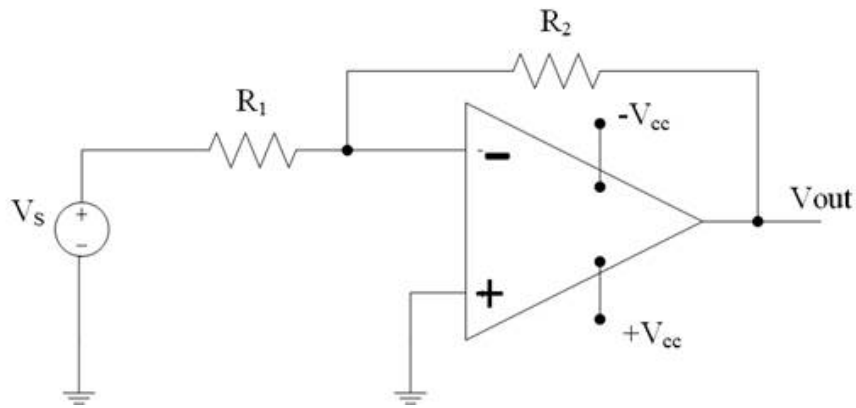

Q8c

Assume that the operational amplifier is ideal.

The opamp has two power inputs $+V_{cc} = +15V$ and $-V_{cc} = -15V$.Given: $V_S = -3.0$ Volts $R_1 = 47 \text{ k}\Omega$ (kilo Ohm) $R_2 = 270 \text{ k}\Omega$ (kilo Ohm)Determine the voltage V_{out} . $V_{out} = -17$ ✖ Volts**Numeric Answer** $V_{out} = 15.0$ Volts


Incorrect

Marks for this submission: 0.00/5.00.

Question 9

Correct

Mark 5.00 out of 5.00

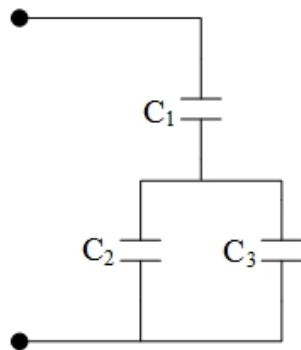

Q9d

Given:


 $C_1 = 20 \text{ }\mu\text{F}$ (micro F) $C_2 = 6 \text{ }\mu\text{F}$ (micro F) $C_3 = 14 \text{ }\mu\text{F}$ (micro F)Find the equivalent capacitance C_{Eq} . $C_{Eq} = 10$ ✔ μF (micro F)**Numeric Answer** $C_{Eq} = 10.0 \text{ }\mu\text{F}$ (micro F)

Correct

Marks for this submission: 5.00/5.00.

Question 10

Correct

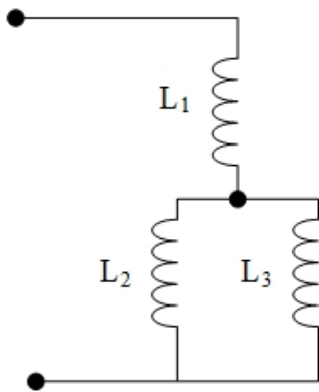Mark 5.00 out of
5.00

Q10d

Given:

$L_1 = 3 \text{ mH (milli H)}$

$L_2 = 10 \text{ mH (milli H)}$

$L_3 = 6 \text{ mH (milli H)}$

Find the equivalent inductance L_{Eq} .

$L_{\text{Eq}} = 6.75 \text{ mH (milli H)}$

Numeric Answer

$L_{\text{Eq}} = 6.750 \text{ mH}$

Correct

Marks for this submission: 5.00/5.00.