

**Started on** Wednesday, 16 November 2016, 11:18 AM

**State** Finished

**Completed on** Wednesday, 16 November 2016, 11:39 AM

**Time taken** 20 mins 19 secs

**Grade** 100.00 out of 100.00

### Question 1

Correct

Mark 100.00 out of 100.00

#### Quiz 9e

A circuit has the following measured voltage and current at the input terminals.

$$v(t) = 12 \cos(250t + 15^\circ) \text{ V}$$

$$i(t) = 15 \sin(250t - 15^\circ) \text{ A}$$

a) What is the frequency  $\omega$  (Omega) in radians of the time varying input?

$$\omega = 250 \text{ rad/sec}$$

b) What is the frequency  $f$  in Hertz of the time varying input?

$$f = 39.79 \text{ Hz}$$

c) What is the period  $T$  in ms (milli sec) of the time varying input?

$$T = 25.13 \text{ ms (milli sec)}$$

d) What is the phase angle  $\Phi_V$  in radians of the terminal voltage in the cosine convention?

$$\Phi_V = .262 \text{ rad (positive radian angle)}$$

e) What is the phase angle  $\Phi_I$  in radians of the terminal current in the cosine convention?

$$\Phi_I = -1.83 \text{ rad (negative radian angle)}$$

f) What is the rms voltage value of the terminal voltage?

$$v_{\text{rms}} = 8.49 \text{ V}_{\text{rms}}$$

g) What is the rms current value of the terminal current?

$$i_{\text{rms}} = \boxed{10.61} \checkmark A_{\text{rms}}$$

**Numeric Answer**

a)  $\omega$  (Omega) = 250 rad/sec

b)  $f = 39.7887$  Hz

c)  $T = 25.1328$  ms (milli sec)

d) Voltage phase angle in radians = 0.2618 rad

e) Current phase angle in radians = -1.8326 rad

f)  $v(t)$  in rms = 8.4853  $V_{\text{rms}}$

g)  $i(t)$  in rms = 10.6066  $A_{\text{rms}}$

**Correct**

Marks for this submission: 100.00/100.00.