

Home ► My courses ► EEE117-2019S-Sec1 ► Homework ►
Homework 4 - Chapter 11

Started on Wednesday, 13 February 2019, 9:27 AM

State Finished

Completed on Wednesday, 13 February 2019, 9:28 AM

Time taken 58 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

P11.1_10ed

What is the phase sequence of each of the following sets of voltages?

a) $v_a = 137 \cos(\omega t + 63^\circ) \text{ V}$ $v_b = 137 \cos(\omega t - 57^\circ) \text{ V}$ $v_c = 137 \cos(\omega t + 183^\circ) \text{ V}$

abc – Positive Phase Sequence: ▼ ✓

b) $v_a = 820 \cos(\omega t - 36^\circ) \text{ V}$ $v_b = 820 \cos(\omega t + 84^\circ) \text{ V}$ $v_c = 820 \sin(\omega t - 66^\circ) \text{ V}$

acb – Negative Phase Sequence: ▼ ✓


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

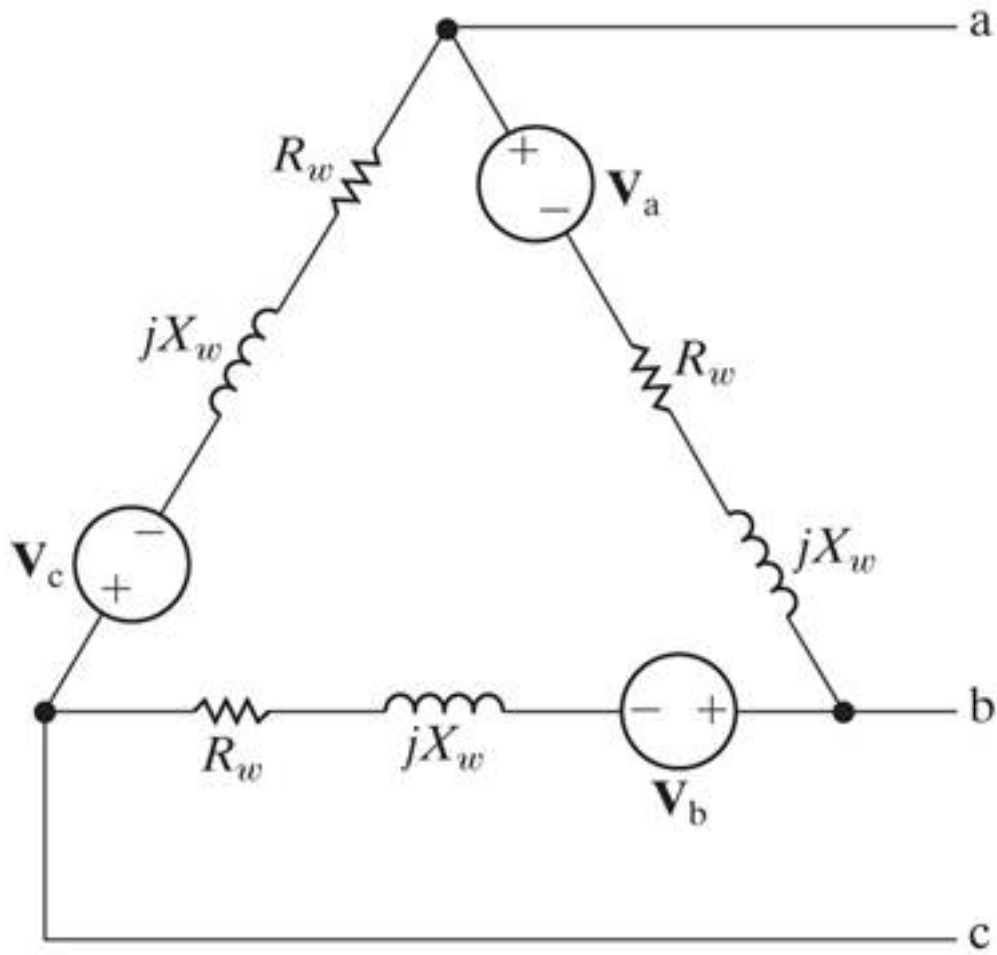

P11.4_10ed

Assume that nodes a,b,c are “open circuited” with no external connections.

Given: $v_a = 188 \cos(\omega t + 60^\circ) \text{ V}$ $v_b = -188 \cos(\omega t) \text{ V}$ $v_c = 188 \cos(\omega t - 60^\circ) \text{ V}$

Determine the current circulating in this Δ -connected generator.

$$I_{\Delta} = \boxed{0} \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

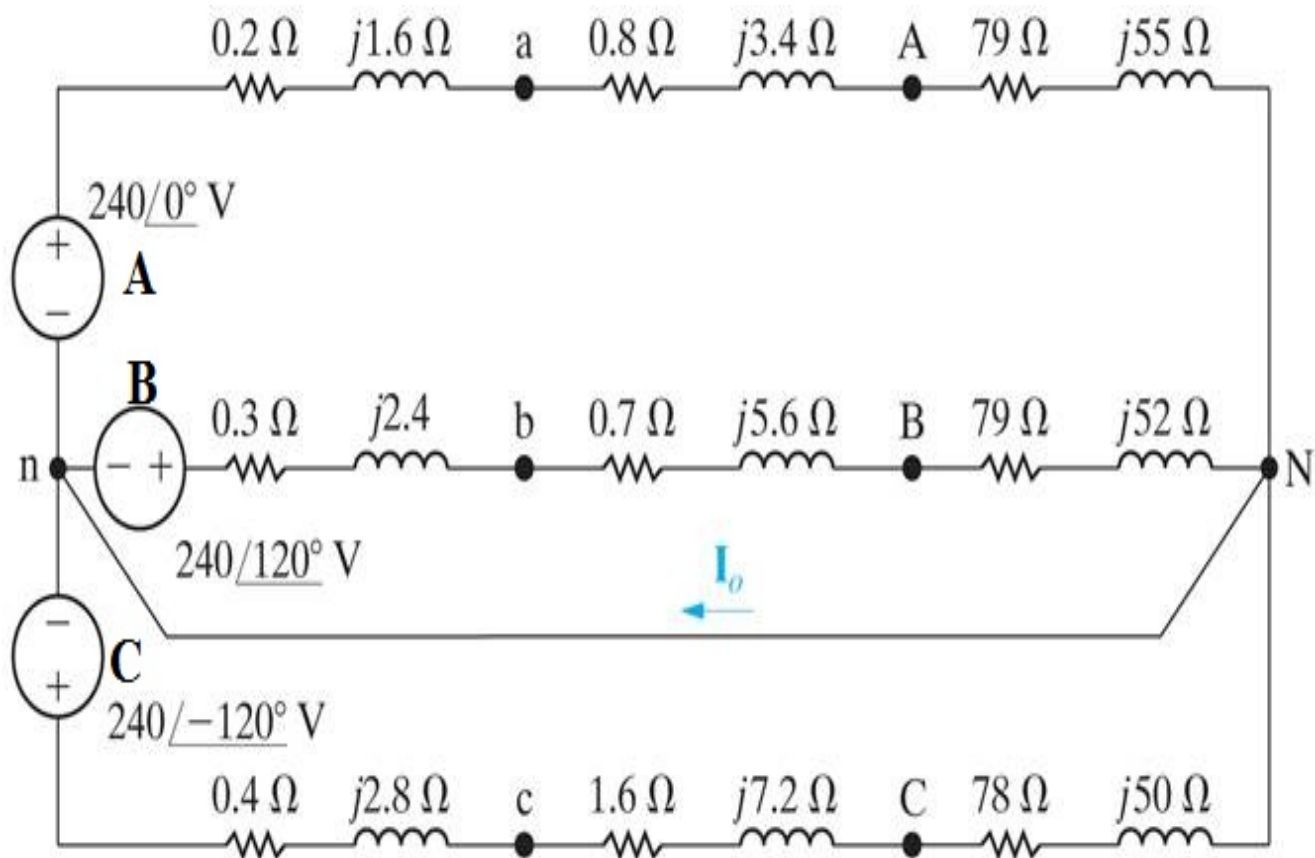

P11.6_8ed

a) Find the current I_0 as shown in the circuit.

$$I_0 = 0 \text{ A}$$

b) Find the voltage V_{AN} .

$$V_{AN} = 231 + j -8.16 \text{ V}$$

c) Find the voltage V_{AB} .

$$V_{AB} = 331 + j -211 \text{ V}$$

d) Is this circuit a balanced or unbalanced three-phase system?

Balanced/Unbalanced? Unbalanced


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

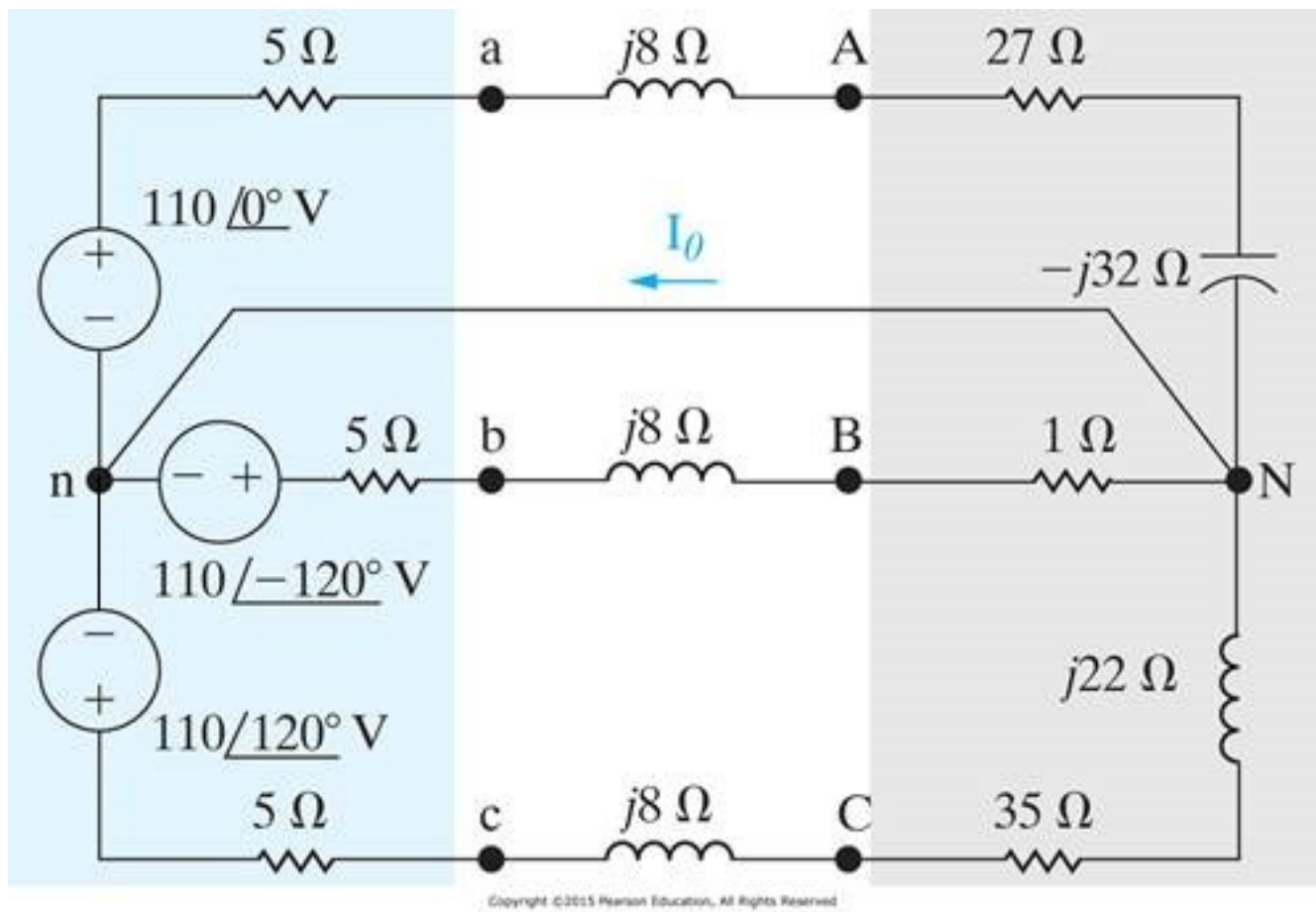

P11.6_10ed

Given that all voltages are rms values.

a) Find the current I_{aA} .

$$I_{aA} = 2.2 + j 1.65 \text{ A}_{\text{rms}}$$

b) Find the current I_{bB} .

$$I_{bB} = -10.92 + j -1.32 \text{ A}_{\text{rms}}$$


c) Find the current I_{cC} .

$$I_{cC} = .26 + j 2.18 \text{ A}_{\text{rms}}$$

d) Find the current I_0 as shown in the circuit.

$$I_0 = \boxed{-8.46} \checkmark + j \boxed{2.51} \checkmark A_{\text{rms}}$$

e) Is this circuit a balanced or unbalanced three-phase system?

Balanced/Unbalanced? Unbalanced ▼ 

Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

P11.19_8ed

A three-phase Δ -connected generator has an internal source impedance of $Z_{\Delta, \text{gen}} = 0.6 + j 4.8 \, \Omega/\Phi$. When the load is removed from the generator, the magnitude of the terminal voltage at the output is 34,500 V (where the load will connect). The generator feeds a Δ -connected load through a transmission line with an impedance of $Z_T = 0.8 + j 6.4 \, \Omega/\Phi$. The per-phase impedance of the load is $Z_{\Delta, \text{load}} = 2,877 - j 864 \, \Omega/\Phi$.

a) Calculate the magnitude of the current in the line feeding the load.

$$|I_{aA}| = |I_{bB}| = |I_{cC}| = \boxed{19.9} \checkmark \text{ A}$$

b) Calculate the magnitude of the line voltage at the terminals of the load.

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = \boxed{34545} \checkmark \text{ V}$$

c) Calculate the magnitude of the line voltage at the terminals of the source.

$$|V_{ab}| = |V_{bc}| = |V_{ca}| = \boxed{34508} \checkmark \text{ V}$$

d) Calculate the magnitude of the phase current in each leg of the load.

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = \boxed{11.5} \checkmark \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

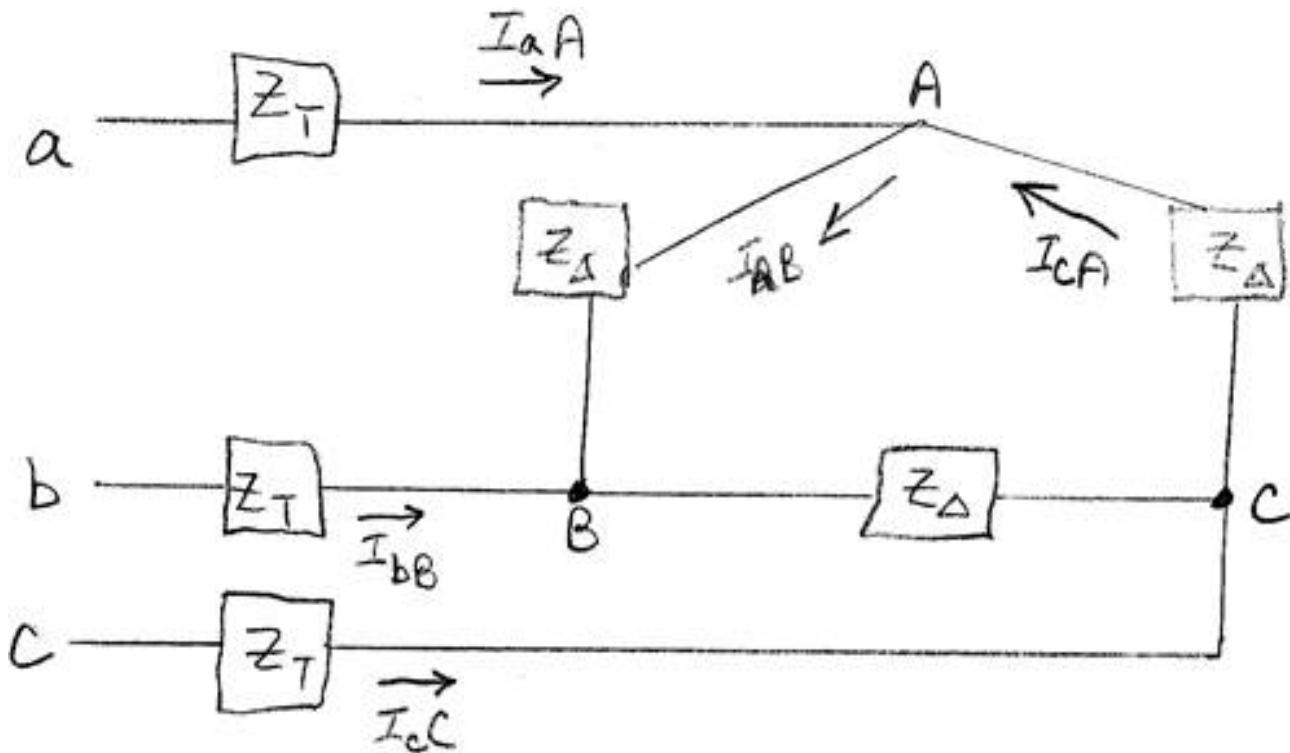

P11.11_7ed

A balanced Δ -connected load has an impedance of $Z_{\Delta} = 60 + j 45 \Omega/\Phi$.

The load is fed through a line have an impedance $Z_T = 0.8 + j 0.6 \Omega/\Phi$.

The phase voltage at the terminals of the load is $|\mathbf{V}_{AB}| = 480 \text{ V}_{\text{rms}}$.

The phase sequence is positive.

Use \mathbf{V}_{AB} as the zero angle reference.

a) Calculate the three phase currents in the load.

$$\mathbf{I}_{AB} = 5.2 + j -3.84 \text{ A}_{\text{rms}}$$

$$\mathbf{I}_{BC} = -5.88 + j -2.51 \text{ A}_{\text{rms}}$$

$$\mathbf{I}_{CA} = .76555 + j 6.35 \text{ A}_{\text{rms}}$$

b) Calculate the three line currents.

$$I_{aA} = 4.35 + j -10.19 A_{rms}$$

$$I_{bB} = -11 + j 1.32 A_{rms}$$

$$I_{cC} = 6.65 + j 8.86 A_{rms}$$

c) Calculate the three line voltages at the sending end of the line.

$$V_{ab} = 499 + j 0 V_{rms}$$

$$V_{bc} = -249 + j -432 V_{rms}$$

$$V_{ca} = -249 + j 432 V_{rms}$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

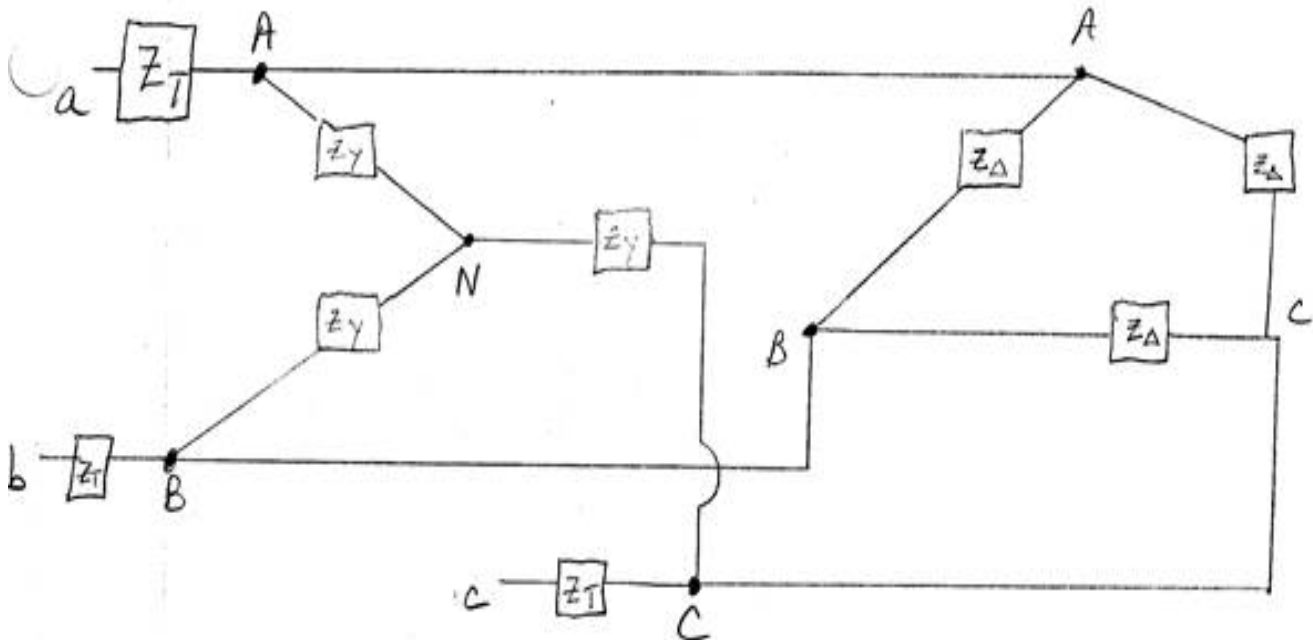

P11.12_7ed

A balanced Y-connected load having an impedance of $Z_Y = 72 + j 21 \Omega/\Phi$ is connected in parallel with a balanced Δ -connected load having an impedance of $Z_\Delta = 150 + j 0 \Omega/\Phi$. The parallel loads are fed from a line having an impedance of $Z_T = 0 + j 1 \Omega/\Phi$. The magnitude of the line-to-neutral voltage of the Y-connected load is $7,650 V_{rms}$.

a) Calculate the magnitude of the current in the line feeding the loads.

$$|I_{aA}| = |I_{bB}| = |I_{cC}| = \boxed{255} \checkmark A_{rms}$$

b) Calculate the magnitude of the phase current in the Δ -connected load.

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = \boxed{88} \checkmark A_{rms}$$

c) Calculate the magnitude of the phase current in the Y-connected load.

$$|I_{AN}| = |I_{BN}| = |I_{CN}| = \boxed{102} \checkmark A_{rms}$$

d) Calculate the magnitude of the line-to-line voltages at the sending end of the line.

$$|\mathbf{V}_{AB}| = |\mathbf{V}_{BC}| = |\mathbf{V}_{CA}| = \boxed{13301} \checkmark V_{\text{rms}}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

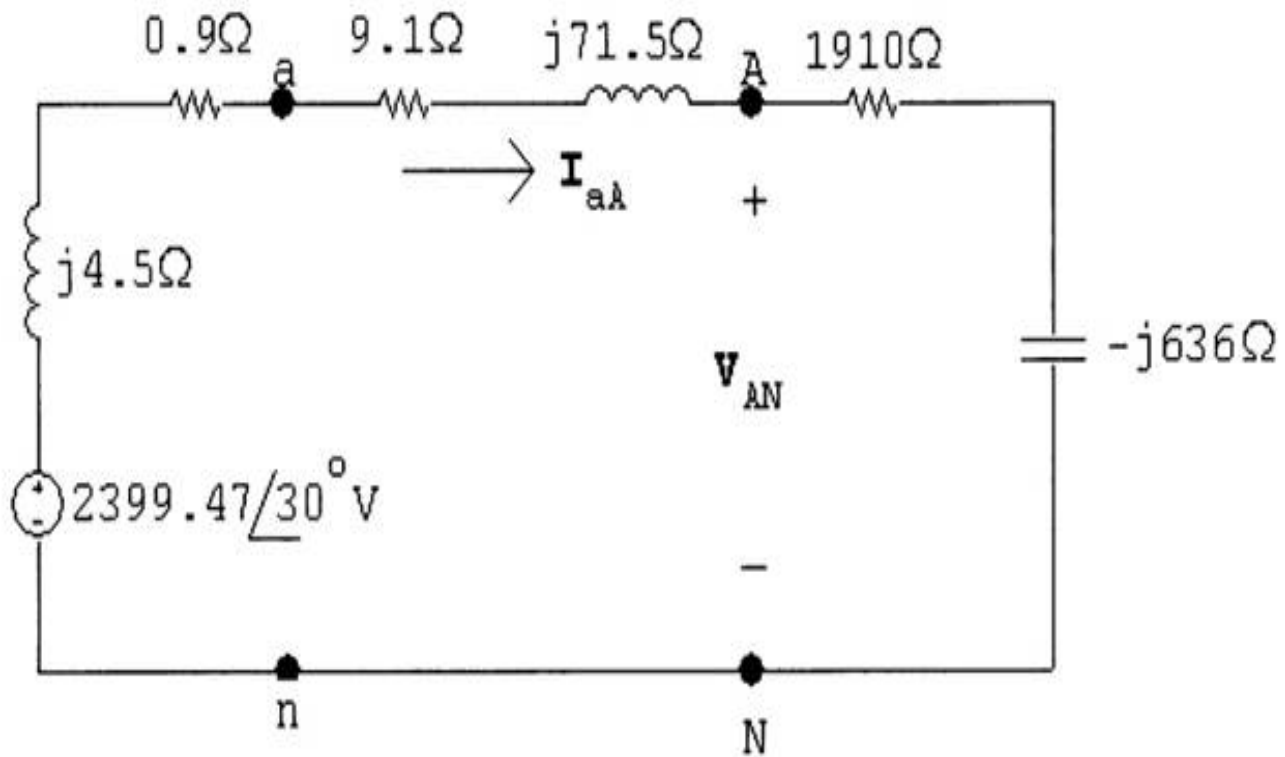

P11.14_7ed

A Δ -connected source is connected to a Y-connected load by means of a balanced three-phase distribution line with an impedance of $Z_T = 9.1 + j71.5 \Omega/\Phi$. The source phase sequence is negative. The voltage $V_{ab} = 4,156$ at angle 0° V_{rms}. The D-connected source impedance of $Z_D = 2.7 + j13.5 \Omega/\Phi$. The load impedance is $Z_Y = 1,910 - j636 \Omega/\Phi$. This figure shows the single-phase equivalent circuit.

a) Determine the magnitude of the line voltage at the terminals of the load.

$$|V_{AN}| = |V_{BN}| = |V_{CN}| = \boxed{2416} \checkmark V_{\text{rms}}$$

b) Determine the magnitude of the phase currents in the Δ -connected source.

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = \boxed{.69} \checkmark A_{\text{rms}}$$

c) Determine the magnitude of the line voltage at the terminals of the source.

$$|V_{ab}| = |V_{bc}| = |V_{ca}| = \boxed{4156} \checkmark V_{\text{rms}}$$

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

P11.23_8ed

The total apparent power supplied in a balanced three-phase Y- Δ system is 3,600 VA. The load line-to-line voltage is 208 V_{rms}. If the line impedance is negligible and the power factor angle of the load is 25°, determine the impedance of the load.

$$Z_{\text{load},\Delta} = \boxed{32.67} \checkmark + j \boxed{15.2} \checkmark \Omega \text{ (Ohms)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

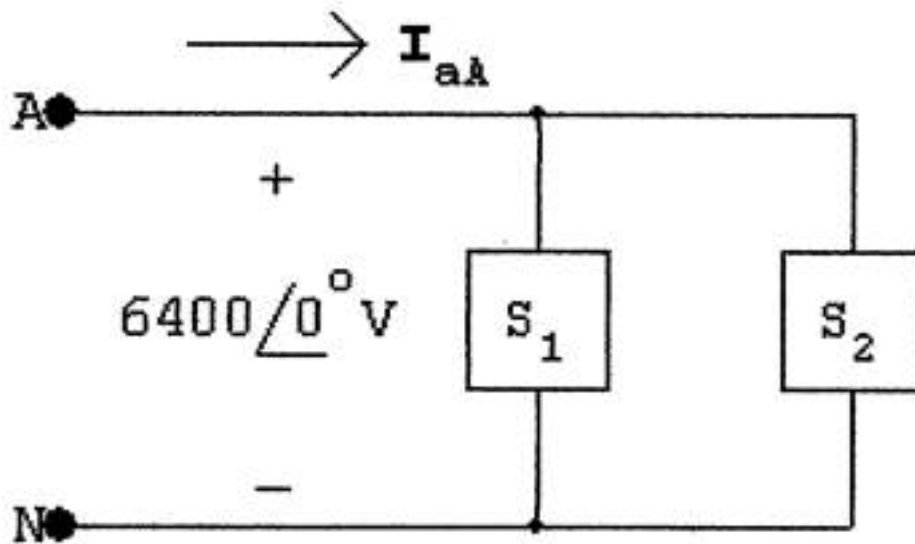

P11.35_8ed

A balanced three-phase source is supplying 1,800 kVA at 0.96 pf leading to two balanced Y-connected parallel loads. The distribution line connecting the source to the load has negligible impedance. The power associated with load 1 is $Z_{\text{load},1} = 192 + j 1,464 \text{ kVA}$.

a) Determine the impedance per phase of load 2 if the line voltage $V_{\text{line}} = 11,085 \text{ Vrms}$ and the impedance components are in series.

$$Z_{\text{load2,phase,series}} = 30.6 \checkmark + j -38.8 \checkmark \Omega (\text{Ohms})$$

b) Repeat a) with the load 2 impedance components are in parallel.

$$Z_{\text{load2,phase,parallel}} = 80 \checkmark + j -62 \checkmark \Omega (\text{Ohms})$$

Correct

Marks for this submission: 10.00/10.00.

Jump to...



Homework 5 - Chapter 12 ▶