

Started on Monday, 3 April 2017, 2:08 AM

State Finished

Completed on Monday, 3 April 2017, 5:15 AM


Time taken 3 hours 6 mins

Grade 77.14 out of 100.00

Question 1

Partially correct

Mark 5.00 out of 10.00

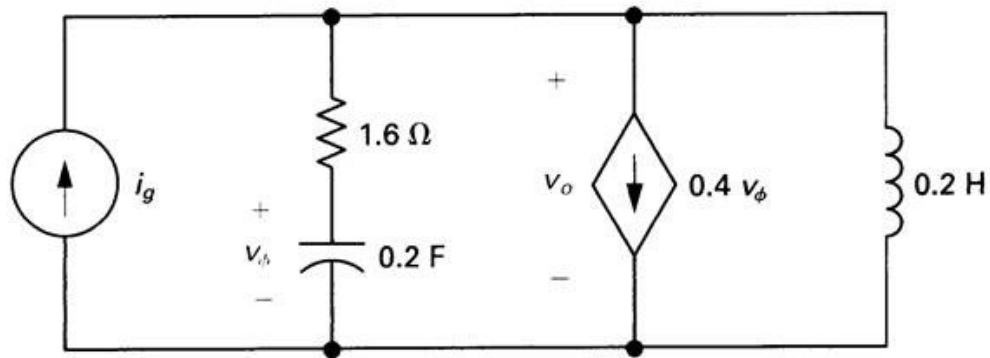

P13.11_6ed

There is no energy stored in the circuit at $t = 0$.Find $v_o(t)$ if $i_g(t) = 15 u(t)$ A.

$$v_o(t) = [\boxed{120} \times t \exp(\boxed{-5} \checkmark t) + \boxed{-225} \times \exp(\boxed{-5} \checkmark t)] u(t) \text{ V}$$

$$v_o(t) = [-45te^{-5t} + 24e^{-5t}]u(t) \text{ V}$$


Partially correct

Marks for this submission: 5.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

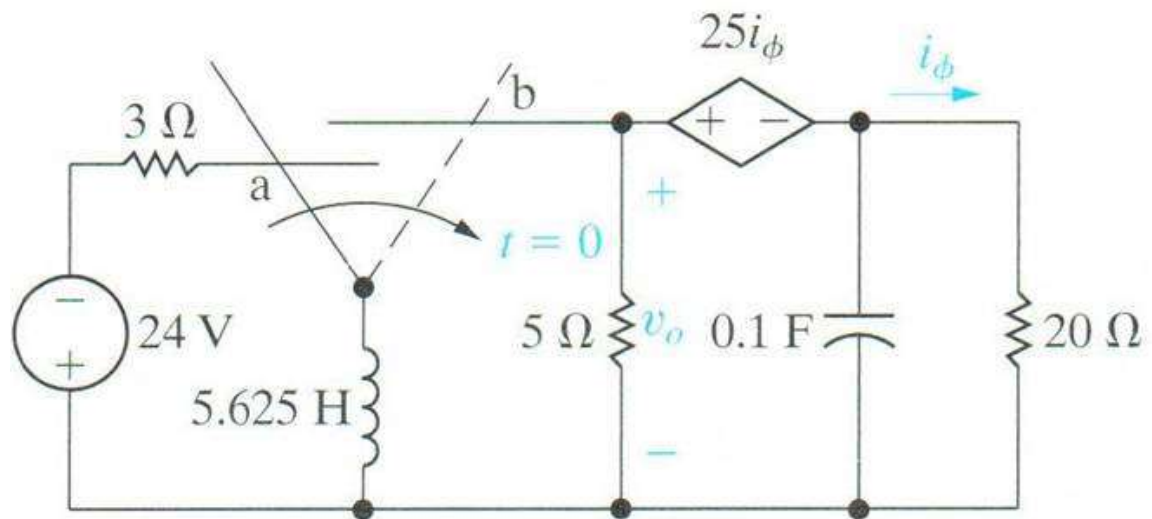

P13.14_7ed

The switch in this circuit is a “make then break” type of switch which allows for continuous current flow. At time $t = 0$, the switch moves from position “a” to position “b”.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V(s) = \boxed{180} \checkmark / (s^2 + \boxed{5} \checkmark s + \boxed{4} \checkmark)$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = [\boxed{60} \checkmark \exp(\boxed{-1} \checkmark t) + \boxed{-60} \checkmark \exp(\boxed{-4} \checkmark t)] u(t) \text{ V}$$

$$V_0(s) = \frac{180}{s^2 + 5s + 4}$$

$$v_0(t) = [60e^{-t} - 60e^{-4t}]u(t) \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Incorrect

Mark 0.00 out of 10.00

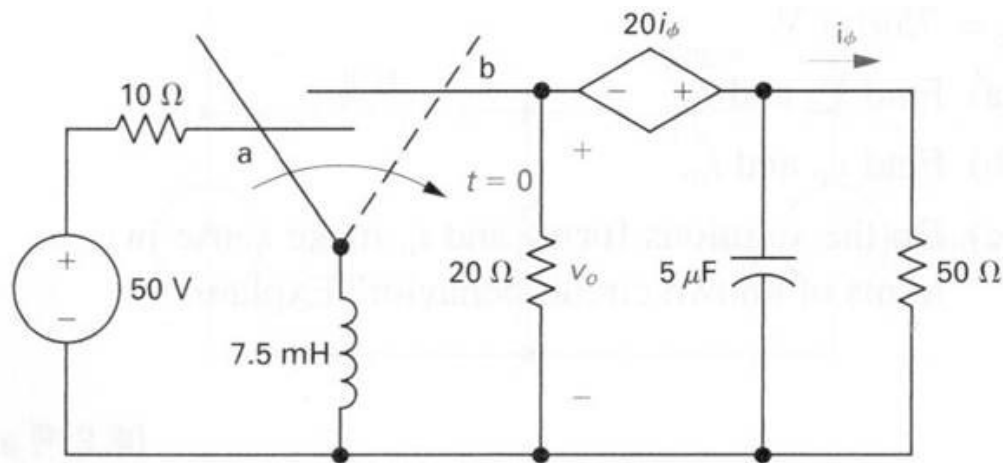

P13.23_6ed

The switch has been in position a for a long time. At $t = 0$, the switch moves instantaneously to position b.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V_o(s) = \frac{-600}{(s + 4 \times 10^6)(s + 1600)}$$

Smaller root first then larger root in the answer above.

b) Find the time domain $v_o(t)$.

$$v_o(t) = [67.56 \exp(-1500t) + 1 \exp(-200t)] u(t) \text{ V}$$

$$V_o = \frac{-600,000}{s^2 + 10,000s + 16 \times 10^6} = \frac{-600,000}{(s + 2,000)(s + 8,000)}$$

$$v_o(t) = [-100e^{-2,000t} + 100e^{-8,000t}] u(t) \text{ Volts}$$


Incorrect

Marks for this submission: 0.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

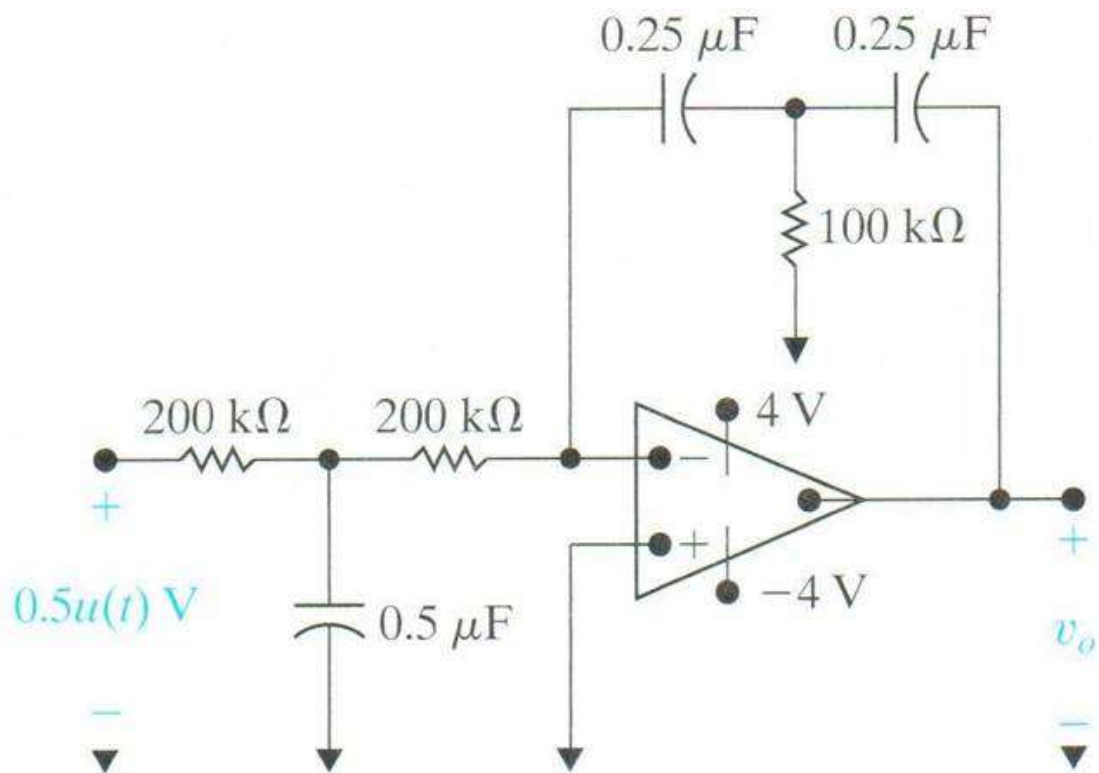

P13.48_7ed

Given: No energy is stored in this circuit for $t < 0$ and you can assume the OpAmp is ideal.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V_o(s) = \boxed{-200} / s^3$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = \boxed{-100} t^{\boxed{2}} u(t) \text{ V}$$

c) Calculate how long in ms (milli sec) until the opamp saturates.

$$t_{\text{saturation}} = \boxed{200} \text{ ms (milli sec)}$$

$$V_0 = \frac{-200}{s^3}$$

$$v_o(t) = [?][?] - 100t^2 u(t) \text{ Volts}$$

c) $t_{\text{saturation}} = 200 \text{ ms (milli sec)}$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

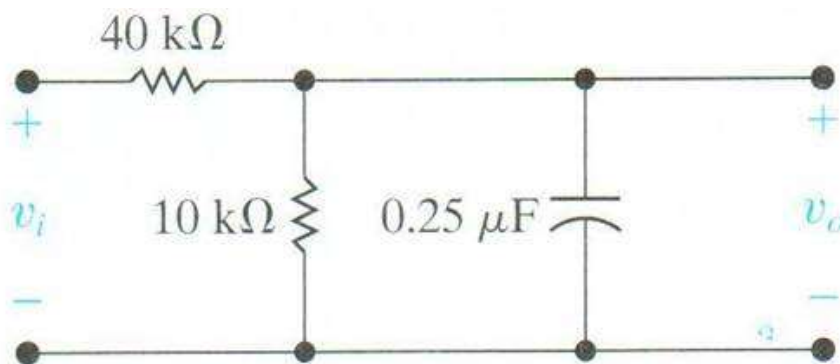

P13.49e_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{100} \checkmark / (s + \boxed{500} \checkmark)$$

$$H(s) = \frac{100}{s+500}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Partially correct

Mark 5.00 out of 10.00

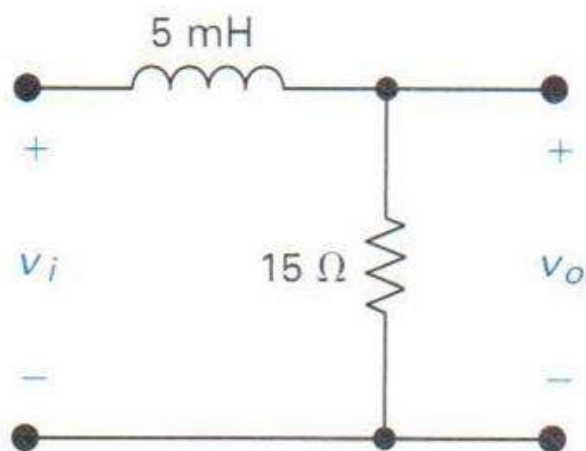

P13.49d_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{2} \times / (s + \boxed{3000} \checkmark)$$

$$H(s) = \frac{3,000}{s+3,000}$$


Partially correct

Marks for this submission: 5.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

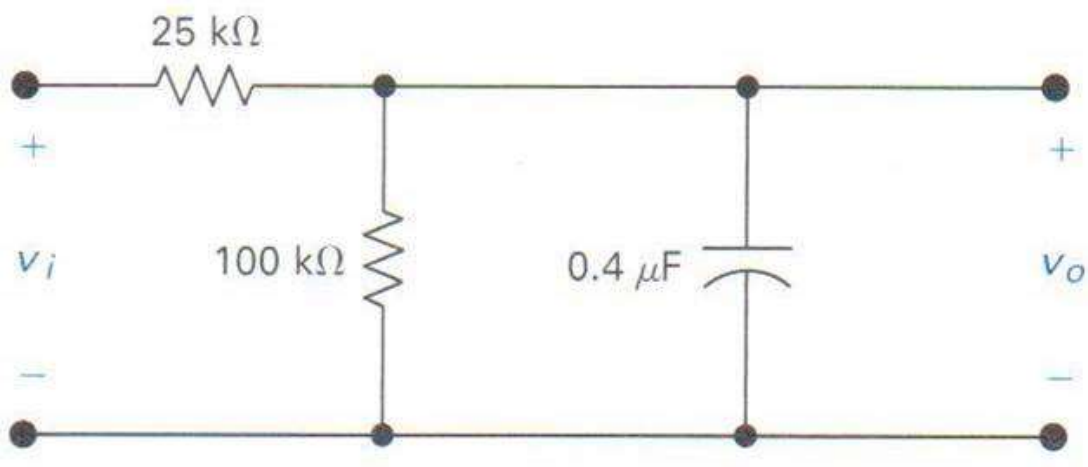

P13.49e_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{100} \checkmark / (s + \boxed{125} \checkmark)$$

$$H(s) = \frac{100}{s+125}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

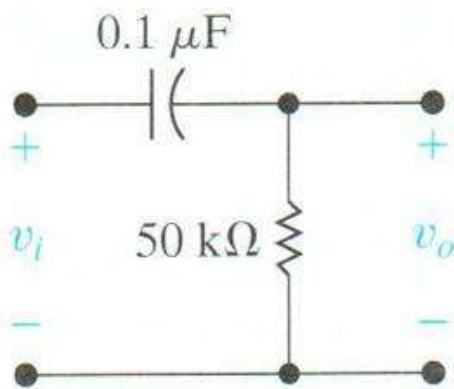

P13.49b_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + \boxed{200} \checkmark)$$

$$H(s) = \frac{s}{s+200}$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Partially correct

Mark 7.14 out of 10.00

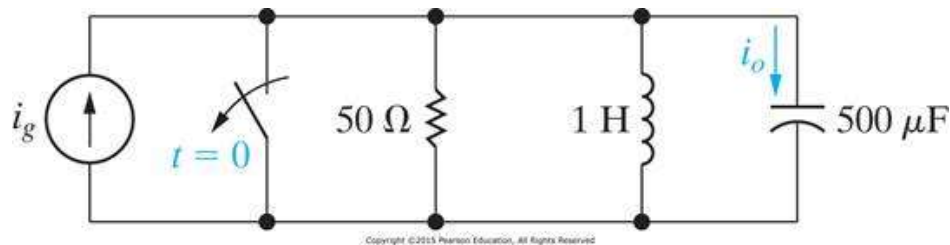

P13.56_10ed

There is no energy stored in this circuit at the time the switch is opened. The sinusoidal current source is generating the signal $25 \cos(200t)$ mA (milli Amp). The desired response signal is the current $i_o(t)$.

a) Find the s domain transfer function $H(s) = I_o/I_g$ for this circuit.

$$H(s) = s^2 / (s^2 + 40 s + 2000)$$

b) Find the s domain form for $I_o(s)$.

$$I_o(s) = .025 s^3 / (\text{There are four factors in the denominator – list each one separately})$$

$$\text{Factor 1: } s + 20 - j 40$$

$$\text{Factor 2: } s + 20 + j 40$$

$$\text{Factor 3: } s + 0 - j 200$$

$$\text{Factor 4: } s + 0 + j 200$$

c) Find the time domain form $i_o(t)$.

$$i_o(t) = [7.197 \times 10^{-4} \exp(-40t) \cos(40t - 97.94^\circ) + .0129 \cos(200t - 11.89^\circ)] u(t) \text{ mA (milli A)}$$

$$H(s) = \frac{I_o}{I_g} = \frac{s^2}{s^2 + 40s + 2,000}$$

$$I_o = \frac{0.025s^3}{(s+20-j40)(s+20+j40)(s+0-j200)(s+0+j200)}$$

$$i_o(t) = [1.4395e^{-20t} \cos(40t - 97.94^\circ) + 25.7514 \cos(200t + 11.89^\circ)] u(t) \text{ mA}$$


Partially correct

Marks for this submission: 7.14/10.00. Accounting for previous tries, this gives 7.14/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

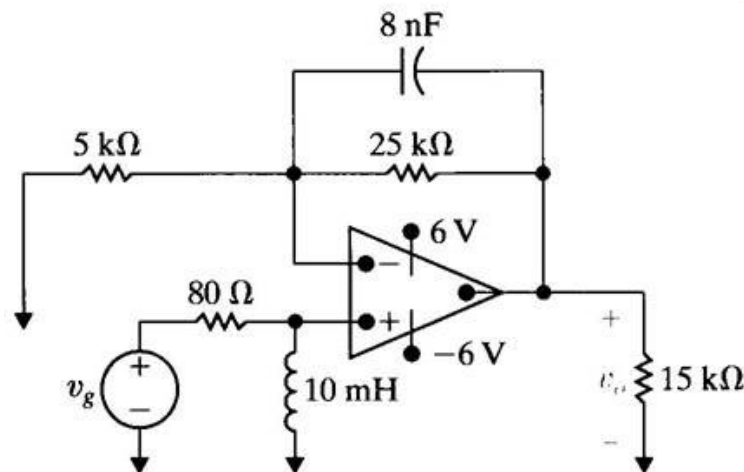

P13.78_7ed and P13.77_10ed

You may assume the opamp is ideal.

a) Find the s domain transfer function $H(s) = V_o/V_g$ for this circuit.

$$H(s) = s * (s + 30000) / [(s + 5,000) * (s + 8000)]$$

b) Find the time domain $v_o(t)$ if $v_g(t) = 600 u(t)$ mV (milli V).

$$v_o(t) = [5 e^{-5,000t} + -4.4 \exp(-8000 t)] u(t) \text{ V}$$

c) Find the steady-state express for $v_o(t)$ if $v_g(t) = 2 \cos(10,000 t)$ V.

$$v_o(t)_{\text{steady-state}} = [4.42 \cos(10000 + -6.34^\circ) u(t) \text{ V}]$$

$$H(s) = \frac{s(s+30,000)}{(s+5,000)(s+8,000)}$$

$$v_o(t) = [5e^{-5,000t} - 4.4e^{-8,000t}]u(t) \text{ Volts}$$

$$v_o(t)_{\text{steady-state}} = 4.4172 \cos(10,000t - 6.34^\circ) u(t) \text{ Volts}$$

Correct

Marks for this submission: 10.00/10.00.