
Started on	Sunday, 16 April 2017, 9:15 PM
-------------------	--------------------------------

State	Finished
--------------	----------

Completed on	Sunday, 16 April 2017, 9:15 PM
---------------------	--------------------------------


Time taken	8 secs
-------------------	--------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 20.00 out of 20.00

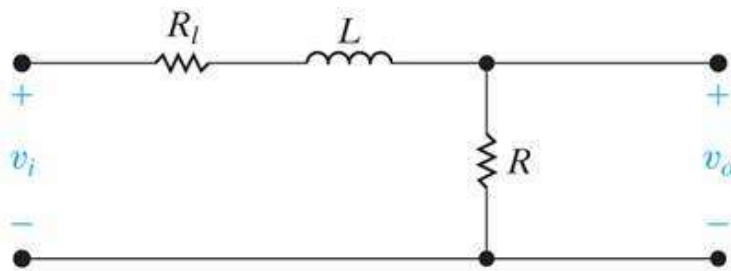

P14.3_9ed

A resistor R_l is added in series with the inductor in this circuit.

Given: $R_l = 75 \, \Omega$ (Ohm) $L = 10 \, \text{mH}$ (mill H) $R = 127 \, \Omega$ (Ohm)

a) Find the s domain transfer function $H(s) = V_o/V_i$.

$$H(s) = \frac{12700}{s + 20200}$$

b) At what frequency will the magnitude of $H(j\omega)$ be maximum?

$$\omega_{H,\max} = 0 \, \text{rad/sec}$$

c) What is maximum value of the magnitude of $H(j\omega)$?

$$H(j\omega)_{\max} = .63$$

d) At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by square root of 2?

$$\omega_{H,\max,\text{sqrt}(2)} = 20200 \, \text{rad/sec}$$

e) Find ω_c (omega_c)

$$\omega_c = 20200 \, \text{rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

f) Find $H(j\omega = 0)$ in polar form..

$$H(j\omega = 0) = \text{Mag } .63 \text{ at angle } 0^\circ \text{ (Degrees)}$$

g) Find $H(j\omega = 0.3\omega_c)$ in polar form.

$$H(j\omega = 0.3\omega_c) = \text{Mag } .602 \text{ at angle } -16.7^\circ \text{ (Degrees)}$$

h) Find $H(j\omega = \omega_c)$ in polar form.

$$H(j\omega = \omega_c) = \text{Mag } .44 \text{ at angle } -45^\circ \text{ (Degrees)}$$

i) Find $H(j\omega = 3\omega_c)$ in polar form.

$$H(j\omega = 3\omega_c) = \text{Mag } .2 \text{ at angle } -71.6^\circ \text{ (Degrees)}$$

Numeric Answer

$$a) \frac{V_o}{V_i} = \frac{12,700}{s + 20,200}$$

$$b) \omega_{H,\max} = 0 \, \text{rad/sec}$$

$$c) H(j\omega)_{\max} = 0.6287$$

$$d) \omega_{H,\max,\text{sqrt}(2)} = 20,200 \, \text{rad/sec}$$

$$e) \omega_c = 20,200 \, \text{rad/sec}$$

f) $H(j\omega = 0) = 0.6287$

g) $H(j\omega = 0.3\omega_c) = 0.6022$ ~~\angle~~ -16.70°

h) $H(j\omega = \omega_c) = 0.4446$ ~~\angle~~ -45°

i) $H(j\omega = 3\omega_c) = 0.1988$ ~~\angle~~ -71.57°


Correct

Marks for this submission: 20.00/20.00.

Question 2

Correct

Mark 20.00 out of 20.00

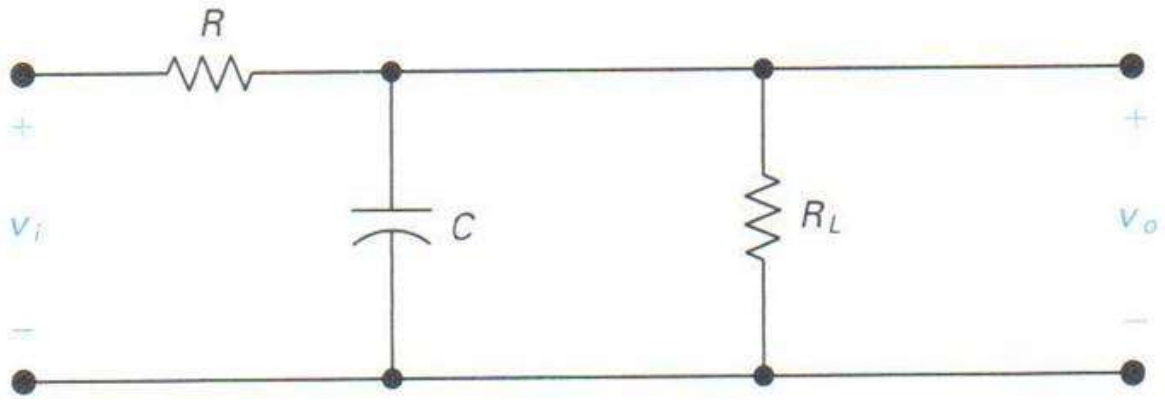

P14.3_6ed

A resistor R_L is connected in parallel with the capacitor in this circuit. The circuit thus becomes a loaded low-pass filter.

Given: $R = 20 \text{ k}\Omega$ (kilo Ohm) $C = 4 \text{ nF}$ $R_L = 300 \text{ k}\Omega$ (kilo Ohm)

a) Find the s domain transfer function $H(s) = V_o/V_i$.

$$H(s) = \boxed{12500} \checkmark / (s + \boxed{13373.33} \checkmark)$$

b) Find ω_c (omega_c)

$$\omega_c = \boxed{13333.3} \checkmark \text{ rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

c) Find $H(j0)$

$$H(j0) = \boxed{.94} \checkmark$$

d) Find $H(j\omega_c)$ i.e. evaluate $H(j\omega)$ at $\omega = \omega_c$

$$H(j\omega_c) = \text{Mag } \boxed{.66} \checkmark \text{ Angle } \boxed{-45} \checkmark$$

e) Find $H(j0.2\omega_c)$ i.e. evaluate $H(j\omega)$ at $\omega = 0.2 \omega_c$

$$H(j0.2\omega_c) = \text{Mag } \boxed{.92} \checkmark \text{ Angle } \boxed{-11.31} \checkmark$$

f) Find $H(j8\omega_c)$ i.e. evaluate $H(j\omega)$ at $\omega = 8\omega_c$

$$H(j8\omega_c) = \text{Mag } \boxed{.116} \checkmark \text{ Angle } \boxed{-82.9} \checkmark$$

Numeric Answer

a) $f = 50 \text{ Hz}$

b) $\omega_c = 13,333.3 \text{ rad/sec}$

c) $H(j0) = 0.9375$

d) $H(j\omega_c) = 0.6629 \angle -45^\circ$

e) $H(j0.2\omega_c) = 0.9193 \angle -11.31^\circ$ This is an exact answer to the passband region.

f) $H(j8\omega_c) = 0.1163 \angle -82.87^\circ$ This is an exact answer to the stopband region.


Correct

Marks for this submission: 20.00/20.00.

Question 3

Correct

Mark 20.00 out of 20.00

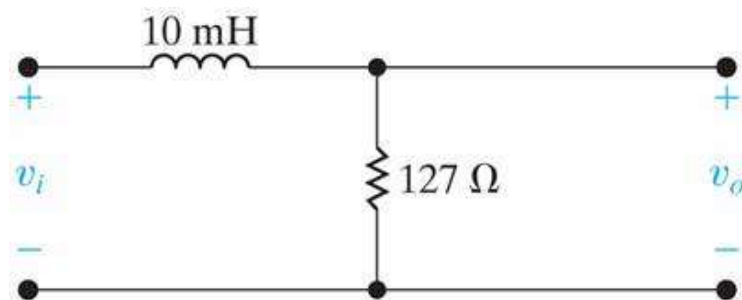

P14.1_9ed

a) Find the cutoff frequency in hertz.

$$f_c = 2021.26 \text{ Hz}$$

b) Find $H(j\omega = 0)$ in polar form.

$$H(j\omega = 0) = \text{Mag } 1 \text{ at angle } 0^\circ \text{ (Degrees)}$$

Now examine the output magnitude and phase as the input frequency varies.

c) Find $H(j\omega = 0.2\omega_c)$ in polar form..

$$H(j\omega = 0.2\omega_c) = \text{Mag } .98 \text{ at angle } -11.31^\circ \text{ (Degrees)}$$

d) Find $H(j\omega = \omega_c)$ in polar form.

$$H(j\omega = \omega_c) = \text{Mag } .71 \text{ at angle } -45^\circ \text{ (Degrees)}$$

e) Find $H(j\omega = 5\omega_c)$ in polar form.

$$H(j\omega = 5\omega_c) = \text{Mag } .196 \text{ at angle } -78.69^\circ \text{ (Degrees)}$$

Now given $v_i(t) = 10 \cos(\omega t)$ V. Write the steady-state expression for v_o for:

f) $\omega = 0.2\omega_c$

$$v_o(t) = 9.81 \cos(2540 t + -11.31^\circ) \text{ Volts}$$

g) $\omega = \omega_c$

$$v_o(t) = 7.07 \cos(12700 t + -45^\circ) \text{ Volts}$$

h) $\omega = 5\omega_c$

$$v_o(t) = 1.96 \cos(63500 t + -78.69^\circ) \text{ Volts}$$

a) $f_c = 2021.27 \text{ Hz}$

b) $H(j\omega = 0) = 1 \angle 0^\circ$

c) $H(j\omega = 0.2\omega_c) = 0.981 \angle -11.31^\circ$

d) $H(j\omega = \omega_c) = 0.707 \angle -45^\circ$

e) $H(j\omega = 5\omega_c) = 0.196 \angle -78.69^\circ$

f) For $\omega = 0.2\omega_c$, $v_o(t) = 9.81 \cos(2,540 t - 11.31^\circ) \text{ Volts}$

g) For $\omega = \omega_c$, $v_o(t) = 7.07 \cos(12,700 t - 45^\circ) \text{ Volts}$

h) For $\omega = 5\omega_c$, $v_o(t) = 1.96 \cos(63,500 t - 78.69^\circ) \text{ Volts}$


Correct

Marks for this submission: 20.00/20.00.

Question 4

Correct

Mark 20.00 out of 20.00

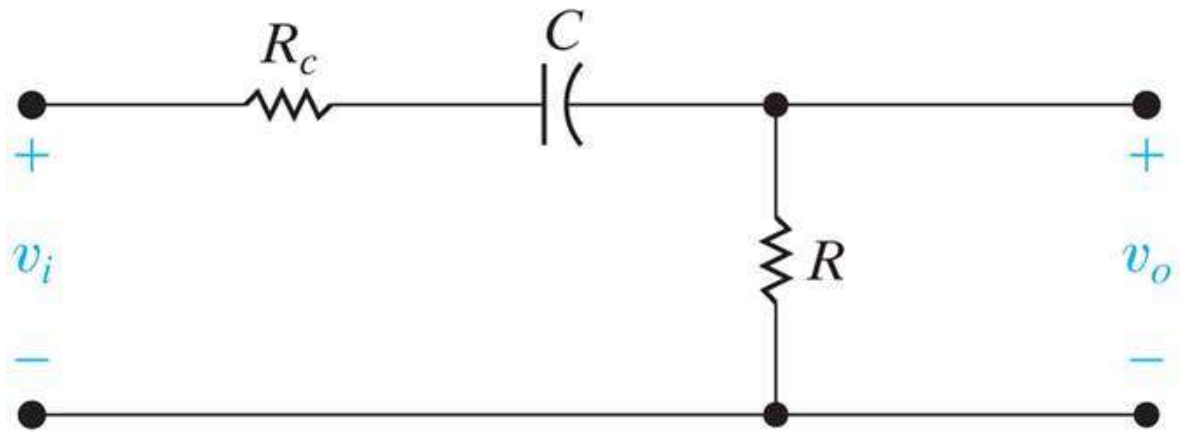

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P14.11_9ed

Given: $R_c = 12.5 \text{ k}\Omega$ (kilo Ohm) $C = 5 \text{ nF}$ $R = 50 \text{ k}\Omega$ (kilo Ohm)

a) Find the cutoff frequency f_c for this high-pass filter.

$$f_c = 509.3 \text{ Hz}$$

b) Find the $H(j\omega)$ for

$$H(j\omega = \omega_c) = .57 \text{ at angle } 45^\circ \text{ (degrees)}$$

$$H(j\omega = 0.2\omega_c) = .16 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = .78 \text{ at angle } 11.31^\circ$$

c) If $v_i(t) = 500 \cos(\omega t) \text{ mV}$ (milli V), write the steady-state output voltage $v_o(t)$ for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 282.85 \cos(\omega t + 45^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 78.45 \cos(\omega t + 78.69^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 392.25 \cos(\omega t + 11.31^\circ) \text{ mV (milli V)}$$

a) $f_c = 509.2958 \text{ Hz}$

b) Find the $H(j\omega)$ for

$$H(j\omega = \omega_c) = 0.5657 \text{ at angle } 45^\circ$$

$$H(j\omega = 0.2\omega_c) = 0.1569 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.7845 \text{ at angle } 11.31^\circ$$

c) If $v_i(t) = 500 \cos(\omega t)$, write the steady-state output voltage $v_o(t)$ for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 282.850 \cos(\omega t + 45^\circ) \text{ mV}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 78.450 \cos(\omega t + 78.69^\circ) \text{ mV}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 392.250 \cos(\omega t + 11.31^\circ) \text{ mV}$$


Correct

Marks for this submission: 20.00/20.00.

Question 5

Correct

Mark 20.00 out of 20.00

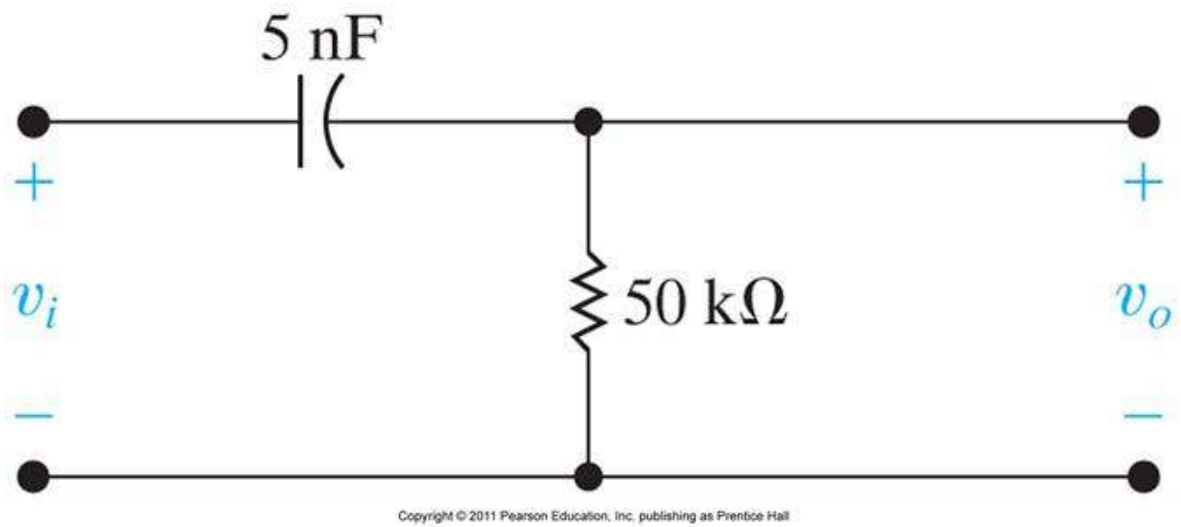

P14.10_9ed

a) Find the cutoff frequency f_c for this high-pass filter.

$$f_c = 636.62 \text{ Hz}$$

b) Find the $H(j\omega)$ for

$$H(j\omega = \omega_c) = 0.71 \text{ at angle } 45^\circ \text{ (degrees)}$$

$$H(j\omega = 0.2\omega_c) = 0.2 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.98 \text{ at angle } 11.31^\circ$$

c) If $v_i(t) = 500 \cos(\omega t)$ mV (milli V), write the steady-state output voltage $v_o(t)$ for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353.55 \cos(\omega t + 45^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 98.1 \cos(\omega t + 78.7^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 490.3 \cos(\omega t + 11.31^\circ) \text{ mV (milli V)}$$

a) $f_c = 636.6198 \text{ Hz}$

b) Find the $H(j\omega)$ for

$$H(j\omega = \omega_c) = 0.7071 \text{ at angle } 45^\circ$$

$$H(j\omega = 0.2\omega_c) = 0.1961 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.9806 \text{ at angle } 11.31^\circ$$

c) If $v_i(t) = 500 \cos(\omega t)$, write the steady-state output voltage $v_o(t)$ for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353.550 \cos(\omega t + 45^\circ) \text{ mV}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 98.050 \cos(\omega t + 78.69^\circ) \text{ mV}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 490.30 \cos(\omega t + 11.31^\circ) \text{ mV}$$

Correct

Marks for this submission: 20.00/20.00.