

| | |
|--------------|------------------------------------|
| Started on | Thursday, 6 October 2016, 10:25 AM |
| State | Finished |
| Completed on | Thursday, 6 October 2016, 11:40 AM |
| Time taken | 1 hour 15 mins |
| Grade | 100.00 out of 100.00 |

Question 1

Correct

Mark 15.00 out of 15.00

Q1c

Consider the sinusoidal voltage $v(t) = 300 \cos(200 \pi t - 60^\circ) V_{\text{rms}}$.

a) What is the maximum amplitude of the voltage?

$V_m =$ ✓

V

b) What is the frequency of $v(t)$ in hertz?

$f =$ ✓

Hz

c) What is the frequency of $v(t)$ in radians per second?

$\omega =$ ✓

rad/sec

d) What is the phase angle in radians?

$\phi \text{ (phi)} =$ ✓

radians

e) What is the period in milliseconds?

$T =$ ✓

ms (milli sec)

Numeric Answer

- a) $V_m = 424.2641 \text{ V}$
- b) $f = 100 \text{ Hz}$
- c) $\omega = 628.3185 \text{ rad/sec}$
- d) $\phi \text{ (phi)} = -1.0472 \text{ radians}$
- e) $T = 10.0 \text{ ms (milli sec)}$

Correct

Marks for this submission: 15.00/15.00.

Question 2

Correct

Mark 5.00 out of 5.00

Q2e

Given: $x(t) = 120 \cos(300 t + 55^\circ) + 415 \cos(300 t - 25^\circ)$

Use the concept of the phasor to combine this sinusoidal function into a single trigonometric expression in the form similar to $x(t) = A \cos (\omega t + \theta^\circ)$.

Magnitude A of $x(t)$ = ✓

Angle θ of $x(t)$ = ✓

° (Degree)

Numeric Answer

$x(t) = 451.5754 \cos(300 t - 9.8291^\circ)$


Correct

Marks for this submission: 5.00/5.00.

Question 3

Correct

Mark 15.00 out of 15.00

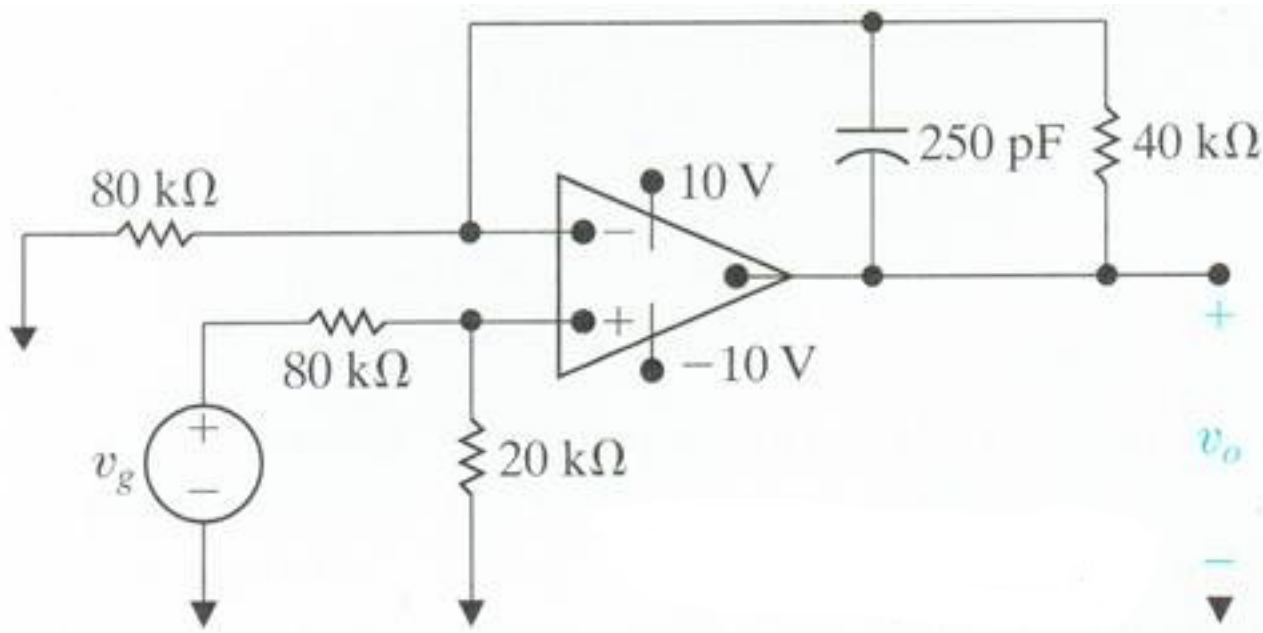

Q3c

Assume the operational amplifier is ideal.

Given $v_g(t) = -38.0 \text{ V}$ (a constant voltage)

Find the steady-state output $v_o(t)$.

$v_o(t) =$ ✓

Volts

Numeric Answer

$v_o(t) = -10 \text{ V}$ since the opamp is in saturation at the negative power supply rail.


Correct

Marks for this submission: 15.00/15.00.

Question 4

Correct

Mark 10.00 out of 10.00

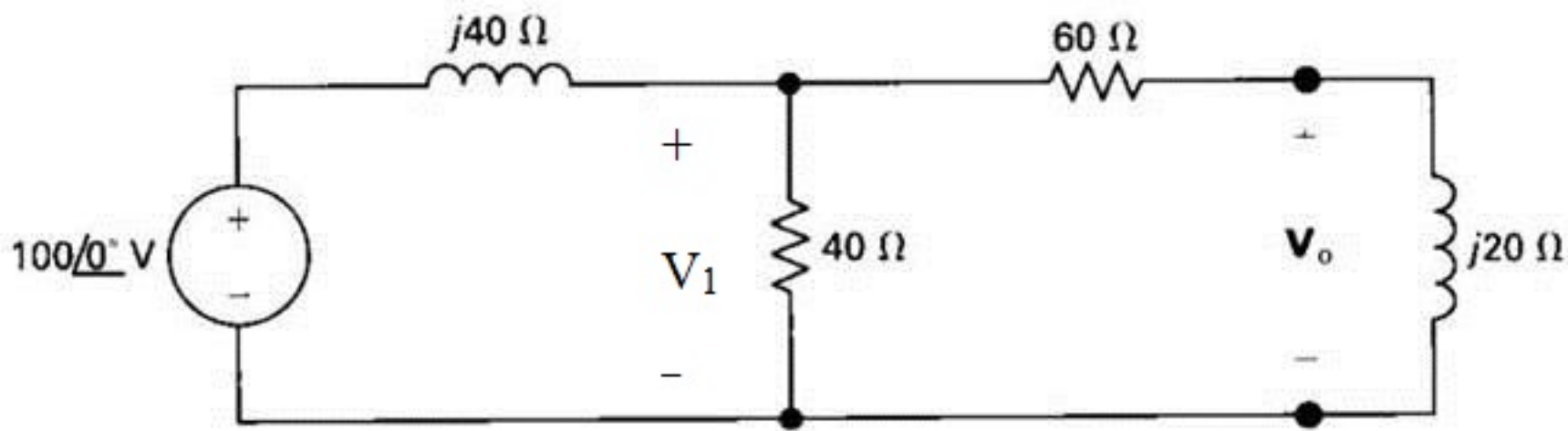

Q4a

Find the phasor voltages V_0 and V_1 . I suggest you use the Node Method.

$V_0 =$ ✓✓

at angle ✓° (Degrees) Volts

$V_1 =$ ✓

at angle ✓° (Degrees) Volts

Express your answer as a positive magnitude and then the angle in the appropriate quadrant.

Numeric Answer

$V_0 =$ 15.811 at angle 18.43° Volts

$V_1 =$ 50.0 at angle -53.13° Volts


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 15.00 out of 15.00

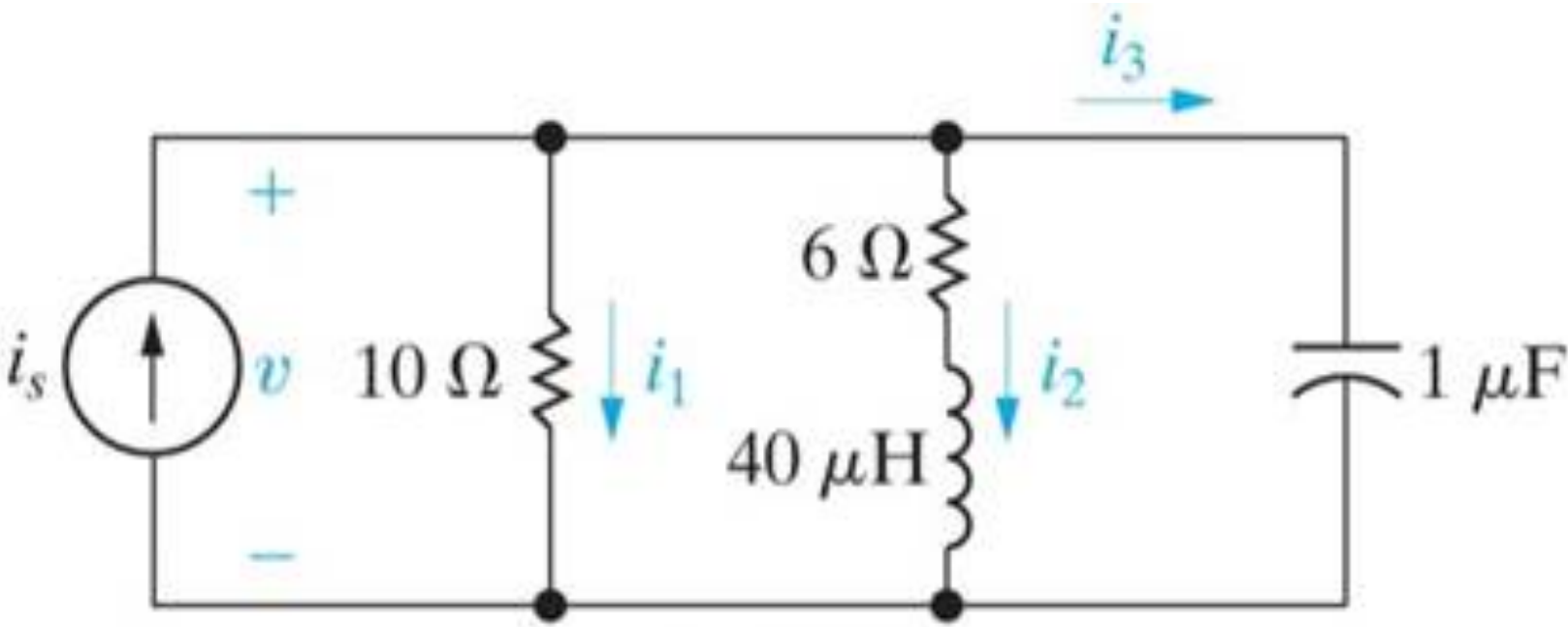

Q5a

Given:

$i_s = 20 \cos(100,000 t + 6.12^\circ)$ Amps

The equivalent admittance of the circuit is $Y_{Eq} = 0.2166$ at angle 6.12° (Degrees) Siemens

Calculate the average power absorbed/delivered by the 10 Ω (Ohm) resistor.

$P_{10\Omega} =$ ✓

W

Numeric Answer

$P_{10\Omega} = 426.2295$ W


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 10.00 out of 10.00

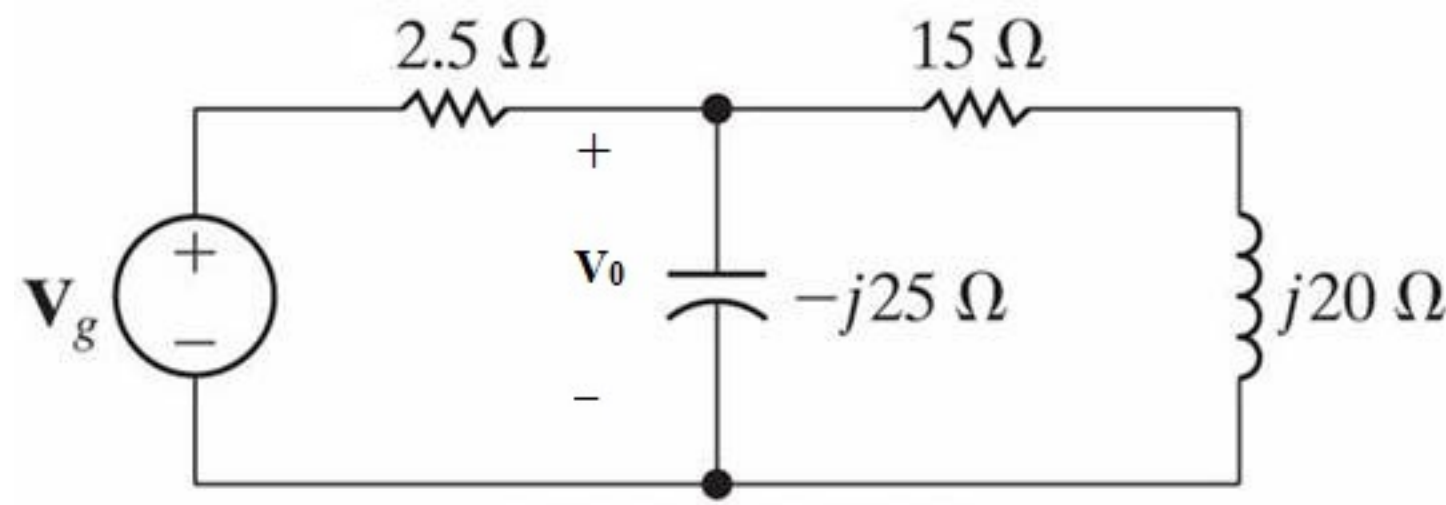

Q6c

Given:

The voltage source $V_g = 160$ at angle 0° V_{rms}
and the voltage $V_0 = 150.9165$ at angle -1.08° V_{rms} .

Find the average and reactive power for the voltage source V_g .

$S_g =$ ✓

$+j$ ✓ VA

“+” = absorbed and “-” = delivered

Numeric Answer

$S_g = -583.0605 + j 182.2064 \text{ VA}$

Correct

Marks for this submission: 0.00/10.00.

Comment:

Your answers are correct.

Due to error in answer guide the answers will be accepted a full points.

Question 7

Correct

Mark 5.00 out of 5.00

Q7a

Find the Laplace Transform of $\left\{\frac{d}{dt}\cos\omega t\right\}$

Select one:

- ☒ a. $\frac{-\omega^2}{s^2+\omega^2}$ ✓
- ☐ b. $\frac{-s^2}{s^2+\omega^2}$
- ☐ c. $\frac{1}{s^2+\omega^2}$
- ☐ d. $\frac{\omega}{s^2+\omega^2}$

Your answer is correct.

$$L\left\{\frac{d}{dt}\cos\omega t\right\}=\frac{-\omega^2}{s^2+\omega^2}$$

The correct answer is: $\frac{-\omega^2}{s^2+\omega^2}$

Correct

Marks for this submission: 5.00/5.00.

Question 8

Correct

Mark 15.00 out of 15.00

Q8a

Given $F(s)=\frac{100(s^2+69)}{(s+10)(s^2+10s+169)}=\frac{100(s^2+69)}{(s+10)(s+5-j12)(s+5+j12)}$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

f(t) = [] ✓
e ^t + ✓ e ^t cos(t + °) u(t) ✓

$$f(t)=\left[100e^{-10t}+83.33e^{-5t}\cos(12t+90^\circ)\right]u(t)$$

Correct

Marks for this submission: 15.00/15.00.

Question 9

Correct

Mark 10.00 out of 10.00

Q9c

Given: $F(s) = \frac{45(s+3)}{(s+6)(s^2+6s+25)}$ which has an inverse transform f(t).

a) Find the initial value of f(t = 0).

f(t = 0) = ✓

b) Find the final value of f(t → ∞)

f(t → ∞) = ✓

Numeric Answer

a) f(t = 0) = 0

b) f(t → ∞) = 0

Correct

Marks for this submission: 10.00/10.00.