

Started on Monday, 19 September 2016, 11:59 AM

State Finished

Completed on Wednesday, 21 September 2016, 12:19 PM


Time taken 2 days

Grade 100.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

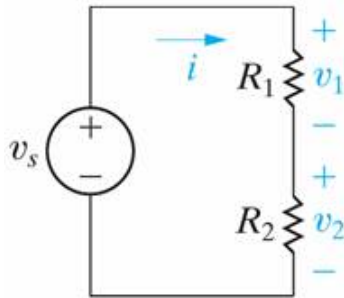

CQ3.05b

Given:

$v_s = 96$ Volts $R_1 = 715 \, \Omega$ (Ohms) $R_2 = 130 \, \Omega$ (Ohms)

Find the voltage v_2 .

Answer: 14.76



Calculated question

The correct answer is: 14.77


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

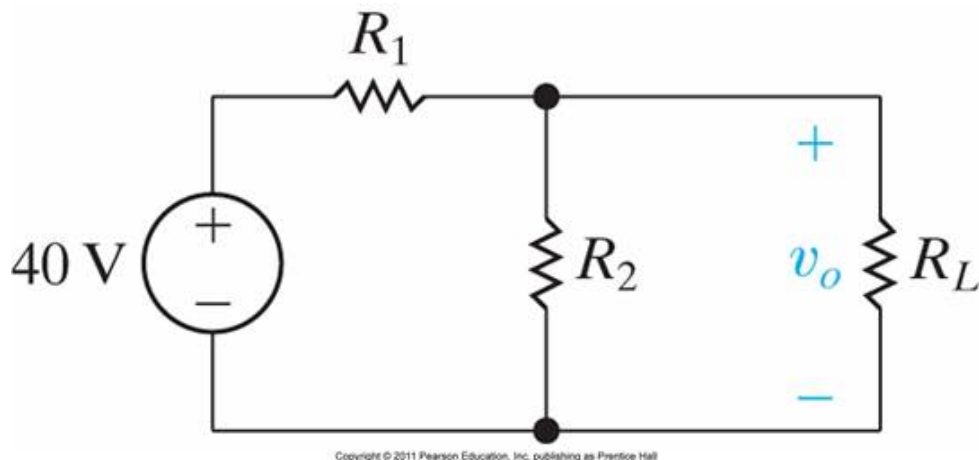

P3.16_9ed

The no-load voltage across R_2 in the voltage-divider circuit shown is 8 V. The smallest load resistor that is ever connected to the divider is 3.6 k Ω (kilo Ohm). When the divider is loaded, v_o is not to drop below 7.5V.

a) Design the divider circuit to meet the specifications just mentioned. Specify the numerical values of R_1 and R_2 when you use a single standard value for each resistor from the textbook's Appendix H. You may use up to two resistors in combination for R_1 and up to another two resistors in combination for R_2 .

$$R_1 = 1200 \text{ } \checkmark \text{ } \Omega \text{ (Ohms)} \quad R_2 = 300 \text{ } \checkmark \text{ } \Omega \text{ (Ohms)}$$

b) Assume the power ratings of commercially available resistors are 1/16, 1/8, 1/4, 1, and 2 W. What power rating would you specify?

$$P_{R1, \text{rating}} = 1 \text{ } \checkmark \text{ } \text{Watt} \quad P_{R2, \text{rating}} = .25 \text{ } \checkmark \text{ } \text{Watt}$$

Numeric Answer


(a) $R_1 = 1,200 \text{ } \Omega$ $R_2 = 303 \text{ } \Omega$
 (b) $P_{R1, \text{rating}} = 1 \text{ Watt}$ $P_{R2, \text{rating}} = 0.25 \text{ W} = \frac{1}{4} \text{ Watt}$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

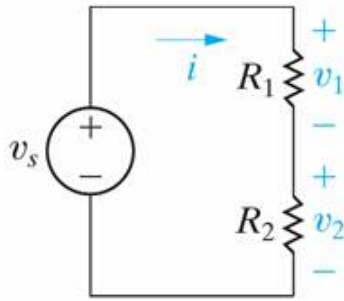Mark 10.00 out of
10.00

CQ3.05c

Given:

 $v_s = 88$ Volts $R_1 = 651 \, \Omega$ (Ohms) $R_2 = 200 \, \Omega$ (Ohms)Find the current i . $i = ??$ mA (milli A)

Answer: 103.41



Calculated question

The correct answer is: 103.41


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

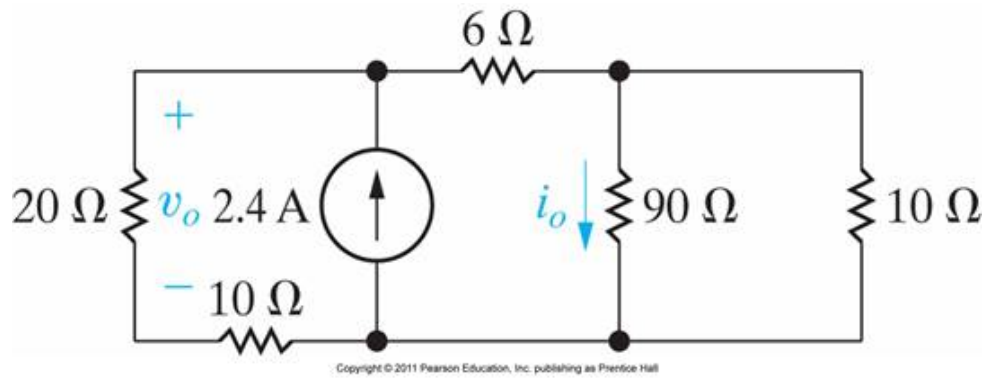

P3.11_9ed

a) Find v_o and i_o .
 $v_o = 16$ ✓ Volts $i_o = 160$ ✓ mA (milli A)
b) Find the power dissipated in the $6\ \Omega$ (Ohm) resistor.
 $P_{6\Omega} = 15.36$ ✓ Watts

c) Find the power absorbed/delivered by the current source.

 $P_{2.4A} = 57.6$ ✗ Watts


“-” = “delivering” and “+” = “absorbing”

Numeric Answera) $v_o = 16\text{ V}$ $i_o = 0.16\text{ A}$ b) $P_{6\Omega} = 15.36\text{ W}$ c) $P_{2.4A} = -57.6\text{ W}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 5

Correct

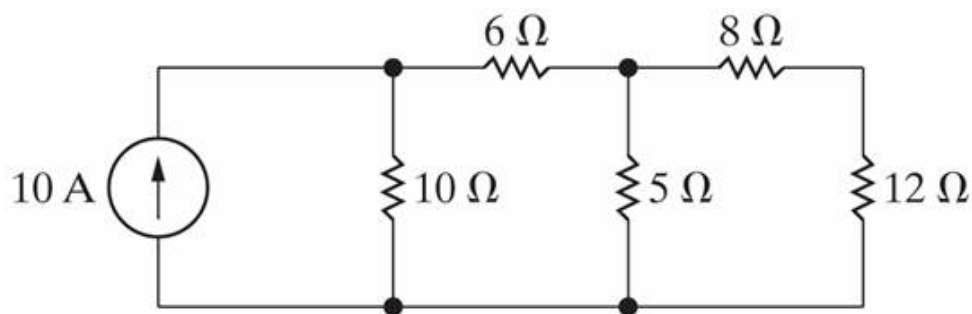Mark 10.00 out of
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P3.10_9ed

a) Find the power dissipated in the 5 Ω (Ohm) resistor.

 $P_{5\Omega} =$ ✓ Watts

b) Find the power dissipated in the 6 Ω (Ohm) resistor.

 $P_{6\Omega} =$ ✓ Watts

“-” = “delivering” and “+” = “absorbing”


Numeric Answera) $P_{5\Omega} = 80 \text{ W}$ b) $P_{6\Omega} = 150 \text{ W}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

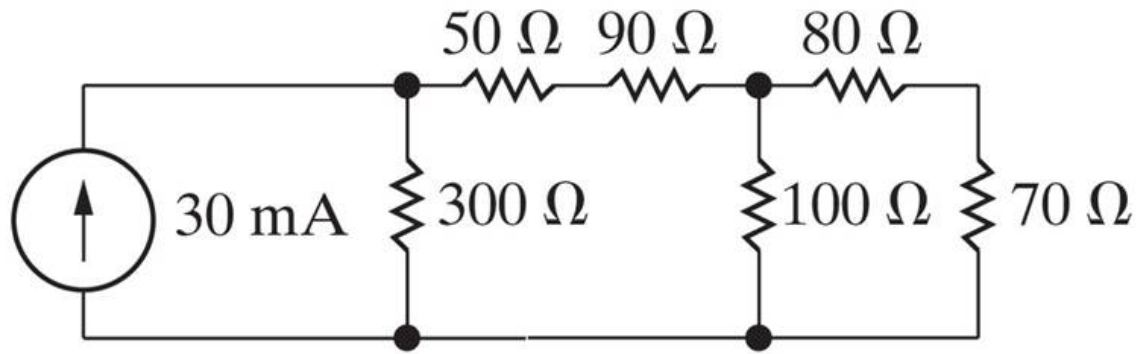

P3.24_10ed

a) Use current division to find the current in the 50 Ω (Ohm) resistor..

$$I_{50\Omega} = 18 \text{ mA}$$

b) Use $I_{50\Omega}$ result from part (a) and current division to find the current in 70 Ω (Ohm) resistor.

$$I_{70\Omega} = 7.2 \text{ mA}$$

Numeric Answer

a) $I_{50\Omega} = 18 \text{ mA}$

b) $I_{70\Omega} = 7.2 \text{ mA}$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

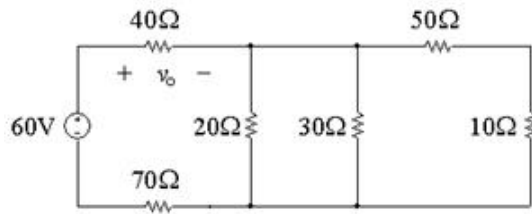

AP3.04_9ed

a) Use voltage division to determine the voltage v_o across the $40\ \Omega$ (Ohm) resistor.

$$v_o = 20 \text{ Volts}$$

b) Use v_o from part a) to determine the current through the $40\ \Omega$ (Ohm) resistor, and use this current and current division to calculate the current in the $30\ \Omega$ (Ohm) resistor.

$$I_{30\Omega} = 166.67 \text{ mA (milli A)}$$

c) How much power is absorbed by the $50\ \Omega$ (Ohm) resistor?

$$P_{50\Omega} = 347.22 \text{ mW (milli W)}$$

“-” = delivering and “+” = absorbing power

Numeric Answer

a) $v_o = 20\ \text{V}$

b) $I_{30\Omega} = 166.67\ \text{mA}$


c) $P_{50\Omega} = 347.22\ \text{mW}$

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

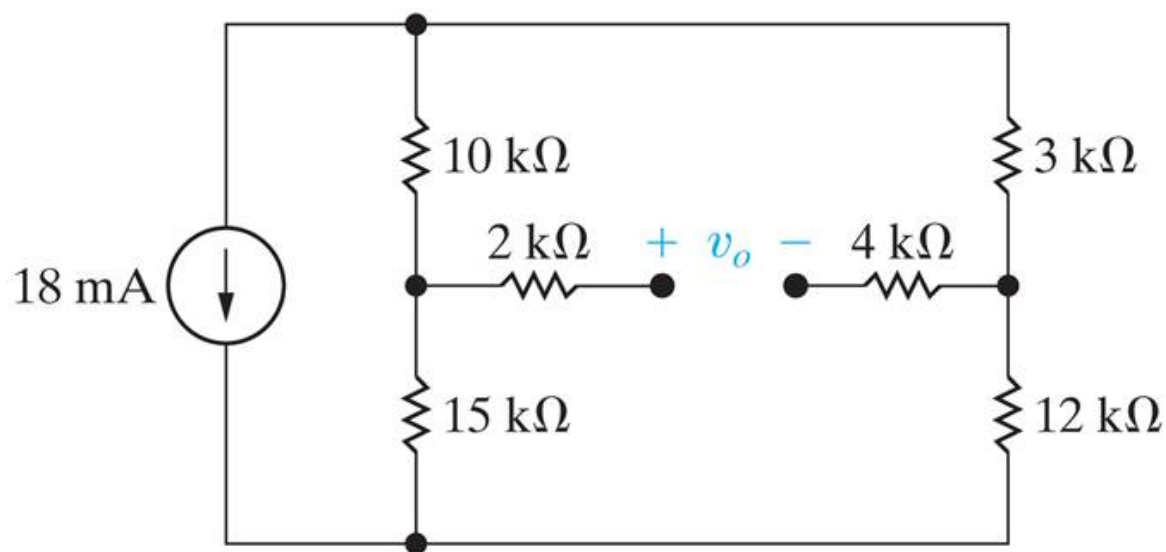Mark 10.00 out of
10.00

Copyright ©2015 Pearson Education, All Rights Reserved

P3.29_10ed

Find the voltage v_o using voltage and/or current division.

Answer: 33.75

**Numeric Answer**

$$v_o = 33.75 \text{ V}$$

The correct answer is: 33.75


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

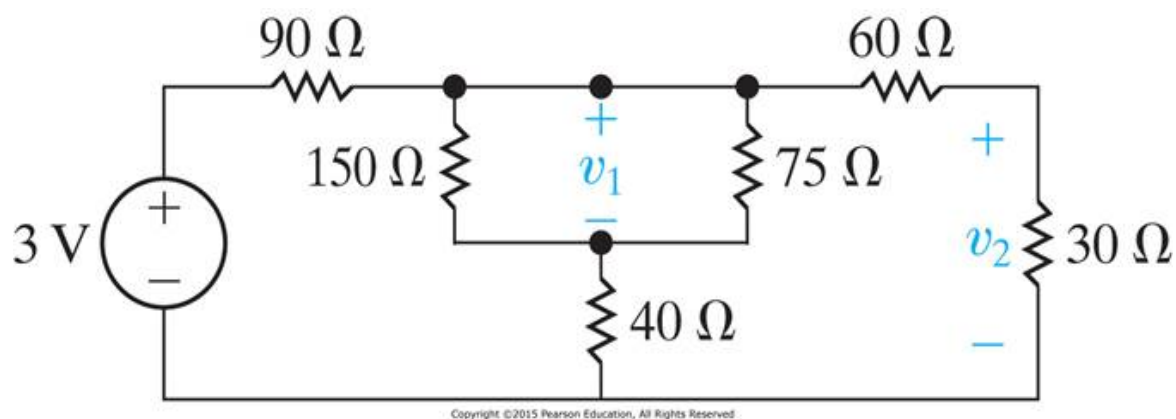

P3.30_10ed


Find the voltage v_1 and v_2 using voltage and/or current division. $v_1 =$ ✓ Volts $v_2 =$ ✓ Volts**Numeric Answer** $v_1 = 5/9 \text{ V} = 0.556 \text{ Volts}$ $v_2 = 3/9 \text{ V} = 0.333 \text{ Volts}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

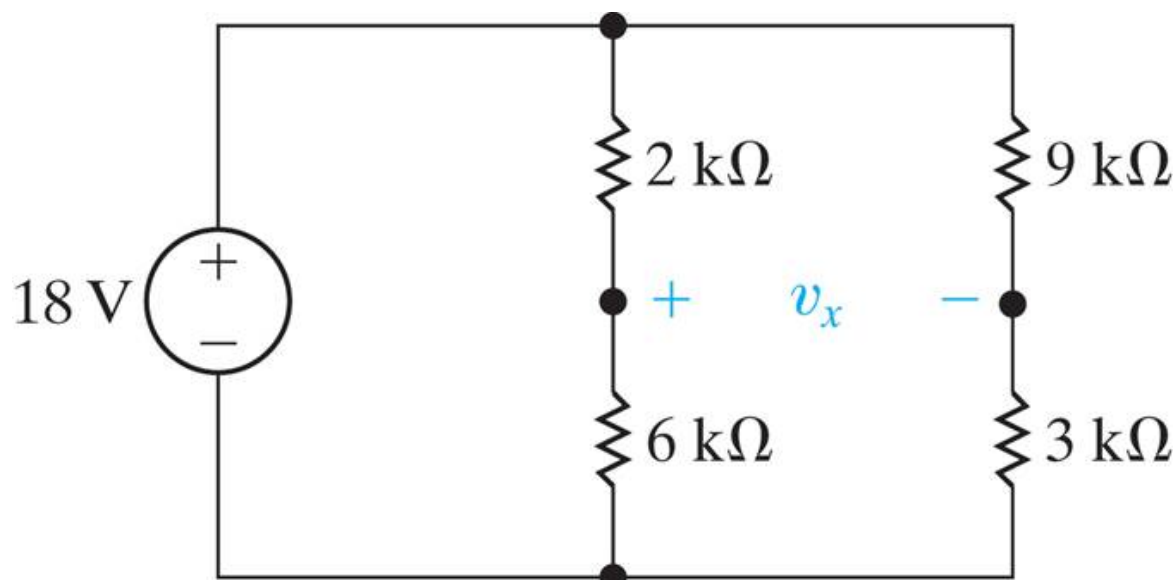

P3.28_10ed

Find the voltage v_x using voltage and/or current division.

Answer: 9

**Numeric Answer**

$$v_x = 9 \text{ V}$$

The correct answer is: 9

Correct

Marks for this submission: 10.00/10.00.