


[Home](#) ► [My courses](#) ► [EEE117-2017S-Tatro](#) ► [Homework](#) ► [Homework 11 - Chapter 14](#)

<b>Started on</b>	Sunday, 16 April 2017, 9:20 AM
<b>State</b>	Finished
<b>Completed on</b>	Sunday, 16 April 2017, 5:42 PM
<b>Time taken</b>	8 hours 21 mins
<b>Grade</b>	<b>100.00</b> out of 100.00

## Question 1

Correct

Mark 20.00 out of 20.00

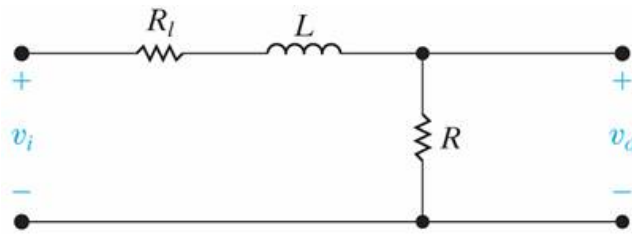

P14.3\_9ed

A resistor  $R_l$  is added in series with the inductor in this circuit.Given:  $R_l = 75 \, \Omega$  (Ohm)  $L = 10 \, \text{mH}$  (mill H)  $R = 127 \, \Omega$  (Ohm)a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \frac{12700}{s + 20200}$$

$$/ (s + 20200)$$

b) At what frequency will the magnitude of  $H(j\omega)$  be maximum?

$$\omega_{H,\max} = 0$$

rad/sec

c) What is maximum value of the magnitude of  $H(j\omega)$ ?

$$H(j\omega)_{\max} = 0.63$$

d) At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by square root of 2?

$$\omega_{H,\max,\text{sqrt}(2)} = 20200$$

rad/sec

e) Find  $\omega_c$  (omega\_c).

$$\omega_c = 20200$$

rad/sec

Now examine the transfer function magnitude and phase as the frequency varies.

f) Find  $H(j\omega = 0)$  in polar form..

$$H(j\omega = 0) = \text{Mag } 0.63$$

$$\text{at angle } 0^\circ \text{ (Degrees)}$$

g) Find  $H(j\omega = 0.3\omega_c)$  in polar form.

$$H(j\omega = 0.3\omega_c) = \text{Mag } 0.602$$

$$\text{at angle } -16.7^\circ \text{ (Degrees)}$$

h) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } 0.44$$

$$\text{at angle } -45^\circ \text{ (Degrees)}$$

i) Find  $H(j\omega = 3\omega_c)$  in polar form.

$$H(j\omega = 3\omega_c) = \text{Mag } 0.2$$

$$\text{at angle } -71.6^\circ \text{ (Degrees)}$$

**Numeric Answer**

a)  $\frac{V_o}{V_i} = \frac{12,700}{s+20,200}$

b)  $\omega_{H,max} = 0 \text{ rad/sec}$

c)  $H(j\omega)_{max} = 0.6287$

d)  $\omega_{H,max,sqrt(2)} = 20,200 \text{ rad/sec}$

e)  $\omega_c = 20,200 \text{ rad/sec}$

f)  $H(j\omega = 0) = 0.6287$

g)  $H(j\omega = 0.3\omega_c) = 0.6022 \angle -16.70^\circ$

h)  $H(j\omega = \omega_c) = 0.4446 \angle -45^\circ$

i)  $H(j\omega = 3\omega_c) = 0.1988 \angle -71.57^\circ$


**Correct**

Marks for this submission: 20.00/20.00.

**Question 2**

Correct

Mark 20.00 out of 20.00

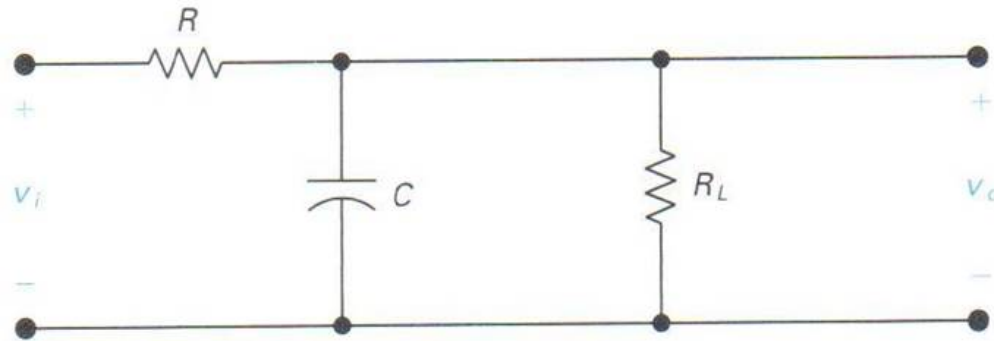

P14.3\_6ed

A resistor  $R_L$  is connected in parallel with the capacitor in this circuit. The circuit thus becomes a loaded low-pass filter.

Given:  $R = 20 \text{ k}\Omega$  (kilo Ohm)  $C = 4 \text{ nF}$   $R_L = 300 \text{ k}\Omega$  (kilo Ohm)

a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \frac{12500}{s + 13373.33}$$

$$/ (s + 13373.33)$$

b) Find  $\omega_c$  (omega\_c)

$$\omega_c = 13333.3$$

rad/sec

Now examine the transfer function magnitude and phase as the frequency varies.

c) Find  $H(j0)$

$$H(j0) = 0.94$$

d) Find  $H(j\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = \omega_c$

$$H(j\omega_c) = \text{Mag } 0.66$$

$$\text{Angle } -45$$

e) Find  $H(j0.2\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 0.2 \omega_c$

$$H(j0.2\omega_c) = \text{Mag } 0.92$$

$$\text{Angle } -11.31$$

f) Find  $H(j8\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 8\omega_c$

$$H(j8\omega_c) = \text{Mag } 0.116$$

$$\text{Angle } -82.9$$

**Numeric Answer**

a)  $f = 50 \text{ Hz}$

b)  $\omega_c = 13,333.3 \text{ rad/sec}$

c)  $H(j0) = 0.9375$

d)  $H(j\omega_c) = 0.6629 \angle -45^\circ$

e)  $H(j0.2\omega_c) = 0.9193 \angle -11.31^\circ$  This is an exact answer to the passband region.

f)  $H(j8\omega_c) = 0.1163 \angle -82.87^\circ$  This is an exact answer to the stopband region.


**Correct**

Marks for this submission: 20.00/20.00.

## Question 3

Correct

Mark 20.00 out of 20.00

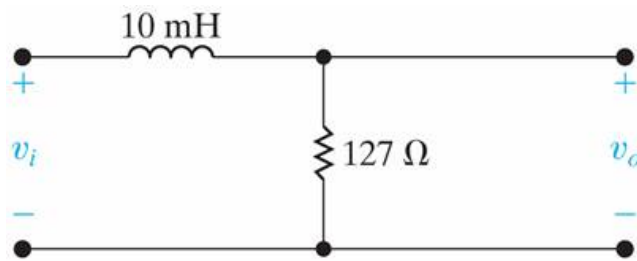

P14.1\_9ed

a) Find the cutoff frequency in hertz.

$$f_c = 2021.26 \quad \checkmark$$

Hz

b) Find  $H(j\omega = 0)$  in polar form.

$$H(j\omega = 0) = \text{Mag } 1 \quad \checkmark$$

at angle  $0 \quad \checkmark$  ° (Degrees)

Now examine the output magnitude and phase as the input frequency varies.

c) Find  $H(j\omega = 0.2\omega_c)$  in polar form..

$$H(j\omega = 0.2\omega_c) = \text{Mag } .98 \quad \checkmark$$

at angle  $-11.31 \quad \checkmark$  ° (Degrees)d) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } .71 \quad \checkmark$$

at angle  $-45 \quad \checkmark$  ° (Degrees)e) Find  $H(j\omega = 5\omega_c)$  in polar form.

$$H(j\omega = 5\omega_c) = \text{Mag } .196 \quad \checkmark$$

at angle  $-78.69 \quad \checkmark$  ° (Degrees)Now given  $v_i(t) = 10 \cos(\omega t)$  V. Write the steady-state expression for  $v_o$  for:f)  $\omega = 0.2\omega_c$ 

$$v_o(t) = 9.81 \quad \checkmark$$

cos( $2540 \quad \checkmark$  t +  $-11.31 \quad \checkmark$  °) Voltsg)  $\omega = \omega_c$ 

$$v_o(t) = 7.07 \quad \checkmark$$

cos( $12700 \quad \checkmark$  t +  $-45 \quad \checkmark$  °) Voltsh)  $\omega = 5\omega_c$ 

$$v_o(t) = 1.96 \quad \checkmark$$

cos( $63500 \quad \checkmark$  t +  $-78.69 \quad \checkmark$  °) Voltsa)  $f_c = 2021.27$  Hzb)  $H(j\omega = 0) = 1 \angle 0^\circ$

c)  $H(j\omega = 0.2\omega_c) = 0.981 \angle -11.31^\circ$

d)  $H(j\omega = \omega_c) = 0.707 \angle -45^\circ$

e)  $H(j\omega = 5\omega_c) = 0.196 \angle -78.69^\circ$

f) For  $\omega = 0.2\omega_c$ ,  $v_o(t) = 9.81 \cos(2,540 t - 11.31^\circ)$  Volts

g) For  $\omega = \omega_c$ ,  $v_o(t) = 7.07 \cos(12,700 t - 45^\circ)$  Volts

h) For  $\omega = 5\omega_c$ ,  $v_o(t) = 1.96 \cos(63,500 t - 78.69^\circ)$  Volts


**Correct**

Marks for this submission: 20.00/20.00.

## Question 4

Correct

Mark 20.00 out of 20.00

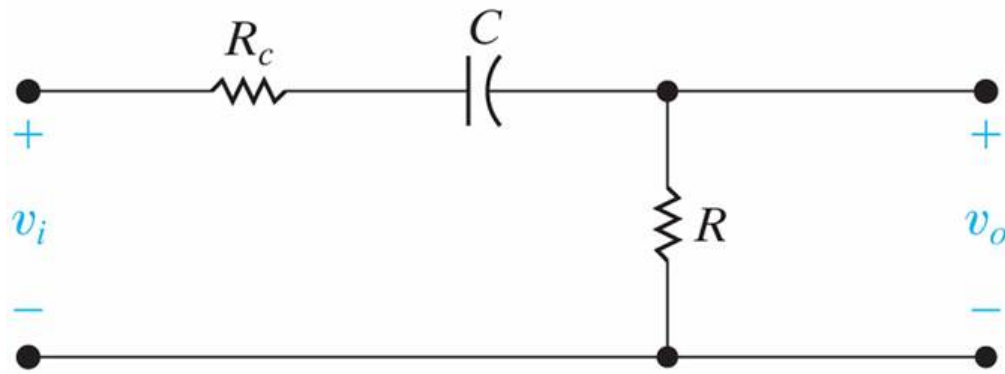

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P14.11\_9ed

Given:  $R_c = 12.5 \text{ k}\Omega$  (kilo Ohm)  $C = 5 \text{ nF}$   $R = 50 \text{ k}\Omega$  (kilo Ohm)a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$$f_c = 509.3 \checkmark$$

Hz

b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.57 \checkmark$$

at angle  $45 \checkmark$  ° (degrees)

$$H(j\omega = 0.2\omega_c) = 0.16 \checkmark$$

at angle  $78.69 \checkmark$  °

$$H(j\omega = 5\omega_c) = 0.78 \checkmark$$

at angle  $11.31 \checkmark$  °c) If  $v_i(t) = 500 \cos(\omega t)$  mV (milli V), write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 282.85 \checkmark$$

 $\cos(\omega t + 45 \checkmark)^\circ$  mV (milli V)

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 78.45 \checkmark$$

 $\cos(\omega t + 78.69 \checkmark)^\circ$  mV (milli V)

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 392.25 \checkmark$$

 $\cos(\omega t + 11.31 \checkmark)^\circ$  mV (milli V)a)  $f_c = 509.2958 \text{ Hz}$ b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.5657 \text{ at angle } 45^\circ$$

$$H(j\omega = 0.2\omega_c) = 0.1569 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.7845 \text{ at angle } 11.31^\circ$$

c) If  $v_i(t) = 500 \cos(\omega t)$ , write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 282.850 \cos(\omega t + 45^\circ) \text{ mV}$$



For  $\omega = 0.2\omega_c$ ,  $v_o(t) = 78.450 \cos(\omega t + 78.69^\circ) \text{ mV}$

For  $\omega = 5\omega_c$ ,  $v_o(t) = 392.250 \cos(\omega t + 11.31^\circ) \text{ mV}$


**Correct**

Marks for this submission: 20.00/20.00.

## Question 5

Correct

Mark 20.00 out of 20.00

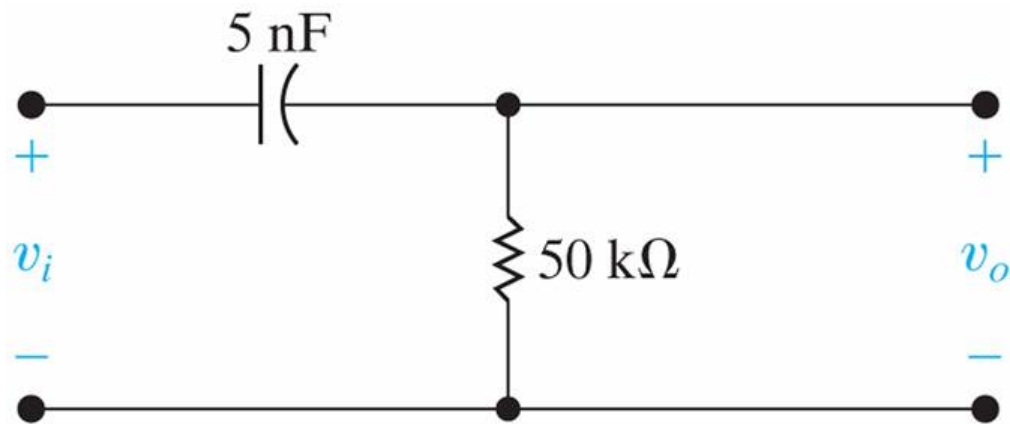

P14.10\_9ed

a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$$f_c = 636.62 \checkmark$$

Hz

b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.71 \checkmark$$

at angle  $45 \checkmark$  ° (degrees)

$$H(j\omega = 0.2\omega_c) = 0.2 \checkmark$$

at angle  $78.69 \checkmark$  °

$$H(j\omega = 5\omega_c) = 0.98 \checkmark$$

at angle  $11.31 \checkmark$  °c) If  $v_i(t) = 500 \cos(\omega t)$  mV (milli V), write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353.55 \checkmark$$

 $\cos(\omega t + 45 \checkmark)^\circ$  mV (milli V)

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 98.1 \checkmark$$

 $\cos(\omega t + 78.7 \checkmark)^\circ$  mV (milli V)

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 490.3 \checkmark$$

 $\cos(\omega t + 11.31 \checkmark)^\circ$  mV (milli V)a)  $f_c = 636.6198$  Hzb) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.7071 \text{ at angle } 45^\circ$$

$$H(j\omega = 0.2\omega_c) = 0.1961 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.9806 \text{ at angle } 11.31^\circ$$

c) If  $v_i(t) = 500 \cos(\omega t)$ , write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353.550 \cos(\omega t + 45^\circ) \text{ mV}$$

For  $\omega = 0.2\omega_c$ ,  $v_o(t) = 98.050 \cos(\omega t + 78.69^\circ)$  mV

For  $\omega = 5\omega_c$ ,  $v_o(t) = 490.30 \cos(\omega t + 11.31^\circ)$  mV

**Correct**

Marks for this submission: 20.00/20.00.