

Started on Sunday, 23 October 2016, 3:34 PM

State Finished

Completed on Sunday, 23 October 2016, 3:36 PM


Time taken 1 min 32 secs

Grade 90.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

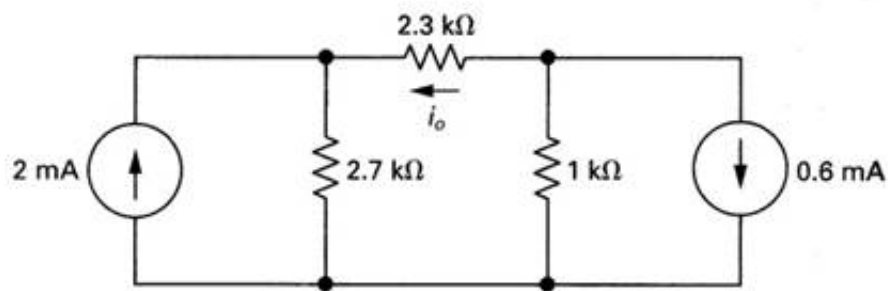

P4.52_6ed

Use source transformations to:

a) Use Find the current i_o through the $2.3 \text{ k}\Omega$ (kilo Ohm) resistor.

$i_o = \{-1.020|-0.980$ ☒ mA (milli Amp)

b) Find the power absorbed/delivered by the 0.6 mA current source.

$P_{0.6\text{mA}} =$ ☒ μW (micro Watt)

Numeric Answers

a) $i_o = -1.0 \text{ mA}$


b) $P_{0.6\text{mA}} = 240 \text{ mW}$ (micro Watt) absorbing

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

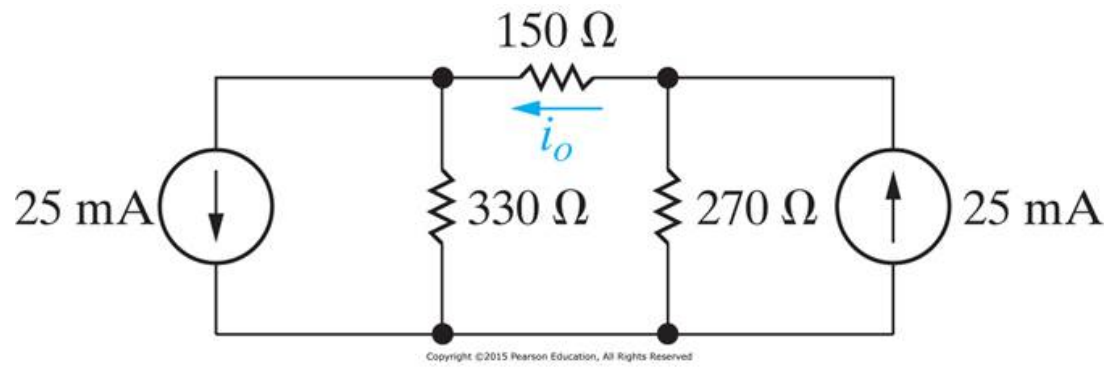Mark 10.00 out of
10.00

P4.61_10ed


Use source transformations to find the current i_o . $i_o =$  mA (milli Amp)**Numeric Answer** $i_o = 20 \text{ mA}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

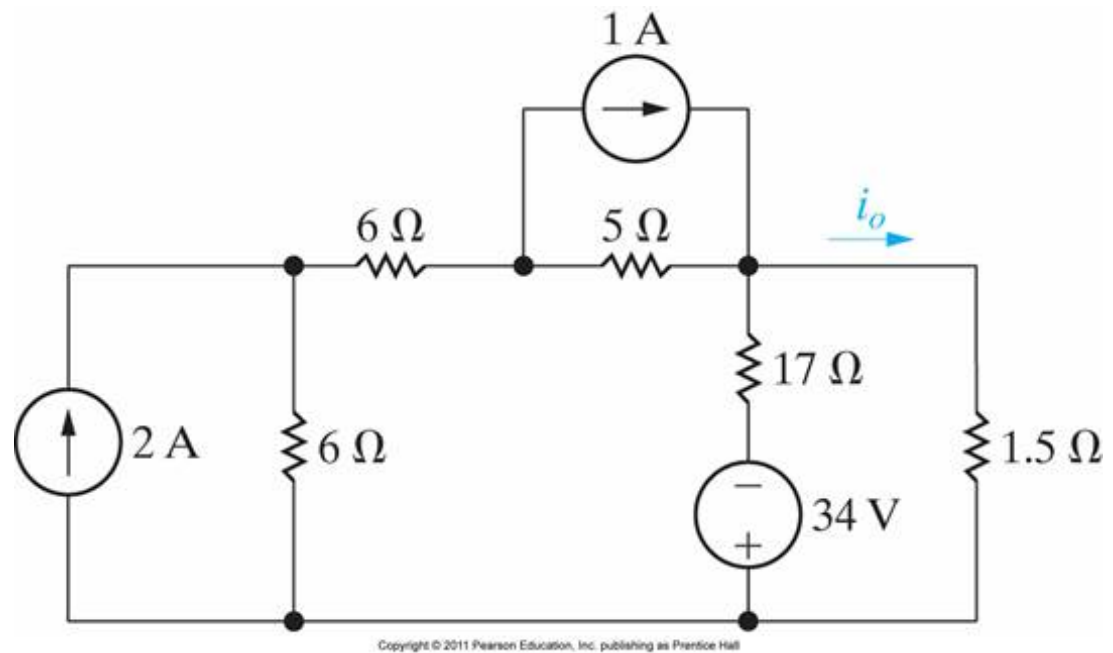

P4.60_9ed

Use source transformations to find the current i_o .

$$i_o = \boxed{-0.85} \checkmark \text{ A}$$

Numeric Answer

$$i_o = -0.85 \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

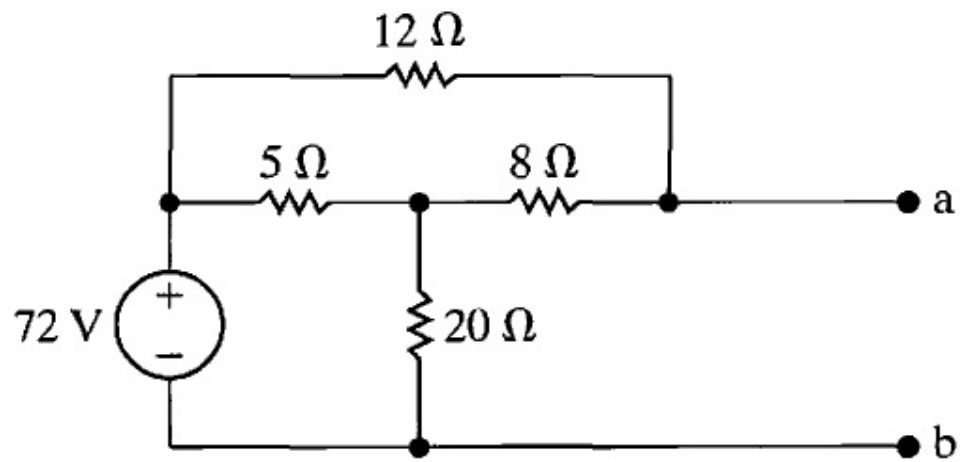

AP4.16_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown

$$V_{Th} = 64.8 \text{ V}$$

$$R_{Th} = 6 \text{ } \Omega \text{ (Ohms)}$$

Numeric Answer

$$V_{Th} = 64.8 \text{ V}$$


$$R_{Th} = 6 \text{ } \Omega$$

Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

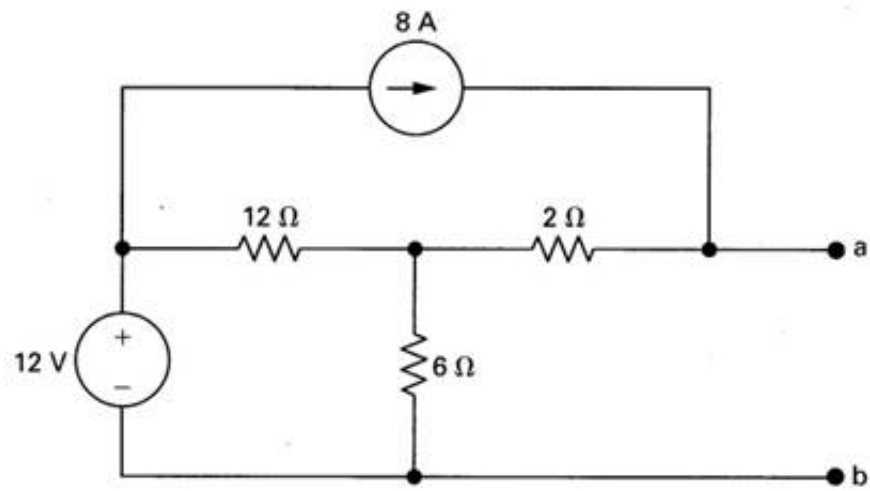Mark 10.00 out of
10.00

P4.59_6ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 52 \text{ V}$$

$$R_{Th} = 6 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{Th} = 52 \text{ V}$$


$$R_{Th} = 6 \text{ } \Omega \text{ (Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 6

Incorrect

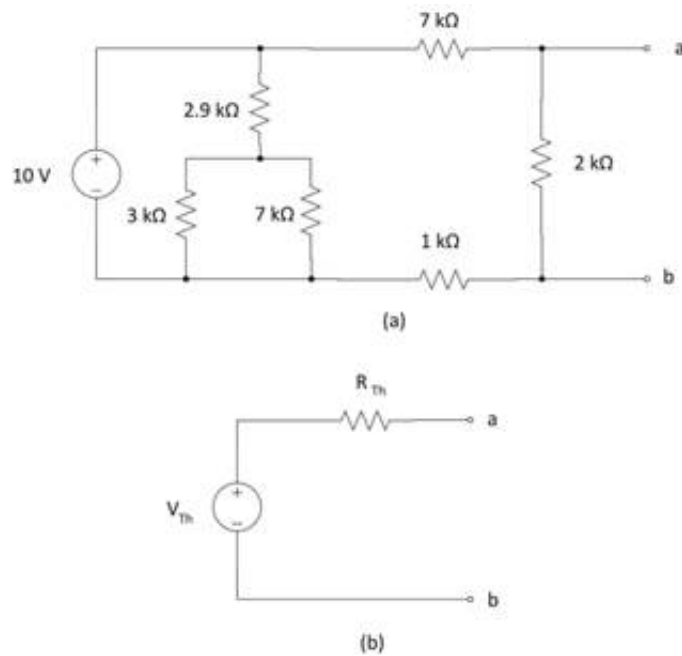Mark 0.00 out of
10.00

AS4-02

The circuit in figure (a) is simplified to its Thévenin equivalent shown in (b).

Find the numerical values for V_{Th} and R_{Th}

$$V_{Th} = 10 \text{ V}$$

$$R_{Th} = 0.57 \text{ k}\Omega \text{ (kilo Ohm)}$$

Numeric Answer

$$V_{Th} = 2 \text{ V}$$

$$R_{Th} = 1.6 \text{ k}\Omega$$


Incorrect

Marks for this submission: 0.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

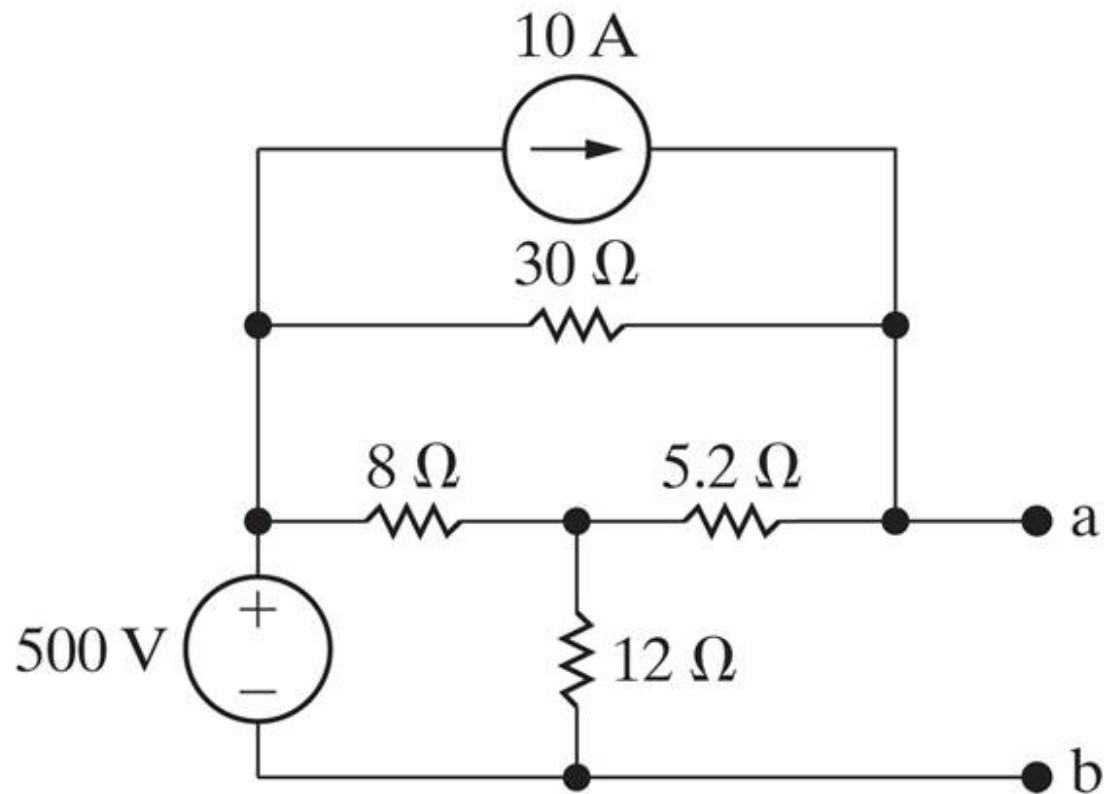

Copyright ©2015 Pearson Education, All Rights Reserved

P4.67_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 425 \text{ V}$$

$$R_{Th} = 7.5 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{Th} = 425 \text{ V}$$


$$R_{Th} = 7.5 \text{ } \Omega \text{ (Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

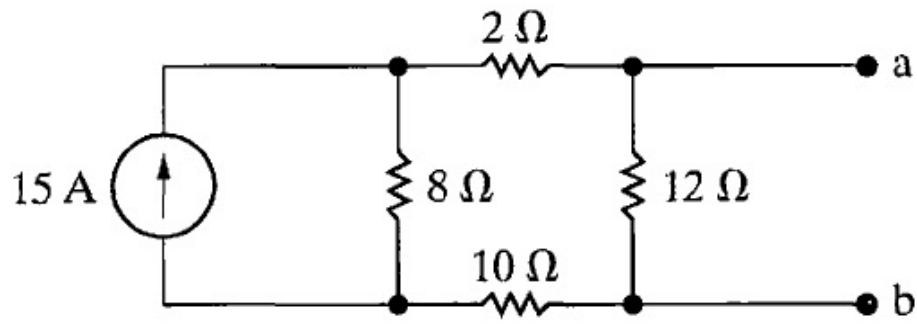Mark 10.00 out of
10.00

AP4.17_9ed

Find the Norton equivalent circuit with respect to the terminals a,b for the circuit.

$$I_N = 6 \text{ A (current directed toward terminal a)}$$

$$R_N = R_{Th} = 7.5\ \Omega \text{ (Ohm)}$$

Numeric Answer

$$I_N = 6\text{ A}$$


$$R_{Th} = 7.5\ \Omega$$

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

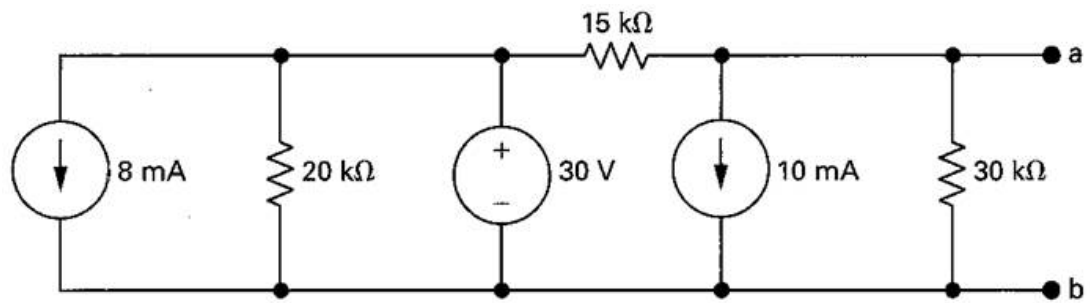Mark 10.00 out of
10.00

P4.62_6ed

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit. The Norton equivalent current should “point up”.

$$I_N = -8 \text{ mA (milli Amp)}$$

$$R_{Th} = 10 \text{ k}\Omega \text{ (kilo Ohm)}$$

Numeric Answer

$$I_N = -8 \text{ mA}$$

$$R_{Th} = 10 \text{ k}\Omega \text{ (Ohm)}$$



Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of
10.00

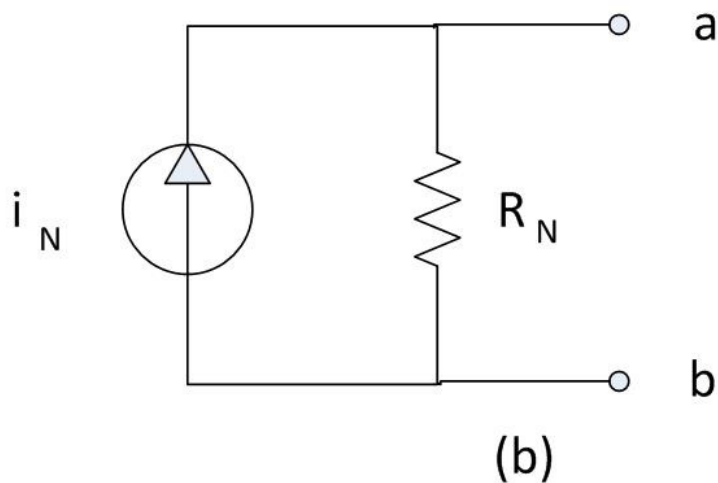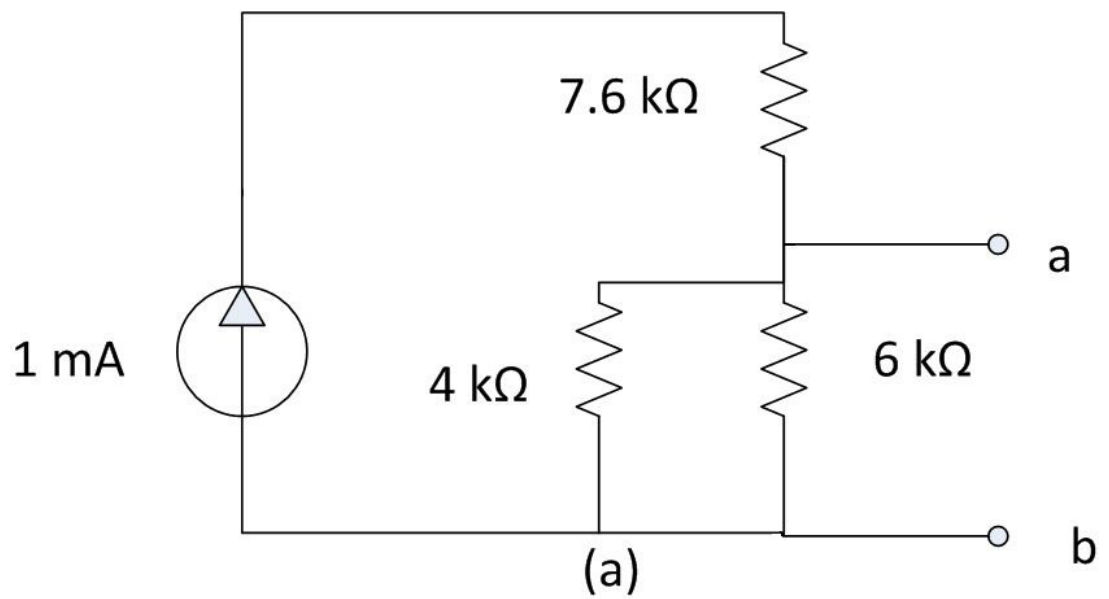

AS4-01

The circuit in figure (a) is simplified to its Norton equivalent shown in (b).

Find the numerical values for I_N and R_N .

$I_N =$ ☒ mA (milli Amp)

$R_N = R_{Th} =$ ☒ kΩ (kilo Ohm)

Numeric Answer

$I_N = 1 \text{ mA}$

$R_N = 2.4 \text{ kΩ}$

Correct

Marks for this submission: 10.00/10.00.

