

Started on Wednesday, 26 October 2016, 12:13 PM

State Finished

Completed on Sunday, 30 October 2016, 4:32 PM


Time taken 4 days 4 hours

Grade 94.50 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

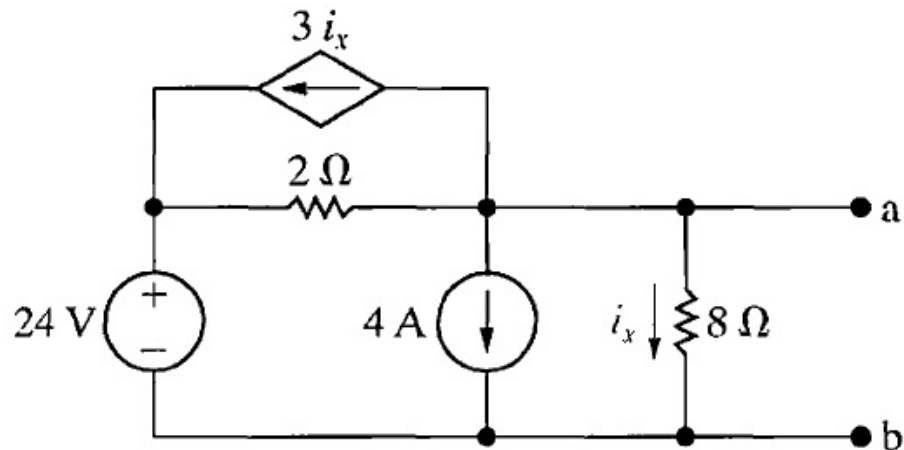

AP4.19_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown

$V_{Th} =$ \checkmark V

$R_{Th} =$ \checkmark Ω (Ohm)

Numeric Answer

$V_{Th} = 8$ V


$R_{Th} = 1$ Ω

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

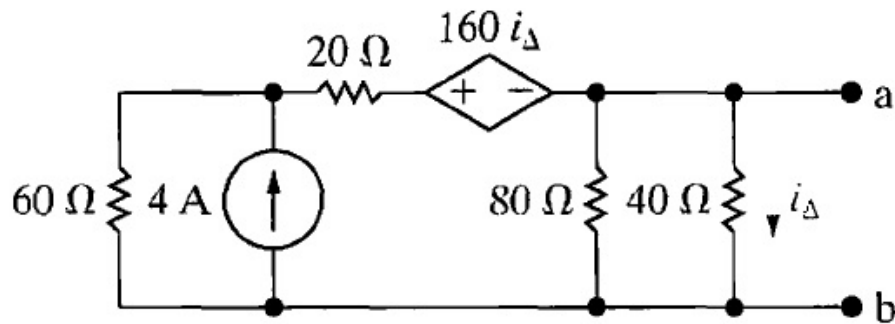Mark 10.00 out of
10.00

AP4.20_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Define the voltage at the left-most node as v , and write two nodal equations with V_{Th} as the right node voltage.

$$V_{Th} = \boxed{30} \checkmark \text{ V}$$

$$R_{Th} = \boxed{10} \checkmark \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{Th} = 30 \text{ V}$$


$$R_{Th} = 10 \text{ } \Omega$$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

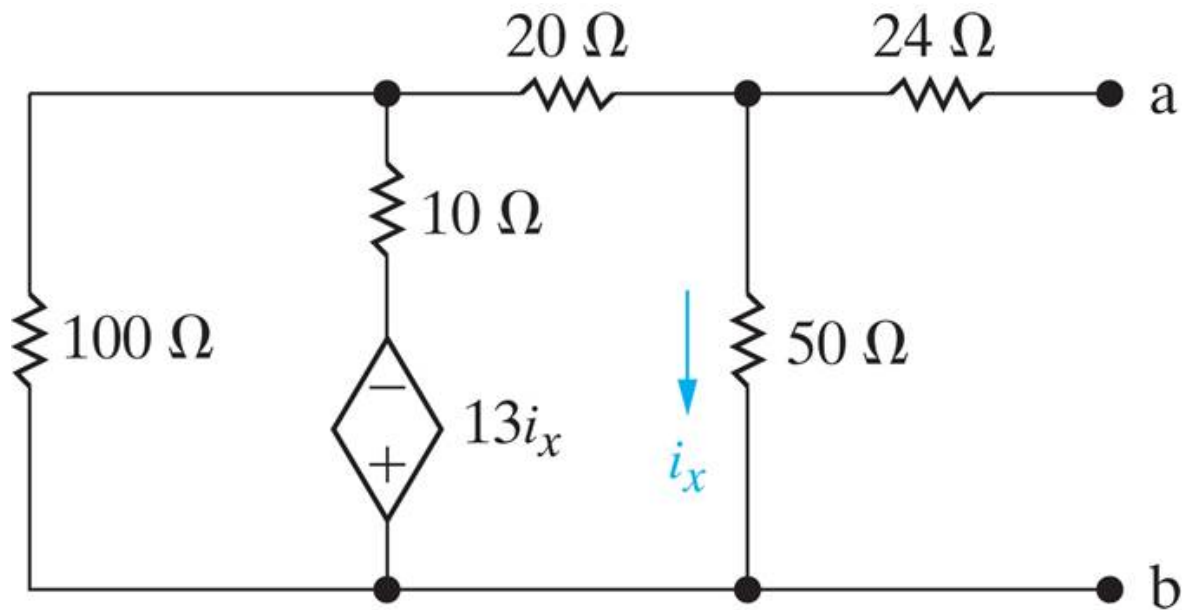Mark 10.00 out of
10.00

Copyright ©2015 Pearson Education, All Rights Reserved

P4.80_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Note that there are no independent sources in this circuit! You will have to provide an excitation to get a response.

$$V_{Th} = 0 \text{ V}$$

$$R_{Th} = 40 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{Th} = 0 \text{ V}$$

$$R_{Th} = 40 \text{ } \Omega$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Partially correct

Mark 5.00 out of 10.00

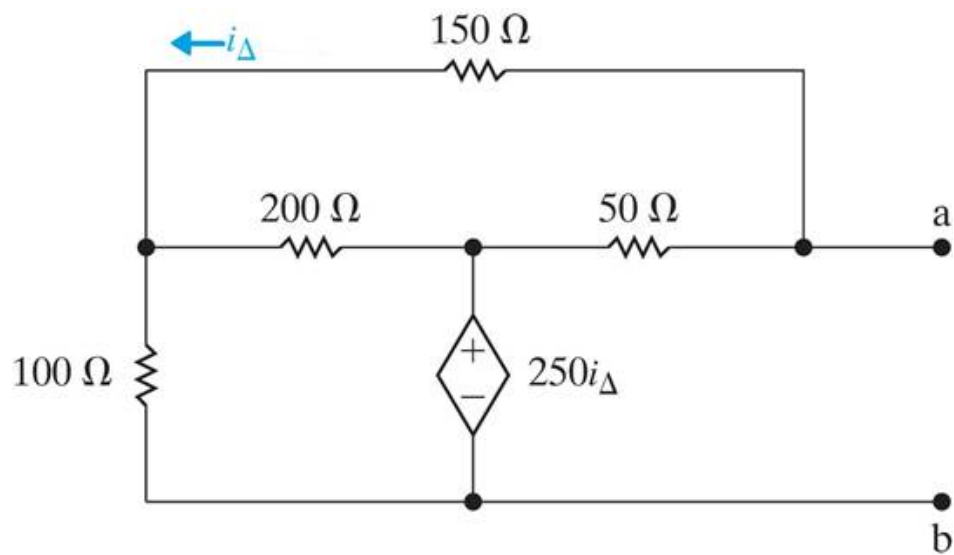

Copyright © 2015 Pearson Education, All Rights Reserved

P4.79_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Note that there are no independent sources in this circuit! You will have to provide an excitation to get a response.

$$V_{Th} = 0 \text{ V}$$

$$R_{Th} = 0 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{Th} = 0 \text{ V}$$

$$R_{Th} = 150.0 \text{ } \Omega$$


Partially correct

Marks for this submission: 5.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

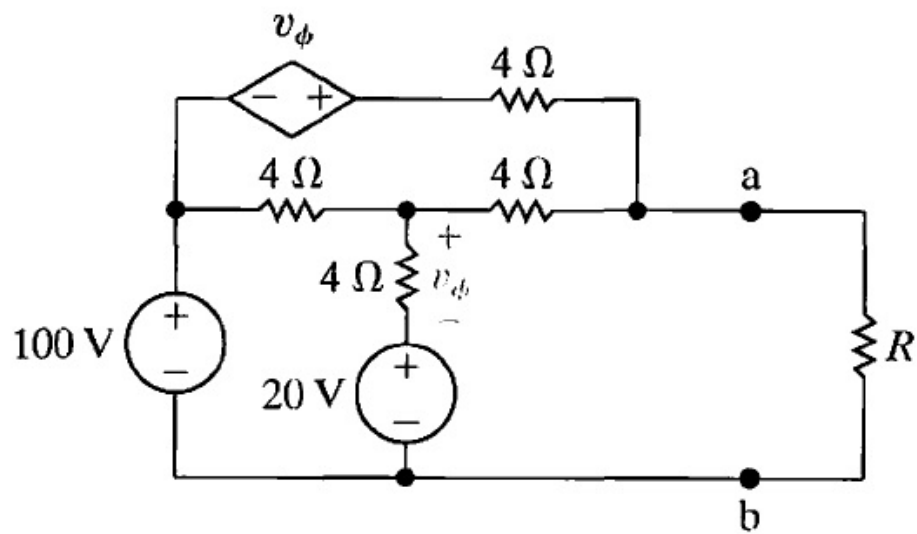

AP4.21_9ed


a) Find the value of R that enable the circuit to deliver maximum power to the terminals a,b $R =$ \checkmark Ω (Ohm)b) Find the maximum power delivered to R $P_R =$ \checkmark W**Numeric Answer** $R = 3 \Omega$ $P_R = 1,200 \text{ W}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 9.50 out of 10.00

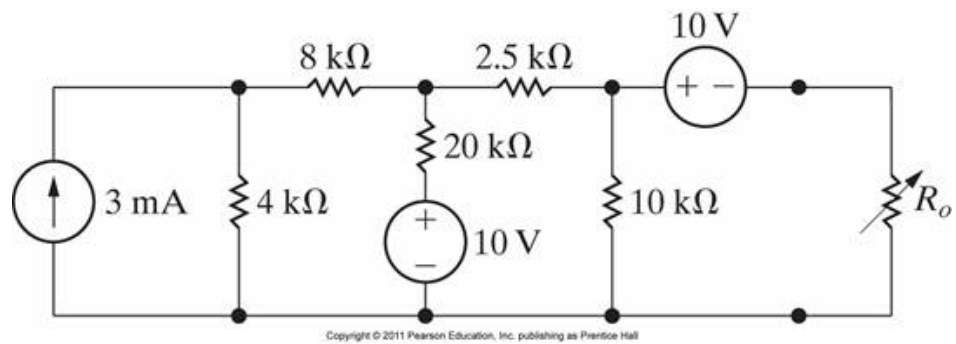

P4.79_9ed

The variable resistor in the circuit is adjusted for maximum power transfer to R_o .

a) Find the value of R_o .

$R_o = \{4.90|5.10 \text{ } \boxed{5} \text{ } \checkmark \text{ } \text{k}\Omega \text{ (kilo Ohm)}$

b) Find the maximum power that can be delivered to R_o .

$P_{\max} = \boxed{957} \text{ } \checkmark \text{ } \mu\text{W (micro W)}$

Numeric Answer

$R = 5\text{k}\Omega \text{ (kilo Ohm)}$

$P_{R_o, \max} = 957.03 \mu\text{W (microwatt)}$


Correct

Marks for this submission: 10.00/10.00. Accounting for previous tries, this gives **9.50/10.00**.

Question 7

Correct

Mark 10.00 out of 10.00

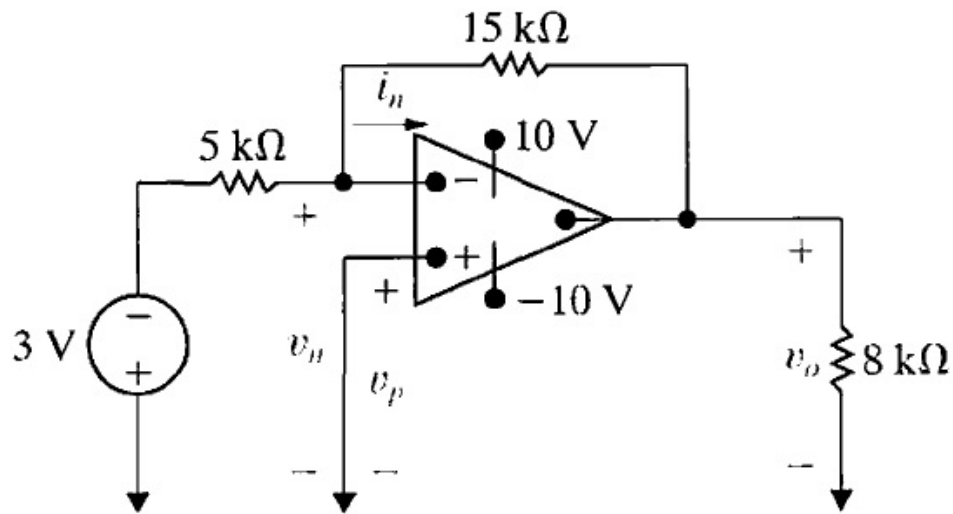

P5.01_9ed

Assume the op amp is ideal.


a) What is the value of the current i_n ? $i_n = 0$ ✓ Ab) What is the value of v_n ? $v_n = 0$ ✓ Vc) Calculate v_o in this circuit. $v_o = 9$ ✓ V**Numeric Answer**a) $i_n = 0$ (zero)b) $v_n = 0$ (zero) Voltsc) $v_o = 9V$ **Correct**

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

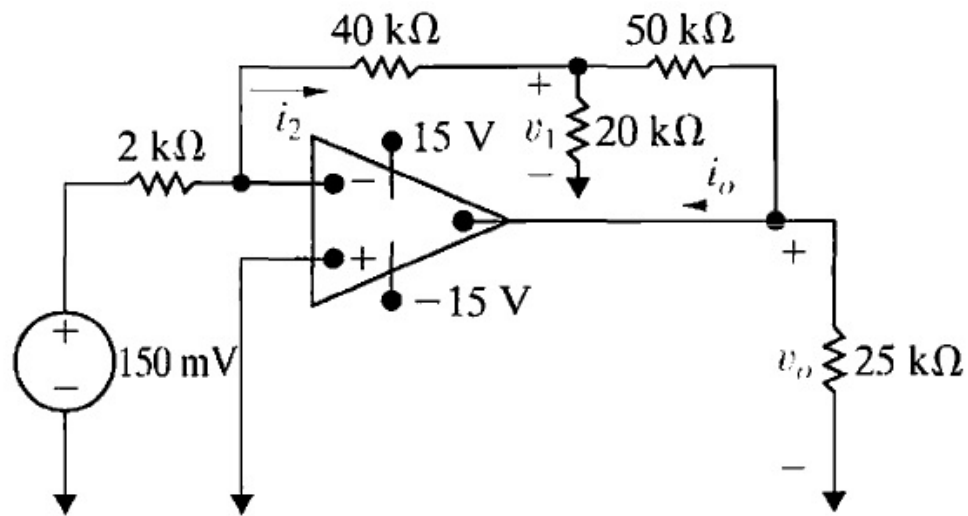

P5.06_9ed

Assume the op amp is ideal.

Calculate v_1 , v_o , i_2 , and i_o .

$$v_1 = -3 \text{ V}$$

$$v_o = -14.25 \text{ V}$$

$$i_2 = 75 \text{ } \mu\text{A (micro Amp)}$$

$$i_o = 795 \text{ } \mu\text{A (micro Amp)}$$

Numeric Answer

$$v_1 = -3 \text{ V} \quad v_o = -14.25 \text{ V}$$

$$i_2 = 75 \text{ } \mu\text{A} \quad i_o = 795 \text{ } \mu\text{A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

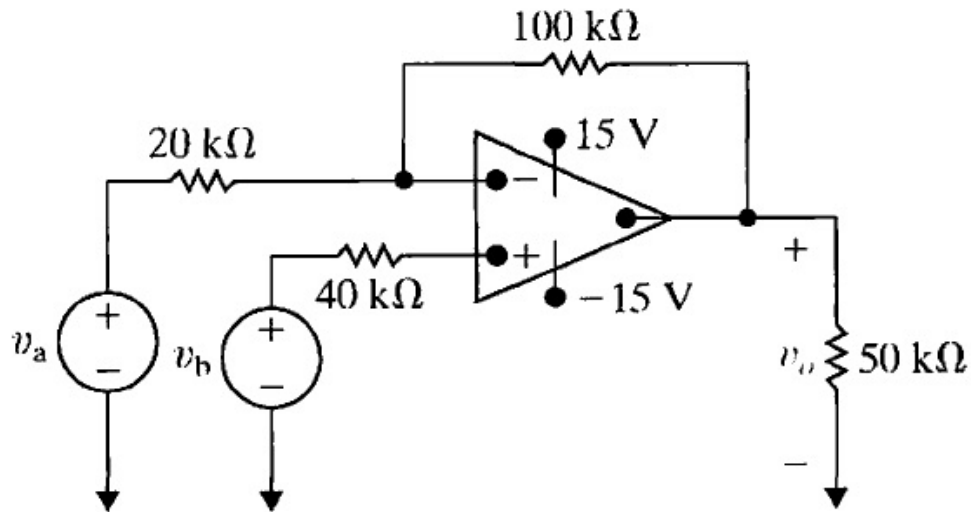

P5.03_9ed

Assume the op amp is ideal.

a) Calculate v_O if $v_a = 4$ V and $v_b = 0$ V. $v_O = -15$ ✓ Vb) Calculate v_O if $v_a = 2$ V and $v_b = 0$ V. $v_O = -10$ ✓ Vc) Calculate v_O if $v_a = 2$ V and $v_b = 1$ V. $v_O = -4$ ✓ Vd) Calculate v_O if $v_a = 1$ V and $v_b = 2$ V. $v_O = 7$ ✓ Ve) Calculate v_O if $v_a = 1.5$ V and $v_b = 4$ V. $v_O = 15$ ✓ Vf) If $v_b = 1.6$ V, specify the range of v_a such that the amplifier does not saturate. -1.08 ✓ $\leq v_a \leq$ 4.92 ✓ V**Numeric Answer**a) If $v_a = 4$ V and $v_b = 0$ V then $v_O = -15.0$ V op amp in saturationb) If $v_a = 2$ V and $v_b = 0$ V then $v_O = -10.0$ Vc) If $v_a = 2$ V and $v_b = 1$ V then $v_O = -4$ Vd) If $v_a = 1$ V and $v_b = 2$ V then $v_O = 7$ Ve) If $v_a = 1.5$ V and $v_b = 4$ V then $v_O = 15$ V op amp in saturationf) Specify the range of v_a required to avoid amplifier saturation.


$$-1.08 \leq v_a \leq 4.92 \text{ V}$$

Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

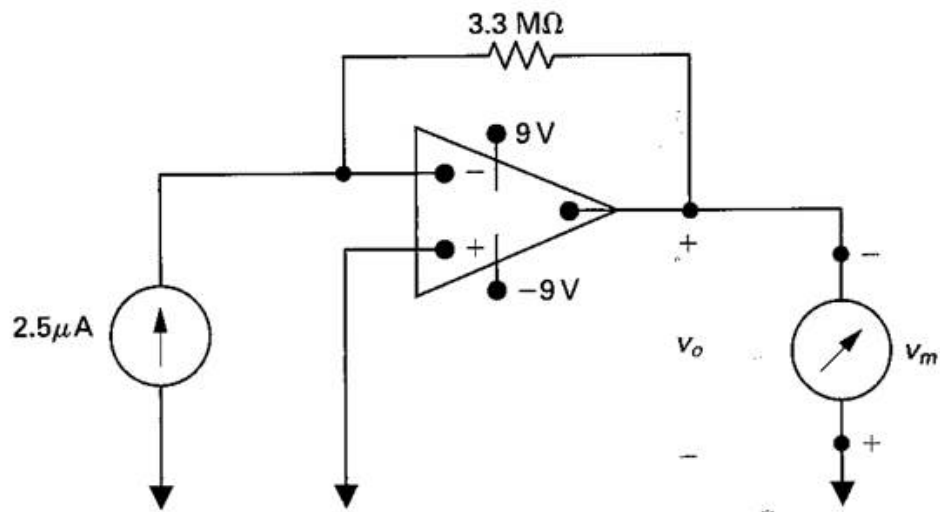Mark 10.00 out of
10.00

P5.01_6ed

Assume the op amp is ideal.

A voltmeter capable of a full-scale reading of 10 V is used to measure the output voltage of this circuit.

What is the reading of the voltmeter?

$$V_m = 8.25 \text{ V}$$

Numeric Answer

$$V_m = 8.25 \text{ V}$$

Correct

Marks for this submission: 10.00/10.00.