

Started on Wednesday, 21 September 2016, 3:41 PM

State Finished

Completed on Wednesday, 21 September 2016, 3:46 PM


Time taken 5 mins 20 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 40.00 out of
40.00

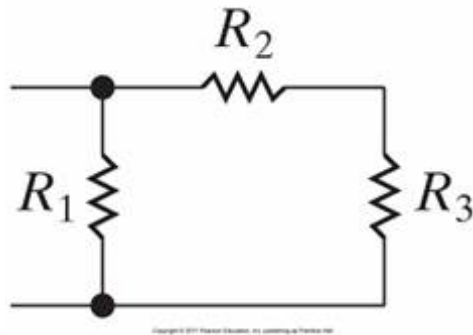

Q3a

Given: $R_1 = 1944 \, \Omega$ (Ohms) $R_2 = 4718 \, \Omega$ (Ohms) $R_3 = 4364 \, \Omega$ (Ohms)

Find the equivalent resistance R_{Eq} .

Answer: 1601.25




Calculated question

The correct answer is: 1601.25

Question 2


Correct

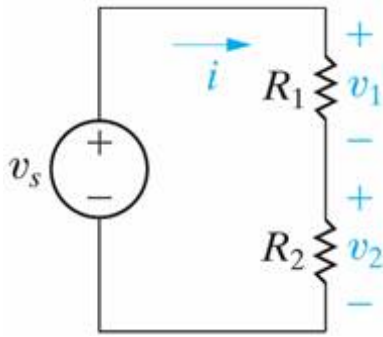
Mark 60.00 out of
60.00


Quiz 3-2d

Given:

$$v_s = 60 \text{ Volts} \quad R_1 = 300 \, \Omega \text{ (Ohms)} \quad R_2 = 500 \, \Omega \text{ (Ohms)}$$

a) Find the voltage v_1 . $v_1 =$  Volts

b) Find the voltage v_2 . $v_2 =$  Volts

c) Find the current i . $i =$  mA (milli Amp)

Numeric Answer

a) $v_1 = 22.50$ Volts

b) $v_2 = 37.50$ Volts

c) $i = 75.0$ mA (milli Amp)