

Home ► My courses ► EEE117-2017S-Tatro ► Homework ► Homework 11 - Chapter 14

---

<b>Started on</b>	Saturday, 8 April 2017, 1:38 PM
-------------------	---------------------------------

---

<b>State</b>	Finished
--------------	----------

---

<b>Completed on</b>	Thursday, 13 April 2017, 6:05 PM
---------------------	----------------------------------

---

<b>Time taken</b>	5 days 4 hours
-------------------	----------------

---


<b>Grade</b>	<b>100.00</b> out of 100.00
--------------	-----------------------------

---

**Question 1**

Correct

Mark 20.00 out of 20.00

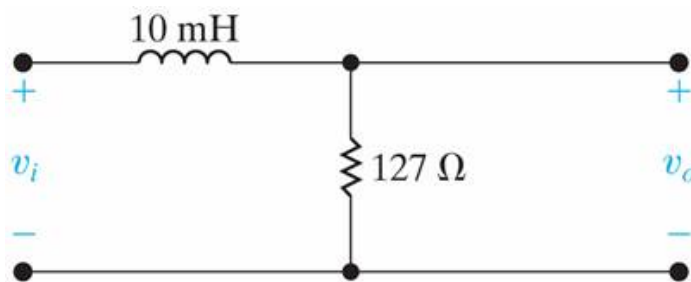

P14.1\_9ed

a) Find the cutoff frequency in hertz.

$$f_c = 2021.27 \text{ Hz}$$

b) Find  $H(j\omega = 0)$  in polar form.

$$H(j\omega = 0) = \text{Mag } 1 \text{ at angle } 0^\circ \text{ (Degrees)}$$

Now examine the output magnitude and phase as the input frequency varies.

c) Find  $H(j\omega = 0.2\omega_c)$  in polar form..

$$H(j\omega = 0.2\omega_c) = \text{Mag } 0.981 \text{ at angle } -11.31^\circ \text{ (Degrees)}$$

d) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } 0.7071 \text{ at angle } -45^\circ \text{ (Degrees)}$$

e) Find  $H(j\omega = 5\omega_c)$  in polar form.

$$H(j\omega = 5\omega_c) = \text{Mag } 0.196 \text{ at angle } -78.69^\circ \text{ (Degrees)}$$

Now given  $v_i(t) = 10 \cos(\omega t)$  V. Write the steady-state expression for  $v_o$  for:f)  $\omega = 0.2\omega_c$ 

$$v_o(t) = 9.81 \cos(2540 t + -11.31^\circ) \text{ Volts}$$

g)  $\omega = \omega_c$ 

$$v_o(t) = 7.07 \cos(12700 t + -45^\circ) \text{ Volts}$$

h)  $\omega = 5\omega_c$ 


$$v_o(t) = 1.96 \cos(63500 t + -78.69^\circ) \text{ Volts}$$

**Correct**

Marks for this submission: 20.00/20.00.

**Question 2**

Correct

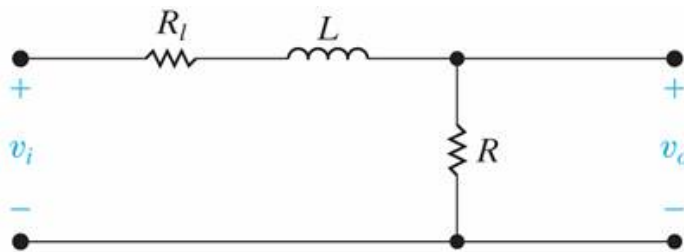Mark 20.00 out of  
20.00

P14.3\_9ed

A resistor  $R_l$  is added in series with the inductor in this circuit.Given:  $R_l = 75 \, \Omega$  (Ohm)  $L = 10 \, \text{mH}$  (mill H)  $R = 127 \, \Omega$  (Ohm)a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \boxed{12700} \checkmark / (s + \boxed{20200} \checkmark)$$

b) At what frequency will the magnitude of  $H(j\omega)$  be maximum?

$$\omega_{H,\max} = \boxed{0} \checkmark \text{ rad/sec}$$

c) What is maximum value of the magnitude of  $H(j\omega)$ ?

$$H(j\omega)_{\max} = \boxed{0.6287} \checkmark$$

d) At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by square root of 2?

$$\omega_{H,\max,\text{sqrt}(2)} = \boxed{20160.7} \checkmark \text{ rad/sec}$$

e) Find  $\omega_c$  (omega\_c)

$$\omega_c = \boxed{20160.7} \checkmark \text{ rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

f) Find  $H(j\omega = 0)$  in polar form..

$$H(j\omega = 0) = \text{Mag } \boxed{0.6287} \checkmark \text{ at angle } \boxed{0} \checkmark^\circ \text{ (Degrees)}$$

g) Find  $H(j\omega = 0.3\omega_c)$  in polar form.

$$H(j\omega = 0.3\omega_c) = \text{Mag } \boxed{0.6022} \checkmark \text{ at angle } \boxed{-16.70} \checkmark^\circ \text{ (Degrees)}$$

h) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } \boxed{0.446} \checkmark \text{ at angle } \boxed{-45} \checkmark^\circ \text{ (Degrees)}$$

i) Find  $H(j\omega = 3\omega_c)$  in polar form.

$$H(j\omega = 3\omega_c) = \text{Mag } \boxed{0.1988} \checkmark \text{ at angle } \boxed{-71.57} \checkmark^\circ \text{ (Degrees)}$$


**Correct**

Marks for this submission: 20.00/20.00.

**Question 3**

Correct

Mark 20.00 out of 20.00

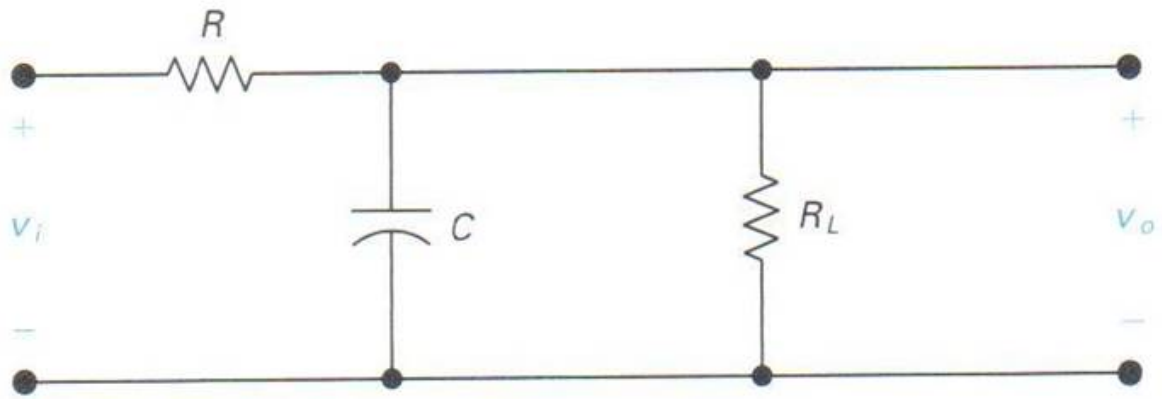

P14.3\_6ed

A resistor  $R_L$  is connected in parallel with the capacitor in this circuit. The circuit thus becomes a loaded low-pass filter.

Given:  $R = 20 \text{ k}\Omega$  (kilo Ohm)  $C = 4 \text{ nF}$   $R_L = 300 \text{ k}\Omega$  (kilo Ohm)

a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \boxed{12500} \checkmark / (s + \boxed{13333.33} \checkmark)$$

b) Find  $\omega_c$  (omega\_c)

$$\omega_c = \boxed{13333.33} \checkmark \text{ rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

c) Find  $H(j0)$

$$H(j0) = \boxed{0.9375} \checkmark$$

d) Find  $H(j\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = \omega_c$

$$H(j\omega_c) = \text{Mag } \boxed{0.6629} \checkmark \text{ Angle } \boxed{-45} \checkmark$$

e) Find  $H(j0.2\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 0.2 \omega_c$

$$H(j0.2\omega_c) = \text{Mag } \boxed{0.9193} \checkmark \text{ Angle } \boxed{-11.31} \checkmark$$

f) Find  $H(j8\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 8\omega_c$

$$H(j8\omega_c) = \text{Mag } \boxed{0.1163} \checkmark \text{ Angle } \boxed{-82.87} \checkmark$$


**Correct**

Marks for this submission: 20.00/20.00.

**Question 4**

Correct

Mark 20.00 out of 20.00

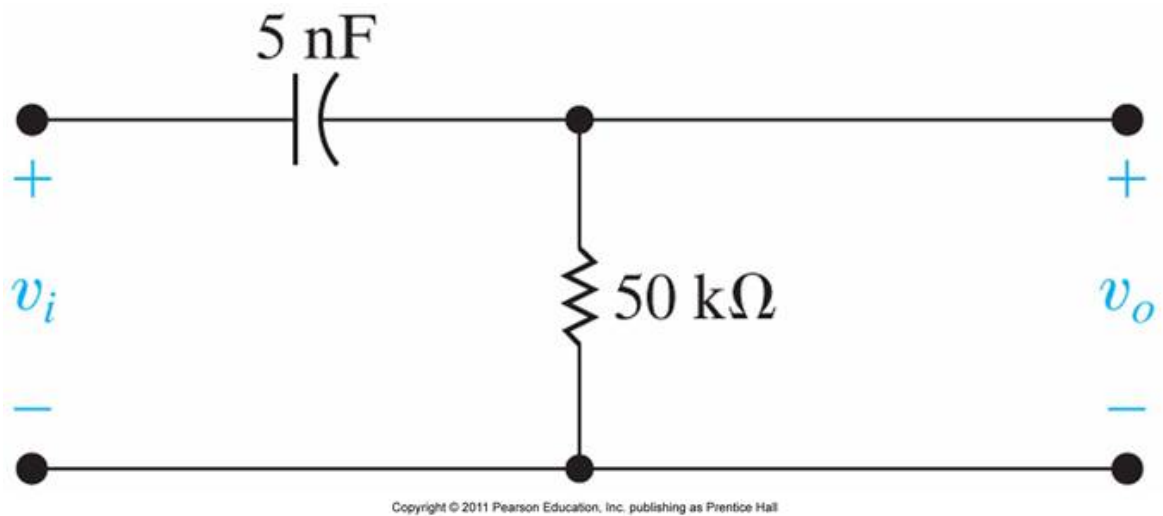

P14.10\_9ed

a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$$f_c = 636.62 \text{ Hz}$$

b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.707 \text{ at angle } 45^\circ \text{ (degrees)}$$

$$H(j\omega = 0.2\omega_c) = 0.196 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.98 \text{ at angle } 11.3^\circ$$

c) If  $v_i(t) = 500 \cos(\omega t)$  mV (milli V), write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353.5 \cos(\omega t + 45^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 98 \cos(\omega t + 78.69^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 490 \cos(\omega t + 11.3^\circ) \text{ mV (milli V)}$$


**Correct**

Marks for this submission: 20.00/20.00.

**Question 5**

Correct

Mark 20.00 out of 20.00

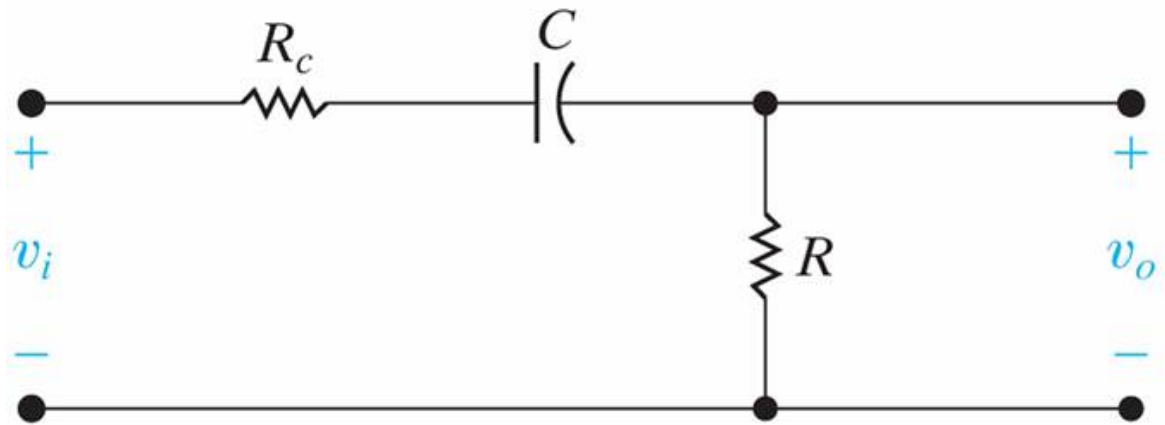

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P14.11\_9ed

Given:  $R_c = 12.5 \text{ k}\Omega$  (kilo Ohm)  $C = 5 \text{ nF}$   $R = 50 \text{ k}\Omega$  (kilo Ohm)a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$$f_c = 509.3 \text{ Hz}$$

b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.565 \text{ at angle } 45^\circ \text{ (degrees)}$$

$$H(j\omega = 0.2\omega_c) = 0.1569 \text{ at angle } 78.69^\circ$$

$$H(j\omega = 5\omega_c) = 0.7845 \text{ at angle } 11.31^\circ$$

c) If  $v_i(t) = 500 \cos(\omega t) \text{ mV}$  (milli V), write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 282.5 \cos(\omega t + 45^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 78.45 \cos(\omega t + 78.69^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 392.25 \cos(\omega t + 11.31^\circ) \text{ mV (milli V)}$$

**Correct**

Marks for this submission: 20.00/20.00.