


Home ► My courses ► **EEE117-2019S-Sec1** ► Exams and Quizzes ►
Exam 3 (Final) - Bode Diagram, Chapters 14, 15, 16, and Bode Diagrams

Started on	Monday, 13 May 2019, 10:10 AM
State	Finished
Completed on	Monday, 13 May 2019, 11:13 AM
Time taken	1 hour 3 mins
Grade	98.00 out of 100.00

Question 1

Correct

Mark 9.00 out of 9.00

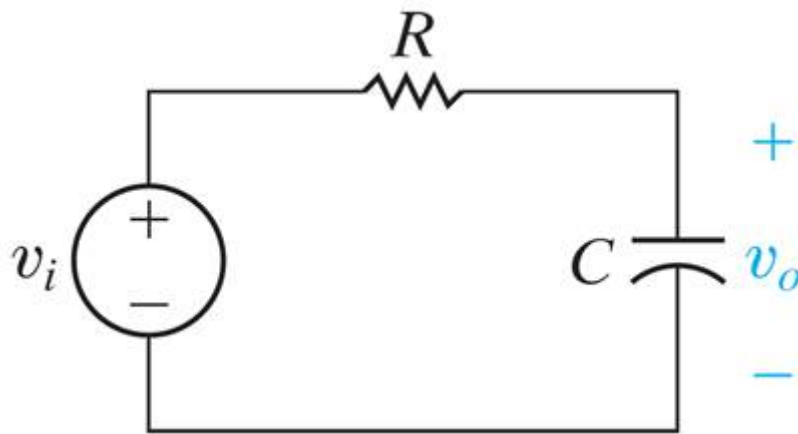

Q1e

Given: $C = 100 \text{ nF}$ (nano F) $R = 99.5 \Omega$ (Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = 100502.513 \checkmark / (s + 100502.513 \checkmark)$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = 100502.513 \checkmark \text{ rad/sec} \quad f_c = 15995.47 \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \ll \omega_c$.

$$\theta(\text{pass band}) = 0 \checkmark^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency ω_c .

$$\theta(\omega_c) = -45 \checkmark^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \gg \omega_c$.

$$\theta(\text{stop band}) = -90 \checkmark^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

$$\text{Filter Type} = \text{Low Pass} \checkmark$$

Numeric Answer

$$\text{a) } H(s) = 100,502.5126 / (s + 100,502.5126)$$

$$\text{b) } \omega_c = 100,502.5126 \text{ rad/sec} \quad f_c = 15,9995.4717 \text{ Hz}$$

$$\text{c) } \theta(\text{pass band}) = 0^\circ$$

$$\text{d) } \theta(\omega_c) = -45^\circ$$

$$\text{e) } \theta(\text{stop band}) = -90^\circ$$

$$\text{f) } \text{Filter Type} = \text{Low Pass}$$


Correct

Marks for this submission: 9.00/9.00.

Question 2

Correct

Mark 9.00 out of 9.00

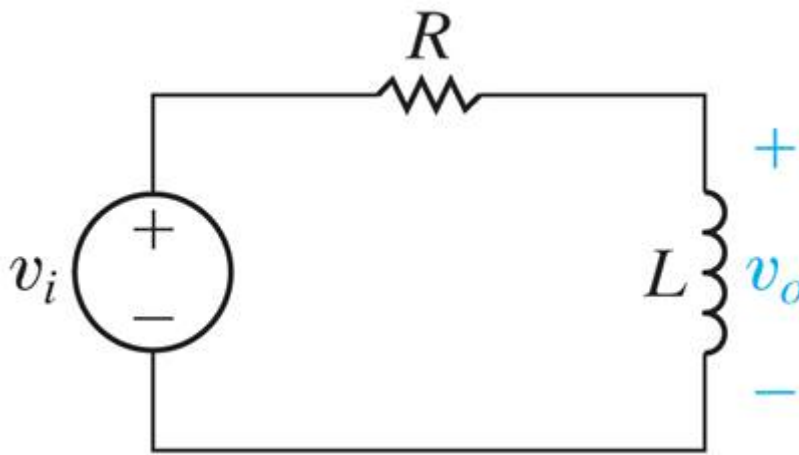

Q2d

Given: $L = 570 \text{ mH}$ (milli H) $R = 3.5 \text{ k}\Omega$ (kilo Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = s / (s + 6140.35) \quad \checkmark$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = 6140.35 \quad \checkmark \text{ rad/sec} \quad f_c = 977.27 \quad \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \gg \omega_c$.

$$\theta(\text{pass band}) = 0 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency $\omega = \omega_c$.

$$\theta(\omega_c) = 45 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \ll \omega_c$.

$$\theta(\text{stop band}) = 90 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

$$\text{Filter Type} = \text{High Pass} \quad \checkmark$$

Numeric Answer

a) $H(s) = s / (s + 6,140.3509)$

b) $\omega_c = 6,140.3509 \text{ rad/sec}$ $f_c = 977.2672 \text{ Hz}$

c) $\theta(\text{pass band}) = 0^\circ$

d) $\theta(\omega_c) = 45^\circ$

e) $\theta(\text{stop band}) = 90^\circ$

f) Filter Type = High Pass


Correct

Marks for this submission: 9.00/9.00.

Question 3

Correct

Mark 9.00 out of 9.00

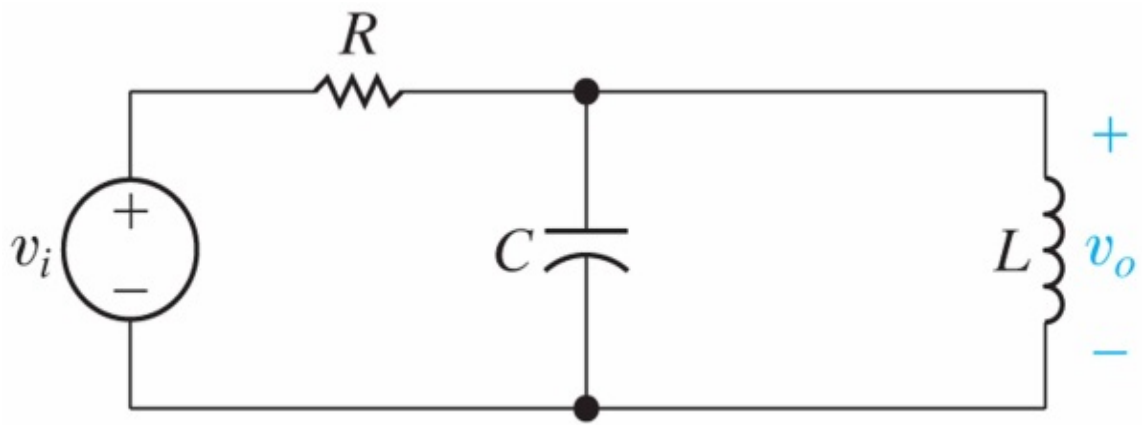

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Q3Pc

Given: $R = 80 \, \Omega$ (Ohm) $C = 5 \, \mu\text{F}$ (micro F) $L = 180 \, \mu\text{H}$ (micro H)a) Find the resonant frequency ω_0 .

$$\omega_0 = 33332 \, \checkmark \text{ rad/sec}$$

b) Find the lower half-power frequency ω_{c1} .

$$\omega_{c1} = 32106 \, \checkmark \text{ rad/sec}$$

c) Find the upper half-power frequency ω_{c2} .

$$\omega_{c2} = 34607.083 \, \checkmark \text{ rad/sec}$$

d) Find the bandwidth β (Beta).

$$\beta = 2500.62 \, \checkmark \text{ rad/sec}$$

e) Find the quality factor Q .

$$Q = 13.33 \, \checkmark$$

f) Identify the filter type of this circuit.

Filter Type = Band Pass ☒**Numeric Answer**a) $\omega_0 = 33,333.3333 \text{ rad/sec}$ b) $\omega_{c1} = 32,106.7626 \text{ rad/sec}$ c) $\omega_{c2} = 34,606.7626 \text{ rad/sec}$ d) $\beta = 2,500 \text{ rad/sec}$ e) $Q = 13.3333$

f) Filter Type = Band Pass


Correct

Marks for this submission: 9.00/9.00.

Question 4

Correct

Mark 9.00 out of 9.00

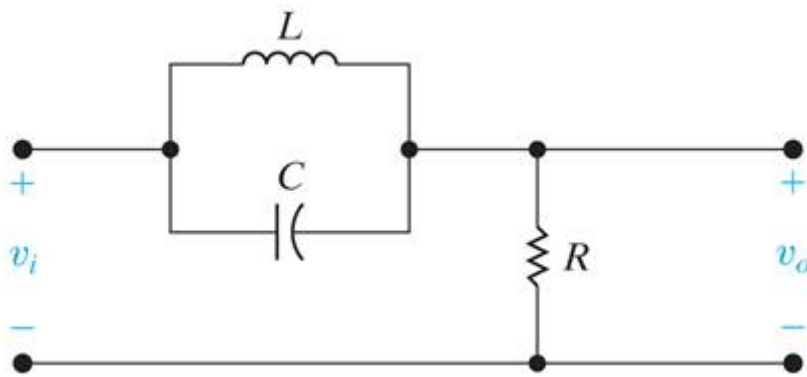

Q4Pb

Given: $R = 750 \, \Omega$ (Ohm) $C = 20 \, \text{nF}$ (nano F) $L = 150 \, \mu\text{H}$ (micro H)a) Calculate ω_0 .

$$\omega_0 = 577.35 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

b) Calculate f_0 .

$$f_0 = 91.88 \, \checkmark \text{ kHz (kilo Hz)}$$

c) Find ω_{c1} .

$$\omega_{c1} = 544.977 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

d) Find ω_{c2} .

$$\omega_{c2} = 611.645 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

e) Find β (Beta).

$$\beta = 66.66 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

f) Find Q .

$$Q = 8.66 \, \checkmark$$

g) Identify the filter type of this circuit.

Filter Type = Band Reject $\blacktriangledown \checkmark$ **Numeric Answer**

a) $\omega_0 = 577.3503 \text{ krad/sec}$

b) $f_0 = 91.8881 \text{ kHz}$

c) $\omega_{c1} = 544.9784 \text{ krad/sec}$

d) $\omega_{c2} = 611.6451 \text{ krad/sec}$

e) $b = 66.6667 \text{ krad/sec}$

f) $\beta = 8.6603$


g) Filter Type = Band Reject

Correct

Question 5

Correct

Mark 9.00 out of 9.00

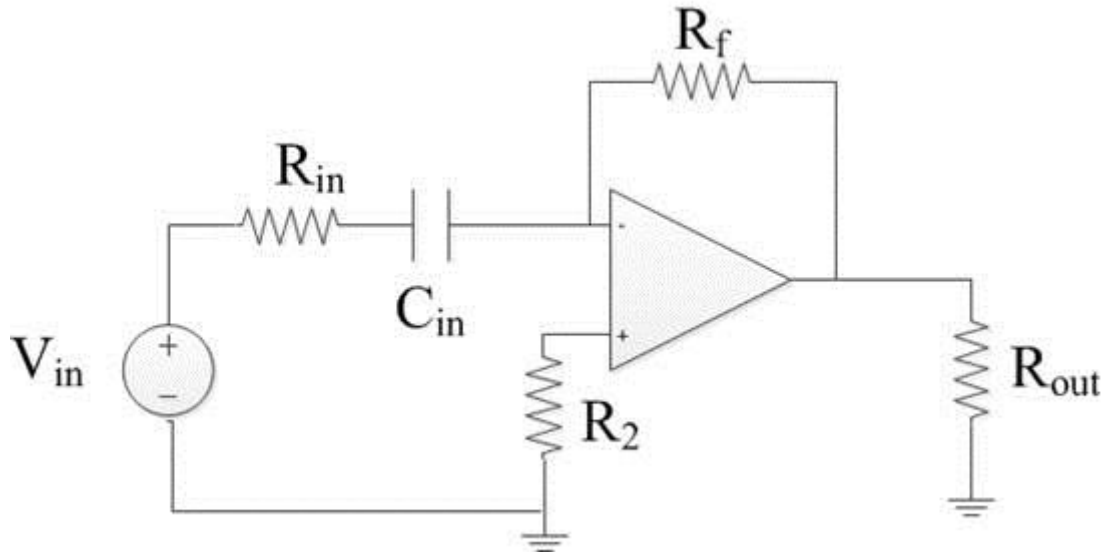

Q5e

Given: $V_{in} = 25 \cos(4,000t)$ Volts

$$R_{in} = 40 \text{ k}\Omega \text{ (kilo Ohm)} \quad C_{in} = 0.1 \text{ }\mu\text{F (micro F)} \quad R_f = 10 \text{ k}\Omega \text{ (kilo Ohm)}$$

$$R_{out} = 1 \text{ k}\Omega \text{ (kilo Ohm)} \quad R_2 = 10 \text{ }\Omega \text{ (Ohm)}$$

The opamp has power input rails at +15V and -15V.

Find the steady-state output voltage V_{out} which is the voltage across the resistor R_{out} .

$$v_{out} = 6.2 \checkmark \cos(4,000 t + 183.6 \checkmark^\circ \text{ (Degrees) Volts}$$

State the voltage magnitude as positive and state the phase angle as a positive angle (counterclockwise from the origin) in the correct quadrant.

Numeric Answer

$$v_{out} = 6.2378 \cos(4,000 t + 183.5763^\circ) \text{ Volts}$$


Correct

Marks for this submission: 9.00/9.00.

Question 6

Correct

Mark 9.00 out of 9.00

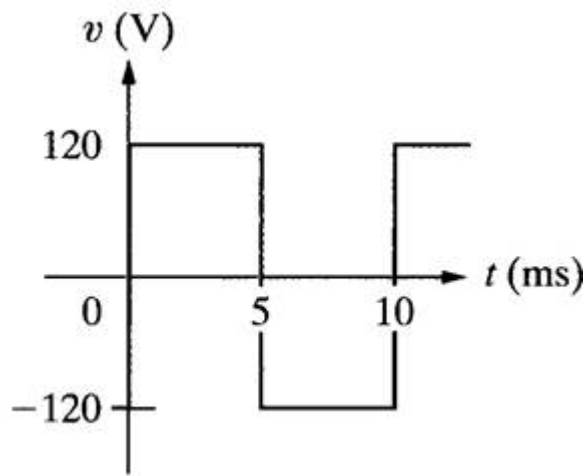

Q6a

Given: The Fourier coefficients for this waveform are

$$a_v = 0 \text{ V} \quad a_n = 0 \text{ V} \quad b_n = 480 / (n\pi) \text{ for } n \text{ odd}$$

Write the following terms of this waveform's Fourier series.

a) What is the average value?

$$\text{Avg} = \boxed{0} \checkmark \text{ Volts}$$

Answers for the next two questions are in the order of magnitude, identify cosine or sine and the frequency of the sinusoid in radians/sec.

b) Find the Fourier Series term for $n = 1$.

$$v_1(t) = \boxed{152} \checkmark \text{ sine } \checkmark (\boxed{628.31} \checkmark \text{ t) Volts}$$

c) Find the Fourier Series term for $n = 5$.

$$v_5(t) = \boxed{30.56} \checkmark \text{ sine } \checkmark (\boxed{3141.59} \checkmark \text{ t) Volts}$$

Numeric Answer

$$\text{a) } a_v = 0 \text{ Volts}$$

$$\text{b) For } n = 1, v_1(t) = 480/\pi \sin(1 \cdot 200\pi) = 152.7887 \sin(628.3185 t) \text{ V}$$

$$\text{c) For } n = 5, v_5(t) = 96/\pi \sin(5 \cdot 200\pi) = 30.5577 \sin(3141.5927 t) \text{ V}$$

Correct

Marks for this submission: 9.00/9.00.

Question 7

Correct

Mark 9.00 out of
9.00

Q7a

Given the “normal” trigonometric form of the Fourier series coefficients for a waveform are

$$a_{\text{avg}} = \text{zero} \quad a_n = -10/n^2 \quad b_n = 20/n$$

Determine the coefficients for the Alternative trigonometric form of the Fourier series in the polar form

$$a_n - jb_n = A_n \angle -\theta_n \quad (\text{Magnitude } A_n \text{ at angle } -\theta_n)$$

a) For the first term in the summation where $n = 1$:

$$A_1 = 22.36 \quad \checkmark \quad \text{Volts}$$

$$-\theta_1 \text{ (Theta 1)} = 116.565 \quad \checkmark \quad ^\circ \text{ (Degrees, angle CW from origin)}$$

b) For the second term in the summation where $n = 2$:

$$A_2 = 10.31 \quad \checkmark \quad \text{Volts}$$

$$-\theta_2 \text{ (Theta 2)} = 104.036 \quad \checkmark \quad ^\circ \text{ (Degrees, angle CW from origin)}$$

c) For the third term in the summation where $n = 3$:

$$A_3 = 6.67 \quad \checkmark \quad \text{Volts}$$

$$-\theta_3 \text{ (Theta 3)} = 99.46 \quad \checkmark \quad ^\circ \text{ (Degrees, angle CW from origin)}$$

CW = Clock-wise

Note that the angle also includes the “-” sign as shown in the polar form.

Numeric Answer

$$\text{a) } A_1 = 22.3607 \text{ Volts} \quad -\theta_1 = 116.5651^\circ$$

$$\text{b) } A_2 = 10.3078 \text{ Volts} \quad -\theta_2 = 104.0362^\circ$$

$$\text{c) } A_3 = 6.7586 \text{ Volts} \quad -\theta_3 = 99.4623^\circ$$


Correct

Marks for this submission: 9.00/9.00.

Question 8

Correct

Mark 9.00 out of 9.00

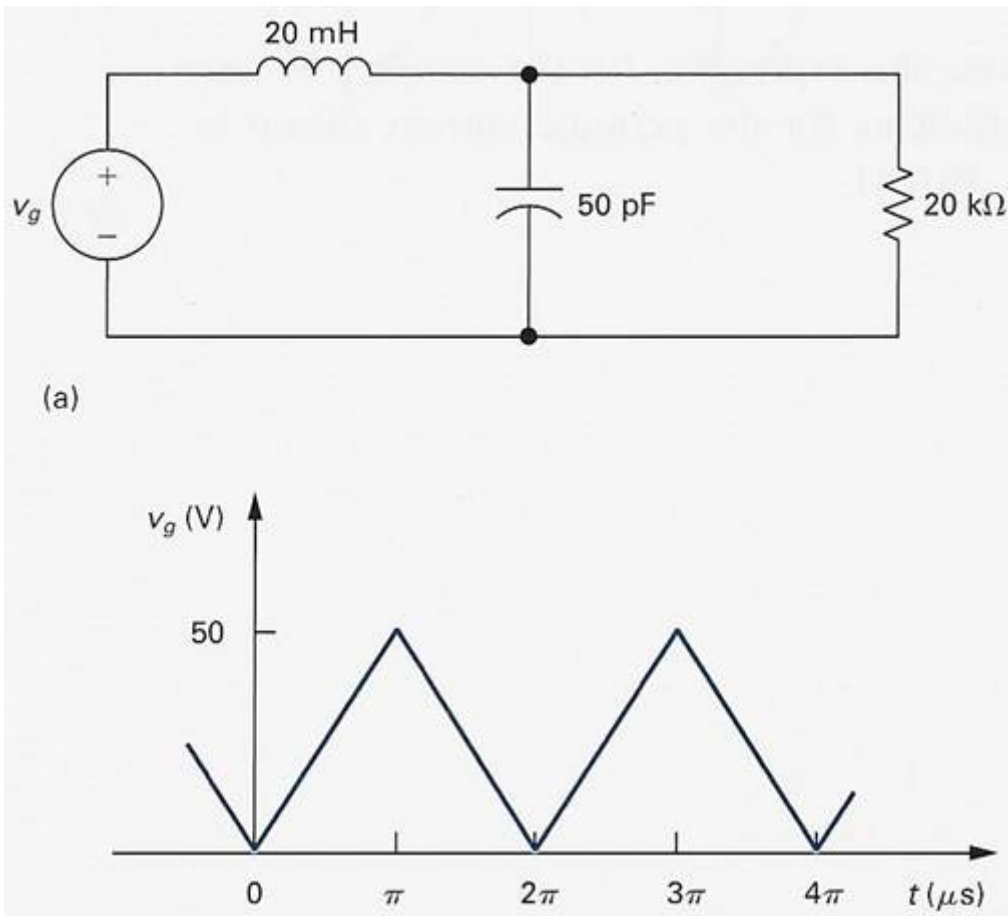

Q8

The triangular-wave voltage source is applied to this circuit.

The Fourier series of this input waveform is

$$v(t) = 25 - \frac{200}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \cos(n\omega_0 t)$$

The s domain transfer function of the circuit is

$$H(s) = \frac{10^{12}}{s^2 + s10^6 + 10^{12}}$$

The desired output is the voltage across the $20\text{ k}\Omega$ (kilo Ohm) resistor.

a) Determine the steady-state output voltage for $n = 1$ written as polar phasor.

$$v_{1,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-20} \checkmark \text{ at angle } \boxed{-90} \checkmark^\circ$$

(Degrees) Volts (negative magnitude and negative angle)

b) Determine the steady-state output voltage for $n = 5$ written as polar phasor.

$$v_{5,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-0.1655} \checkmark \text{ at angle } \boxed{11.77} \checkmark^\circ$$

(Degrees) Volts (negative magnitude and positive angle)

c) Determine an estimate of the time varying power across the $20\text{ k}\Omega$ (kilo Ohm) resistor based on the voltage from $n = 1$ term only.

$$P_{20W,\text{steady-state}} = \boxed{10.3} \checkmark \text{ mW (milli W)}$$

Numeric Answer

- a) $v_{1'20W, \text{steady-state}}(t) = -20.2642$ at angle -90° V
- b) $v_{5'20W, \text{steady-state}}(t) = -0.1654$ at angle 11.77° V
- c) $P_{20W, \text{steady-state}} = 10.266$ mW


Correct

Marks for this submission: 9.00/9.00.

Question 9

Correct

Mark 9.00 out of 9.00

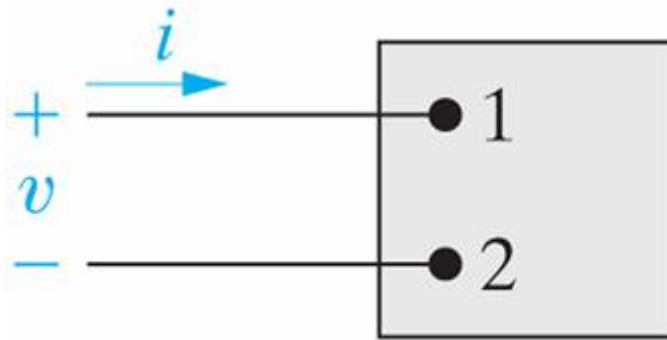

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

Q9a

The voltage and current at terminals of this network are

$$v(t) = 60 + 170 \cos(120 \pi t + 15^\circ) + 30 \sin(360 \pi t + 12^\circ) \text{ Volts}$$

$$i(t) = 5 + 12 \sin(120 \pi t + 35^\circ) + 3 \cos(360 \pi t - 30^\circ) \text{ Amps}$$

a) Estimate the average power at terminals?

$$P = \boxed{669.29} \checkmark \text{ W}$$

b) What is the rms value of the voltage of this truncated series?

$$V_{\text{rms}} = \boxed{136.01} \checkmark V_{\text{rms}}$$

c) What is the rms value of the current of this truncated series?

$$I_{\text{rms}} = \boxed{10.07} \checkmark A_{\text{rms}}$$

Numeric Answer

- a) $P = 678.9714$ W
- b) $V_{\text{rms}} = 136.0147$ V_{rms}
- c) $I_{\text{rms}} = 10.0747$ I_{rms}

Correct

Marks for this submission: 9.00/9.00.

Question 10

Correct

Mark 9.00 out of 9.00

Q10c

Given
$$H(s) = \frac{(45,000)(s+200)}{(s+2,000)(s+9,000)}$$

a) What is the zero of this function in the form $s + z_1$?

$z_1 =$ ✓

b) What are the two poles of this function in the form $s + p_{1,2}$?

$p_1 =$ ✓ (positive lower value)

$p_2 =$ ✓ (positive higher value)

c) What is the *gain* K in dB after putting this function in *Standard Form*?

$K =$ ✓ dB

For the following use the Bode diagram straight-line approximation conventions (do not plot the function)

d) Find the magnitude of this transfer function at $\omega = 2,000$ rad/sec.

$|H(j\omega = 2,000 \text{ rad/sec})| =$ ✓ dB

e) Find the phase angle at $\omega = 2,000$ rad/sec

$\theta(j\omega = 2,000 \text{ rad/sec}) =$ ✓ ° (Degrees)

a) $z_1 = 200$

b) $p_1 = 2,000$ $p_2 = 9,000$

c) K in dB = -6.0206 dB

d) $|H(j\omega = 2,000 \text{ rad/sec})| = 14$ dB

e) $\theta(j\omega = 200 \text{ rad/sec}) = 45^\circ$

Correct

Marks for this submission: 9.00/9.00.

Question 11

Complete

Mark 8.00 out of 10.00

You created a hand-drawn Bode Diagram of a given transfer function in-class on May 6th. That in-class work has been manually graded. The instructor will enter your score here after you have completed this online exam.

Comment:

Jump to...▼